

Transformed Circuit

These basic relationships may also be

represented in the complex-frequency domain. Ideal energy sources, for example, which were given in time domain as $v(t)$ and $i(t)$, may now be represented by their transforms $V(s) = \mathcal{L}[v(t)]$ and $I(s) = \mathcal{L}[i(t)]$. The resistor, defined by the v - i relationship

$$v(t) = R i(t) \quad (7.1)$$

is defined in the frequency domain by the transform of Eq. 7.1, or

$$V(s) = R I(s) \quad (7.2)$$

For an inductor, the defining v - i relationships are

$$\begin{aligned} v(t) &= L \frac{di}{dt} \\ i(t) &= \frac{1}{L} \int_{0^-}^t v(\tau) d\tau + i(0^-) \end{aligned} \quad (7.3)$$

Transforming both equations, we obtain

$$\begin{aligned} V(s) &= sLI(s) - Li(0^-) \\ I(s) &= \frac{1}{sL} V(s) + \frac{i(0^-)}{s} \end{aligned} \quad (7.4)$$

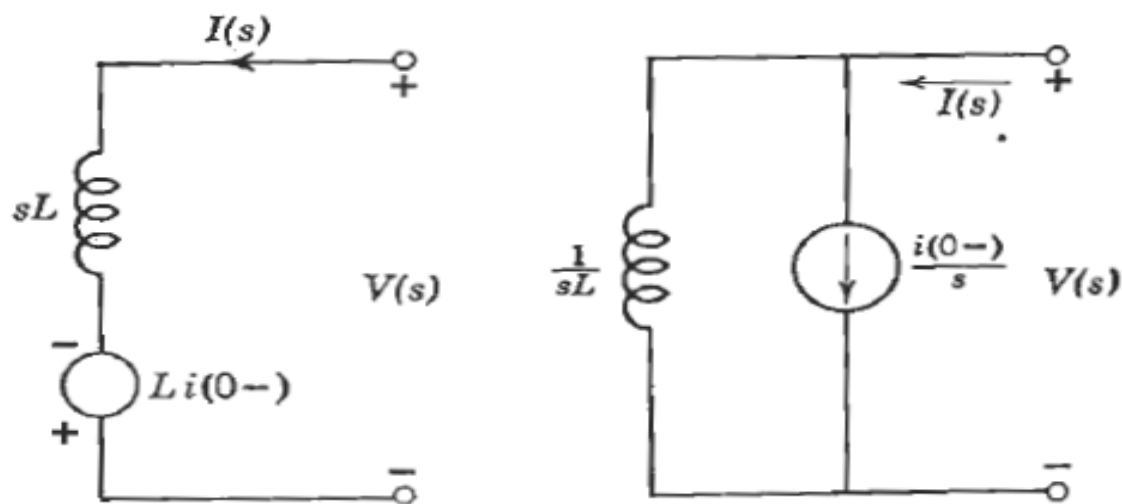


FIG. 7.1. Inductor.

The transformed circuit representation for an inductor is depicted in Fig. 7.1. For a capacitor, the defining equations are

$$v(t) = \frac{1}{C} \int_{0-}^t i(\tau) d\tau + v(0-) \quad (7.5)$$

$$i(t) = C \frac{dv}{dt}$$


The frequency domain counterparts of these equations are then

$$V(s) = \frac{1}{sC} I(s) + \frac{v(0-)}{s} \quad (7.6)$$

$$I(s) = sC V(s) - C v(0-)$$

Thevenin's and Norton's Theorem


In network analysis, the objective of a problem is often to determine a *single* branch current through a given element or a *single* voltage across an element. In problems of this kind, it is generally not practicable to write a complete set of mesh or node equations and to solve a system of equations for this one current or voltage. It is then convenient to use two very important theorems on equivalent circuits, known as *Thévenin's and Norton's theorems*.

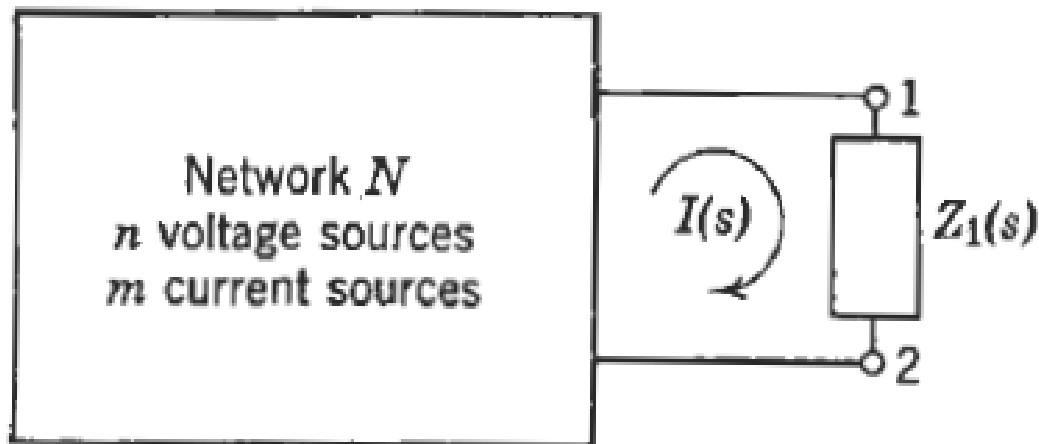

The System Function

As we discussed earlier, a linear system is one in which the excitation $e(t)$ is related to the response $r(t)$ by a linear differential equation. When the Laplace transform is used in describing the system, the relation between the excitation $E(s)$ and the response $R(s)$ is an algebraic one. In particular, when we discuss initially inert systems, the excitation and response are related by the system function $H(s)$ as given the relation

$$R(s) = E(s)H(s) \quad (7.42)$$

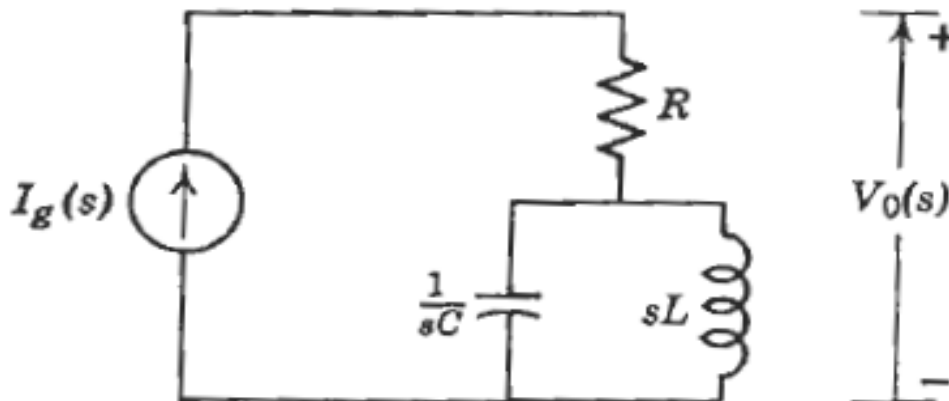

the system function may assume many forms and may have special names such as *driving-point admittance*, *transfer impedance*, *voltage* or *current-ratio transfer function*. This is because the form of the system function depends on whether the excitation is a voltage or current source, and whether the response is a specified current or voltage. We now discuss some specific forms of system functions.

Impedance

When the excitation is a current source and the response is a voltage, then the system function is an impedance. When both excitation and response are measured between the same pair of terminals, we have a driving-point impedance. An example of a driving-point impedance is given in Fig. 7.25, where

$$H(s) = \frac{V_o(s)}{I_o(s)} = R + \frac{(1/sC)sL}{sL + 1/sC} \quad (7.43)$$


Admittance

When the excitation is a voltage source and the response is a current, $H(s)$ is an admittance. In Fig. 7.26, the transfer admittance I_2/V_g is obtained from the network as

$$H(s) = \frac{I_2(s)}{V_g(s)} = \frac{1}{R_1 + sL + 1/sC_1} \quad (7.44)$$

Voltage-ratio transfer function

When the excitation is a voltage source and the response is also a voltage, then $H(s)$ is a voltage-ratio transfer function. In Fig. 7.27, the voltage-ratio transfer function $V_o(s)/V_g(s)$ is obtained as follows. We first find the

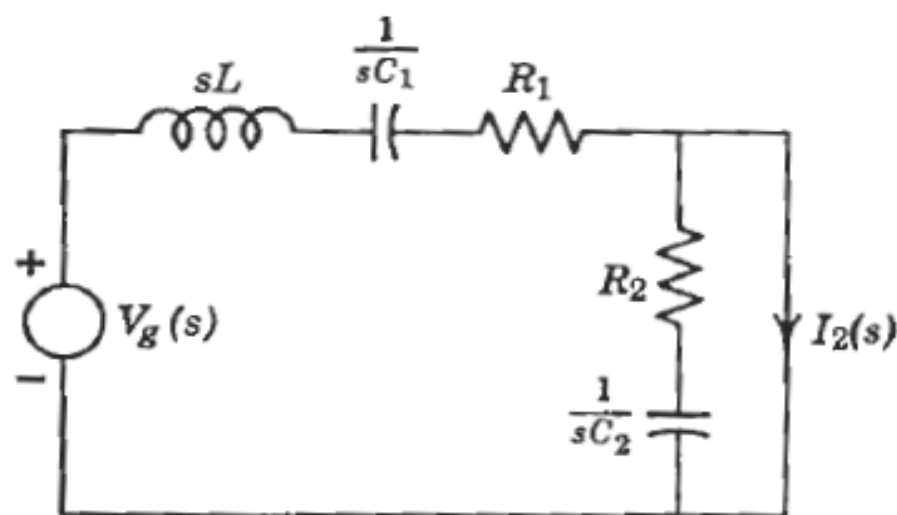

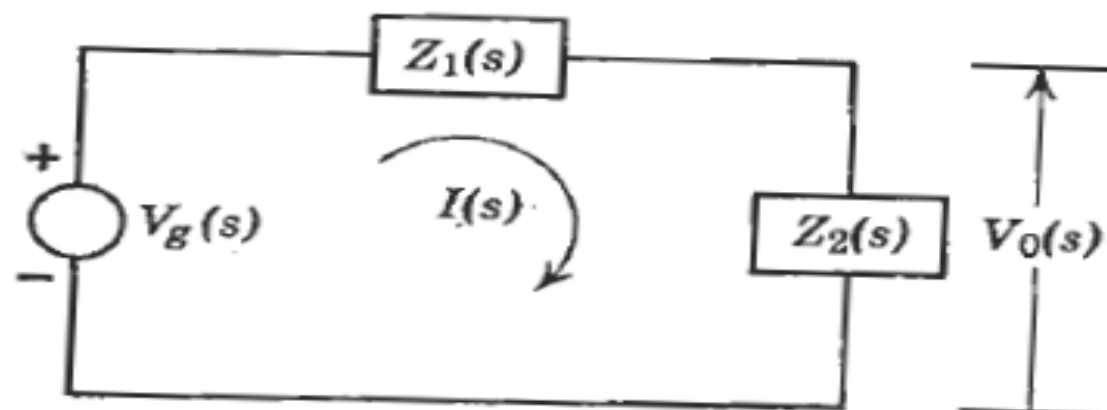


FIG. 7.27

current

$$I(s) = \frac{V_g(s)}{Z_1(s) + Z_2(s)}$$

Since

$$V_0(s) = Z_2(s) I(s)$$

then

$$\frac{V_0(s)}{V_g(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$

Current-ratio transfer function

When the excitation is a current source and the response is another current in the network, then $H(s)$ is called a current-ratio transfer function. As an example, let us find the ratio I_o/I_o for the network given in Fig. 7.28. Referring to the depicted network, we know that

$$I_o(s) = I_1(s) + I_o(s), \quad I_1(s) \frac{1}{sC} = I_o(s)(R + sL) \quad (7.48, 7.49)$$

Eliminating the variable I_1 , we find

$$I_o(s) = I_o(s) \left(1 + \frac{R + sL}{1/sC} \right) \quad (7.50)$$

so that the current-ratio transfer function is

$$\frac{I_o(s)}{I_o(s)} = \frac{1/sC}{R + sL + 1/sC} \quad (7.51)$$

