

# Two Port Network

# CHARACTERISTICS AND PARAMETERS OF TWO PORT NETWORKS:


- Relationship of two-port variables,
- short-circuit Admittance parameters,
- open circuit impedance Parameters,
- Transmission parameters,
- hybrid parameters,
- relationships between parameter sets,
- Inter-connection of two port networks.

# What is network

- When a number of impedances are connected together to form a system that consist of set of interconnected circuits performing specific function, is called as a network
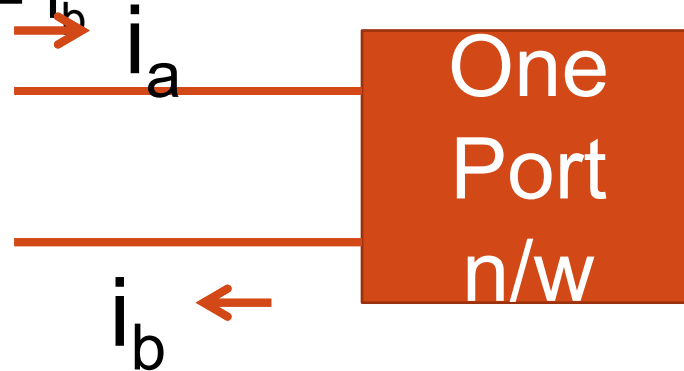
# One Port Network


- A pair of terminals at which a signal may enter or leave a network is called a port n/w or one port n/w.
- By KCL,  $i_a = i_b$


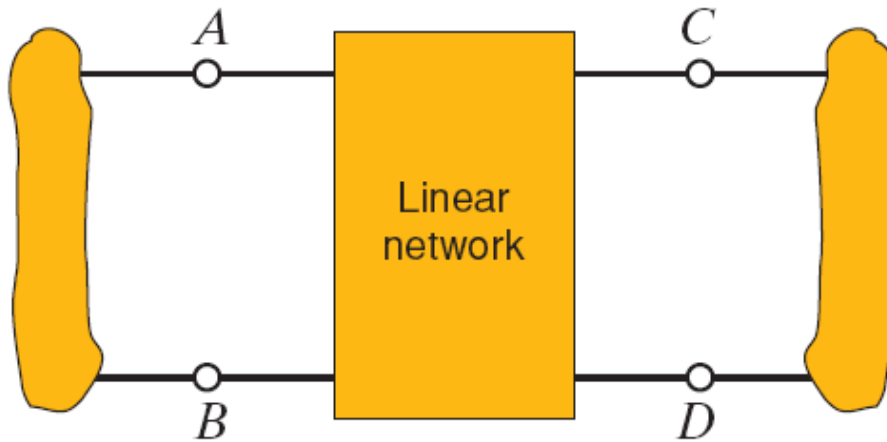
# Two Port Parameters

- It represented by a black box with four variables, two voltage ( $V_1$ ,  $V_2$ ) and two currents ( $I_1$ ,  $I_2$ ), which are available for measurements
- Out of these four variables, which two variables may be considered 'independent' and which two 'dependent' is generally decided by the problem under consideration.





A two-port model is a description of a network that relates voltages and currents at two pairs of terminals

## LEARNING GOALS

Study the basic types of two-port models

Admittance parameters

Impedance parameters

Hybrid parameters

Transmission parameters

# Two Port Networks

## Network Equations:

Impedance  
Z parameters

$$\begin{aligned}V_1 &= z_{11}I_1 + z_{12}I_2 \\V_2 &= z_{21}I_1 + z_{22}I_2\end{aligned}$$

Admittance  
Y parameters

$$\begin{aligned}I_1 &= y_{11}V_1 + y_{12}V_2 \\I_2 &= y_{21}V_1 + y_{22}V_2\end{aligned}$$

Transmission  
A, B, C, D  
parameters

$$\begin{aligned}V_1 &= AV_2 - BI_2 \\I_1 &= CV_2 - DI_2\end{aligned}$$

Inverse  
Transmission  
parameters

$$\begin{aligned}V_2 &= b_{11}V_1 - b_{12}I_1 \\I_2 &= b_{21}V_1 - b_{22}I_1\end{aligned}$$

Hybrid  
H parameters

$$\begin{aligned}V_1 &= h_{11}I_1 + h_{12}V_2 \\I_2 &= h_{21}I_1 + h_{22}V_2\end{aligned}$$

Inverse  
Hybrid  
H parameters

$$\begin{aligned}I_1 &= g_{11}V_1 + g_{12}I_2 \\V_2 &= g_{21}V_1 + g_{22}I_2\end{aligned}$$

# Open circuit Impedance (Z) parameter

- Useful in designing impedance matching and power distribution system.
- Two port network can either be voltage or current driven.
- The input and output terminal voltage can be presented as follows:


$$(V_1, V_2) = f(I_1, I_2)$$




$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[V] = [Z][I]$$

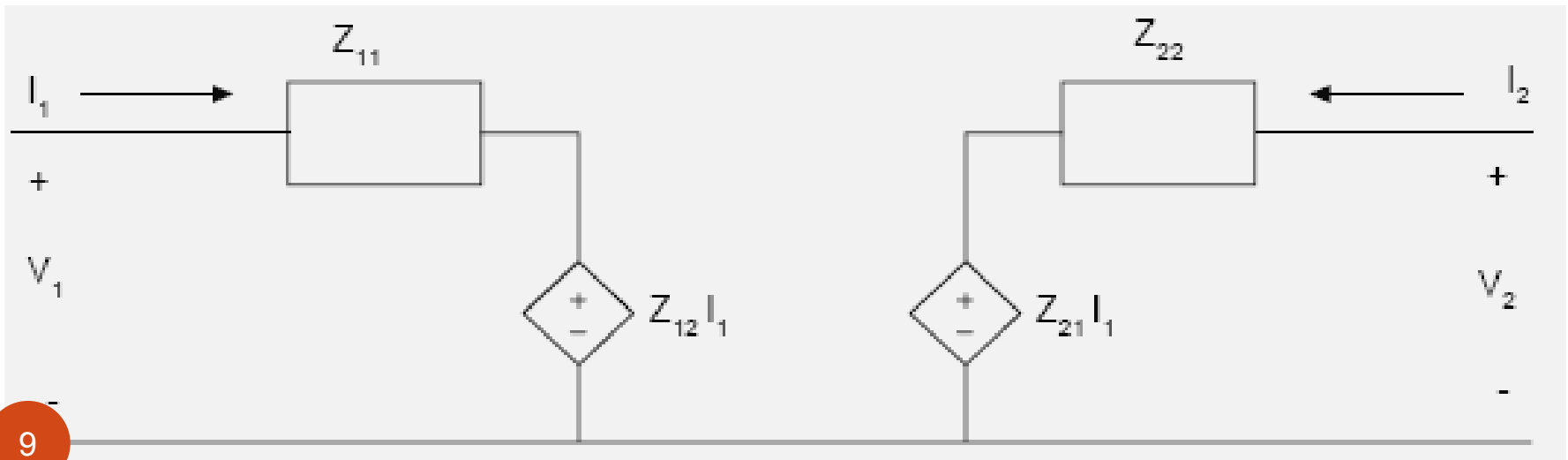- where impedance parameters of the system is  $z = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$
- $V_1 = z_{11}I_1 + z_{12}I_2$
- $V_2 = z_{21}I_1 + z_{22}I_2$



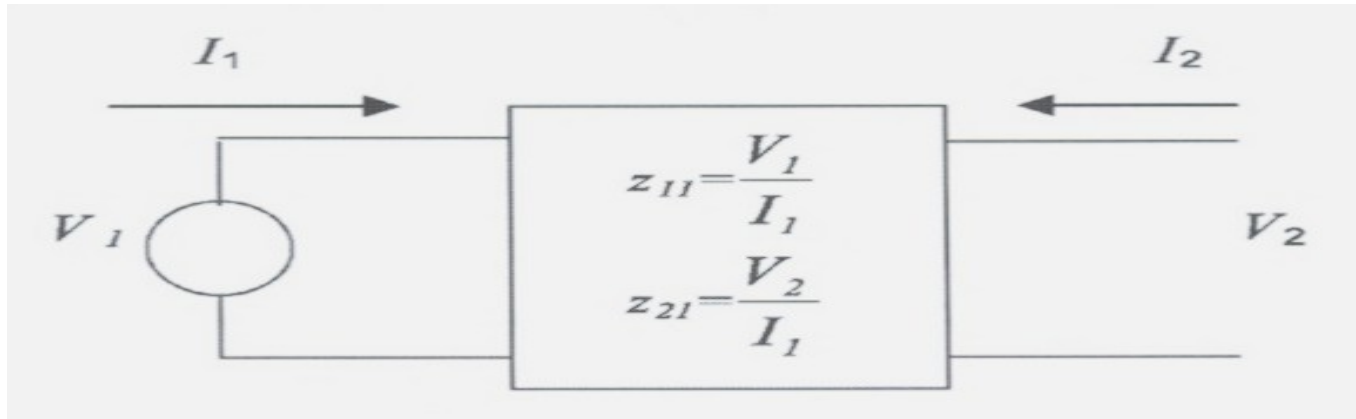- Case –I Assuming the output of the two port to be open circuit,  $I_2 = 0$




$$z_{11} = \frac{V_1}{I_1} \quad \Big| \quad I_2 = 0$$

Input driving point impedance with the output port open circuit

$$z_{21} = \frac{V_2}{I_1} \quad \Big| \quad I_2 = 0$$

Forward transfer impedance with the output port open circuit

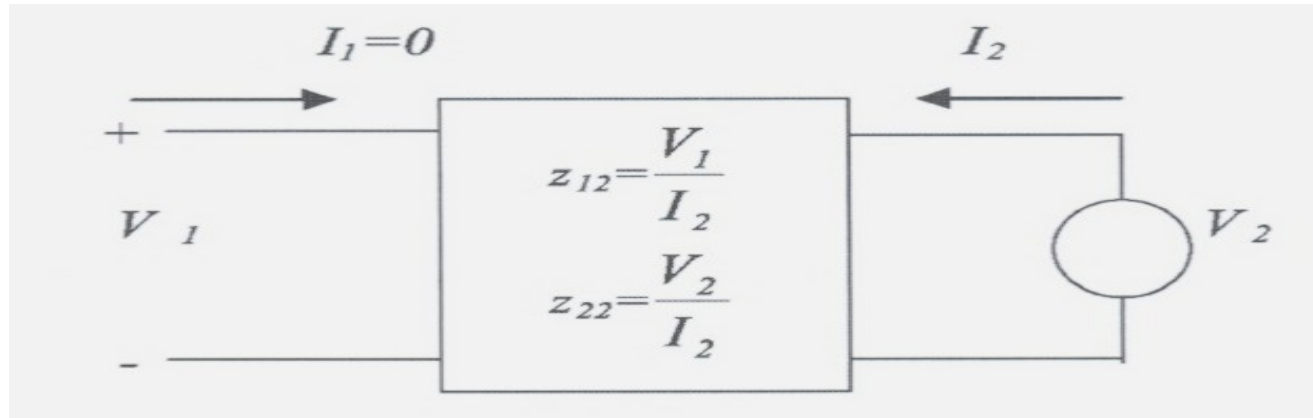- Case –II Assuming the input of the same two port to be open circuit,  $I_1 = 0$




$$z_{12} = \frac{V_1}{I_2} \quad \Big| \quad I_1 = 0$$

Reverse Transfer impedance with the input port open circuit

$$z_{22} = \frac{V_2}{I_2} \quad \Big| \quad I_1 = 0$$

output driving point impedance with the input port open circuit

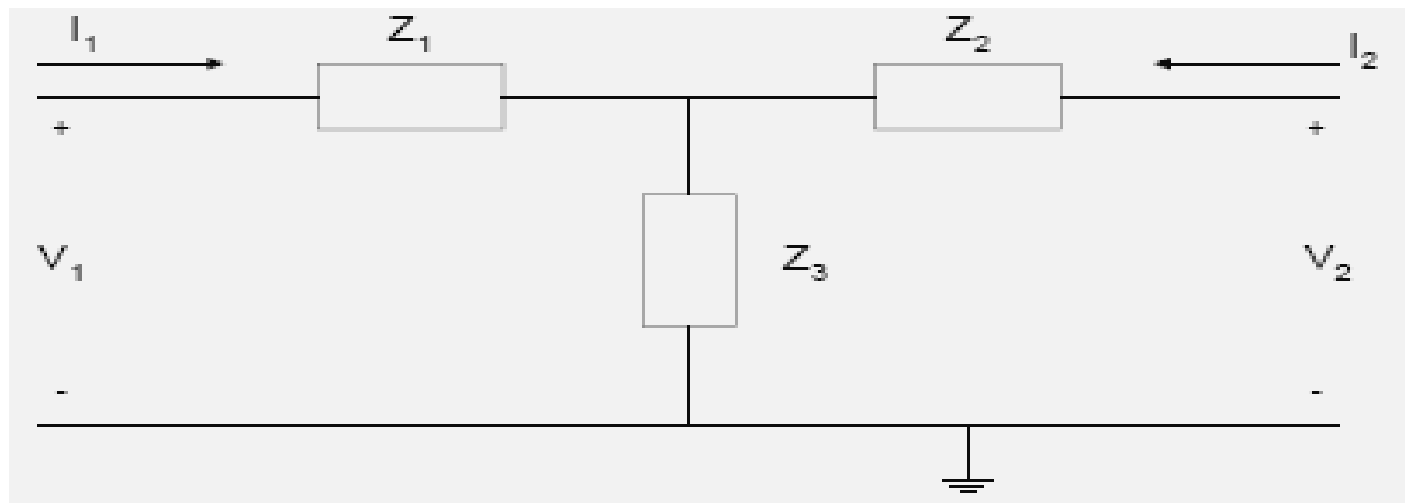For the T-network shown in Figure, find the z-parameters.



- Using KVL

$$V_1 = Z_1 I_1 + Z_3 (I_1 + I_2) = (Z_1 + Z_3) I_1 + Z_3 I_2$$

$$V_2 = Z_2 I_2 + Z_3 (I_1 + I_2) = (Z_3) I_1 + (Z_2 + Z_3) I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_1 + Z_3 & Z_3 \\ Z_3 & Z_2 + Z_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

and the z-parameters are

$$[Z] = \begin{bmatrix} Z_1 + Z_3 & Z_3 \\ Z_3 & Z_2 + Z_3 \end{bmatrix}$$

# Short Circuit Admittance ( $y$ ) parameter

- Useful for describing the network when impedance parameters may not be existed.
- This is solved by finding the second set of parameters by expressing the terminal current in term of the voltage.
- The input and output terminal current can be presented as follows:

$$(I_1, I_2) = f(V_1, V_2)$$


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[I] = [Y][V]$$


where admittance parameters of the system is  $y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

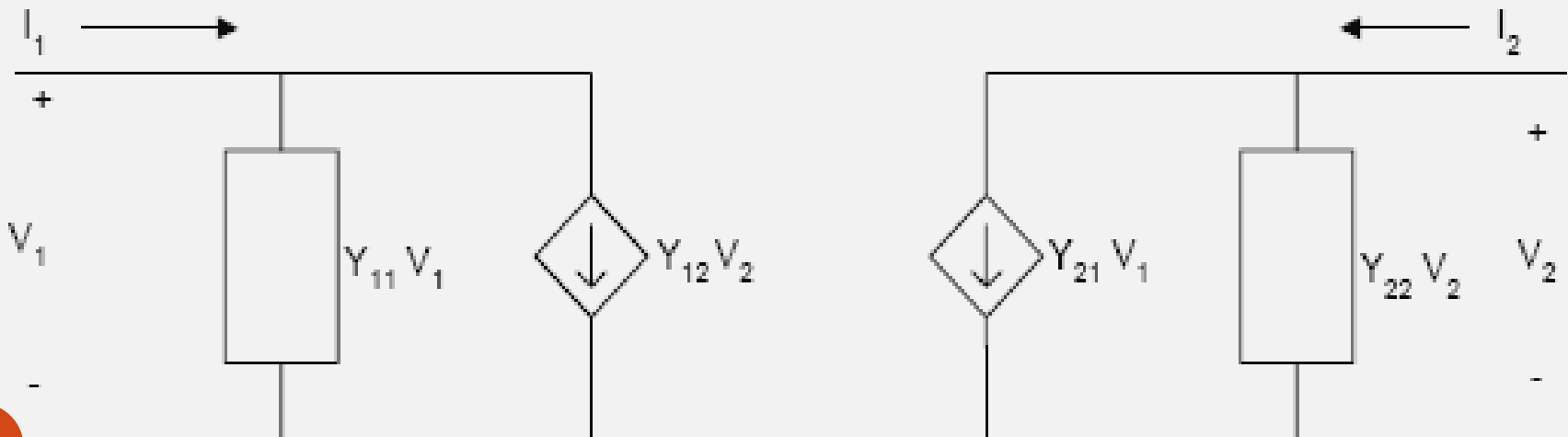

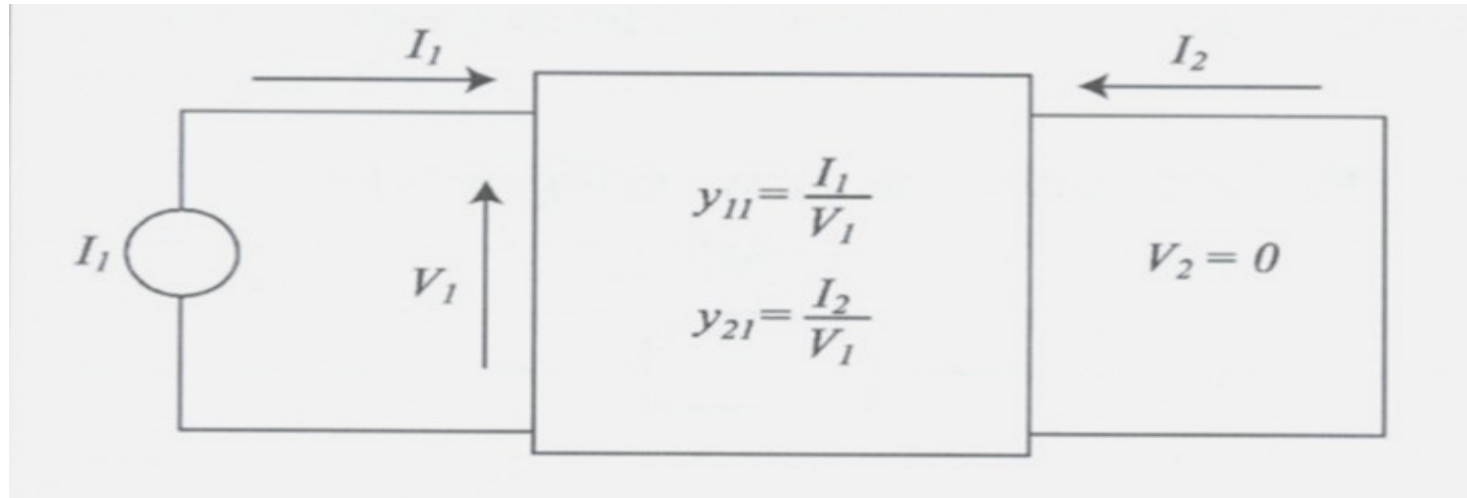- Case –I Assuming the output of the two port to be short circuit,  $V_2 = 0$



$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

Input driving point  
admittance


when port 2 is shorted.

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

Forward transfer admittance when  
port 2 is shorted.



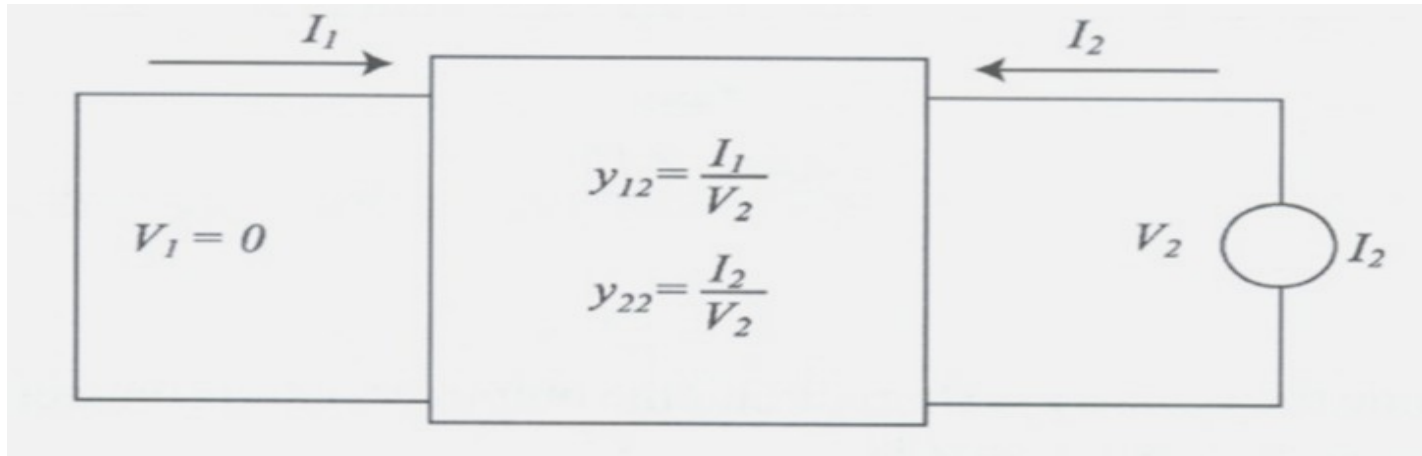- Case –I Assuming the input of the same two port to be short circuit,  $V_1 = 0$




$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

Reverse transfer admittance when port 1 is shorted.

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

output driving point admittance when port 1 is shorted.

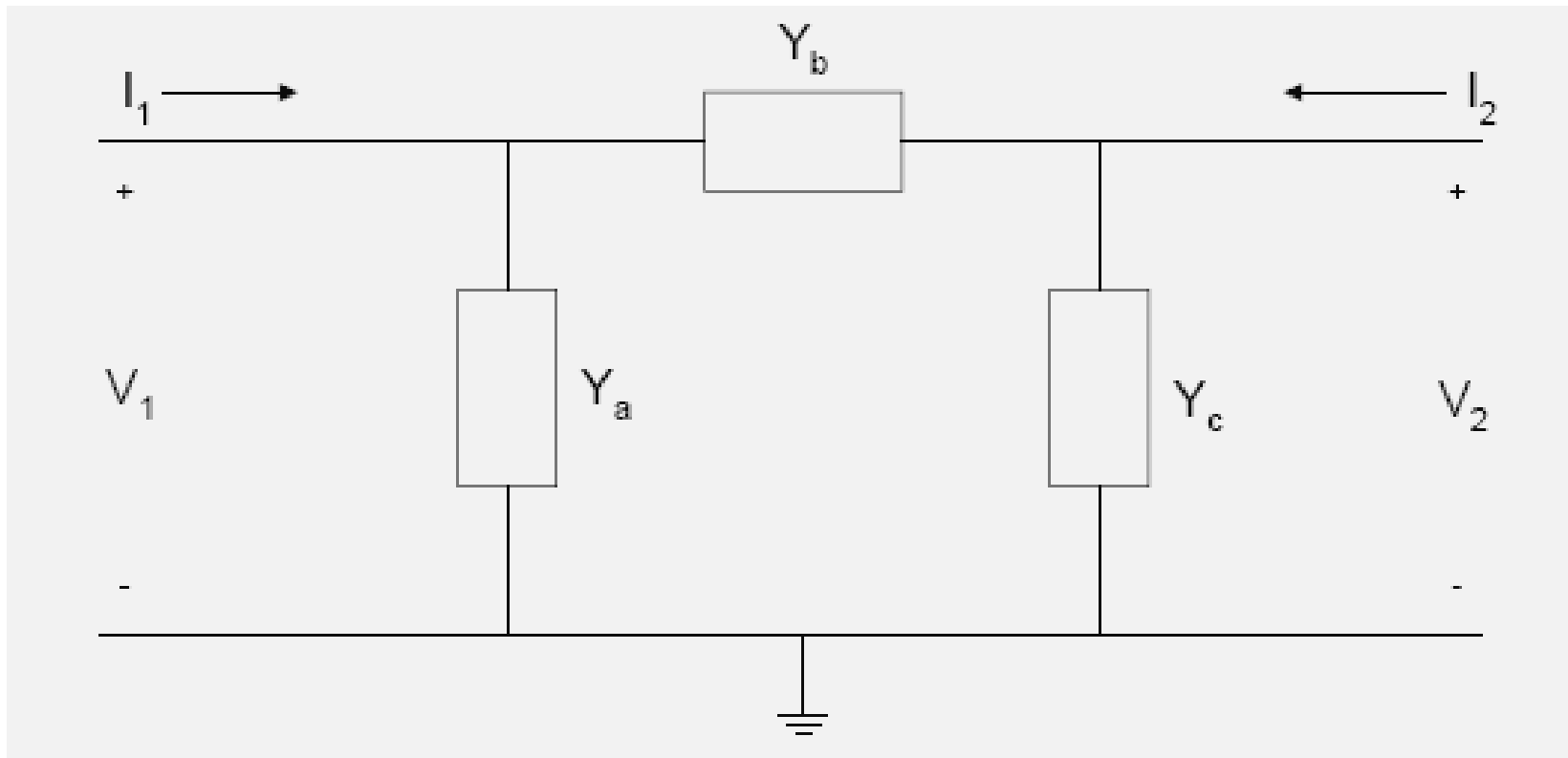Find the  $y$ -parameters of the pi ( $\pi$ ) network shown in Figure



Using KCL, we have

$$I_1 = V_1 Y_a + (V_1 - V_2) Y_b = V_1 (Y_a + Y_b) - V_2 Y_b$$

$$I_2 = V_2 Y_c + (V_2 - V_1) Y_b = -V_1 Y_b + V_2 (Y_b + Y_c)$$

$$[Y] = \begin{bmatrix} Y_a + Y_b & -Y_b \\ -Y_b & Y_b + Y_c \end{bmatrix}$$

# Transmission (T) or Chain or ABCD Parameter

- Used in Analysis of power transmission line.
- The input and output terminal current and voltage can be presented as follow:

$$(V_1, I_1) = f(V_2, -I_2)$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$


- where Transmission parameters of the system is  $T = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

- Equivalent circuit for this parameter is not possible.

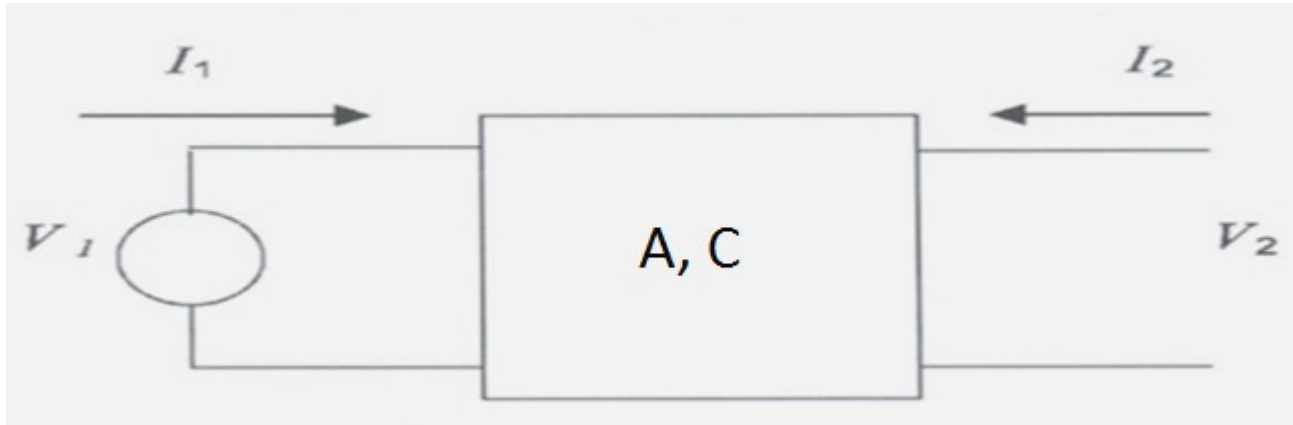- Case –I Assuming the output of the two port to be open circuit,  $I_2 = 0$



$$A = \frac{V_1}{V_2}$$

$$I_2 = 0$$


Open circuit Voltage ratio

$$C = \frac{I_1}{V_2}$$

$$I_2 = 0$$

Open circuit transfer admittance

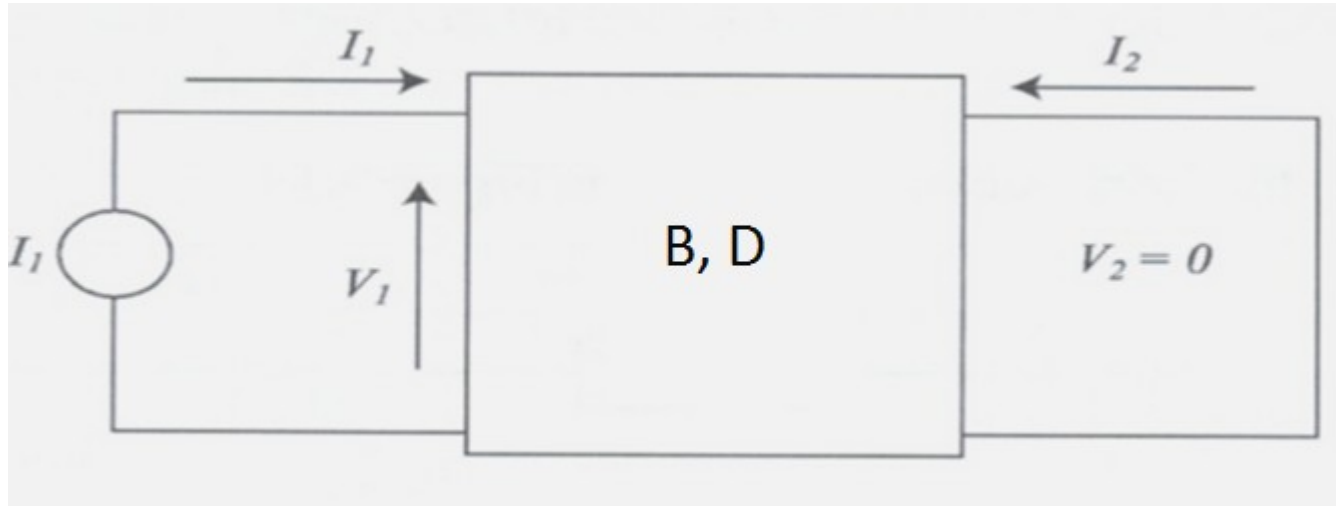- Case –II Assuming the output of the two port to be short circuit,  $V_2 = 0$



$$B = \frac{V_1}{-I_2} \quad \Big| \quad V_2 = 0$$

Negative short circuit transfer impedance

$$D = \frac{I_1}{-I_2} \quad \Big| \quad V_2 = 0$$

Negative short circuit current ratio