

Hybrid (H) Parameter

- The third possible set of parameters is known as hybrid parameters or h-parameters.
- The input and output terminal current and voltage can be presented as follow:

$$(V_1, I_2) = f(I_1, V_2)$$


$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$V_1 = h_{11}I_1 + h_{12}V_2$$


$$I_2 = h_{21}I_1 + h_{22}V_2$$

Where $\mathbf{h} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$

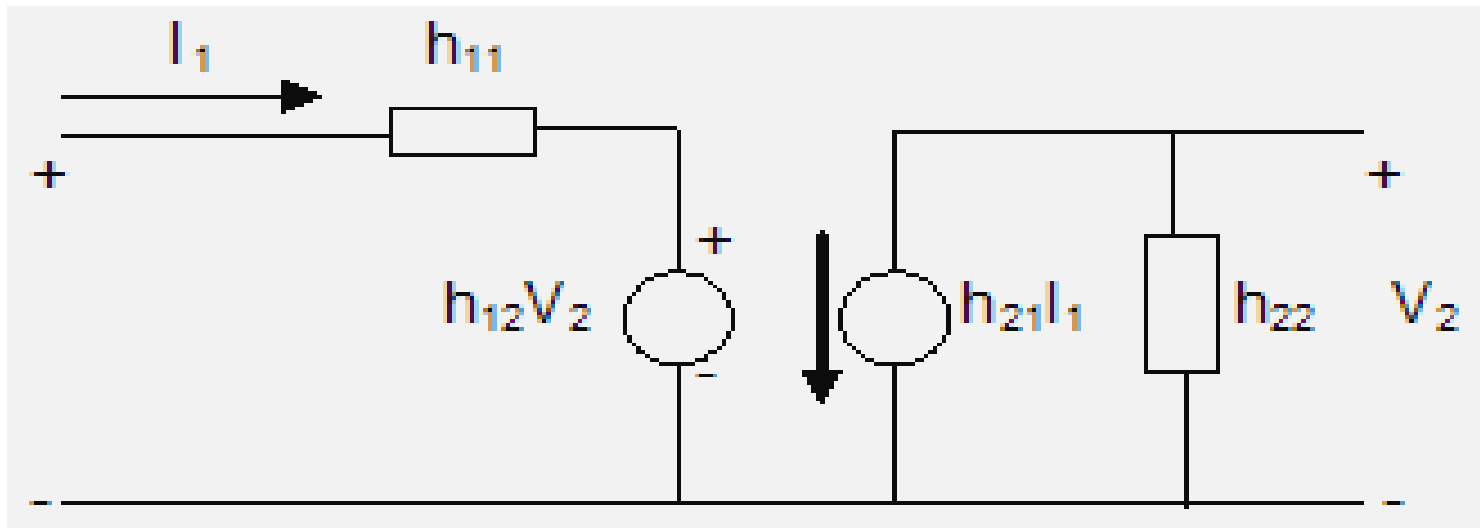These parameters are very useful in analyzing the transistor compare to the z-parameters and y-parameters.



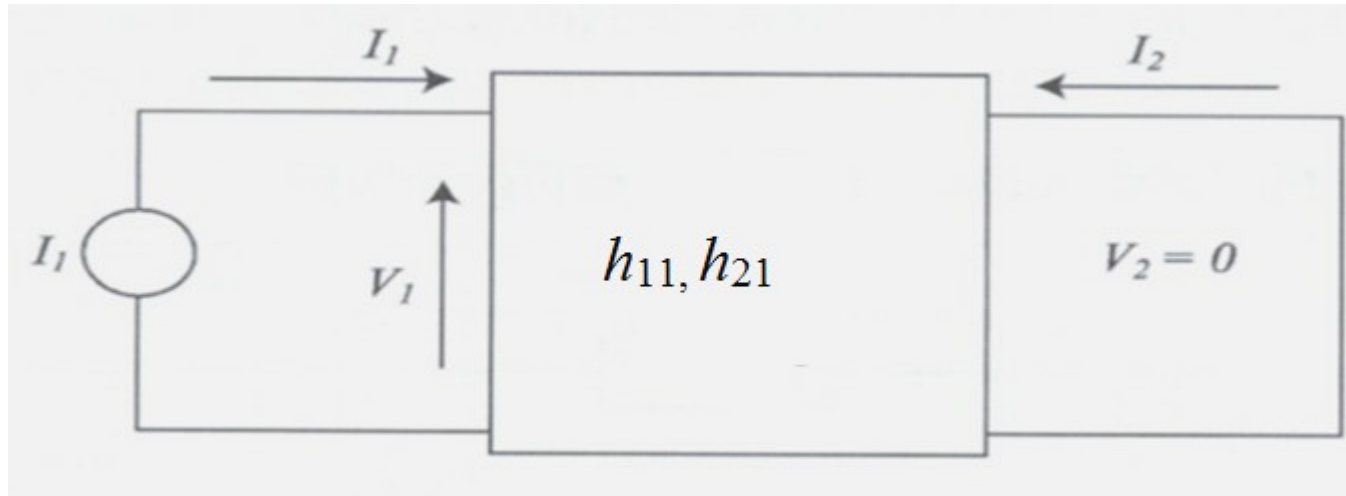Case –I Assuming the output of the two port to be short circuit, $V_2 = 0$




$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

short circuit input impedance

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

short circuit forward current gain

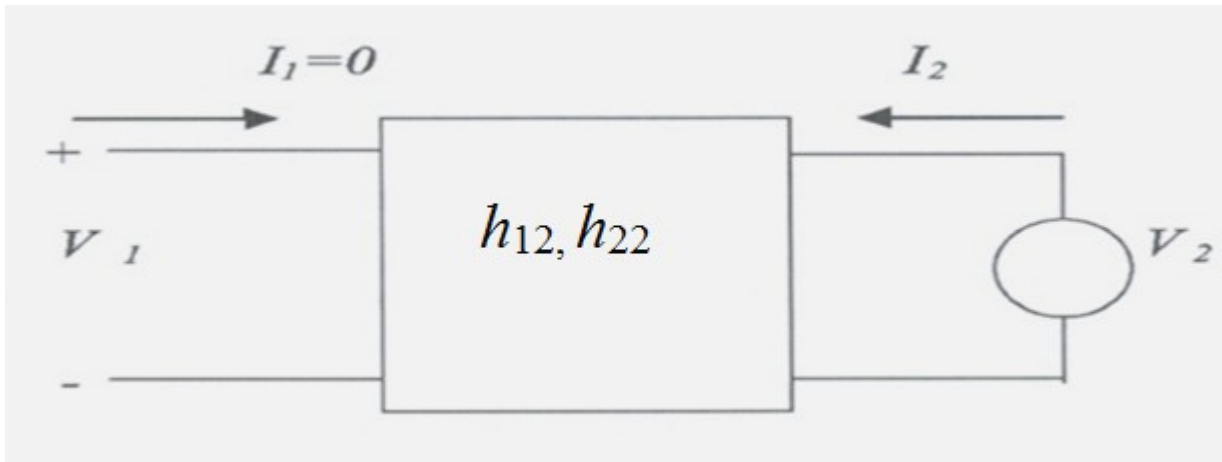Case –II Assuming the input of the same two port to be open circuit, $I_1 = 0$




$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

open circuit reverse voltage gain

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

open circuit output admittance

Circuit based on π network

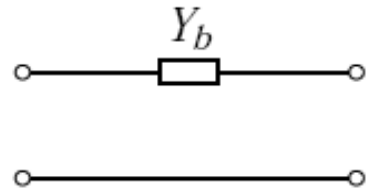


$$Y_b \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 1 & \frac{1}{Y_b} \\ 0 & 1 \end{bmatrix}$$




$$\begin{bmatrix} Y_c & 0 \\ 0 & Y_d \end{bmatrix}$$

does not exist

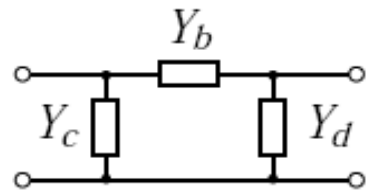

$$\begin{bmatrix} Y_b + Y_c & -Y_b \\ -Y_b & Y_b + Y_d \end{bmatrix}$$
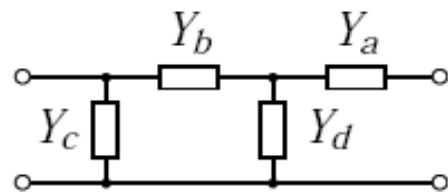
$$\frac{1}{Y_b} \begin{bmatrix} Y_b + Y_d & 1 \\ Y_b Y_c + Y_b Y_d + Y_c Y_d & Y_b + Y_c \end{bmatrix}$$




$$\frac{1}{Y_a + Y_b + Y_d} \begin{bmatrix} (Y_b + Y_c)(Y_a + Y_d) + Y_b Y_c & -Y_a Y_b \\ -Y_a Y_b & Y_a(Y_b + Y_d) \end{bmatrix}$$

$$\frac{1}{Y_a Y_b} \begin{bmatrix} Y_a(Y_b + Y_d) & Y_a + Y_b + Y_d \\ Y_a(Y_b Y_c + Y_b Y_d + Y_c Y_d) & (Y_b + Y_c)(Y_a + Y_d) + Y_b Y_c \end{bmatrix}$$

Circuit based on T network


Y

A

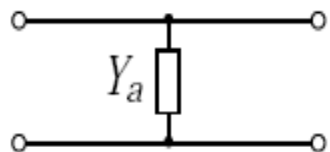


does not exist
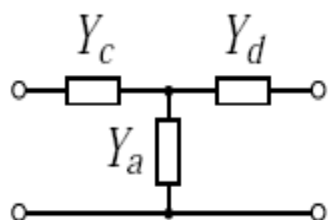
$$\begin{bmatrix} 1 & 0 \\ Y_a & 1 \end{bmatrix}$$



$$\frac{1}{Y_a + Y_c + Y_d} \begin{bmatrix} Y_c(Y_a + Y_d) & -Y_c Y_d \\ -Y_c Y_d & Y_d(Y_a + Y_c) \end{bmatrix}$$
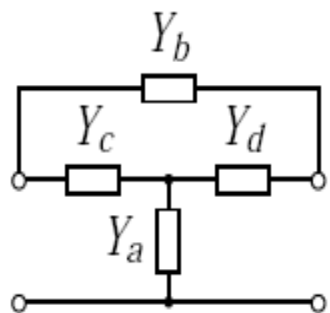
$$\frac{1}{Y_c Y_d} \begin{bmatrix} Y_d(Y_a + Y_c) & Y_a + Y_c + Y_d \\ Y_a Y_c Y_d & Y_c(Y_a + Y_d) \end{bmatrix}$$



$$\frac{1}{Y_a + Y_c + Y_d} \begin{bmatrix} (Y_c + Y_b)(Y_a + Y_d) + Y_b Y_c & -Y_b(Y_a + Y_c + Y_d) - Y_c Y_d \\ -Y_b(Y_a + Y_c + Y_d) - Y_c Y_d & (Y_a + Y_c)(Y_b + Y_d) + Y_b Y_d \end{bmatrix}$$

$$\frac{1}{Y_b(Y_a + Y_c + Y_d) + Y_c Y_d} \begin{bmatrix} (Y_a + Y_c)(Y_b + Y_d) + Y_b Y_d & Y_a + Y_c + Y_d \\ Y_a(Y_b Y_c + Y_b Y_d + Y_c Y_d) & (Y_b + Y_c)(Y_a + Y_d) + Y_b Y_c \end{bmatrix}$$

Y-Parameters into ABCD parameters

$$[Y] \quad (I_1, I_2) = f(V_1, V_2)$$

$$[I] = [Y][V]$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- (2)}$$

[T] or
[ABCD]

$$(V_1, I_1) = f(V_2, -I_2)$$

$$V_1 = AV_2 + B(-I_2) \quad \text{--- (3)}$$

$$I_1 = CV_2 + D(-I_2) \quad \text{--- (4)}$$

Aim is to express A, B, C, D in terms of Y_{11}, Y_{12}, Y_{21} & Y_{22}

Convert ① & ② in terms of ③ & ④
Equation ② can be written as

$$V_1 = -\frac{Y_{22}}{Y_{21}} V_2 + \frac{1}{Y_{21}} I_2$$

$$\text{or } V_1 = -\frac{Y_{22}}{Y_{21}} V_2 - \frac{1}{Y_{21}} (-I_2) \quad \text{--- (5)}$$

Comparing with eq (3) we have

$$A = -\frac{Y_{22}}{Y_{21}} \quad \& \quad B = -\frac{1}{Y_{21}}$$

By eliminating V_1 between eq ① & ② we get

$$I_1 = -\frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{21}} V_2 - \frac{Y_{11}}{Y_{21}} (-I_2) \quad \text{--- (6)}$$

By comparing it with eq (4) we have

$$C = -\frac{Y_{11}Y_{22} - Y_{12}Y_{21}}{Y_{21}} \quad \& \quad D = -\frac{Y_{11}}{Y_{21}}$$

Similarly we can get $[Y]$ in terms of $[A B C D]$

RELATIONSHIPS BETWEEN PARAMETER SETS (Contd.)

Z parameters in terms of Y parameters

$$(V_1, V_2) = f(I_1, I_2)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[V] = [Z][I]$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

$$(I_1, I_2) = f(V_1, V_2)$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[I] = [Y][V]$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (3)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (4)}$$

$$[V] = [Z][I]$$

$$[I] = [Y][V]$$

$$[Z]^{-1}[V] = [Z]^{-1}[Z][I] \\ = [I]$$

$$[I] = [Z]^{-1}[V] \\ = [Y][V]$$

$$\therefore [Y] = [Z]^{-1}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}^{-1}$$

$$I = [Y][V]$$

$$[Y^{-1}][I] = [V]^{-1}[I]$$

$$[Y^{-1}][I] = [V]$$

$$[Z][I] = [V]$$

$$\therefore [Y]^{-1} = [Z]$$

$$\& [Z] = [Y]^{-1}$$

$$\therefore [Z] = [Y]^{-1}$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1}$$

$$(V_1, V_2) = f(I_1, I_2)$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)} \quad \times Z_{22}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)} \quad \times Z_{12}$$

$$(I_1, I_2) = f(V_1, V_2)$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (3)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (4)}$$

$$V_1 Z_{22} = Z_{11} Z_{22} I_1 + Z_{12} Z_{22} I_2$$

$$V_2 Z_{12} = Z_{21} Z_{12} I_1 + Z_{12} Z_{22} I_2$$

$$V_1 Z_{22} - V_2 Z_{12} = I_1 (Z_{11} Z_{22} - Z_{21} Z_{12})$$

$$I_1 = \frac{Z_{22}}{Z_{11} Z_{22} - Z_{12} Z_{21}} V_1 - \frac{Z_{12}}{Z_{11} Z_{22} - Z_{12} Z_{21}} V_2$$

$$I_1 = \frac{Z_{22}}{\Delta Z} V_1 + \frac{-Z_{12}}{\Delta Z} V_2$$

Comparing with eq (3)

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

we have

$$Y_{11} = \frac{Z_{22}}{\Delta Z} \quad \text{where } \Delta Z = Z_{11}Z_{22} - Z_{12}Z_{21}$$

$$Y_{12} = -\frac{Z_{12}}{\Delta Z}$$

Similarly by eliminating I_1 between (1) & (11)
we get

$$Y_{21} = -\frac{Z_{21}}{\Delta Z}$$

$$Y_{22} = \frac{Z_{11}}{\Delta Z}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{Z_{22}}{\Delta Z} & -\frac{Z_{12}}{\Delta Z} \\ -\frac{Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{bmatrix} \quad \text{or } [Y] = \frac{1}{\Delta Z} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix}$$
$$\text{or } [Y] = [Z]^{-1}$$

$$b_{21} = \frac{1}{z_{12}} = -\frac{\Delta y}{y_{12}} = \frac{a_{21}}{\Delta a} = \frac{h_{22}}{h_{12}} = -\frac{g_{11}}{g_{12}}$$

$$b_{22} = \frac{z_{11}}{z_{12}} = \frac{y_{22}}{y_{12}} = \frac{a_{11}}{\Delta a} = \frac{\Delta h}{h_{12}} = -\frac{1}{g_{12}}$$

$$h_{11} = \frac{\Delta z}{z_{22}} = \frac{1}{y_{11}} = \frac{a_{12}}{a_{22}} = \frac{b_{12}}{b_{11}} = \frac{g_{22}}{\Delta g}$$

$$h_{12} = \frac{z_{12}}{z_{22}} = -\frac{y_{12}}{y_{11}} = \frac{\Delta a}{a_{22}} = \frac{1}{b_{11}} = -\frac{g_{12}}{\Delta g}$$

$$h_{21} = -\frac{z_{21}}{z_{22}} = \frac{y_{21}}{y_{11}} = -\frac{1}{a_{22}} = -\frac{\Delta b}{b_{11}} = -\frac{g_{21}}{\Delta g}$$

$$h_{22} = \frac{1}{z_{22}} = \frac{\Delta y}{y_{11}} = \frac{a_{21}}{a_{22}} = \frac{b_{21}}{b_{11}} = \frac{g_{11}}{\Delta g}$$

$$g_{11} = \frac{1}{z_{11}} = \frac{\Delta y}{y_{22}} = \frac{a_{21}}{a_{11}} = \frac{b_{21}}{b_{22}} = \frac{h_{22}}{\Delta h}$$

$$g_{12} = -\frac{z_{12}}{z_{11}} = -\frac{y_{12}}{y_{22}} = -\frac{\Delta a}{a_{11}} = -\frac{1}{b_{22}} = -\frac{h_{12}}{\Delta h}$$

$$g_{21} = \frac{z_{21}}{z_{11}} = -\frac{y_{21}}{y_{22}} = \frac{1}{a_{11}} = \frac{\Delta b}{b_{22}} = -\frac{h_{21}}{\Delta h}$$

$$g_{22} = \frac{\Delta z}{z_{11}} = \frac{1}{y_{22}} = \frac{a_{12}}{a_{11}} = \frac{b_{12}}{b_{22}} = \frac{h_{11}}{\Delta h}$$

$$\Delta z = z_{11}z_{22} - z_{12}z_{21}$$

$$\Delta y = y_{11}y_{22} - y_{12}y_{21}$$

$$\Delta a = a_{11}a_{22} - a_{12}a_{21}$$

$$\Delta b = b_{11}b_{22} - b_{12}b_{21}$$


$$\Delta h = h_{11}h_{22} - h_{12}h_{21}$$

$$\Delta g = g_{11}g_{22} - g_{12}g_{21}$$

INTERCONNECTION OF TWO-PORT NETWORKS

Three ways that two ports are interconnected:


* Parallel

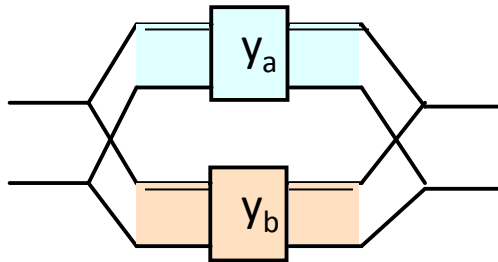

Y parameters

$$[y] = [y_a] + [y_b]$$


* Series

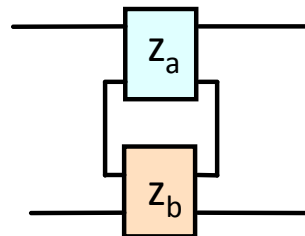

Z parameters

$$[z] = [z_a] + [z_b]$$

* Cascade

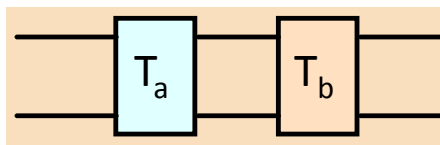


ABCD parameters


$$[T] = [T_a] [T_b]$$

Interconnections permit the description of complex systems in terms of simpler components or subsystems

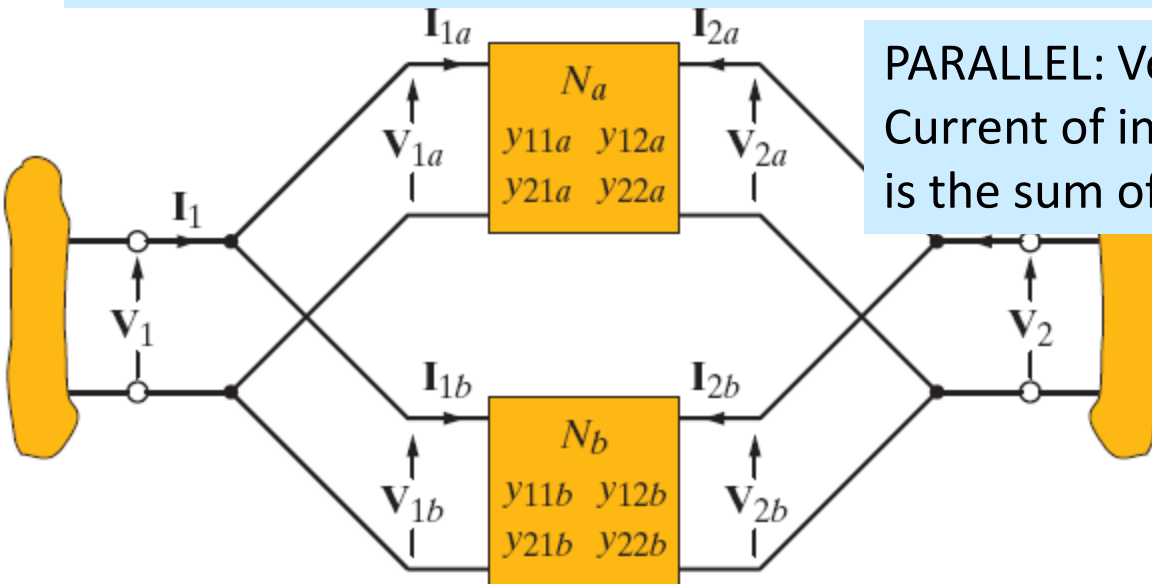
The basic interconnections to be considered are: *parallel*, *series* and *cascade*



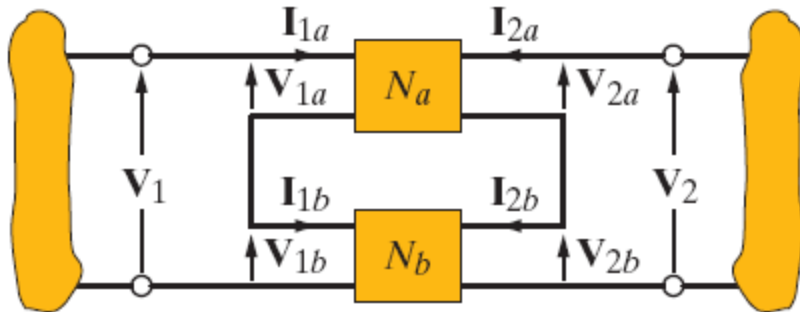PARALLEL: Voltages are the same.
Current of interconnection is the sum of currents




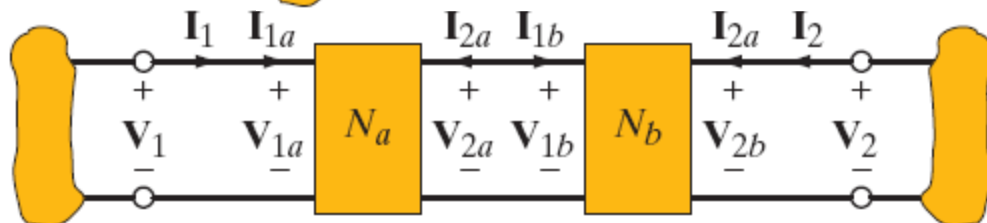
SERIES: Currents are the same.
Voltage of interconnection is the sum of voltages



CASCADE:
Output of first subsystem acts as input for the second

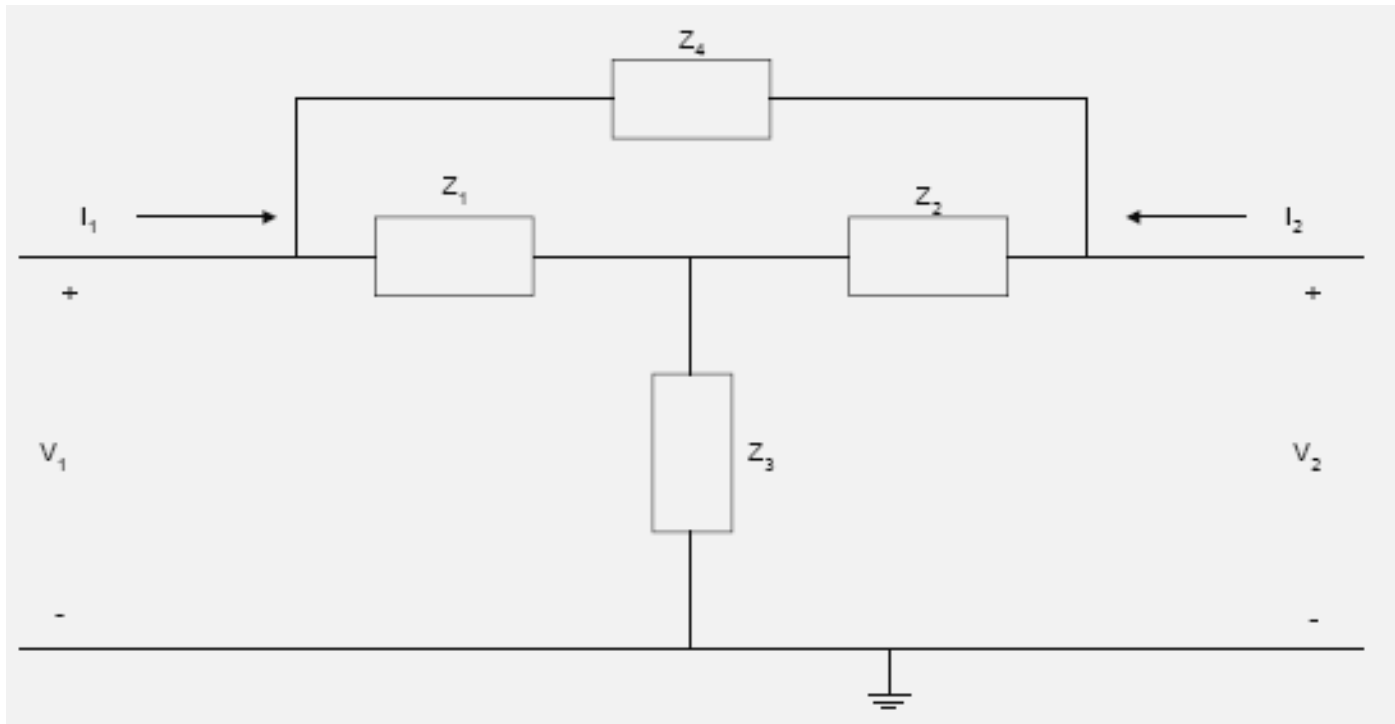Find the equivalent y -parameters for the bridge T-network



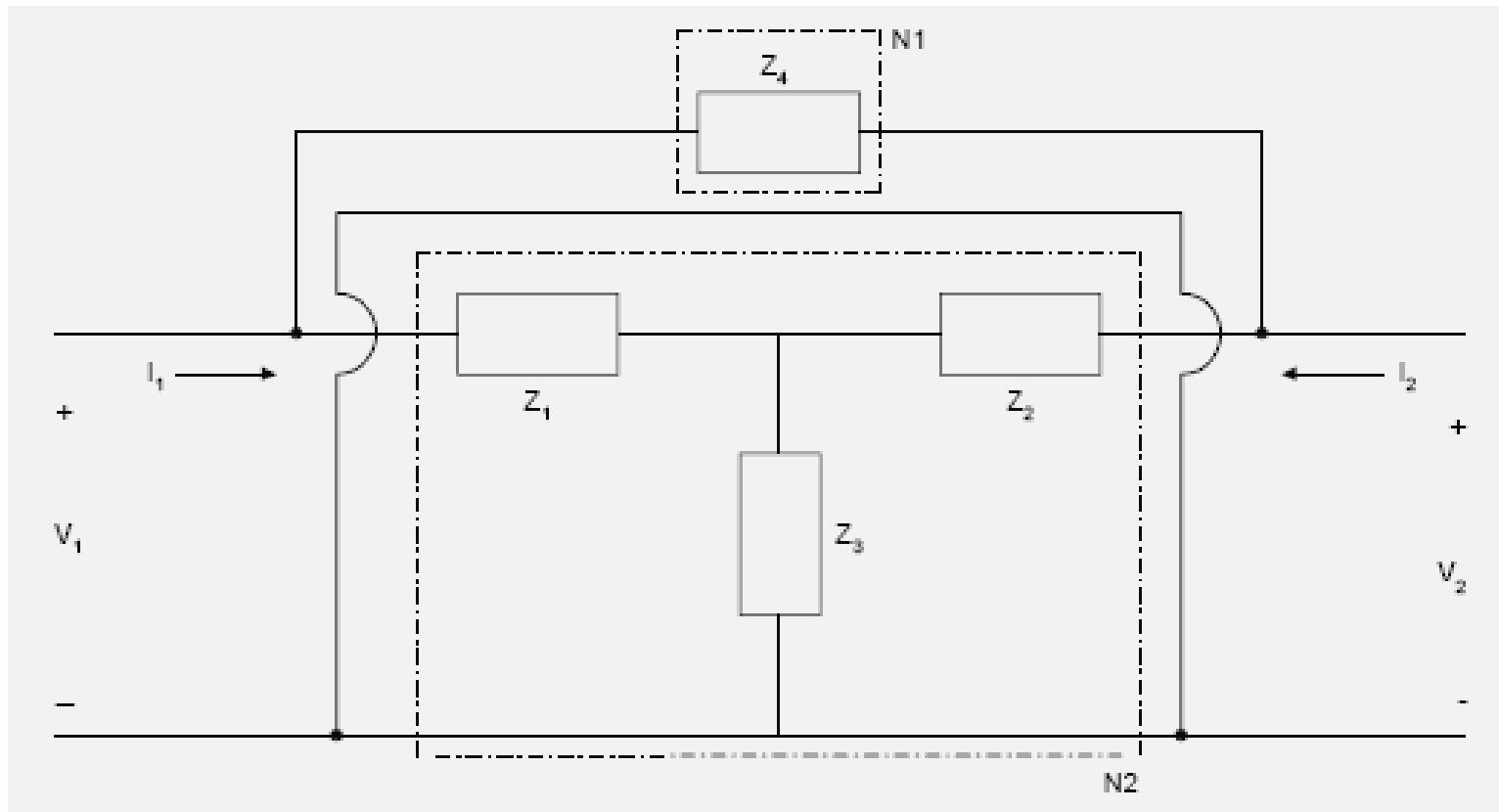

the z-parameters of network N2 are

$$[Z] = \begin{bmatrix} Z_1 + Z_3 & Z_3 \\ Z_3 & Z_2 + Z_3 \end{bmatrix}$$

We can convert the z-parameters to y-parameters

$$y_{11} = \frac{Z_2 + Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}$$

$$y_{12} = \frac{-Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}$$

$$y_{21} = \frac{-Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}$$

$$y_{22} = -\frac{Z_1 + Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}$$

$$y_{11} = \frac{1}{Z_4}$$

$$y_{12} = -\frac{1}{Z_4}$$

$$y_{21} = -\frac{1}{Z_4}$$

$$y_{22} = \frac{1}{Z_4}$$

$$y_{11eq} = \frac{1}{Z_4} + \frac{Z_2 + Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}$$

$$y_{12eq} = -\frac{1}{Z_4} - \frac{Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}$$

$$y_{21eq} = -\frac{1}{Z_4} - \frac{Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}$$

$$y_{22eq} = \frac{1}{Z_4} + \frac{Z_1 + Z_3}{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}$$

SERIES PARALLEL CONNECTION


I/P ports are in series
O/P ports are in parallel

$$I_1 = I_{1a} = I_{1b}$$

$$V_1 = V_{1a} + V_{1b}$$

$$V_2 = V_{2a} = V_{2b}$$

$$I_2 = I_{2a} + I_{2b}$$

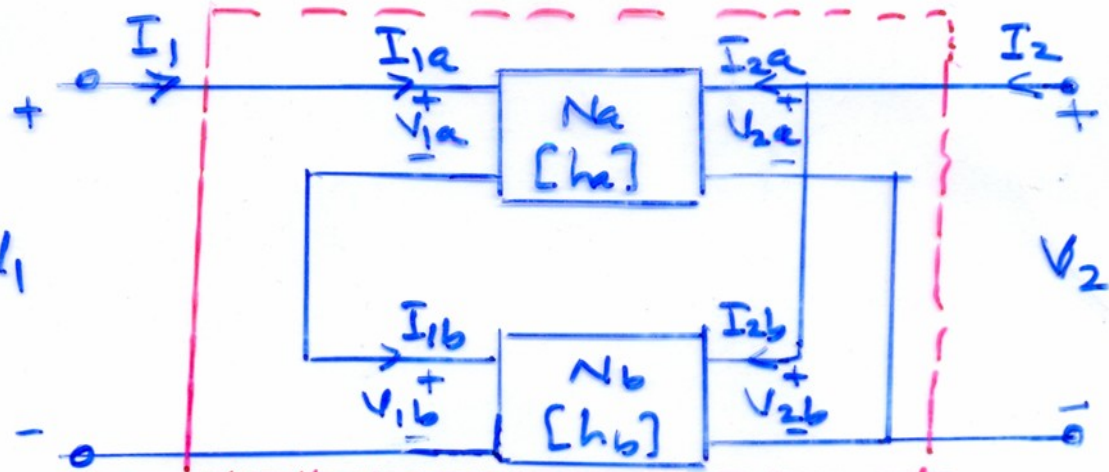

Series - Parallel Connection
of Two two-port Networks

$$\begin{bmatrix} V_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} h_{11b} & h_{12b} \\ h_{21b} & h_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ V_{2b} \end{bmatrix}$$

and

$$\begin{bmatrix} V_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} h_{11a} & h_{12a} \\ h_{21a} & h_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ V_{2a} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ I_{2a} \end{bmatrix} + \begin{bmatrix} V_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} h_{11a} & h_{12a} \\ h_{21a} & h_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ V_{2a} \end{bmatrix} + \begin{bmatrix} h_{11b} & h_{12b} \\ h_{21b} & h_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ V_{2b} \end{bmatrix}$$

$$= \begin{bmatrix} h_{11a} & h_{12a} \\ h_{21a} & h_{22a} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} h_{11b} & h_{12b} \\ h_{21b} & h_{22b} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$= \left(\begin{bmatrix} h_{11a} & h_{12a} \\ h_{21a} & h_{22a} \end{bmatrix} + \begin{bmatrix} h_{11b} & h_{12b} \\ h_{21b} & h_{22b} \end{bmatrix} \right) \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$= \begin{bmatrix} h_{11a} + h_{11b} & h_{12a} + h_{12b} \\ h_{21a} + h_{21b} & h_{22a} + h_{22b} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$h_{11} = h_{11a} + h_{11b}$$

$$h_{12} = h_{12a} + h_{12b}$$

$$h_{21} = h_{21a} + h_{21b}$$

$$h_{22} = h_{22a} + h_{22b}$$

The overall h-parameter matrix for Series parallel connected two port networks is simply the sum of h-parameter matrices of each individual two-port network connected in Series parallel. Parallel-Series $[g] = [g_a] + [g_b]$

* Series-Series or Series

$$[Z] = [Z_a] + [Z_b]$$


* Parallel-Parallel or Parallel

$$[Y] = [Y_a] + [Y_b]$$

* Cascade or Tandem

$$[T] = [T_a] \times [T_b]$$

CASCADE CONNECTIONS

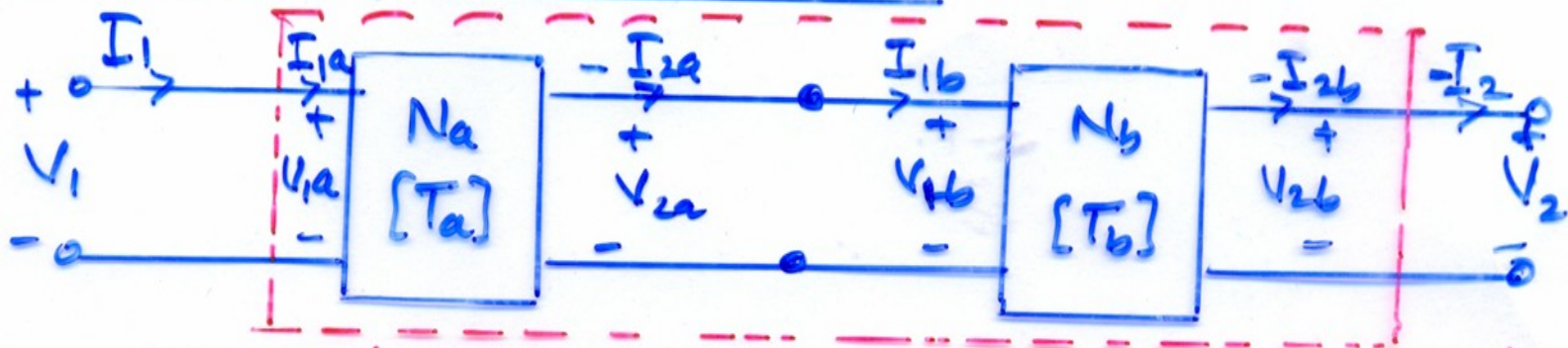

Cascade Connection of Two 2-port Networks

output port of one becomes the input port of the second.

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} \quad \& \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

now $I_1 = I_{1a}$

$-I_{2a} = I_{1b}$

$I_{2b} = I_2$

$V_1 = V_{1a}$

$V_{2a} = V_{1b}$

$V_{2b} = V_2$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix}$$

$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$= \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

$$A = A_a A_b + B_a C_b$$

$$B = A_a B_b + B_a D_b$$

$$C = C_a A_b + D_a C_b$$

$$D = C_a B_b + D_a D_b$$

$$\text{or } [T] = [T_a] \times [T_b]$$

The overall T-parameter matrix for cascade connected two-port networks is simply the matrix product of the T-parameter matrices of each individual two port network in cascade.


Similarly for inverse transmission parameters

$$[T'] = [T'_b][T'_a]$$

TWO PORT PARAMETERS

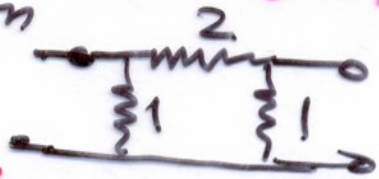1. Find 'h' parameters in terms of z-parameters
2. Find Y parameters in terms of z-parameters
3. Obtain the relationship between z-parameters & ABCD parameters
4. Two networks are connected in parallel. Find the 'Y' parameters of overall network
5. Find ABCD parameters in terms of z-parameters
6. Find Symmetrical & Reciprocal conditions for 'Y' parameters
7. Find ABCD parameters in terms of 'h' parameters
8. Derive equivalent parameters in terms of ABCD parameters for a Cascade Connection of 2-port n/w.


Two identical sections of n/w shown are connected in parallel. Find 'Y' parameters of resulting n/w.




For the n/w shown find Z-parameters




Find Z parameters of the network shown

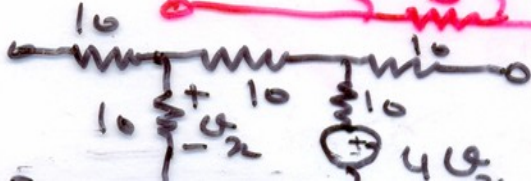

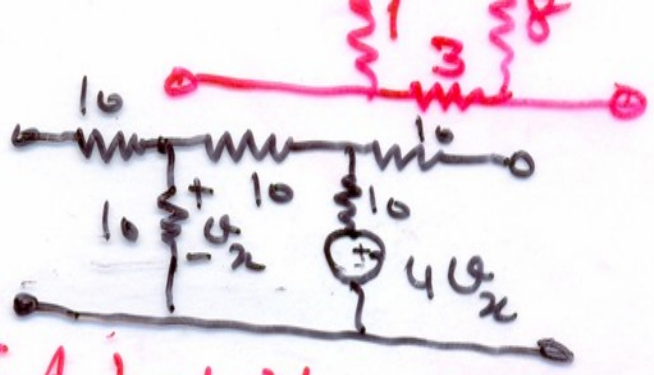
Z-parameters
 • Find Z parameters of the network shown



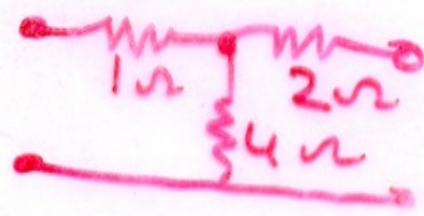
• For the n/w shown find hybrid parameters & transmission parameters




equivalent T & Π n/ws
 circuit shown

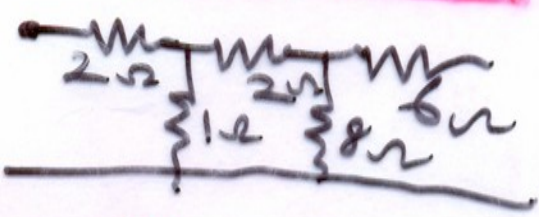

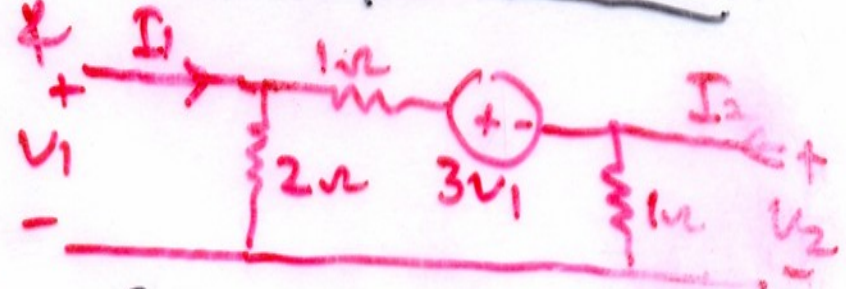• Determine Z-parameters & Y parameters of the n/w shown.



• ABCD parameters of the n/w shown

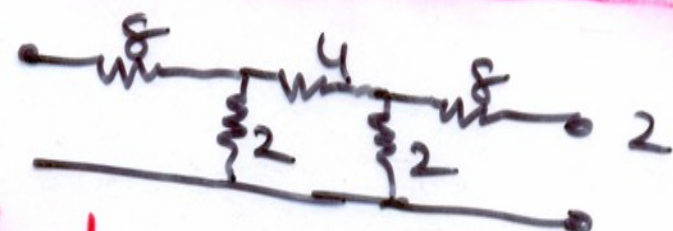

• Find Y-parameters of the n/w shown.



REVISION

- Z-parameters are also called open ckt parameters (T/F)
- Y-parameters are also called short ckt parameters
- ABCD parameters are also called Transmission (T/F) parameters or T-parameters (T/F)

$$[Z] = [Y]^{-1} \quad (T/F); \quad \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [Z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[Y] = [Z]^{-1} \quad (T/F);$$

$$\begin{bmatrix} 2 & 4 \\ 3 & 8 \end{bmatrix}^{-1} = \frac{1}{4} \begin{bmatrix} 8 & -4 \\ -3 & 2 \end{bmatrix} \quad [T/F]$$

$$V_1 = 2 I_1 + 3 I_2$$

$$V_2 = 4 I_1 + 8 I_2$$

$$Z_{11} = \quad \quad \quad Z_{12} =$$

$$Z_{22} = \quad \quad \quad Z_{21} =$$

$$V_1 = 3V_2 + 6(-I_2)$$

$$I_1 = 4V_2 + 5(-I_2)$$

$$A =$$

$$B =$$

$$C =$$

$$D =$$

Home work

Find out Z & Y parameters for which A, B, C, D are known above.

'h' or Hybrid parameters !


CONVERSION OF PARAMETERS [SUMMARY]

$$\Delta x = x_{11}x_{22} - x_{12}x_{21}$$

Parameter

In terms of

	Z		Y		T
Z	$\begin{matrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{matrix}$		$\begin{matrix} \frac{y_{22}}{\Delta y} & -\frac{y_{12}}{\Delta y} \\ -\frac{y_{21}}{\Delta y} & \frac{y_{11}}{\Delta y} \end{matrix}$		$\begin{matrix} \frac{A}{C} & \frac{\Delta T}{C} \\ \frac{1}{C} & \frac{D}{C} \end{matrix}$
Y	$\begin{matrix} \frac{z_{22}}{\Delta z} & -\frac{z_{12}}{\Delta z} \\ -\frac{z_{21}}{\Delta z} & \frac{z_{11}}{\Delta z} \end{matrix}$		$\begin{matrix} y_{12} & y_{22} \\ y_{21} & y_{22} \end{matrix}$		$\begin{matrix} \frac{D}{B} & -\frac{\Delta T}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{matrix}$
T	$\begin{matrix} \frac{z_{11}}{z_{21}} \\ \frac{1}{z_{21}} \end{matrix}$	$\begin{matrix} \frac{\Delta z}{z_{21}} \\ \frac{z_{22}}{z_{21}} \end{matrix}$	$\begin{matrix} -\frac{y_{22}}{y_{21}} & -\frac{1}{y_{21}} \\ -\frac{\Delta y}{y_{21}} & -\frac{y_{11}}{y_{21}} \end{matrix}$		$\begin{matrix} A & B \\ C & D \end{matrix}$

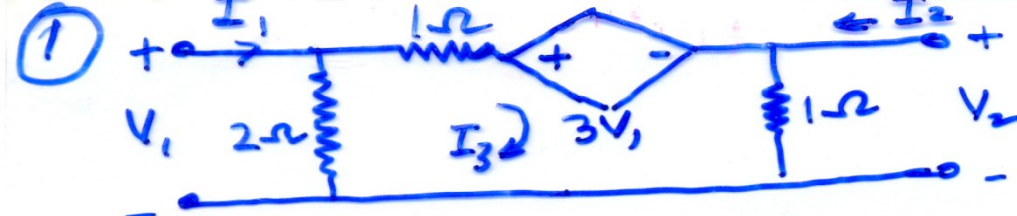

Apply KVL in three loops $[Y] = [Z]^{-1} = \begin{bmatrix} -\frac{3}{2} & -1 \\ 2 & 2 \end{bmatrix}$

Find Y & Z parameters for above ckt



Connected in Parallel.


Determine Y parameters



$$Y_A = [Z_A]^{-1} = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix}^{-1}$$

$$Y_A = Y_B$$
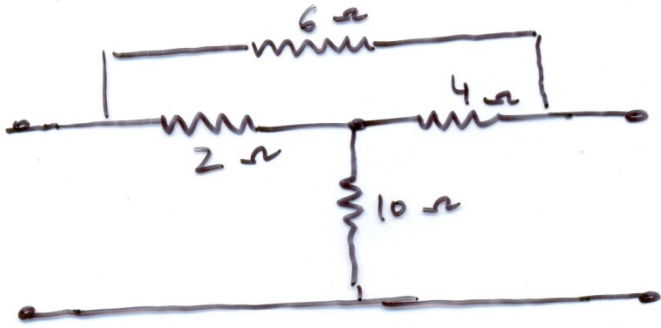
$$Y = \begin{bmatrix} 4/3 & -2/3 \\ -2/3 & 4/3 \end{bmatrix}$$



$$[Z] = \begin{bmatrix} \frac{35}{3} & \frac{32}{3} \\ \frac{32}{3} & \frac{38}{3} \end{bmatrix}$$

- Loop method
- Parallel networks
- Y-Δ conversion