

Synthesis of R-C Impedance /R-L Admittance Networks

Properties of R-C Impedance or R-L Admittance Networks

- 1. The poles and zeros lie on the negative real axis including origin of the complex s-plane.
- 2. The poles and zeros interlace (or alternate) along the negative real axis.
- 3. The residues of the poles must be real and positive.
- 4. The singularity nearest to or at the origin must be a pole.

Function $Z_{R-C}(s)$ or $Y_{R-L}(s) \rightarrow \infty$ with $s \rightarrow 0$

- 5. The singularity nearest to or at the minus infinity must be a zero.

Function $Z_{R-L}(s)$ or $Y_{R-C}(s) \rightarrow 0$ with $s \rightarrow \infty$

Synthesis of R-C Impedance /R-L Admittance Networks

- If the following represent $Z_{R-C}(s)$ or Y_{R-L} N/W

(a) $F(s) = \frac{(s+1)(s-3)}{[(s+4)(s+8)]}$ No (1)

(b) $F(s) = \frac{(s+2)(s+5)}{[s(s+1)]}$ No (2)

(c) $F(s) = \frac{s(s+8)}{[(s+1)(s+9)]}$ **No (4)**

(d) $F(s) = \frac{(s+1)(s+4)}{[s(s+2)(s+6)]}$ Yes

SYNTHESIS OF R-C IMPEDANCES OR R-L ADMITTANCES

Consider the following example.

$$F(s) = \frac{3(s + 2)(s + 4)}{s(s + 3)} \quad (11.48)$$

The partial fraction expansion of the remainder function is obtained as

$$F(s) = \frac{8}{s} + \frac{1}{s + 3} + 3 \quad (11.49)$$

where $F(\infty) = 3$. If $F(s)$ is an impedance $Z(s)$, it must be an *R-C* impedance and it is realized in the series Foster form in Fig. 11.16. On the other hand, if $F(s)$ represents an admittance, we realize $Y(s)$ as an *R-L* network in the parallel Foster form (Fig. 11.17).

Cont...

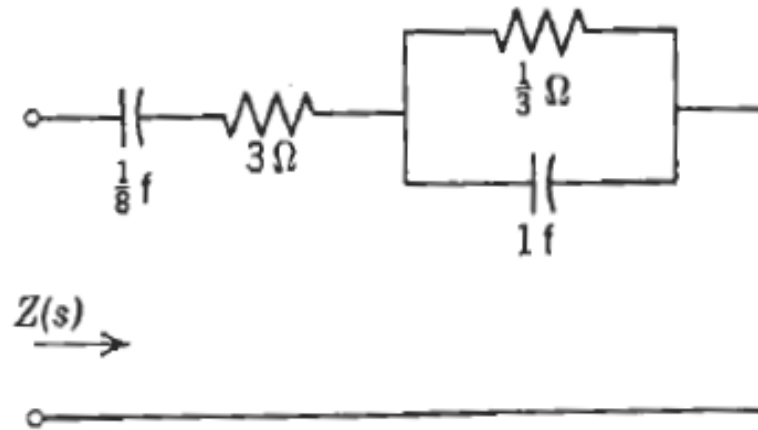


FIG. 11.16

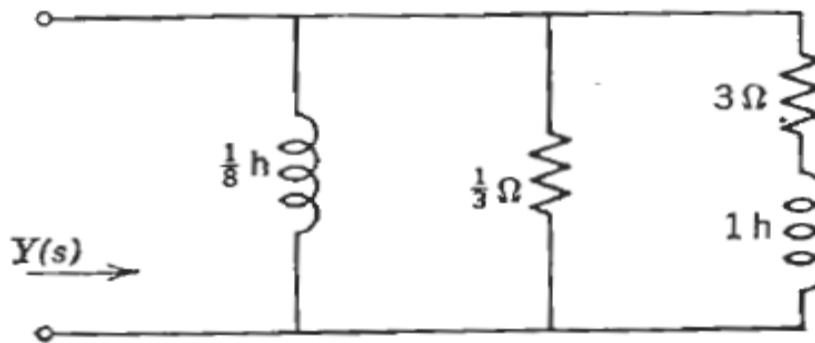


FIG. 11.17

Cont..

For example, the continued fraction expansion of $F(s)$ in Eq. 11.48 is

$$\begin{array}{r}
 s^2 + 3s \overline{) 3s^2 + 18s + 24} \quad (3) \\
 \underline{3s^2 + 9s} \\
 9s + 24 \overline{) s^2 + 3s} \quad \left(\frac{1}{9}s\right) \\
 \underline{\frac{1}{9}s \cdot 9s + 24} \quad (27) \\
 s^2 + \frac{8}{9}s \\
 \underline{\frac{1}{3}s \cdot 9s + 24} \quad (27) \\
 9s \\
 \underline{24 \cdot \frac{1}{3}s} \quad (s/72) \\
 \frac{1}{3}s \\
 \underline{\hspace{1em}}
 \end{array}$$

Cont..

If $F(s)$ is an impedance $Z(s)$, the resulting network is shown in Fig. 11.18. If $F(s)$ is an admittance $Y(s)$, we have the R - L network of Fig. 11.19.

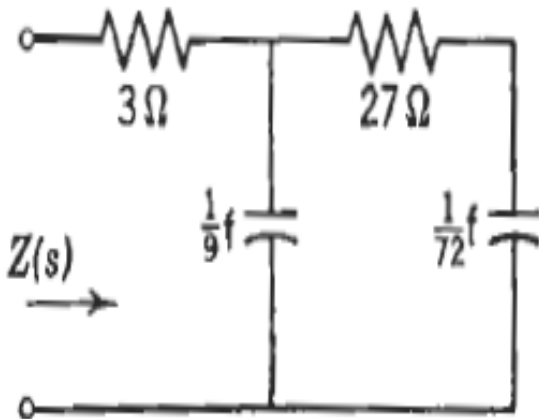


FIG. 11.18

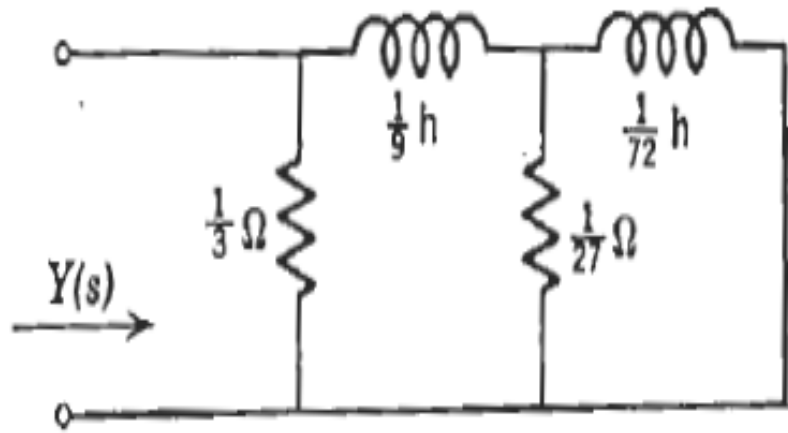


FIG. 11.19

PROPERTIES OF R - L IMPEDANCES AND R - C ADMITTANCES

The immittance that represents a series Foster R - L impedance or a parallel Foster R - C admittance is given as

$$F(s) = K_{\infty}s + K_0 + \frac{K_i s}{s + \sigma_i} + \cdots \quad (11.50)$$

The significant difference between an R - C impedance and an R - L impedance is that the partial fraction expansion term for the R - C “tank” circuit is $K_i/(s + \sigma_i)$; whereas, for the R - L impedance, the corresponding term must be multiplied by an s in order to give an R - L tank circuit consisting of a resistor in parallel with an inductor.

The properties of $R-L$ impedance or $R-C$ admittance functions can be derived in much the same manner as the properties of $R-C$ impedance functions. Without going into the derivation of the properties, the more significant ones are given in the following:

1. Poles and zeros of an $R-L$ impedance or $R-C$ admittance are located on the negative real axis, and they alternate.
2. The singularity nearest to (or at) the origin is a zero. The singularity nearest to (or at) $s = \infty$ must be a pole.
3. The residues of the poles must be real and *negative*.

Cont..

Because of the third property, a partial fraction expansion of an R - L impedance function would yield terms as

$$- \frac{K_i}{s + \sigma_i} \quad (11.51)$$

This does not present any trouble, however, because the term above does not represent an R - L impedance at all. To obtain the Foster form of an R - L impedance, we will resort to the following artifice. Let us first expand $Z(s)/s$ into partial fractions. If $Z(s)$ is an R - L impedance, we will state without proof here that the partial fraction expansion of $Z(s)/s$ yields positive residues.⁵ Thus, we have

$$\frac{Z(s)}{s} = \frac{K_0}{s} + K_\infty + \frac{K_i}{s + \sigma_i} + \dots \quad (11.52)$$