

Transfer Functions , Zeros of Transmission and Network Synthesis with 1 ohm Terminations

TRANSFER FUNCTIONS

- **Properties of Transfer Functions [$T(s)$]**
- (I) $T(s)$ is real for real s . This property is satisfied when $T(s)$ is a rational function with real coefficients.

(II)(a) $T(s)$ has no poles in the right half of s -plane

(b) There are no multiple poles on the $j\omega$ axis.

(c) If $T(s) = P(s) / Q(s)$, then the degree of numerator polynomial $P(s)$ cannot exceed the degree of denominator $Q(s)$ by more than unity.

(d) $Q(s)$ must be Hurwitz polynomial.

(III) Suppose $P(s)$ and $Q(s)$ are given in terms of even and odd parts as

$$P(s) = M_1(s) + N_1(s) = \text{even} + \text{odd} \text{ and}$$

$$Q(s) = M_2(s) + N_2(s) = \text{even} + \text{odd}$$

Properties of Transfer Functions (Contd)

$$\text{Then } T(s) = \frac{P(s)}{Q(s)} = \frac{M_1(s) + N_1(s)}{M_2(s) + N_2(s)} \quad \text{or}$$

$$T(j\omega) = \frac{P(j\omega)}{Q(j\omega)} = \frac{M_1(j\omega) + N_1(j\omega)}{M_2(j\omega) + N_2(j\omega)} \quad \text{which shows that Amplitude}$$

Response is an even function in ω and the phase response is an odd function in ω .

(Already discussed while doing Amplitude and phase responses)

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

- $V_2 / V_1 = z_{21} / z_{11}$

$$V_2 / V_1 = -y_{21} / y_{11}$$

Generally there are source and load impedances to be accounted for.

Properties of Transfer Functions (Contd)

- For two port networks ,

$$z_{12} = V_1 / I_2 \quad I_1=0 \quad \text{and} \quad z_{21} = V_2 / I_1 \quad \text{when} \quad I_2 = 0$$

$$V_2 / V_1 = z_{21} / z_{11} \quad (\text{in terms of open circuit impedances})$$

$$V_2 / V_1 = - y_{21} / y_{22} \quad (\text{in terms of short circuit admittances})$$

When the network is terminated at output port by a resistance R then the transfer impedance of the overall network is

$$Z_{21} = \frac{V_2}{I_1} = \frac{z_{21}R}{z_{22} + R} \quad (V_2 = -I_2 R)$$

$$Y_{21} = \frac{I_2}{V_1} = \frac{y_{21}G}{y_{22} + G} \quad (V_2 = -I_2 R)$$

Properties of Transfer Functions (Contd)

- When both the ports are terminated in resistors the voltage ratio transfer function V_2 / V_g is given by

$$\frac{V_2}{V_g} = \frac{z_{21}R_2}{(z_{11} + R_1)(z_{22} + R_2) - z_{21}z_{12}} \quad \text{where}$$

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

$$V_1 = V_g - I_1R_1$$

$$V_2 = -I_2R_2$$

similarly we can describe other transfer functions such as current ratio transfer functions in terms of open and short circuit parameters.

Specific Properties of Open-Circuit and Short-circuit Parameters

- I) The poles of $z_{21}(s)$ are also the poles of $z_{11}(s)$ and $z_{22}(s)$. However , not all the poles of $z_{11}(s)$ and $z_{22}(s)$ are the poles of $z_{21}(s)$.
- (II) The poles of $y_{12}(s)$ are also the poles of $y_{11}(s)$ and $y_{22}(s)$. However , not all the poles of $y_{11}(s)$ and $y_{22}(s)$ are the poles of $y_{12}(s)$

Example Π - network . Series branch 5F capacitor .Parallel branches 1/2 H and 1/3 H

The y-parameters for this Π - network are

$$y_{11}(s) = 2/s + 5s , \quad y_{22}(s) = 3/s + 5s , \quad y_{12}(s) = - 5s$$

It can be (seen that $y_{11}(s)$ and $y_{22}(s)$ have poles at $s = 0$ and at $s = \infty$, whereas $y_{12}(s)$ has pole only at $s = \infty$. Thus the property is verified.

(III) Suppose $y_{11}(s)$, $y_{22}(s)$ & $y_{12}(s)$ all have poles at $s=s_1$

Let residue of the poles at s_1 of the function $y_{11}(s)$ be k_{11} .

Let residue of the poles at s_1 of the function $y_{22}(s)$ be k_{22} .

Similarly, let the residue of the poles at s_1 of the function $y_{12}(s)$ be k_{12} .

General property of L-C , R-C ,or R-L two port networks is that

$$k_{11} k_{22} - k_{12}^2 \geq 0 \text{ This equation is known as RESIDUE CONDITION}$$

Specific Properties of Open-Circuit and Short-circuit Parameters

General property of L-C , R-C , or R-L two port networks is that

$k_{11} k_{22} - k_{12}^2 \geq 0$. This equation is known as RESIDUE CONDITION

Consider the same above example of L-C Π - network whose y-parameters are

$$y_{11}(s) = 2/s + 5s , \quad y_{22}(s) = 3/s + 5s , \quad y_{12}(s) = - 5s$$

(i) Corresponding to pole at $s=\infty$,

$$k_{11} = 5 , \quad k_{22} = 5 \quad \text{and} \quad k_{12} = - 5$$

$$k_{11} k_{22} - k_{12}^2 = (5)(5) - (- 5)^2 = 0 \quad \text{residue condition is satisfied.}$$

(ii) Corresponding to pole at $s=0$,

$$k_{11} = 2 , \quad k_{22} = 3 \quad \text{and} \quad k_{12} = - 0$$

$$k_{11} k_{22} - k_{12}^2 = (2)(3) - (0)^2 = 6 > 0 \quad \text{residue condition is satisfied}$$

Specific Properties of Open-Circuit and Short-circuit Parameters

- Ex : The open –circuit impedance functions of a typical network are

$$Z_{11} = \frac{4s^4 + 7s^2 + 1}{s(4s^2 + 3)}, \quad Z_{22} = \frac{s(2s^2 + 3)}{4s^2 + 3}, \quad Z_{21} = \frac{2s}{4s^2 + 3}$$

Show that the residue condition is satisfied at the poles at $s = \pm \sqrt{3}/2$, $s=0$, and at $s=\infty$

SOLUTION By partial fraction method we have

$$Z_{11} = s + 1/3s + (8/3) / 4(s^2 + 3/4)$$

$$Z_{22} = 0 + s/2 + (3s/2) / 4(s^2 + 3/4)$$

$$Z_{21} = 0 + 0 + 2s / 4(s^2 + 3/4)$$

- (i) **For the pole at $s = \pm \sqrt{3}/2$**

the residues of Z_{11} , Z_{22} and Z_{21} are

$$k_{11} = (1/4)(8/3) = 2/3, \quad k_{22} = (1/4)(3/20) = 3/8 \quad \text{and} \quad k_{12} = (1/4)(2) = 1/2$$

$$k_{11} k_{22} - k_{12}^2 = (2/3)(3/8) - (1/2)^2 = (1/4) - (1/4) = 0 \quad (\geq 0)$$

Specific Properties of Open-Circuit and Short-circuit Parameters

(ii) For the pole at $s=0$ the residues of Z_{11} , Z_{22} and Z_{21} are

$$k_{11} = 1/3, \quad k_{22} = 0 \text{ and } k_{12} = 0$$

$$k_{11} k_{22} - k_{12}^2 = (1/3) (0) - (0)^2 = 0 \quad (\geq 0)$$

(iii) For the pole at $s=\infty$ the residues of Z_{11} , Z_{22} and Z_{21} are

$$k_{11} = 1, \quad k_{22} = 1/2 \text{ and } k_{12} = 0$$

$$k_{11} k_{22} - k_{12}^2 = (1) (1/2) - (0)^2 = 1/2 \quad (\geq 0)$$

Zeroes of Transmission

- A zero of Transmission is a zero of transfer Function. At a zero of transmission, there is a zero output for an input of the same frequency.
- The zeroes of transmission of a 2-port network are defined as the frequencies at which the network results in zero output for a finite input.
- $s = 0$ means $\omega = 0$ Capacitor in Series behaves open circuit.
 $1 / cs$ or $1 / \omega c = \text{infinity}$
 $s = 0$ means $\omega = 0$ Inductance in parallel branch acts short cct.
 Ls or $L\omega = 0$ at $s/\omega = 0$

At $s = 0$ Single L in SHUNT or Single C in SERIES give zero output

Similarly at $S = \infty$, C in SHUNT arm or L in SERIES arm give Zero output

Zeroes of Transmission (Contd)

- L-C parallel combination in series arm

$z(s) = (1/cs) / (s^2 + 1/LC)$ gives zero output when $z(s) = \infty$
means open circuit.

$$s^2 = -1/LC$$

$$s = \pm j / \sqrt{LC}$$

Zeroes at $\pm j / \sqrt{LC}$

L-C Series combination in shunt arm

$$z(s) = Ls + 1/cs = (s^2 + 1/LC) / (1/L) s$$

= 0 at $s^2 = -1/LC$ or $s = \pm j / \sqrt{LC}$ zeros

Zeroes of Transmission (Contd)

- R-C parallel combination in series arm

$$z(s) = (1/C)/(s + 1/RC)$$
$$= \infty \text{ at } s = - (1 / RC) \quad \text{OC , } z = \infty$$

- R-C Series combination in shunt arm

$$z(s) = (s + 1/RC) / (1/R)s$$
$$= 0 \text{ at } s = - (1/RC) \quad \text{SC , } z(s) = 0$$

- R-L Series combination in parallel arm

$$z(s) = Ls + R = L\{s + R/L\}$$
$$= 0 \text{ at } s = - (R/L)$$

- R-L parallel combination in series arm

$$z(s) = (Rs) / (s + R/L)$$
$$= \infty \text{ at } s = - R/L \quad \text{OC , } z = \infty$$

Synthesis with 1 ohm termination

- 3. Identify $N(s)$ of $Y_{21}(s)$ as Even or odd. $Y_{21}(s) = 1/(S^3 + 2s^2 + 2s + 1)$

In this case Even .

- 4. $D(s)$ of $Y_{21}(s)$

Even part $2s^2 + 1$

Odd part $S^3 + 2s$

- 5. $Y_{21}(s) = 1/(S^3 + 2s)$

$y_{21}(s)$

----- = -----

$1 + (2s^2 + 1)/(S^3 + 2s)$ $1 + y_{22}(s)$

$y_{21}(s) = 1/(S^3 + 3s)$ and $y_{22}(s) = (2s^2 + 1)/(S^3 + 2s)$

- 6. Synthesize $y_{22}(s)$ in Ladder n /w to have three zeros at $s = \infty$

USE CAUER - I NETWORK

(Degree of Denominator higher , so invert .First element will be series element L and y_{22} . from 1 ohm side)