

# Synthesis of Transfer Functions of 2 –port n /w with 1 ohm terminated Load

- L –C Networks with zeros at  $S = 0$  or  $s = \infty$
- Steps to be followed
- 1. Identify no of zeros of transfer function and where they are located.  $S = 0$  or  $s = \infty$  .
- 2. Identify the circuit ( LP filter or HP filter ) or how L & C located.
- 3. Identify N(s) of  $Z_{21}(s) / Y_{21}(s)$  whether Even or Odd.
- 4. Segregate D(s) of  $Z_{21}(s) / Y_{21}(s)$  into Even and Odd parts .

5. Express  $Z_{21}(s) / Y_{21}(s)$  as

$$Z_{21} = \frac{z_{21}(s)}{1 + z_{22}(s)} \quad \text{or} \quad Y_{21} = \frac{y_{21}(s)}{1 + y_{22}(s)}$$

(Divide N(s) & D(s) By even part if N(s) is odd and by odd part if N(s) is even)

6. Synthesise  $z_{22}(s)$  or  $y_{22}(s)$  as Ladder network starting from 1 ohm side .
7. NOTE: If  $Z_{21}(s)$  has all ZEROS at  $S = \infty$  only then CAUER – I NETWORK.  
 If  $Z_{21}(s)$  has all ZEROS AT  $S = 0$  only then CAUER – II NETWORK

# Synthesis with 1 ohm termination

- $Z_{21}(s) = 1 / (S^3 + 3s^2 + 3s + 2)$
- 1. No of zeros of transmission = 3 and are at  $s = \infty$
- 2. Identify the L-C circuit as LP filter.

Circuit shown in next slide

# Synthesis with 1 ohm termination

- 3. Identify  $N(s)$  of  $Z_{21}(s)$  as Even or odd.  $Z_{21}(s) = 1/(S^3 + 3s^2 + 3s + 2)$

In this case Even .

- 4.  $D(s)$  of  $Z_{21}(s)$

Even part  $3s^2 + 2$

Odd part  $S^3 + 3s$

- 5.  $Z_{21}(s) = 1/(S^3 + 3s)$

$z_{21}(s)$

$$\frac{\text{-----}}{\text{-----}} = \frac{\text{-----}}{\text{-----}}$$

$$1 + (3s^2 + 2)/(S^3 + 3s) \quad 1 + z_{22}(s)$$

$$z_{21}(s) = 1/(S^3 + 3s) \quad \text{and} \quad z_{22}(s) = (3s^2 + 2)/(S^3 + 3s)$$

- 6. Synthesize  $z_{22}(s)$  in Ladder n /w to have three zeros at  $s = \infty$

USE CAUER - I NETWORK

(Degree of Denominator higher , so invert .First element will be shunt element C and  $y_{22}$ . from 1 ohm side )

# Synthesis with 1 ohm termination

- $Y_{21}(s) = 1 / (S^3 + 2s^2 + 2s + 1)$
- 1. No of zeros of transmission = 3 and are at  $s = \infty$
- 2. Identify the L-C circuit as LP filter.

## Synthesis with 1 ohm termination

- $Z_{21}(s) = S^3 / ( S^3 + 3s^2 + 4s + 2 )$
- 1. No of zeros of transmission = 3 and are at  $s = 0$
- 2. Identify the L-C circuit as HP filter.

Circuit shown in next slide

# Synthesis with 1 ohm termination

- 3. Identify  $N(s)$  of  $Z_{21}(s)$  as Even or odd.  $Z_{21}(s) = S^3 / (S^3 + 3s^2 + 4s + 2)$   
In this case Odd .

4.  $D(s)$  of  $Z_{21}(s)$

Even part  $3s^2 + 2$

Odd part  $S^3 + 4s$

5.  $Z_{21}(s) = S^3 / (3s^2 + 2)$

$$\frac{S^3}{1 + (S^3 + 4s)/(3s^2 + 2)} = \frac{z_{21}(s)}{1 + z_{22}(s)}$$

$$z_{21}(s) = S^3 / (3s^2 + 2) \quad \text{and} \quad z_{22}(s) = (S^3 + 4s) / (3s^2 + 2)$$

6. Synthesize  $z_{22}(s)$  in Ladder n /w to have three zeros at  $s = 0$

USE CAUER -II NETWORK  $z_{22}(s) = (4s + S^3) / (2 + 3s^2)$

(Degree of Denominator Lower , so invert .First element will be shunt element L and  $y_{22}$ . from 1 ohm side .  $Y_2$  ,  $z_3$  and  $y_4$  respectively )

## Synthesis with 1 ohm termination

- $Y_{21}(s) = S^3 / ( S^3 + 3s^2 + 3s + 2 )$
- 1. No of zeros of transmission = 3 and are at  $s = 0$
- 2. Identify the L-C circuit .

# Synthesis with 1 ohm termination

- 3. Identify  $N(s)$  of  $Y_{21}(s)$  as Even or odd.  $Y_{21}(s) = S^3 / (S^3 + 3s^2 + 3s + 2)$   
In this case Odd .

4.  $D(s)$  of  $Z_{21}(s)$

Even part  $3s^2 + 2$

Odd part  $S^3 + 3s$

5.  $Y_{21}(s) = S^3 / (3s^2 + 2)$

$$\frac{Y_{21}(s)}{1 + (S^3 + 3s) / (3s^2 + 2)} = \frac{Y_{21}(s)}{1 + Y_{22}(s)}$$

$$Y_{21}(s) = S^3 / (3s^2 + 2) \quad \text{and} \quad Y_{22}(s) = (S^3 + 3s) / (3s^2 + 2)$$

6. Synthesize  $y_{22}(s)$  in Ladder n /w to have three zeros at  $s = 0$

USE CAUER -II NETWORK  $Z_{22}(s) = (4s + S^3) / (2 + 3s^2)$

(Degree of Denominator Lower , so invert .First element will be series element C and  $y_{22}$ . from 1 ohm side .  $Z_2$  ,  $Y_3$  and  $Z_4$  respectively )



# Synthesis with 1 ohm termination

- $Y_{21}(s) = S^2 / (S^3 + 3s^2 + 4s + 2)$
- 1. Two zeros of transmission are at  $s = 0$  and one at  $s = \infty$
- 2. Identify the L-C circuit .This is neither as HP filter and nor as LP filter type circuit.
- 3. Identify N(s) of  $Z_{21}(s)$  as Even or odd.  $Z_{21}(s) = S^2 / (S^3 + 3s^2 + 4s + 2)$   
In this case Even

4. D(s) of  $Y_{21}(s)$

Even part  $3s^2 + 2$

Odd part  $S^3 + 4s$

$$S^2 / (S^3 + 4s)$$

$$y_{21}(s)$$

$$5. \quad Y_{21}(s) = \frac{S^2 / (S^3 + 4s)}{1 + (3s^2 + 2) / (S^3 + 4s)} = \frac{y_{21}(s)}{1 + y_{22}(s)}$$

$$y_{21}(s) = S^2 / (S^3 + 3s) \quad \text{and} \quad y_{22}(s) = (3s^2 + 2) / (S^3 + 4s)$$

$$6 \quad y_{22}(s) = (3s^2 + 2) / s(s^2 + 4s).$$

7. A parallel inductor gives a zero of transmission at  $s = 0$

# Synthesis with 1 ohm termination

- $Y_{22}(s) = (3s^2 + 2) / s(s^2 + 4s)$ .  
=  $(1/2s) + (5s/2) / (s^2 + 4)$   
=  $(1/2s) + 1 / [ (2/5)s + (8/5)s ]$   
=  $Y_A + Y_B$   
 $Y_A = (1/2s)$  represents an inductance of 2H  
 $Y_B = 1 / [ (2/5)s + (8/5)s ] = 1 / Z_B$   
or  $Z_B$  represents that it is a combination of two elements in series  
which give zeros at  $s = 0$  and at  $s = \infty$

These give an inductor of  $(2/5)$  H and a capacitor of  $(5/8)$  F  
overall network as looked from 1 ohm side is shown on the next slide.

# Synthesis with 1 ohm termination

- $Y_{21}(s) = 1 / (s^3 + 2s^2 + 2s + 1)$

T- n/w series branches  $L = (3/2)$  H and  $(1/2)$  H . Shunt branch  $(4/3)$  F

- $Y_{21}(s) = s^3 / (s^3 + 3s^2 + 3s + 2)$

T- n/w series branches  $C = (3/7)$  F and  $(3/2)$  F . Shunt branch  $(7/9)$  H

- $Z_{21}(s) = s / (s^3 + 3s^2 + 3s + 2)$

$(9/7)$  H in series with  $(7/6)$  F with  $(1/3)$ F capacitor in parallel with 1 ohm resistor