

Lecture 13

MOSFET

4.4 The MOSFET as an Amplifier and as a Switch

- We use MOSFET in the design of amplifier circuits since they act as a **voltage-controlled current source** in the Saturation region

- i.e. Changes in v_{GS} gives rise to changes in i_D

- How to achieve **Linear Amplification**? i.e. an amplifier whose output signal (i.e. the Drain current i_D) is linearly related to the input signal (i.e. v_{GS})

- We'll have to find a way around the highly non-linear (square-law) relationship of i_D to v_{GS} :

$$i_D = \frac{1}{2} k_n \frac{W}{L} [(v_{GS} - V_t)^2]$$

DC Biasing is a Fundamental Step towards designing a Linear MOSFET Amplifier

- The technique we use to obtain linear amplification out of a fundamentally non-linear device is called **DC biasing**

- Two Steps:

1. Bias the MOSFET to operate at a certain DC voltage V_{GS} and corresponding I_D and then,
2. Superimpose a small AC signal to be amplified v_{gs} on top of the DC bias voltage V_{GS}


Large-Signal Operation

Common Source (CS) (grounded source) Amplifier

- Called *Common Source* since the grounded source is common to both the input port (between G and S) and the output port (between D and S)
- Changes in $v_i = v_{GS}$, causes changes in i_D and we use a resistor R_D to get an output voltage v_o :


$$v_o = v_{DS} = V_{DD} - R_D i_D$$

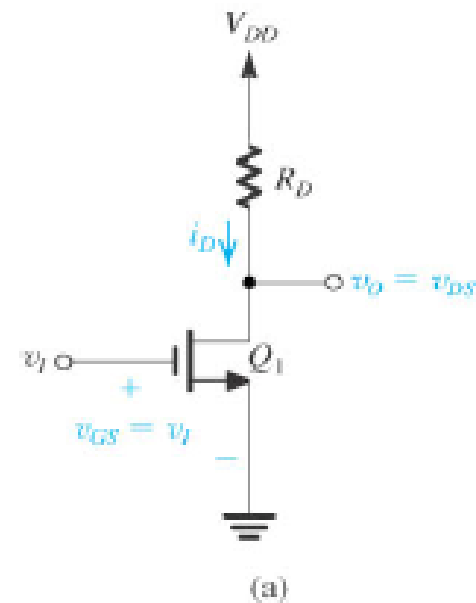- A DC power supply V_{DD} is needed to turn the MOSFET on and to supply the necessary power for its operation



Voltage Amplifier

Large-Signal Operation *cont.*

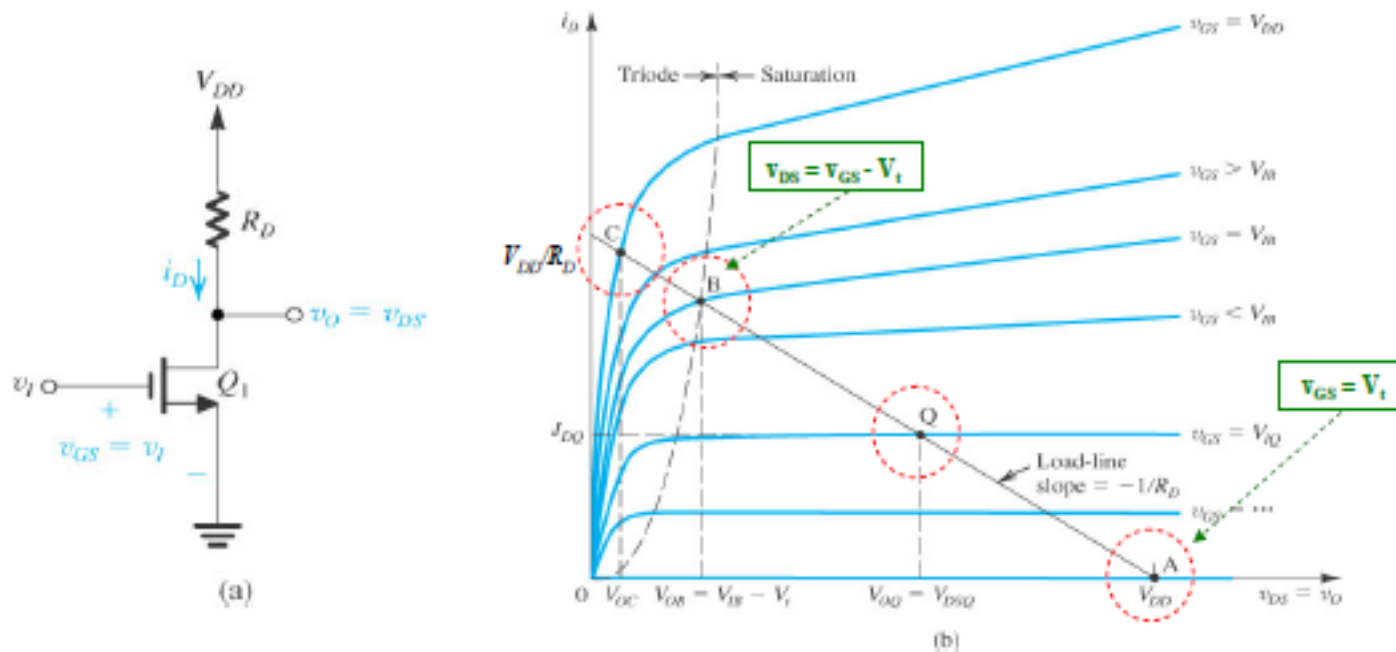

- Governed by the *intersection* of the MOSFET i_D - v_{DS} characteristic and the **Load Line** imposed by connecting the drain to V_{DD} via R_D
- For any given $v_i (=v_{GS})$, we locate the corresponding i_D - v_{DS} curve and find v_o from the point of intersection of this curve with the load line
- As $v_i = v_{GS}$ is increased, the operating point slides on the load line from point A (cutoff), through Saturation, to point C (Triode)