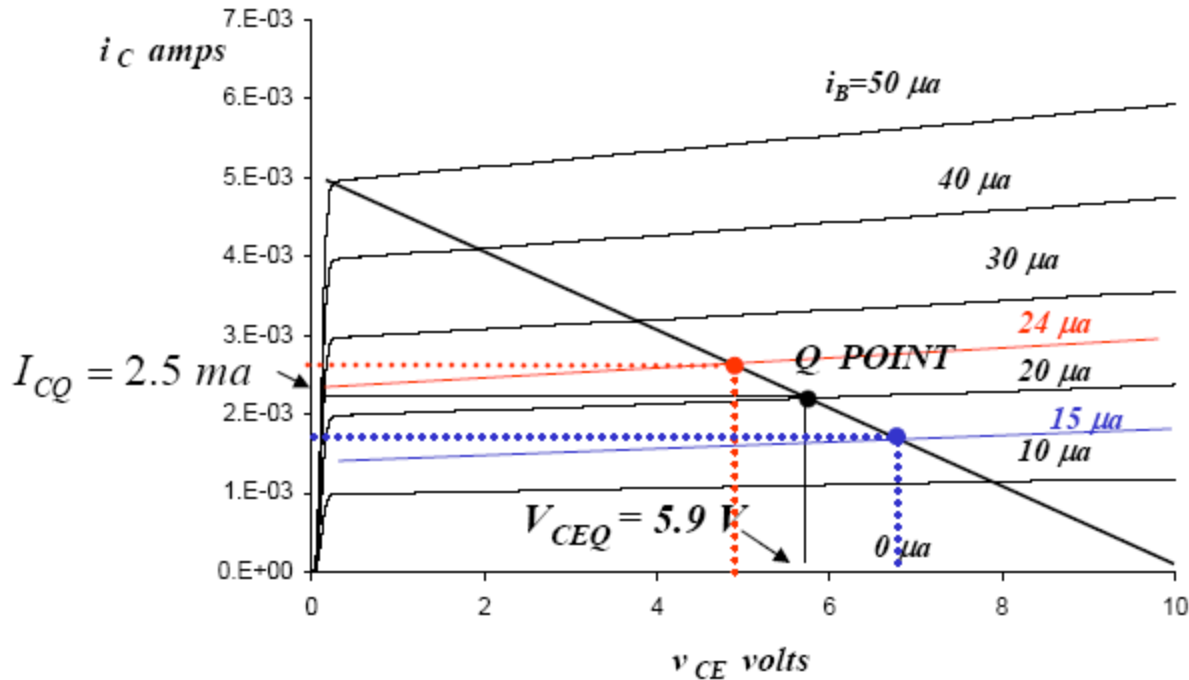


# Lecture 19

BJT

# AC Characteristics-Collector Circuit






Using these max and min values for the base current on the collector circuit load line, we find:

At Max Input Voltage:  $V_{CE} = 5 \text{ V}$ ,  $i_C = 2.7 \text{ mA}$

At Min Input Voltage:  $V_{CE} = 7 \text{ V}$ ,  $i_C = 1.9 \text{ mA}$

Recall: At Q-point:  $V_{CE} = 5.9 \text{ V}$ ,  $i_B = 2.5 \text{ mA}$

# AC Characteristics-Collector Circuit

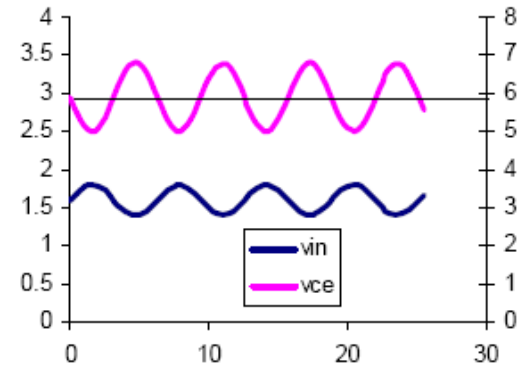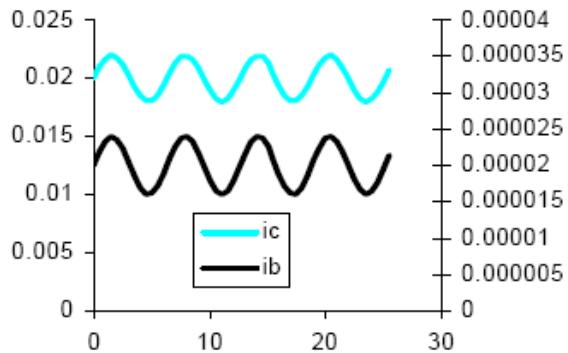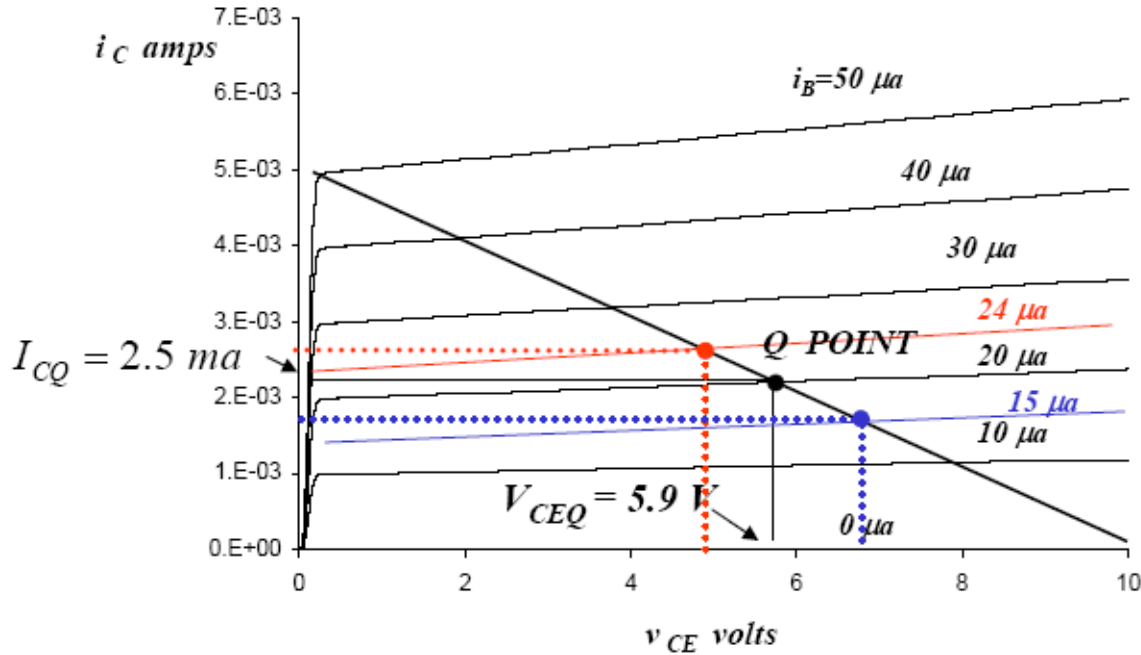

# BJT AC Analysis - Amplifier Gains

From the values calculated from the base and collector circuits we can calculate the amplifier gains:

- $\beta = 125$

- Current gain  $= \Delta i_c / \Delta i_b = (2.7 - 1.9)\text{m} / (24 - 15) \mu$   
 $= .8/9 * 10^3 = 88.9$

- Voltage gain  $= V_o / V_i = \Delta V_{CE} / \Delta V_{BE}$   
 $= (5 - 7) / (.63 - .59) = -2/0.04 = -50$

- Voltage gain  $= V_o / V_s = \Delta V_{CE} / \Delta V_{in}$   
 $= (5 - 7) / .4 = -2 / .4 = -5$



# BJT AC Analysis - Summary

- Once we complete DC analysis, we analyze the circuit from an AC point of view.
- AC analysis can be performed via a graphical processes
  - Find the maximum and minimum values of the input parameters (e.g., base current for a BJT)
  - Use the transistor characteristics to calculate the output parameters (e.g., collector current for a BJT).
- Calculate the gains for the amplifier

# The pnp Transistor

- Basically, the *pnp* transistor is similar to the *npn* except the parameters have the opposite sign.
  - The collector and base currents flows out of the transistor; while the emitter current flows into the transistor
  - The base-emitter and collector-emitter voltages are negative
- Otherwise the analysis is identical to the *npn* transistor.

# The PNP Transistor

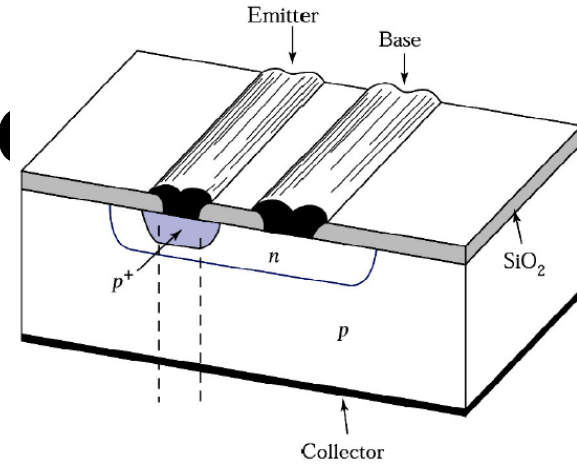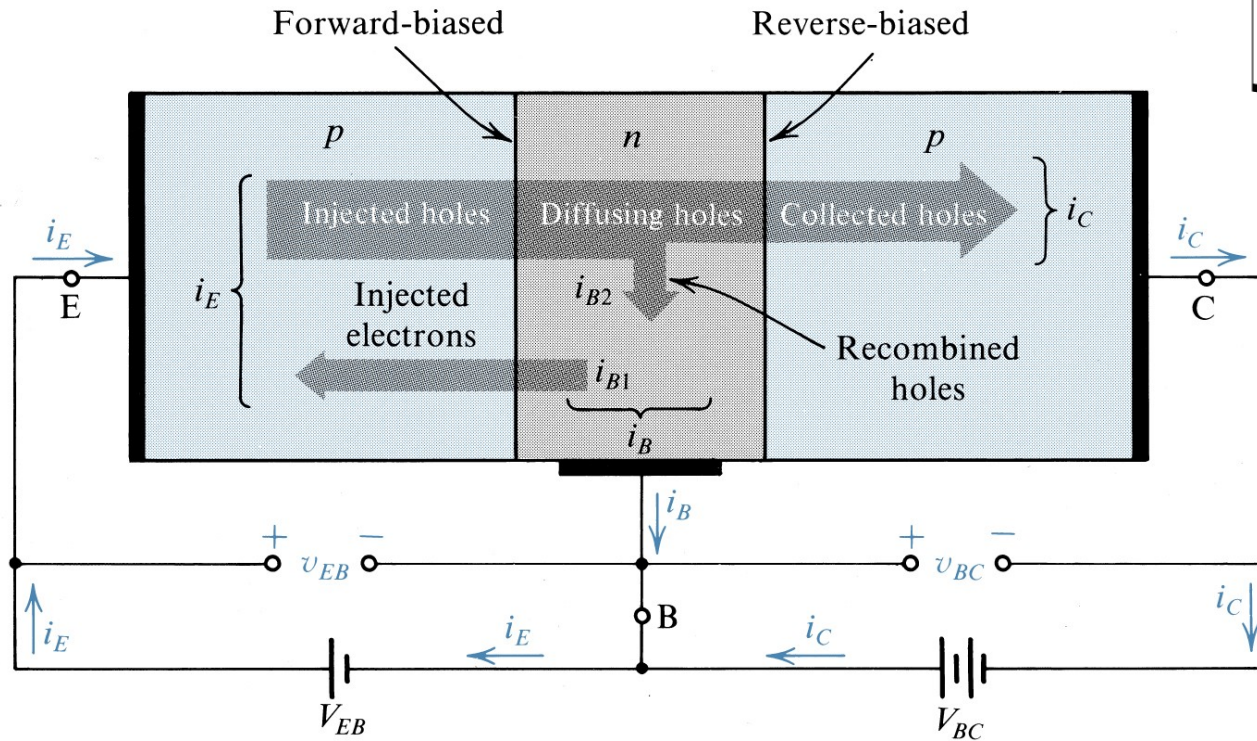

Current flow in a pnp transistor biased to operate in the active mode.

# The pnp Transistor

- Two junctions
  - Collector-Base and Emitter-Base
- Biasing
  - $v_{BE}$  Forward Biased
  - $v_{CB}$  Reverse Biased

