

Lecture 25


Op- Amp

Op-Amp

- Introduction of Operation Amplifier (Op-Amp)
- Analysis of ideal Op-Amp applications
- Comparison of ideal and non-ideal Op-Amp
- Non-ideal Op-Amp consideration

Operational Amplifier (Op-Amp)

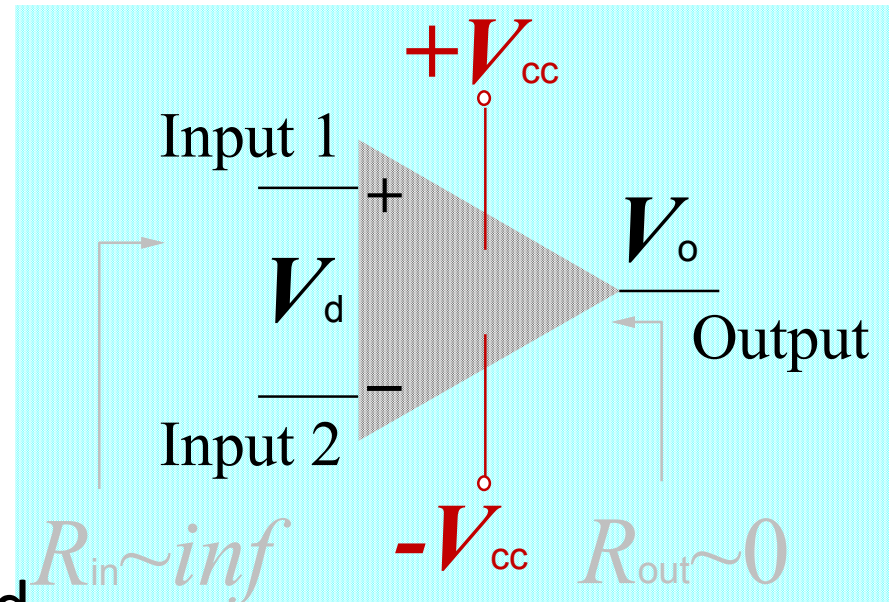
- Very high differential gain
- High input impedance
- Low output impedance
- Provide voltage changes (amplitude and polarity)
- Used in oscillator, filter and instrumentation
- Accumulate a very high gain by multiple stages




$$V_o = G_d V_d$$

G_d : differential gain normally very large, say 10^5

IC Product

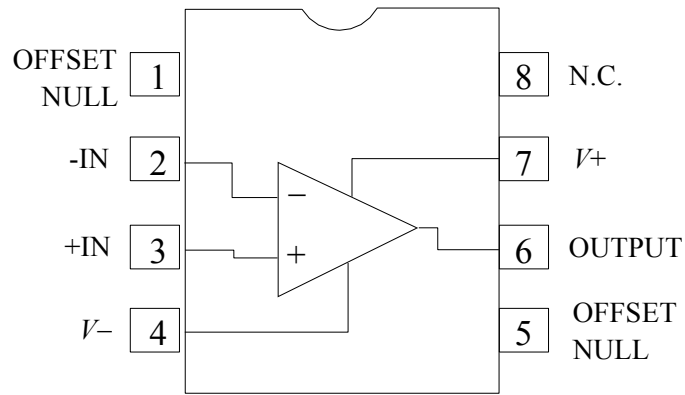


DIP-741

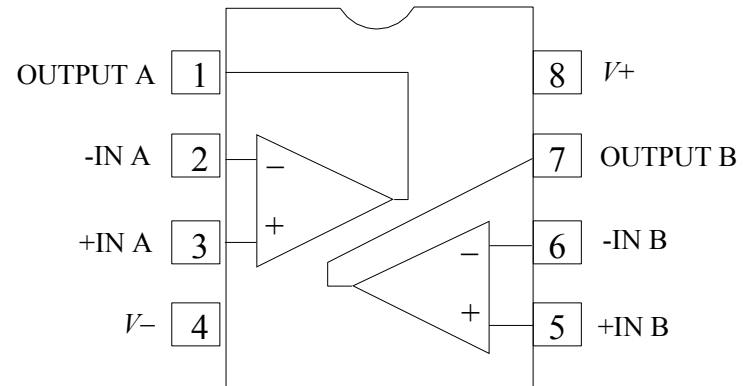


Dual op-amp 1458 device

Single-Ended Input

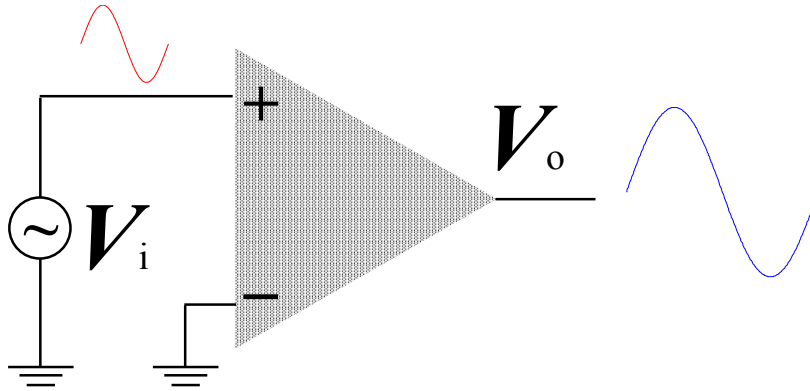


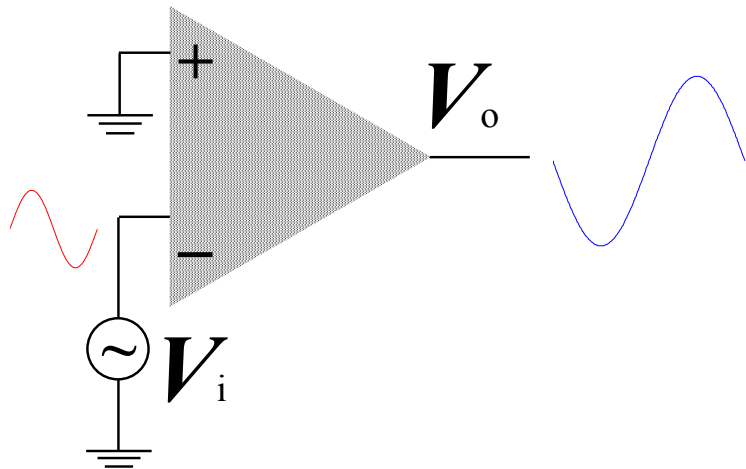- + terminal : Source
- - terminal : Ground
- 0° phase change




- + terminal : Ground
- - terminal : Source
- 180° phase change


Double-Ended Input

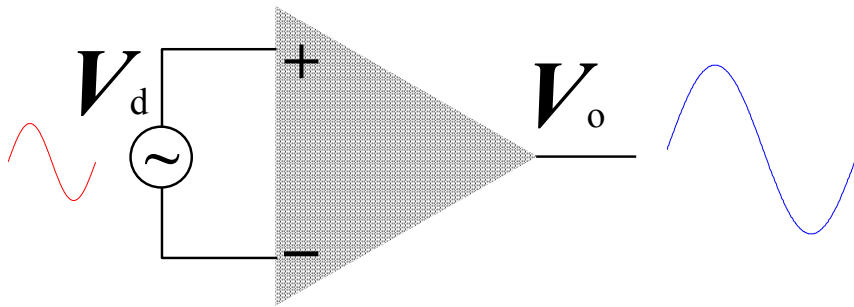

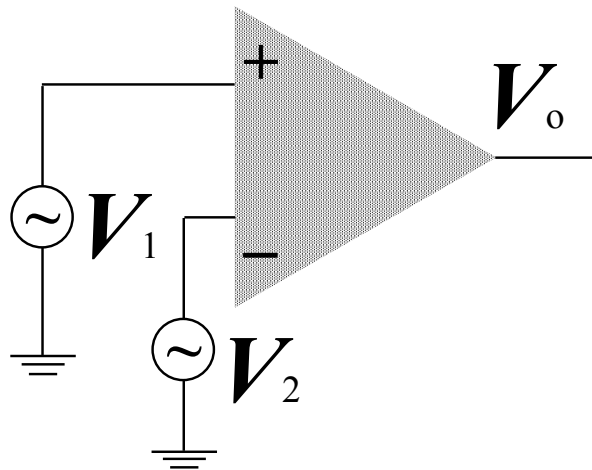
- Differential input
- $V_o = V_+ - V_-$
- 0° phase shift change between V_o and V_d



Qu: What V_o should be if,

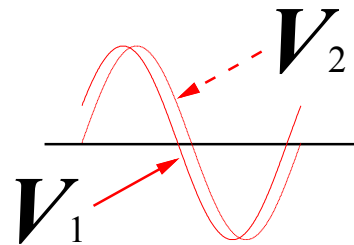


Ans: (A or B) ?

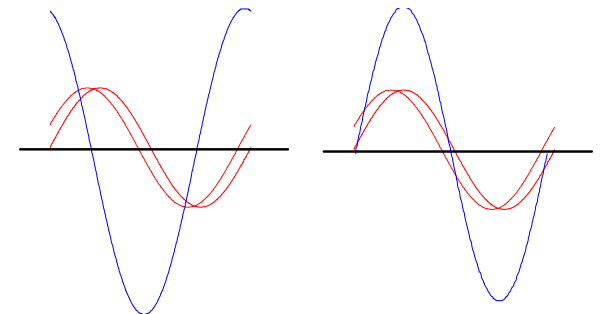

(A)

(B)


Distortion

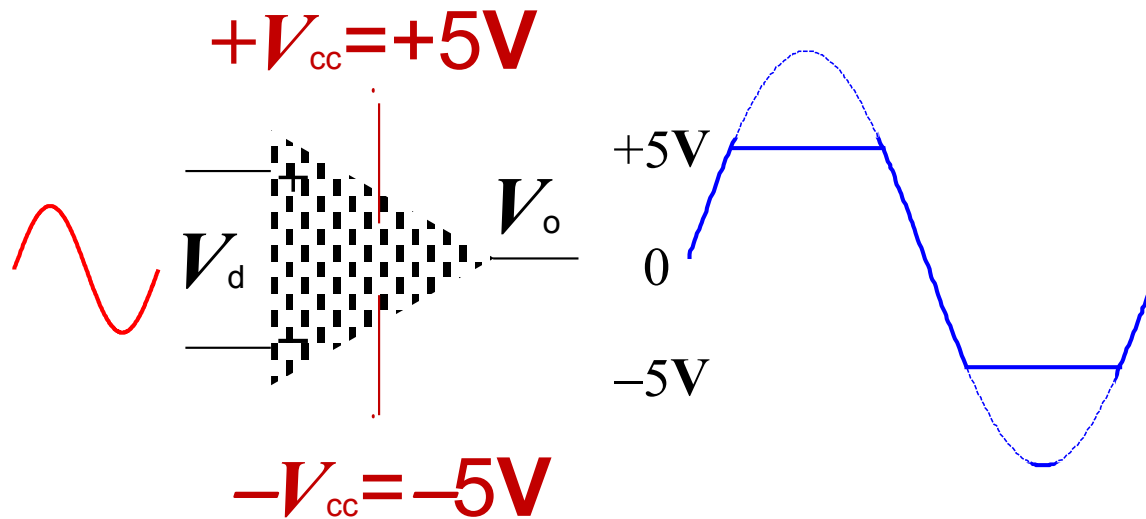

The output voltage never exceeds the DC voltage supply of the Op-Amp

Common-Mode Operation

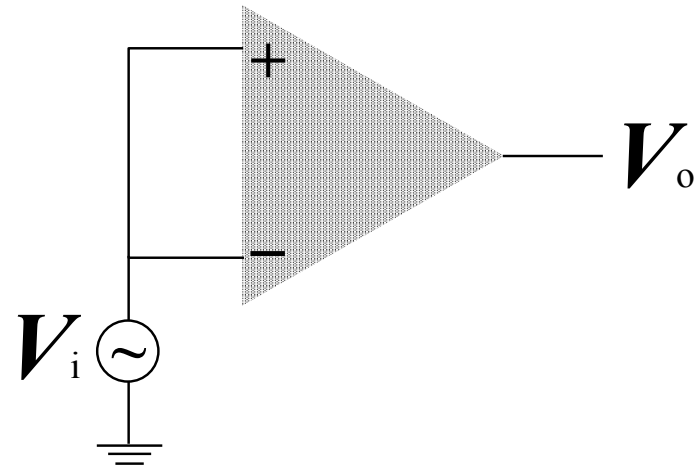- Same voltage source is applied at both terminals
- Ideally, two input are equally amplified
- Output voltage is ideally zero due to differential voltage is zero
- Practically, a small output signal can still be measured



Note for differential circuits:
Opposite inputs : highly amplified
Common inputs : slightly amplified

⇒ Common-Mode Rejection

Common-Mode Rejection Ratio (CMRR)

Differential voltage input :

$$V_d = V_+ - V_-$$

Common voltage input :


$$V_c = \frac{1}{2}(V_+ + V_-)$$

Output voltage :

$$V_o = G_d V_d + G_c V_c$$

G_d : Differential gain

G_c : Common mode gain

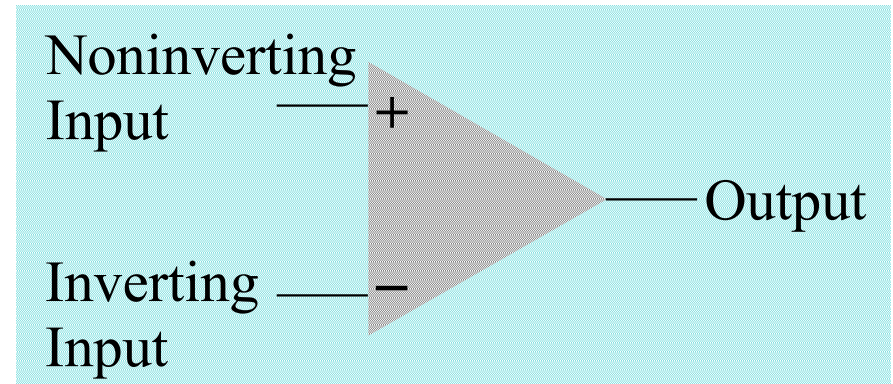

Common-mode rejection ratio:

$$\text{CMRR} = \frac{G_d}{G_c} = 20 \log_{10} \frac{G_d}{G_c} \text{ (dB)}$$



Note:

When $G_d \gg G_c$ or $\text{CMRR} \rightarrow \infty$

$\Rightarrow V_o = G_d V_d$

CMRR Example

What is the CMRR?

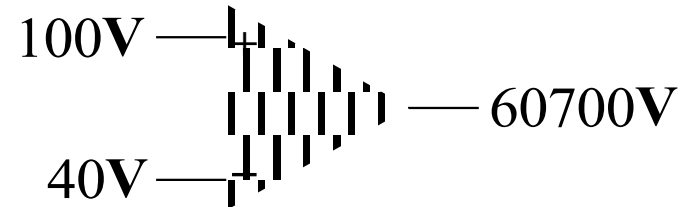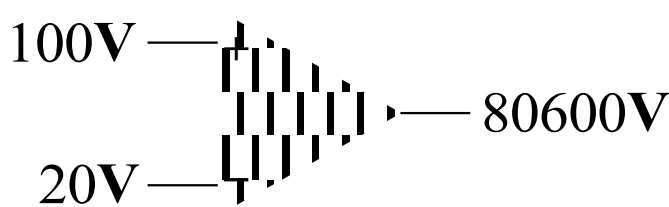

Solution :

$$\left. \begin{aligned} V_{d1} &= 100 - 20 = 80\text{V} \\ V_{c1} &= \frac{100 + 20}{2} = 60\text{V} \end{aligned} \right\} (1)$$

$$\left. \begin{aligned} V_{d2} &= 100 - 40 = 60\text{V} \\ V_{c2} &= \frac{100 + 40}{2} = 70\text{V} \end{aligned} \right\} (2)$$

From (1) $V_o = 80G_d + 60G_c = 80600\text{V}$

From (2) $V_o = 60G_d + 70G_c = 60700\text{V}$


$G_d = 1000$ **and** $G_c = 10 \Rightarrow \text{CMRR} = 20 \log(1000/10) = 40\text{dB}$

NB: This method is Not work! Why?

Op-Amp Properties

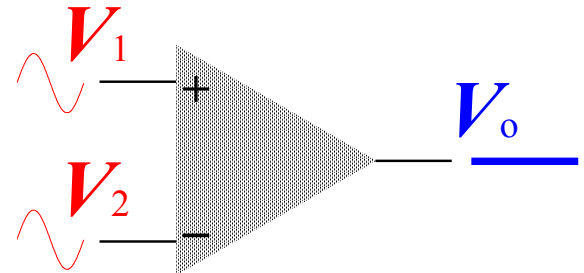
(1) Infinite Open Loop gain

- The gain without feedback
- Equal to differential gain
- Zero common-mode gain
- Practically, $G_d = 20,000$ to $200,000$



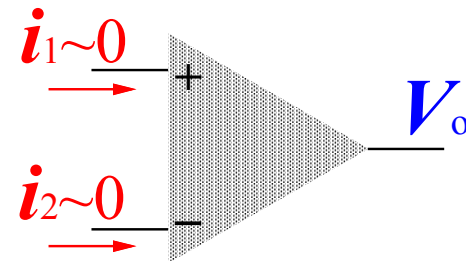
(2) Infinite Input impedance

- Input current $i_i \sim 0A$
- T- Ω in high-grade op-amp
- m-A input current in low-grade op-amp



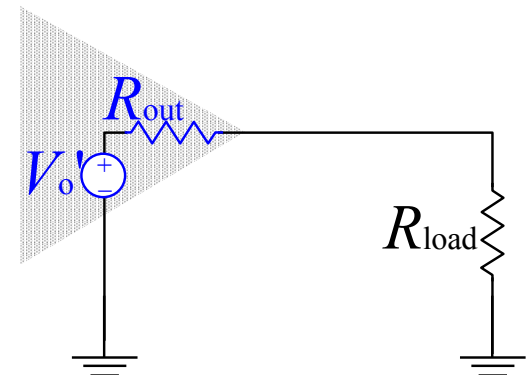(3) Zero Output Impedance


- act as perfect internal voltage source
- No internal resistance
- Output impedance in series with load
- Reducing output voltage to the load
- Practically, $R_{out} \sim 20-100 \Omega$



$$V_{load} = V_o' \frac{R_{load}}{R_{load} + R_{out}}$$

Frequency-Gain Relation

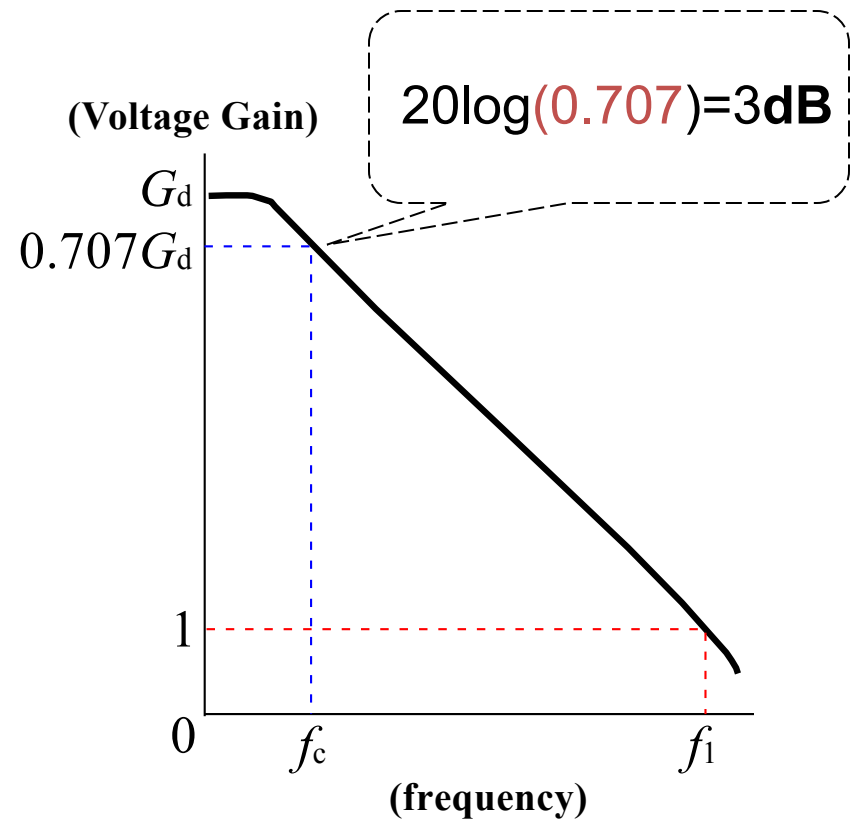- Ideally, signals are amplified from DC to the highest AC frequency
- Practically, bandwidth is limited
- 741 family op-amp have an
- ~~Limit bandwidth of few KHz.~~ ~~unity~~ at unity
- Cutoff frequency f_c : the gain drop by 3dB from dc gain G_d



$$\text{GB Product : } f_1 = G_d f_c$$

GB Product

Example: Determine the cutoff frequency of an op-amp having a unit gain frequency $f_1 = 10 \text{ MHz}$ and voltage differential gain $G_d = 20 \text{ V/mV}$

Sol:

Since $f_1 = 10 \text{ MHz}$


By using GB production equation

$$f_1 = G_d f_c$$

$$f_c = f_1 / G_d = 10 \text{ MHz} / 20 \text{ V/mV}$$



$$= 10 \times 10^6 / 20 \times 10^3$$

$$= 500 \text{ Hz}$$

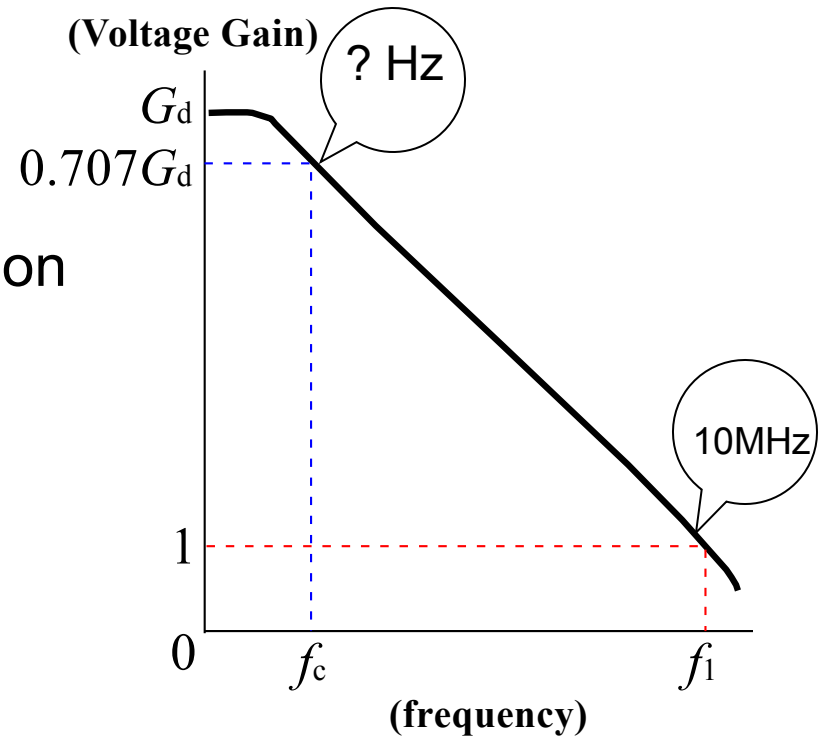

Ideal Vs Practical Op-Amp

	Ideal	Practical
Open Loop gain A	∞	10^5
Bandwidth BW	∞	10-100Hz
Input Impedance Z_{in}	∞	$>1M\Omega$
Output Impedance Z_{out}	0Ω	10-100 Ω
Output Voltage V_{out}	Depends only on $V_d = (V_+ - V_-)$ Differential mode signal	Depends slightly on average input $V_c = (V_+ + V_-)/2$ Common-Mode signal
CMRR	∞	10-100dB

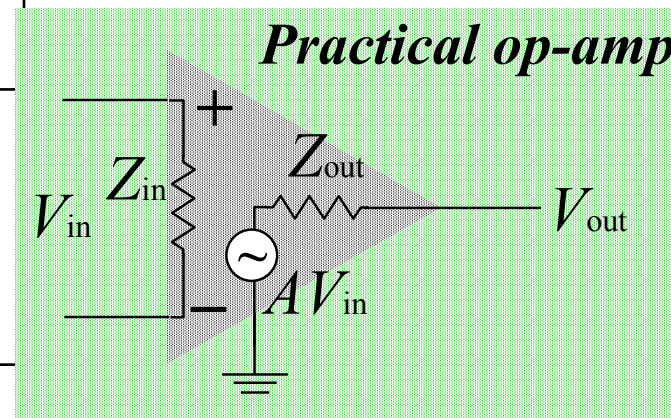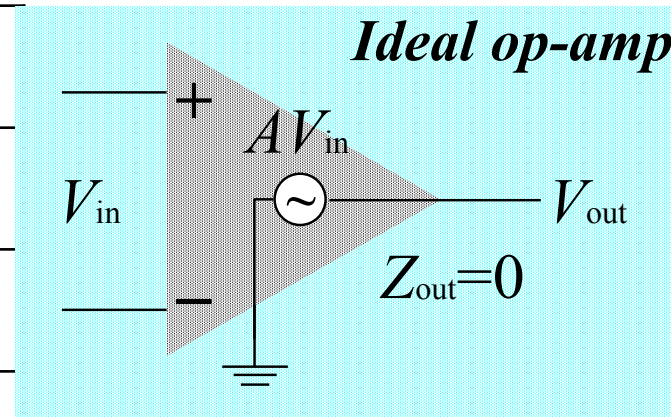

Ideal Op-Amp Applications

Analysis Method :

Two ideal Op-Amp Properties:

- (1) The voltage between V_+ and V_- is zero $V_+ = V_-$
- (2) The current into both V_+ and V_- terminals is zero

For ideal Op-Amp circuit:

- (1) Write the kirchhoff node equation at the noninverting terminal V_+
- (2) Write the kirchhoff node equation at the inverting terminal V_-
- (3) Set $V_+ = V_-$ and solve for the desired closed-loop gain