

Lecture-6

phase shift in star-delta transformation, sequence impedances.

Topic Covered

- ▶ Modeling
- ▶ Transformer connections
- ▶ Modeling of Synchronous Generator










Modeling Aspects for Static Apparatus










- ▶ Transmission Lines, feeder cables etc
- ▶ Two winding and Three Winding Transformers
 - Positive sequence Data = Negative sequence Data.
 - Zero Sequence Data different
Rule of Thumb for Lines---
Zero Sequence Data about Three Times Positive Sequence Data.
 - Zero Sequence Modes of Transformers.

Transformer connections

+ ve/- ve sequence connections

Zero sequence connections

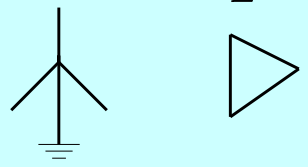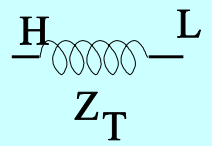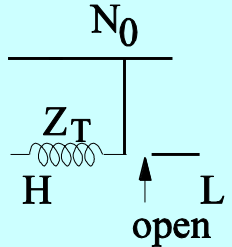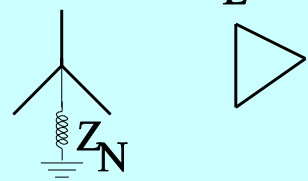
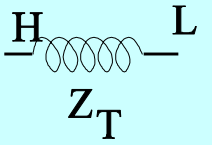
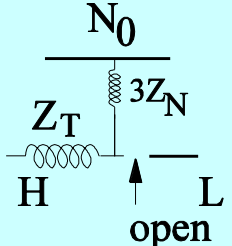
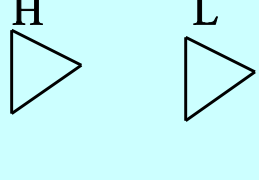
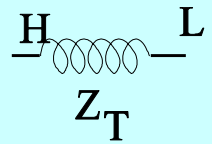
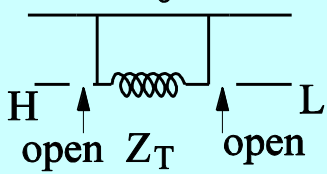
<p>H L</p>  <p>(a)</p>	<p>N_1 or N_2</p>  <p>Z_T</p>	<p>N_0</p>  <p>open</p>
<p>H L</p>  <p>(b)</p>	<p>N_1 or N_2</p>  <p>Z_T</p>	<p>N_0</p>  <p>open</p>
<p>H L</p>  <p>(c)</p>	<p>N_1 or N_2</p>  <p>Z_T</p>	<p>N_0</p>  <p>open Z_T open</p>

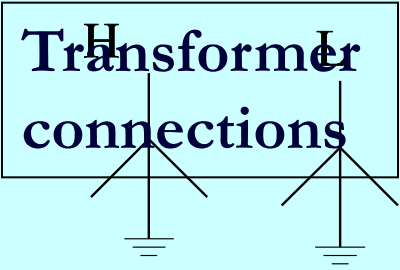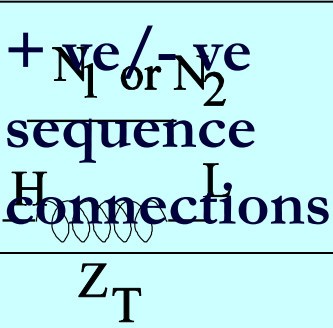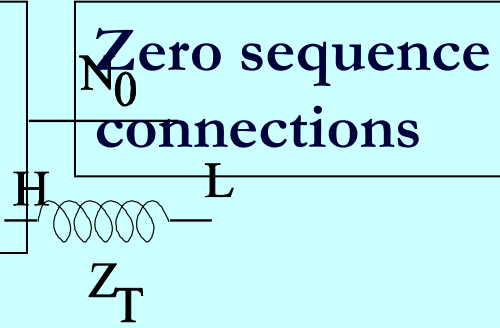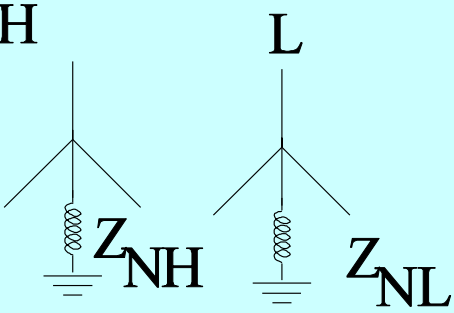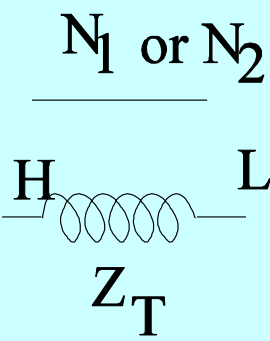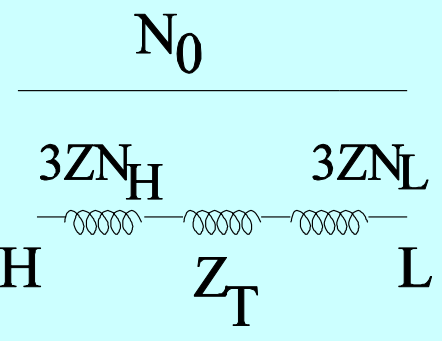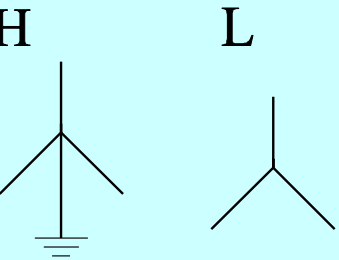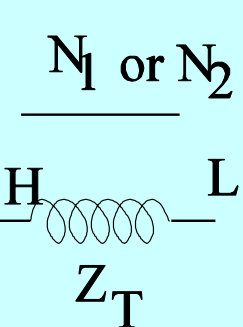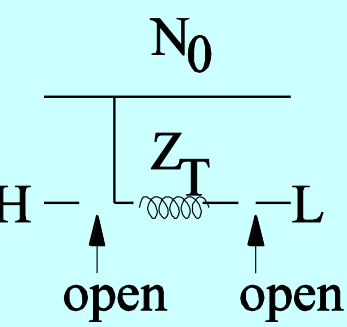	Transformer connections	+ve/-ve sequence connections	Zero sequence connections
			
(d)			
(e)			
(f)			

Transformer connections

+ ve / - ve sequence connections

Zero sequence connections
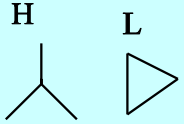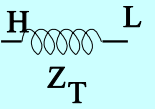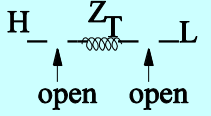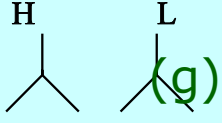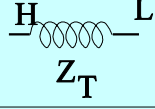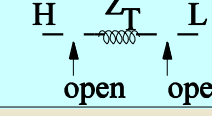
<p>H L</p> 	<p>N_1 or N_2</p>  <p>Z_T</p>	<p>N_0</p>  <p>↑ open ↑ open</p>
<p>H L</p>  <p>(g)</p>	<p>N_1 or N_2</p>  <p>Z_T</p>	<p>N_0</p>  <p>↑ open ↑ open</p>

(h)

Modeling of Rotating Machines

Modeling of Synchronous Generator

- ▶ X_d'' = Subtransient reactance; determines the current during the first cycle after fault occurs. In about 0.1 s reactance increases to
- ▶ X_d' = Transient reactance; assumed to determine current after several cycles at 60Hz. In about 0.5–2 s reactance increases to
- ▶ X_d = Synchronous reactance; this is the value that determines the current flow after a steady state condition is reached.
- ▶ Synchronous generator data available from manufacturers includes two values of direct axis reactance – X_{dV} and X_{dI} . The X_{dV} value should be used for short – circuit calculations.

Modeling of Synchronous Motors and Condensers

- ▶ During fault motor acts as a generator to supply fault current
- ▶ The rotor carrying the field winding is driven by the inertia of the rotor and load. Stator excitation is reduced due to drop in voltage.
- ▶ The fault current diminishes as the rotor decelerates
- ▶ The generator equivalent circuit is used for synchronous motor.
- ▶ The constant driving voltage and three reactance $X_{d''}$, $X_{d'}$ and X_d are used to establish the current values at three points in time.
- ▶ Synchronous condensers can be treated in same manner as synchronous motors.