

Power System-II

Lecture-1

Power System Transients on a transmission line,
short circuit of synchronous
machine at no load and on full load.

Topic Covered

- ▶ Introduction of Power System
- ▶ Complications
- ▶ Electrical Transient
- ▶ RC Circuit Response

Simple Power System

- **Every power system has three major components:**
 - **generation:** source of power, ideally with a specified voltage and frequency
 - **load or demand:** consumes power; ideally with a constant resistive value
 - **transmission system:** transmits power; ideally as a perfect conductor
- **Additional components include:**
 - **distribution system:** local reticulation of power,
 - **control equipment:** coordinate supply with load.

Complications

- ▶ No ideal voltage sources exist.
- ▶ Loads are seldom constant and are typically not entirely resistive.
- ▶ Transmission system has resistance, inductance, capacitance and flow limitations.
- ▶ Simple system has no redundancy so power system will not work if any component fails.

Power

- Power:
 - Instantaneous rate of consumption of energy,
 - How hard you work!
- ▶ Power = voltage x current for dc
- Power Units:

Watts = amps times volts (W)

kW - 1×10^3 Watt

MW - 1×10^6 Watt

GW - 1×10^9 Watt

Energy

▶ Energy:

- Integration of power over time,
- Energy is what people really want from a power system,
- How much work you accomplish over time.

▶ Energy Units:

Joule = 1 watt-second (J)

kWh - kilowatthour (3.6×10^6 J)

Btu - 1055 J;

1 MBtu = 0.292 MWh


Electrical Transients

- ▶ Time Scale in Power System Studies:
planning, Load Flow, Dynamic Stability
Switching, external disturbances
- Frequency Content
- Differential Equations Solution
- Distributed and Lumped Parameters

CCT Parameters

- ▶ In Steady State and Transient
- ▶ Mathematical Presentation & Physical Interpretation

Simple RC Circuit, Closing Ideal Sw.

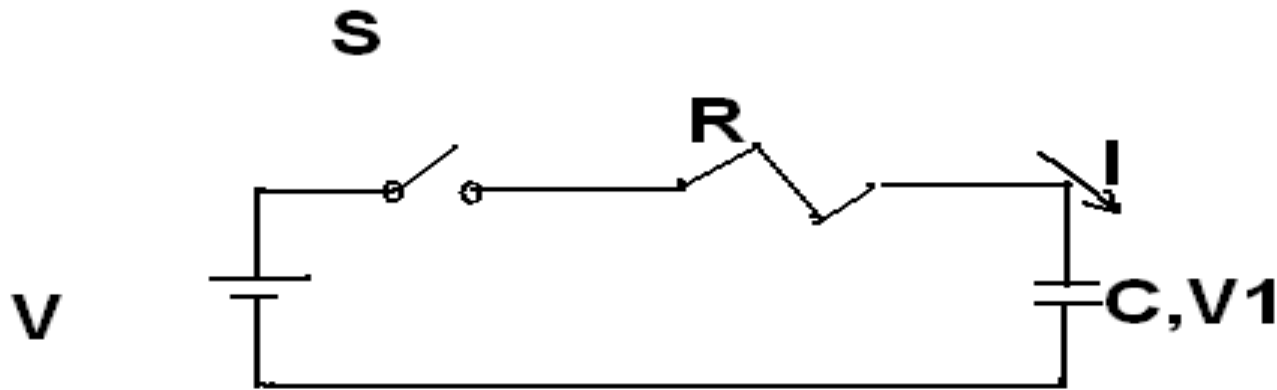

Equations of RC Circuit

$$V = IR + \frac{1}{C} \int Idt \quad I = \frac{dQ}{dt} = C \frac{dV_1}{dt}$$

$$V = RC \frac{dV_1}{dt} + V_1$$

$$\frac{dV_1}{V - V_1} = \frac{dt}{RC}$$

RC Circuit Response

$$\ln(V - V_1) = -\frac{t}{RC} + \text{Cons.}$$

$$V_1 = V - [V - V_1(0)]e^{-t/RC}$$

$$V_1 = V - Ae^{-t/RC}$$

RC Circuit Response

$$\ln(V - V_1) = -\frac{t}{RC} + \text{Cons.}$$


$$V_1 = V - [V - V_1(0)]e^{-t/RC}$$

$$V_1 = V - Ae^{-t/RC}$$

RC Circuit Discharge

$$RC \frac{dV_1}{dt} + V_1 = 0$$

$$V_1 = V_1(0)e^{-t/RC}$$

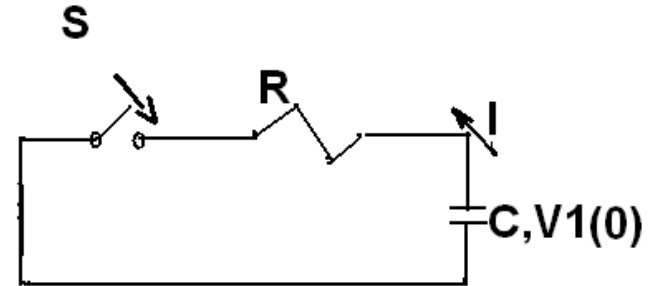

Capacitor Voltage of RC CCT

