

Section D

- Design of Combinational Elements and regular array logic
 - VHDL Programming

TOPIC COVERED

- **DESIGN OF COMBINATIONAL ELEMENTS & REGULAR ARRAY LOGIC** : NMOS PLA –
- Programmable Logic Devices - Finite State Machine PLA – Introduction to FPGA.
- **VHDL PROGRAMMING:** RTL Design – Combinational logic – Types – Operators – Packages –
- Sequential circuit – Sub-programs – Test benches. (Examples: address, counters, flipflops, FSM,
- Multiplexers / De-multiplexers).

VHDL Introduction

VHDL Introduction

- V- VHSIC
 - Very High Speed Integrated Circuit
- H- Hardware
- D- Description
- L- Language

VHDL Benefits


1. Public Standard
2. Technology and Process Independent
 - Include technology via libraries
3. Supports a variety of design methodologies
 1. Behavioral modeling
 2. Dataflow or RTL (Register Transfer Language) Modeling
 3. Structural or gate level modeling

VHDL Benefits (cont)

4. Supports Design Exchange
 - VHDL Code can run on a variety of systems
5. Supports Design Reuse
 - Code “objects” can be used in multiple designs
6. Supports Design Hierarchy
 - Design can be implemented as interconnected submodules

VHDL Benefits (cont)

 7. Supports Synchronous and Asynchronous Designs
8. Supports Design Simulation
 - Functional (unit delay)
 - Timing (“actual” delay)
9. Supports Design Synthesis
 - Hardware implementation of the design obtained directly from VHDL code.



10. Supports Design Documentation
 - Original purpose for VHDL – Department of Defense

VHDL Design Units

- Entity Declaration
 - Describes external view of the design (e.g. I/O)
- Architecture Body (AB)
 - Describes internal view of the design
- Configuration Declaration
- Package Declaration
 - Library Declaration
- Package Body

Architecture Body (AB)

- The architecture body contains the internal description of the design entity. The VHDL specification states that a single design entity can contain multiple architecture bodies. Each AB can be used to describe the design using a different level of abstraction.

VHDL Statement Terminator

Each VHDL Statements is terminated using a semicolon

;

VHDL Comment Operator

To include a comment in VHDL, use the comment operator

-- This is a comment

-- This is an example of a comment

y <= 0; -- can occur at any point

Signal Assignment Operator

To assign a value to a signal data object in VHDL,
we use the

signal assignment operator



Example:

```
y <= '1';  -- signal y is assigned the value ONE
```


Complete AND GATE Example

```
Library altera;
Use altera.maxplus2.all;
Library ieee;
Use ieee.std_logic_1164.all;
Use ieee.std_logic_arith.all;
Entity and_example is
    port(a,b: in std_logic;
         ya,yb,yc: out std_logic);
End entity and_example;
Architecture test of and_example is
begin
    --- dataflow model (ya)
        ya <= a and b;
    -- structural model (yb)
        and2:a_7408 port map(a,b,yb);
```


```
-- behavioral model (yc)
process(a,b)
begin
    yc <= '0';
    if((a='1') and (b = '1')) then
        yc <= '1';
    else yc <= '0';
    end if;
end process;
End architecture test;
```

AND GATE Example (cont)

 When synthesized, we obtain the following logic circuit



Synthesis tool creates three AND gates.

 


Maxplus II Block Diagram

VHDL Example - Hardware

- It is important to remember that VHDL is a “hardware” language, so you must think and code in “hardware.”
- Statements within the architecture body run “concurrently.” That is, order does not matter!!!
 - We’ll introduce “sequential” statements later when I introduce “process blocks”

VHDL Example – Hardware

- Example – Logic Circuit

 

-- Code Fragment A

Architecture test of example is

begin

```
y1 <= a and b;
```


```
y2 <= c and d;
```

```
y  <= y1 or y2;
```

```
end architecture test;
```


VHDL Example – Hardware

- Example – Logic Circuit

 

-- Code Fragment B

Architecture test of example is

begin

 y <= y1 or y2;


 y2 <= c and d;

 y1 <= a and b;

end architecture test;

VHDL Example – Hardware

- Example – Logic Circuit

 

-- Code Fragment C

Architecture test of example is

begin

 y2 <= c and d;

 y <= y1 or y2;

 y1 <= a and b;

end architecture test;

All three code fragments produce the same result

VHDL Syntax

VHDL Syntax – Entity Declaration

Describes I/O of the design. I/O Signals are called **ports**.

The syntax is:

Entity design_name **is**

port(signal1,signal2,.....:mode type;
signal3,signal4,.....:mode type);

End entity design_name;

VHDL Syntax – Entity Example

Entity my_example is


```
port( a,b,c: in std_logic;
```

```
      s: in std_logic_vector(1 downto 0);
```

```
      e,f: out std_logic;
```

```
      y: out std_logic_vector(4 downto 0));
```

```
end entity my_example;
```

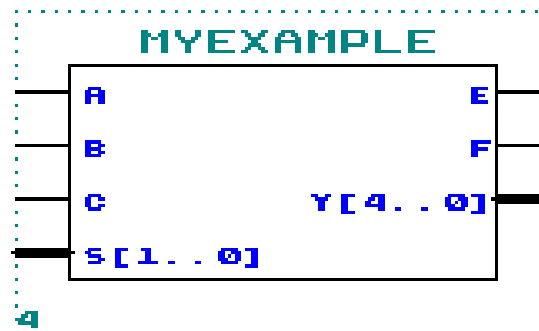

Maxplus II Block Diagram

Architecture Body Syntax

- ***Architecture*** name ***of*** entity_name ***is***
internal signal and constant declarations

Begin

Concurrent statement 1;

Concurrent statement 2;

Concurrent statement 3;

Concurrent statement 4;

End architecture name;

VHDL Program Template

Library altera;

Use altera.maxplus2.all;

Library ieee;

Use ieee.std_logic_1164.all;

Use ieee.std_logic_arith.all;

Entity design_name **is**

port(signal1,signal2,.....:mode type;
 signal3,signal4,.....:mode type);

End entity design_name;

Architecture name **of** entity_name **is**
 internal signal and constant
 declarations

Begin

 Concurrent statement 1;

 Concurrent statement 2;

 Concurrent statement 3;


 Concurrent statement 4;

End architecture name;

Simple Concurrent Statements

Assignment Operator

- Assignment operator `<=`
 - Ex: `y <= a and b;` -- defines a **AND** gate
 - For **simulation** purposes only, you may specify a delay.
 - Ex: `y <= a and b after 10 ns;`
 - This is useful if you want to also use VHDL to generate a known test waveform or vector. This is known as a “test bench.” However, we will use Maxplus II to generate test vectors. Note, you **cannot** specify a delay for **synthesis** purposes.

 

Simple Concurrent Statements

Logical Operators


- Logical operators
 - *And, or, nand, nor, xor, xnor, not*
 - Operates on `std_logic` or Boolean data objects
 - All operators (except for the not operator) require at least two arguments
 - Ex: `y <= a and b;` -- AND gate

Simple Concurrent Statements

Logical Operators

- Logical operators


 
- Examples $y \leftarrow a \text{ and not } b;$



- Use parenthesis to define order of execution

- Ex: $y \leftarrow (a \text{ and } b) \text{ or } c;$

  - $y \leftarrow a \text{ and } (b \text{ or } c);$



Complex Concurrent Statements with-select-when

- **with-select-when**

Syntax is

with select_signal ***select***

signal_name <= value1 ***when*** value1_of_select_sig,
value2 ***when*** value2_of_select_sig,
value3 ***when*** value3_of_select_sig,
value_default ***when others;***

Complex Concurrent Statements

With-select-when

- **Example**

---- library statements (not shown)

```
entity my_test is
```

```
  port( a3,a2,a1,a0: in std_logic_vector(3 downto 0);
```

```
        s: in std_logic_vector(1 downto 0);
```

```
        y: out std_logic_vector(3 downto 0));
```

```
end entity my_test;
```

```
architecture behavior of my_test is
```

```
  begin
```

```
    with s select
```

```
  y <= a3 when "11",
```

```
    a2 when "10",
```

```
    a1 when "01",
```

```
    a0 when others; -- default condition
```

```
end architecture behavior;
```


Complex Concurrent Statements With-select-when

- What is the logic expression for y?

$$y_n = a_{0n} \overline{s_1} s_0 + a_{1n} s_1 \overline{s_0} + a_{2n} \overline{s_1} \overline{s_0} + a_{3n} s_1 s_0$$

$$n = 0, 1, 2, 3$$

 - What is this in hardware?
 - A 4-bit 4X1 MUX



VHDL Data Objects

- VHDL is an Object Oriented Programming (OOP) Language. Objects can have values, attributes and methods. We will primarily use the following VHDL data objects:

Signals

Constants

Variables

Data Objects

Signals

- **Signals**

Signals are data objects in which the value of the object can be changed. There is an implied or explicit delay between the signal assignment and when the signal is updated. We will use signals to represent nets (i.e. wires) in our circuits.

They can be implemented in hardware.

Signals are defined in port statements and architecture declaration blocks.

Data Objects

Constants

- **Constants**

Constants are data objects in which the value of the object cannot be changed. They are defined within an architecture or process declaration block. They cannot be implemented in hardware.

Data Objects Constants

Syntax:

constant name: type := value;

Example:

```
constant s0: std_logic_vector(1 downto 0) := "01";
```

Notes:

1. Use a set of single apostrophes to enclose a single bit (e.g. '1').
2. Use a set of quotations to enclose multiple bits (e.g. "01").

Data Objects

Variables

- **Variables**

Variables are data objects in which the value of the object can be changed. This change occurs instantaneously. Variables can only be defined within a ***process declaration*** block. They cannot be implemented in hardware.

More about variables later

Sequential Statements

Process Statements

In VHDL, sequential statements are executed within a **process** block. Syntax is:


```
[label:] process (sensitivity list)  
    constant or variable declarations  
begin  
    sequential statements;  
end process [label];
```

The sensitivity list contains all of the inputs to the process block.

Sequential Statements

Process Statements (cont)

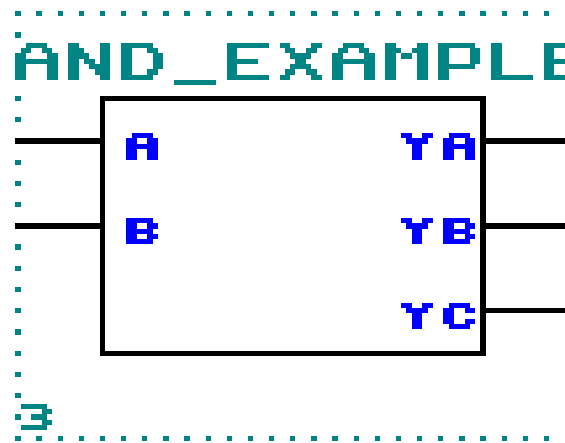A process block is considered a **single** concurrent statement. Let's review our AND example



Sequential Statements

Process Statements - Example

```
---- library statements
entity and_example is
  port(a,b: in std_logic;
        ya,yb,yc: out std_logic);
End entity and_example;
Architecture test of and_example is
begin
  --- dataflow model
  ya <= a and b;


  --- structural model
  a_7408 port map(a,b,yb);
```

```
-- Process Block
process(a,b)
begin
  yc <= '0';
  if ((a='1') and (b = '1')) then yc <= '1';
  else yc <= '0';
  end if;
end process;
End architecture test;
```

Sequential Statements

Process Statements

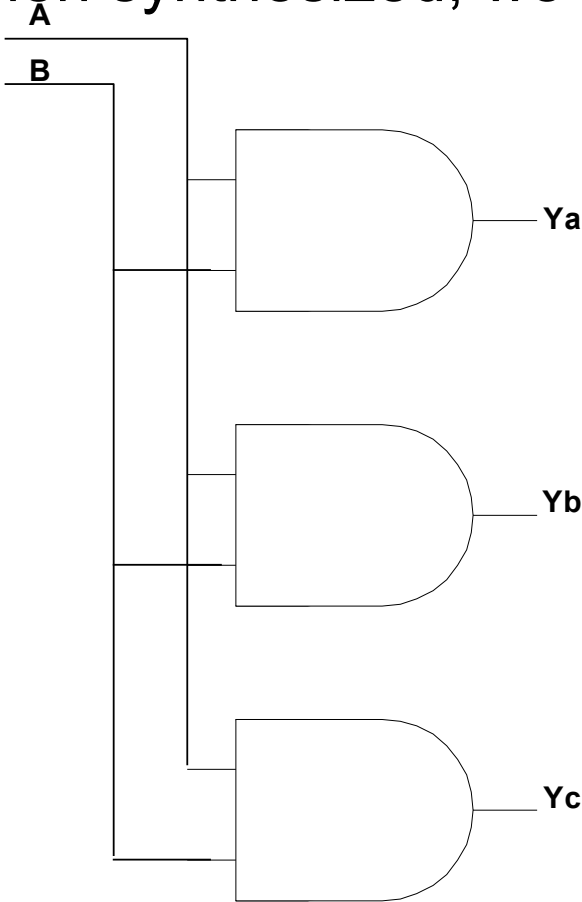When synthesized, we obtain the following logic circuit



The process statement synthesizes into an AND gate just like the dataflow and structural statements. Note, the process block synthesized AND gate “runs” concurrently with the other synthesized AND gates.

Sequential Statements Implied Registers

Registers

Sequential Statements

Implied Registers

Positive edge triggered D-FF with asynchronous reset

Process (d,clock,reset)

begin

if (reset = '0') then

q <= '0';


elsif(clock'event and clock='1') then

q <= d;

end if;

end process;

In hardware, this becomes

 

A clock'event is a 0 to 1 or 1 to 0 transition on the clock line.

Sequential Statements


Implied Registers

How does this produce a register?

1. If $\text{reset} = 0$, q is set to 0 (asynchronous reset)
2. If clock line makes a transition from 0 to 1
 - Clock'event and $\text{clock} = 1$
then q is assigned to d

But, we have not defined an output for

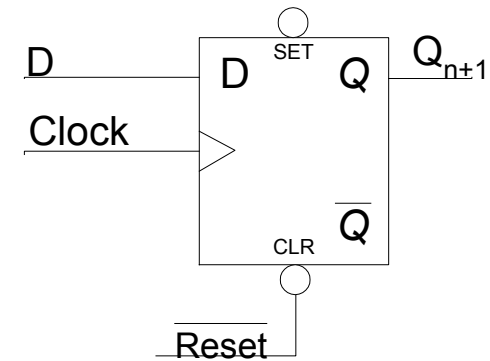1. $\text{Reset} = 1$,
2. A non Clock'event , or
3. Clock'Event and $\text{Clock} = 0$




So, VHDL **assumes** we want to retain the current value of q for these **conditions** and synthesizes a D-FF for us.

Sequential Statements

Implied Registers

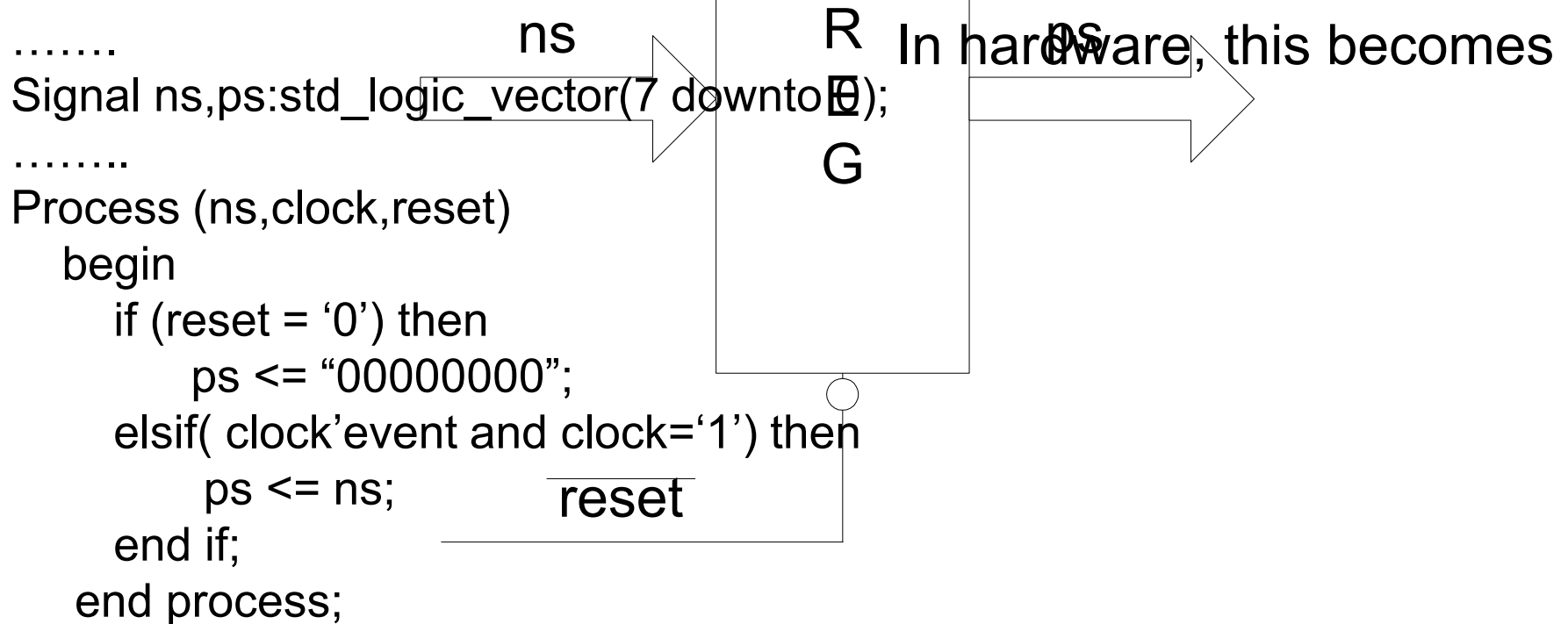We can easily extend this to a register block by using a *std_logic_vector* datatype instead of a *std_logic* datatype.



Sequential Statements

Implied Registers

We can also define a S0 (reset state) and use it to reset the register.

```
.....  
Signal ns,ps:std_logic_vector(7 downto 0);  
Constant S0:std_logic_vector(7 downto 0) := "00000000";  
.....  
Process (ns,clock,reset)  
begin  
    if (reset = '0') then  
        ps <= s0;  --- use 'reset' state  
    elsif( clock'event and clock='1') then  
        ps <= ns;  
    end if;  
end process;
```

Sequential Statements

Case -When Statement

Use a *CASE-WHEN* statement when priority is not needed.
All FSMs will be implemented using Case-when statements.


Syntax is:

```
Case expression is  
  when choice_1 =>  
    sequential statements;  
  when choice_2 =>  
    sequential statements;  
    .....  
  when choice_n =>  
    sequential statements;  
  when others => -- default condition  
    sequential statements;  
end case;
```

VHDL FSM Example 1

2-bit Up Counter

◆ State Diagram

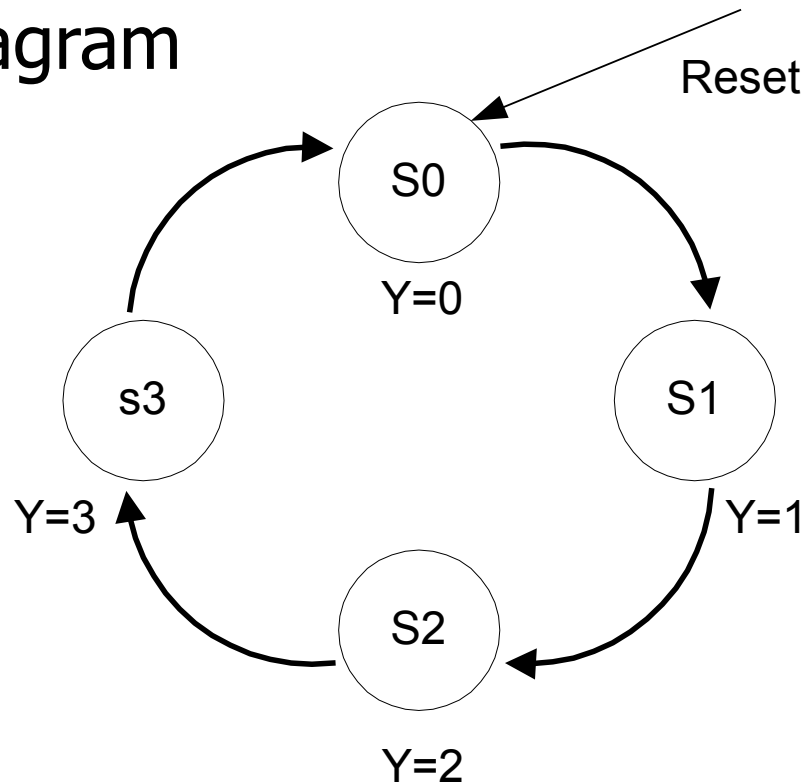

VHDL FSM Example 1

- State Table

ps	ns	y
S0	S1	0
S1	S2	1
S2	S3	2
S3	S0	3

Let S0 = 00


S1 = 01

S2 = 10

S3 = 11

Let S0 = reset state

Recall Moore FSM

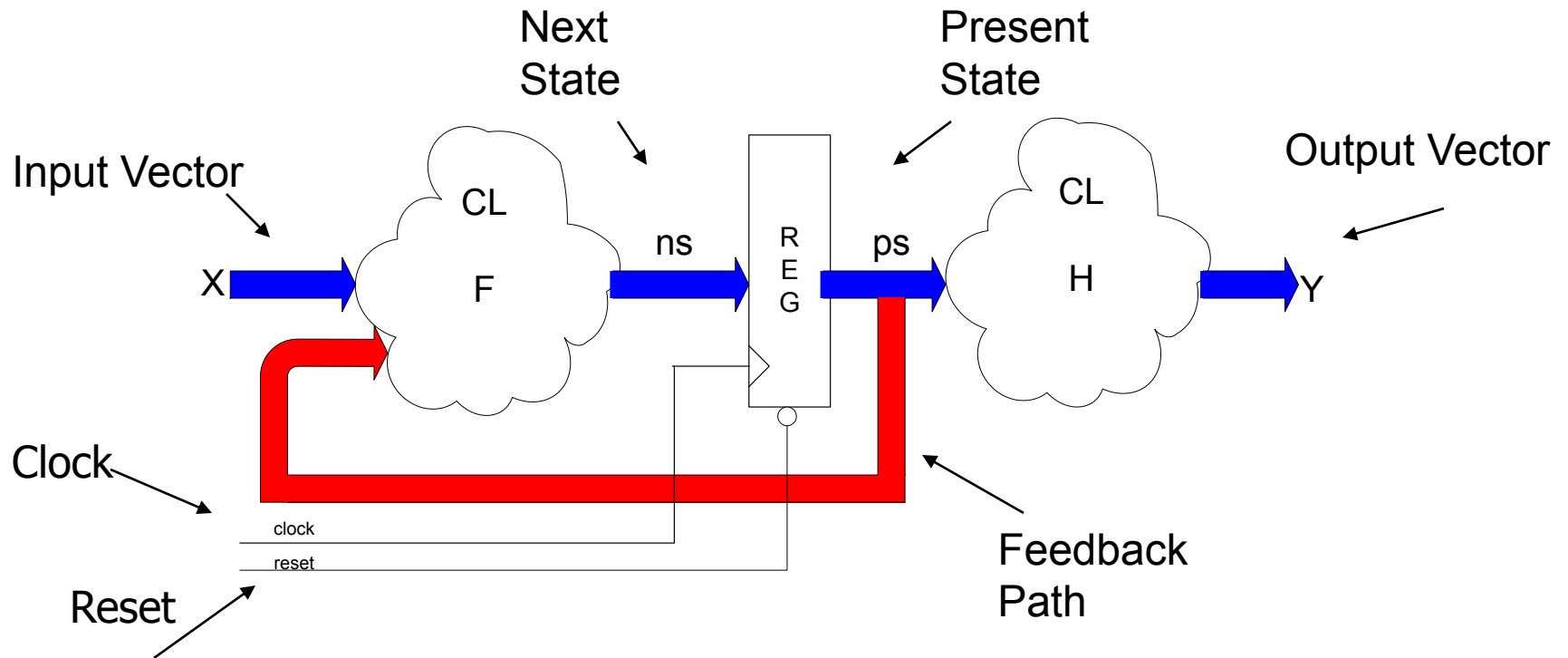

Use a case statement to implement the design since priority is not needed

VHDL Code - Header Info

```
-----  
--  
-- Program: fsm1.vhd  
--  
-- Description: 2-bit up counter.  
--  
-- Author: R.J. Perry  
-- Date:  
-- Revisions:  
-----  
-- Signal I/O  
-----  
-- Signal name      Direction      Description  
-- clock,reset      in             clock,reset  
-- count            out            output count  
-----
```


VHDL Code - Entity Declaration

```
-- Call Altera and IEEE packages
library altera;
use altera.maxplus2.all;
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

-- define entity
entity fsm1 is
  port ( clk,reset: in std_logic;
         count: out std_logic_vector(1 downto 0)
       );
end entity fsm1;
```

VHDL Code - Architecture Dec

```
-- define architecture
```

```
architecture fsm of fsm1 is
```

```
-- define constants
```

```
    constant s0: std_logic_vector(1 downto 0) := "00";
```

```
    constant s1: std_logic_vector(1 downto 0) := "01";
```

```
    constant s2: std_logic_vector(1 downto 0) := "10";
```

```
    constant s3: std_logic_vector(1 downto 0) := "11";
```


```
    signal ns,ps: std_logic_vector(1 downto 0);
```

```
begin
```

VHDL Code -- F Logic

```
--  
-- this process executes the F logic  
--  
process ( ps) ← Input into F logic  
begin  
  ns <= s0; -- This is the default output  
  case ps is  
    when s0 => ns <= s1;  
    when s1 => ns <= s2;  
    when s2 => ns <= s3;  
    when s3 => ns <= s0;  
    when others => ns <= s0; -- default condition  
  end case;  
end process;
```


State Diagram for F Logic

 

Note: we only need to “describe” the behavior
VHDL will “figure out” the functional relationships

VHDL Code -- Register Logic

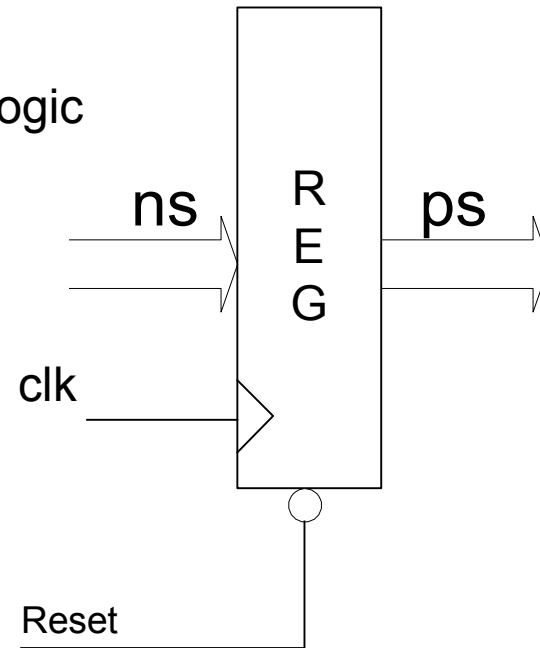
```
--  
-- This process includes the registers  
-- implicitly  
--  
reg: process (clk, reset, ns)  
  begin  
    if(reset = '0') then  
      ps <= s0;  
    elsif (clk'event and clk = '1') then  
      ps <= ns;  
    end if;  
  end process reg;
```



VHDL Code -- H Logic


```
--  
-- Use concurrent statement to implement H Logic  
--
```

```
count <= ps;
```

 


```
end architecture fsm;
```

Recall – Gate Level Logic Diagram

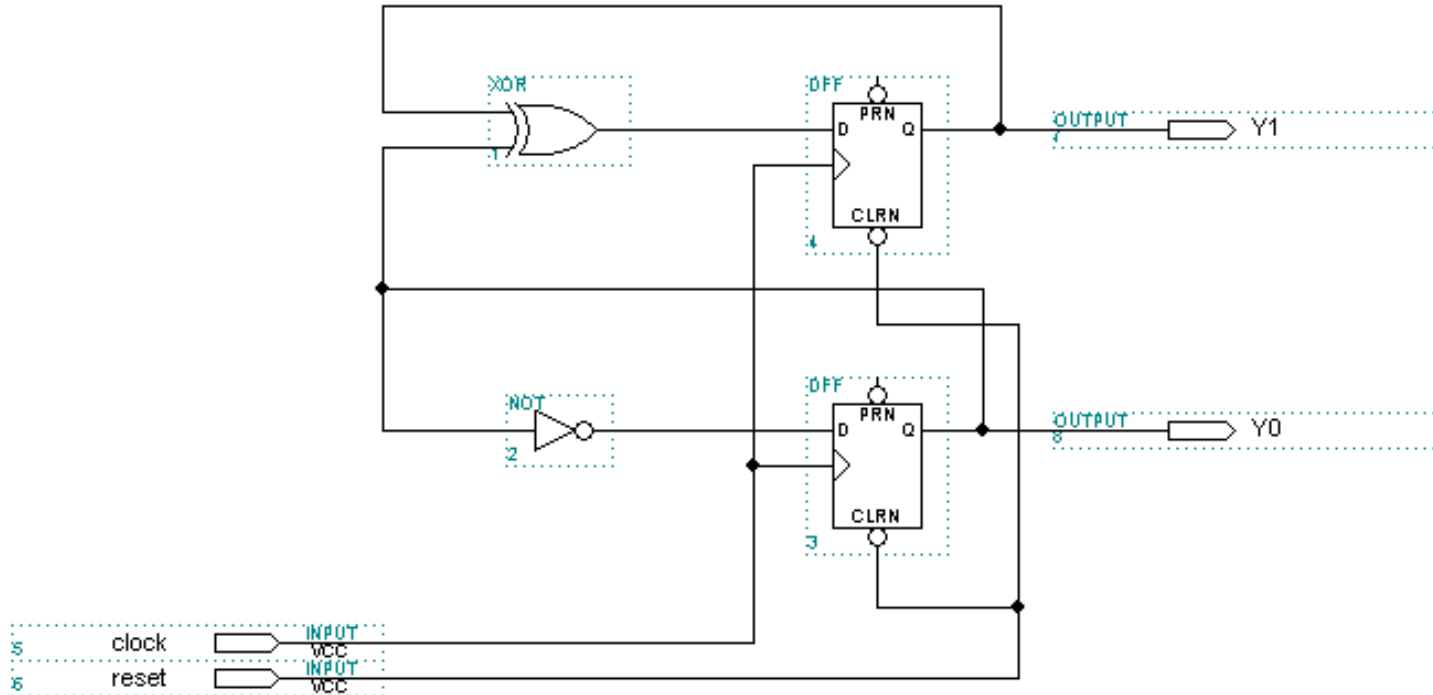

Maxplus II “Produces”

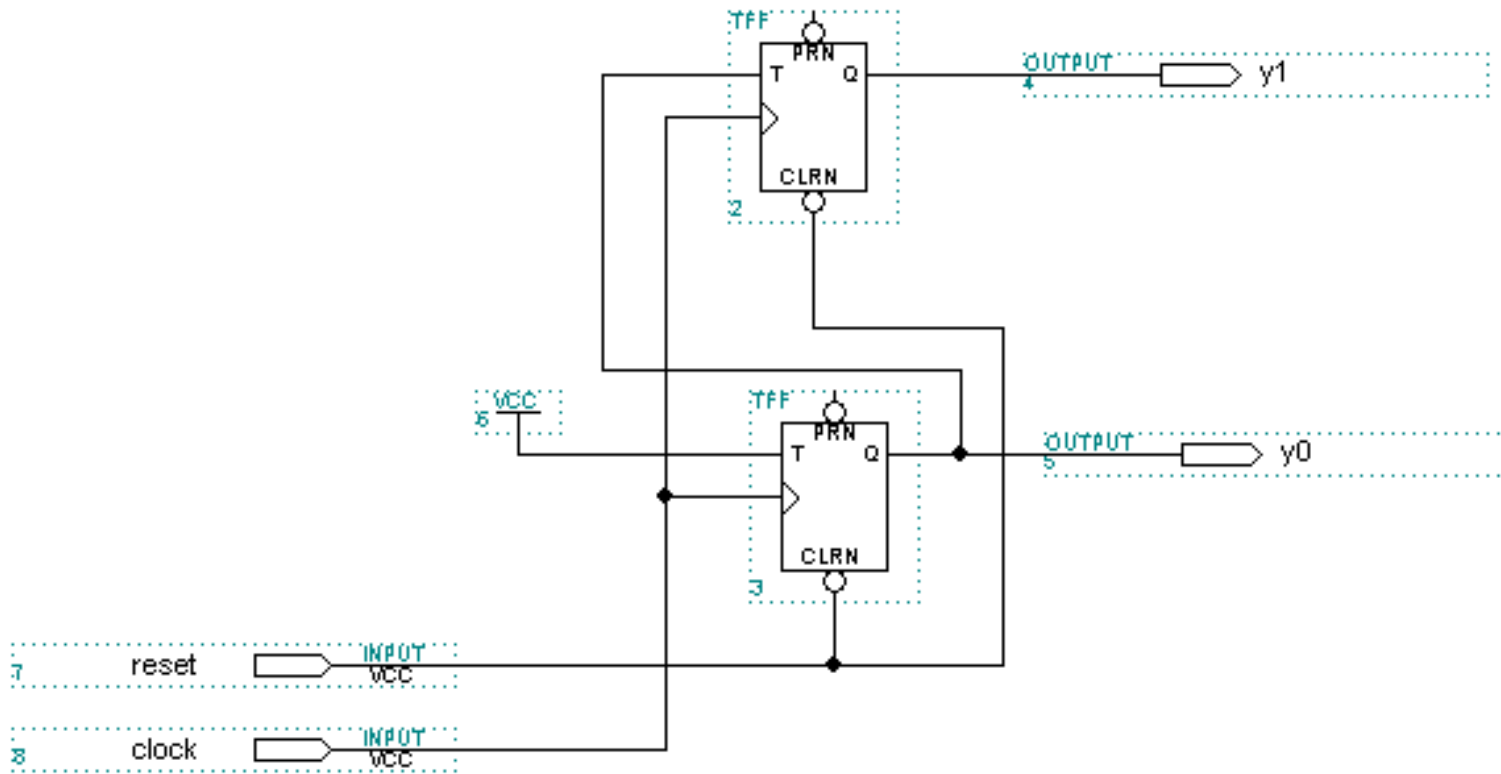

Is this correct?

T = Toggle FF

We have,

$$n_{s0} \leq \overline{p_{s0}}$$

OK, same as before

$$n_{s1} \leq \overline{p_{s1} p_{s0}} + \overline{p_{s0} p_{s1}} = p_{s1} \oplus p_{s0}$$

T input

OK, same as
before

How does this code
fit into our Moore FSM architecture?