

Oscillator

- Introduction of Oscillator
- Linear Oscillator
 - Wien Bridge Oscillator
 - RC Phase-Shift Oscillator
 - LC Oscillator
 - Crystal Oscillator
- Stability

Oscillators

Oscillation: an effect that repeatedly and regularly fluctuates about the mean value

Oscillator: circuit that produces oscillation

Characteristics: wave-shape, frequency, amplitude, distortion, stability


Application of Oscillators

- Oscillators are used to generate signals, e.g.
 - Used as a local oscillator to transform the RF signals to IF signals in a receiver;
 - Used to generate RF carrier in a transmitter
 - Used to generate clocks in digital systems;
 - Used as sweep circuits in TV sets and CRO.

Linear Oscillators

1. Wien Bridge Oscillators
2. RC Phase-Shift Oscillators
3. LC Oscillators
4. Stability

Integrand of Linear Oscillators

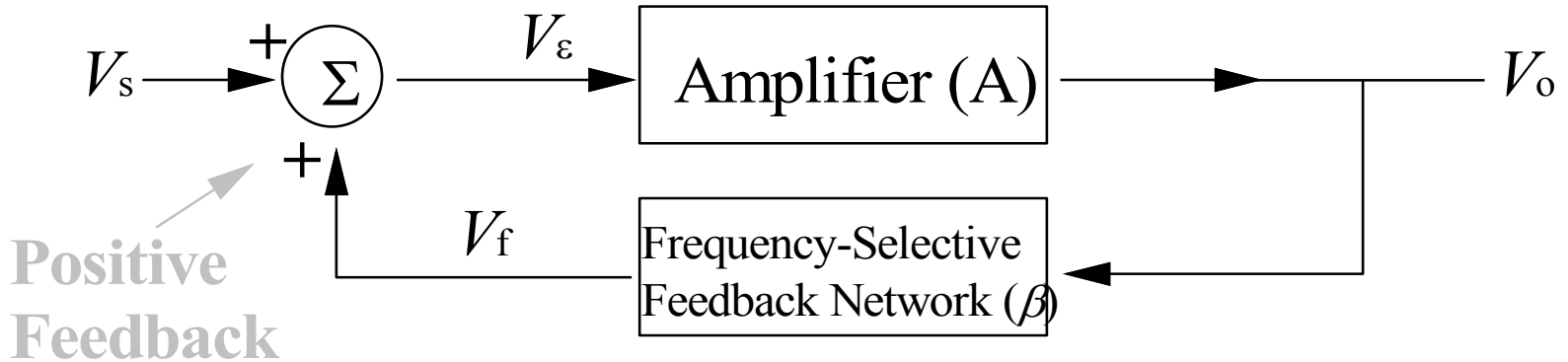


For sinusoidal input is connected

“**Linear**” because the output is approximately sinusoidal

A linear oscillator contains:

- a frequency selection feedback network
- an amplifier to maintain the loop gain at **unity**

Basic Linear Oscillator

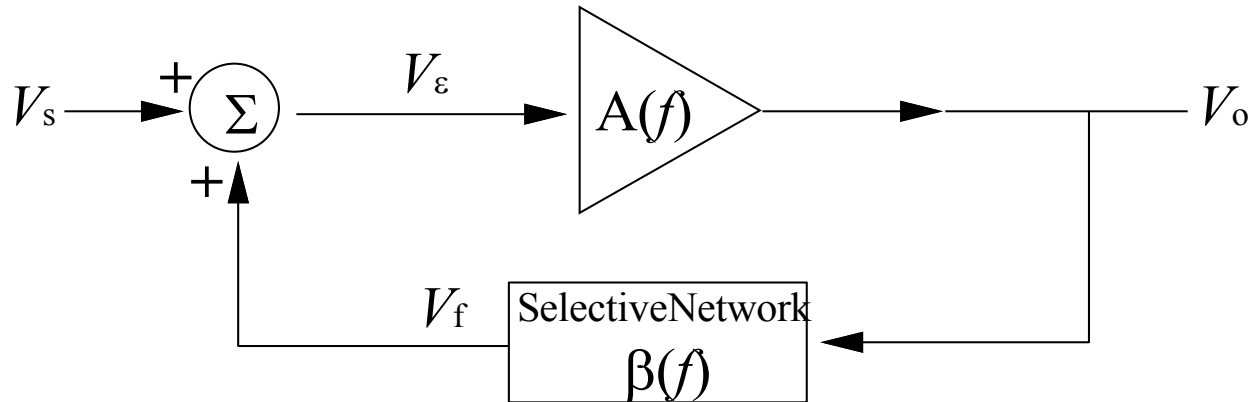

$$V_o = AV_\epsilon = A(V_s + V_f) \quad \text{and} \quad V_f = \beta V_o$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$


If $V_s = 0$, the only way that V_o can be nonzero is that **loop gain $A\beta=1$** which implies that

$$|A\beta| = 1 \quad (\mathbf{Barkhausen\ Criterion})$$

$$\angle A\beta = 0$$

Wien Bridge Oscillator

Frequency Selection Network

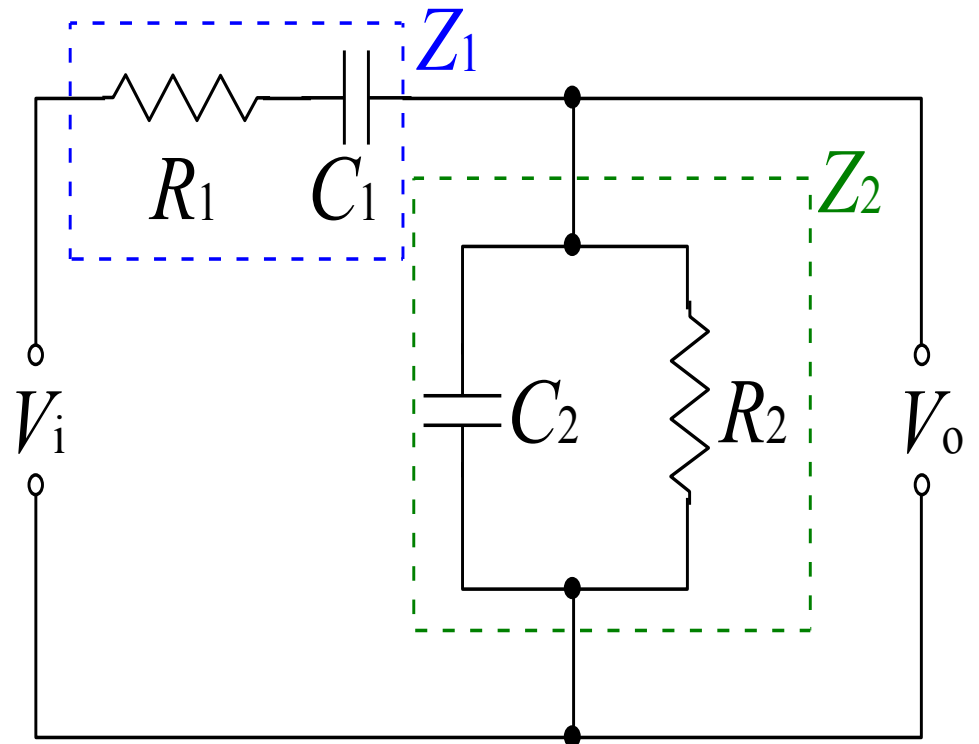

Example

By setting $\omega = \frac{1}{RC}$, we get

Imaginary part = 0 and $\beta = \frac{1}{3}$

Due to **Barkhausen Criterion**,


Loop gain $A_v\beta=1$

where

A_v : Gain of the amplifier


$$A_v\beta = 1 \Rightarrow A_v = 3 = 1 + \frac{R_f}{R_1}$$
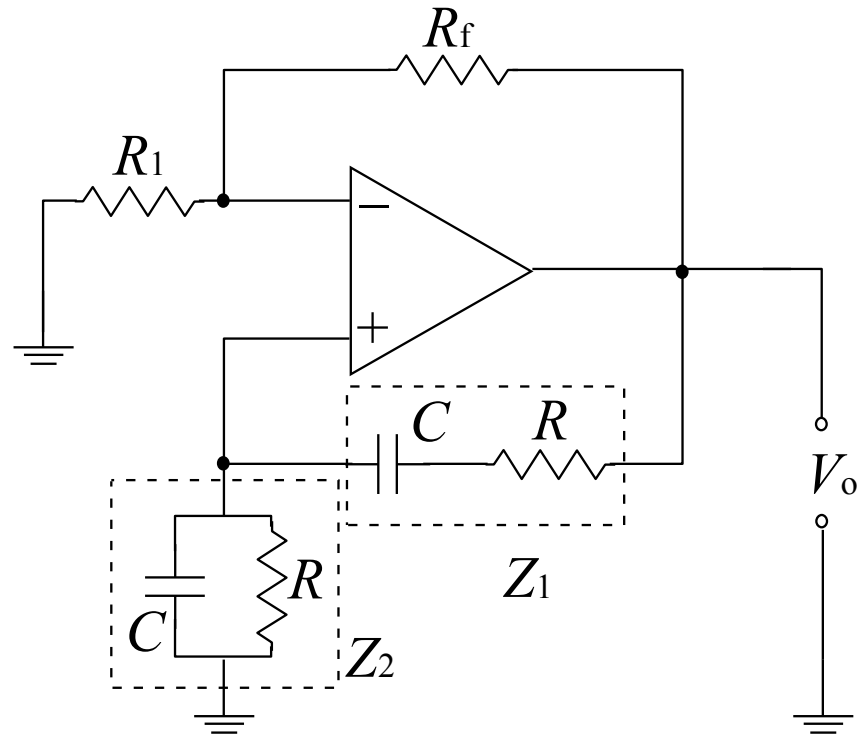
$$\text{Therefore, } \frac{R_f}{R_1} = 2$$



Wien Bridge Oscillator

RC Phase-Shift Oscillator

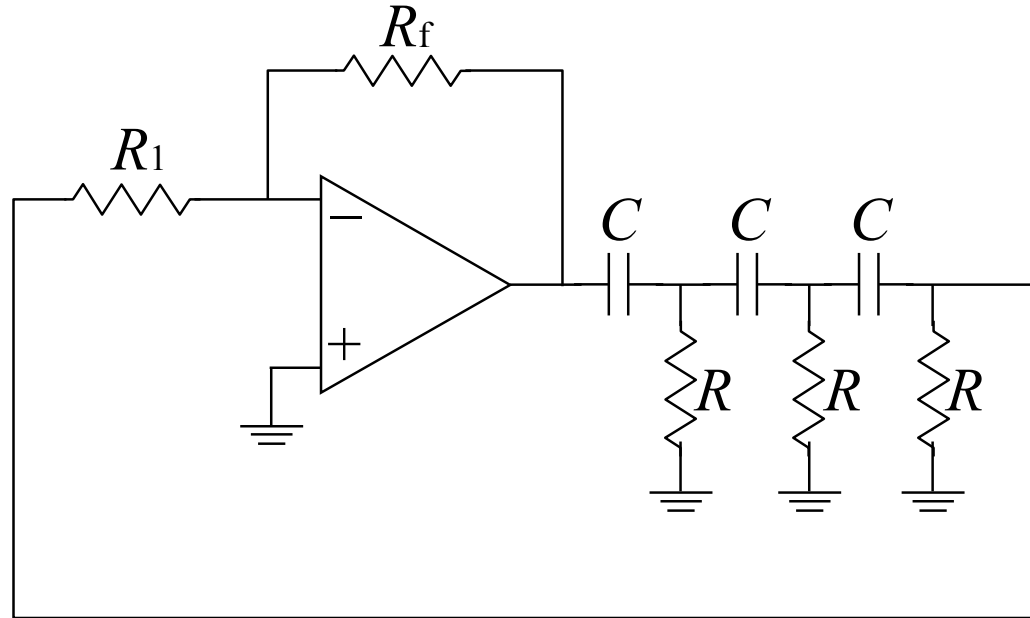


- Using an inverting amplifier
- The additional 180° phase shift is provided by an RC phase-shift network

LC Oscillators


- The frequency selection network (Z_1 , Z_2 and Z_3) provides a phase shift of 180°
- The amplifier provides an additional shift of 180°

Two well-known Oscillators:

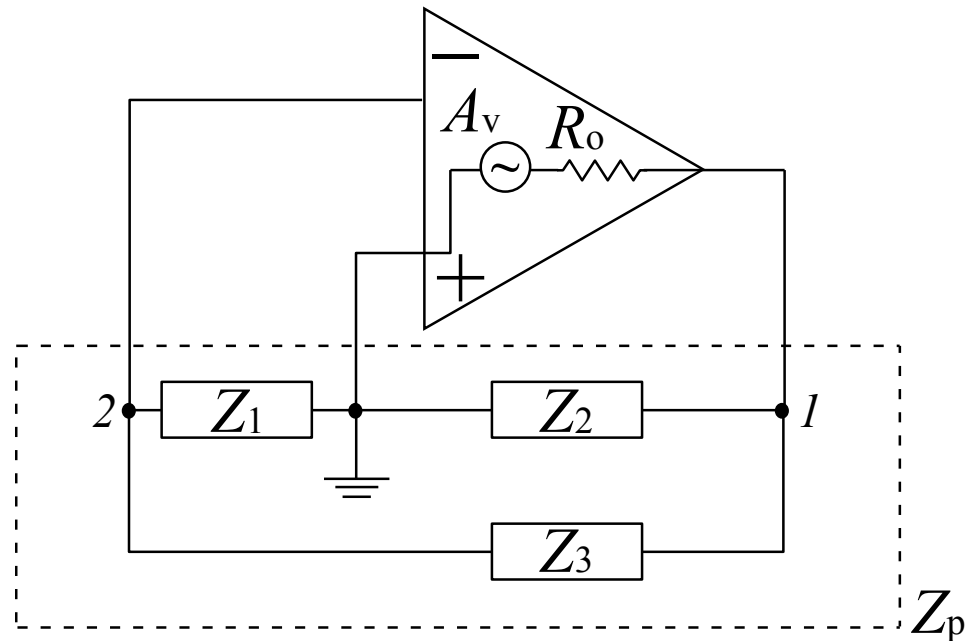- Colpitts Oscillator
- Harley Oscillator




Hartley Oscillator

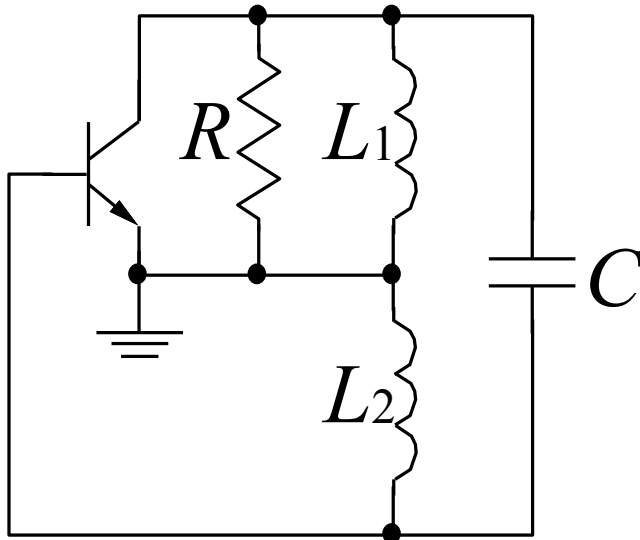

$$\omega_o = \frac{1}{\sqrt{(L_1 + L_2)C}}$$

$$g_m = \frac{L_1}{RL_2}$$


Colpitts Oscillator

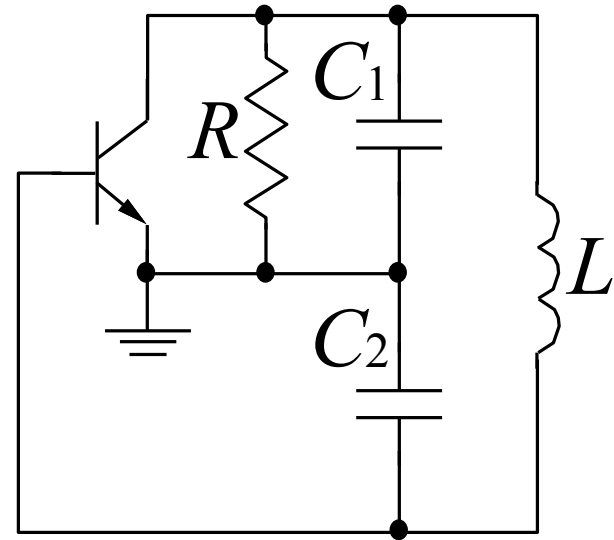

$$\omega_o = \frac{1}{\sqrt{LC_T}} \quad C_T = \frac{C_1 C_2}{C_1 + C_2}$$

$$g_m = \frac{C_2}{RC_1}$$

Colpitts Oscillator

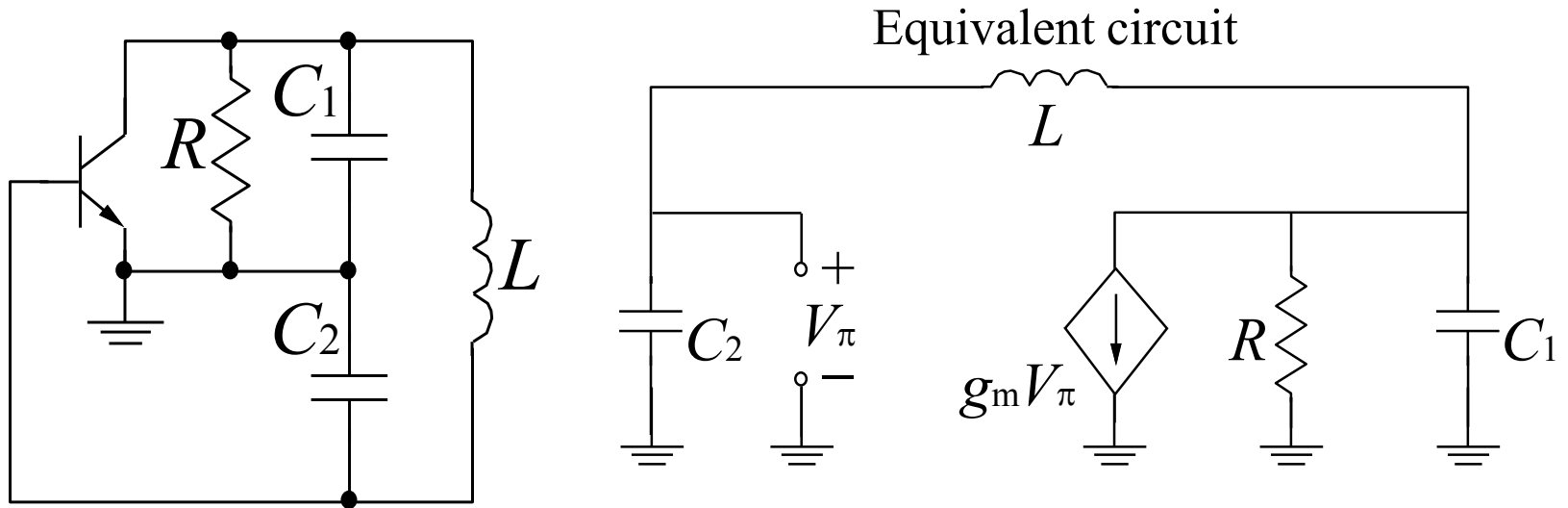

In the equivalent circuit, it is assumed that:


- Linear small signal model of transistor is used
- The transistor capacitances are neglected
- Input resistance of the transistor is large enough

- **Crystal oscillators**

- **frequency stability** is determined by the ability of the circuit to select a particular frequency
- in tuned circuits this is described by the **quality factor, Q**
- **piezoelectric crystals** act like resonant circuits with a very high Q – as high as 100,000



(a) Circuit symbol

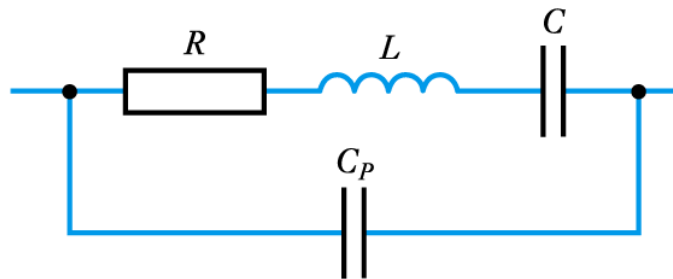

(b) Equivalent circuit

- A typical crystal oscillator

