



Chapter 8

Oscillator and Power Amplifier



Outline

- Oscillator
- Power amplifier




Oscillator

- Basic principles of sinusoidal oscillator.
- The Wien-bridge oscillator
- The phase shift oscillator

Basic Principles of Sinusoidal Oscillator

- The oscillator feedback loop

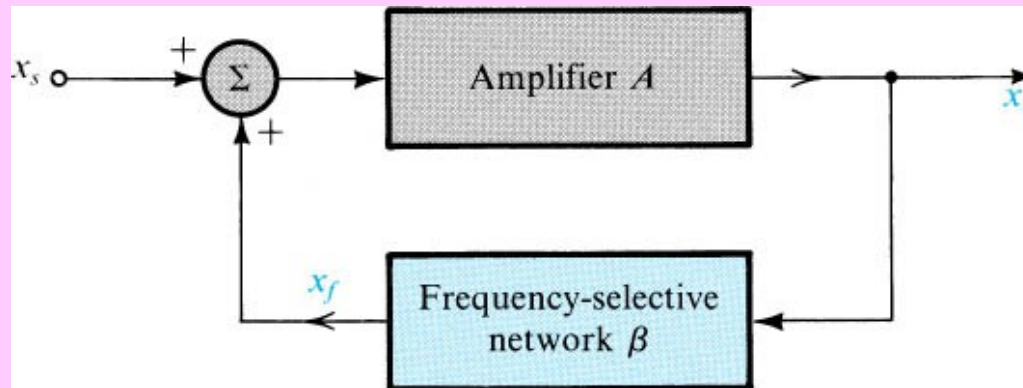

- The basic structure of a sinusoidal oscillator.
- A positive-feedback loop is formed by an amplifier and a frequency-selective network.



Basic Principles of Sinusoidal Oscillator

- Feedback signal x_f is summed with a positive sign
- The gain-with-feedback is

$$A_f(s) = \frac{A(s)}{1 - A(s)\beta(s)}$$

- The oscillation criterion


$$L(j\omega_0) = A(j\omega_0)\beta(j\omega_0) = 1$$





Basic Principles of Sinusoidal Oscillator

- Nonlinear amplitude control
 - To ensure that oscillations will start, the $A\beta$ is slightly greater than unity.
 - As the power supply is turned on, oscillation will grow in amplitude.
 - When the amplitude reaches the desired level, the nonlinear network comes into action and cause the $A\beta$ to exactly unity.

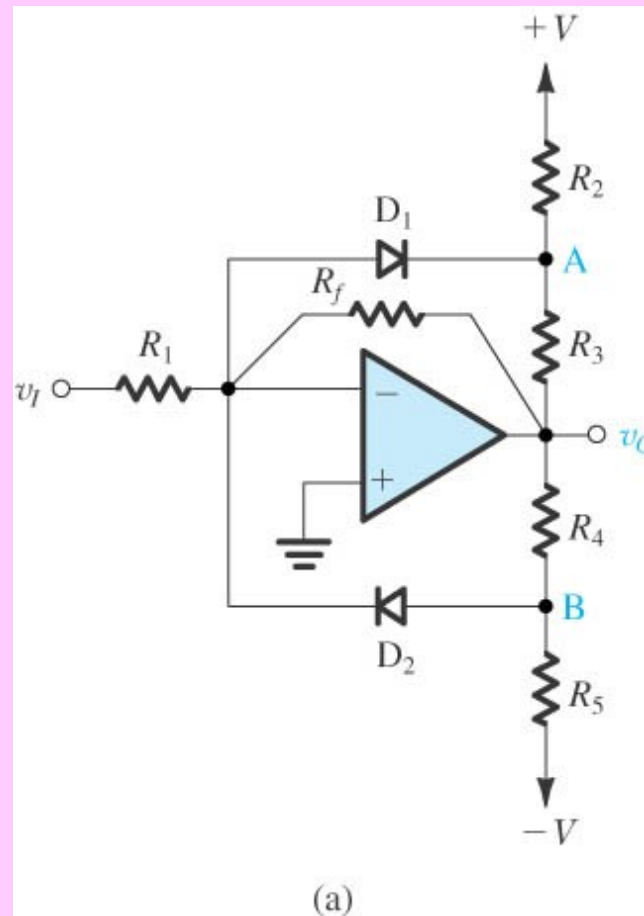A Popular Limiter Circuit for Amplitude Control



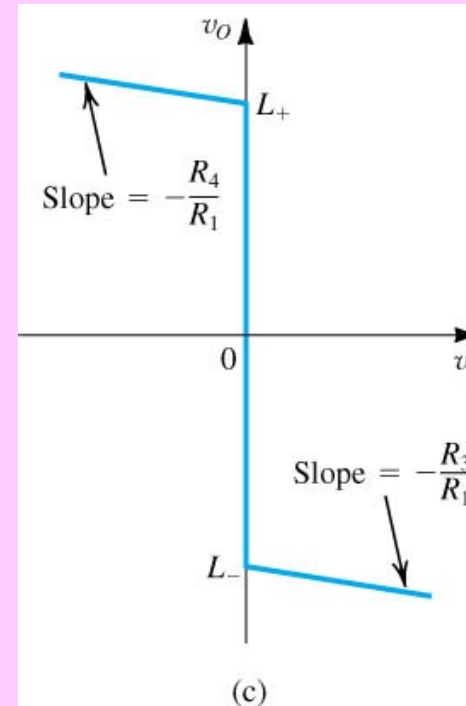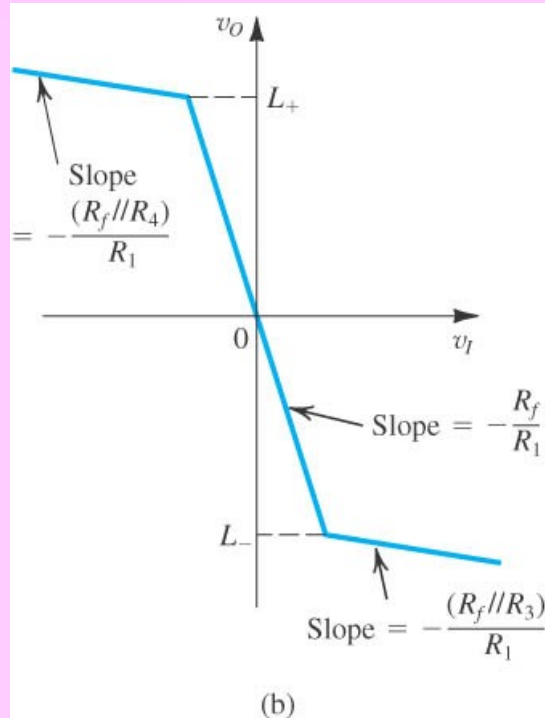A Popular Limiter Circuit for Amplitude Control




- Transfer characteristic of the limiter circuit;
- When R_f is removed, the limiter turns into a comparator with the characteristic shown.



Oscillator Circuits

- Op Amp-RC Oscillator Circuits
 - The Wien-Bridge Oscillator
 - The phase-Shift Oscillator
- LC-Tuned Oscillator
 - Colpitts oscillator
 - Hareley oscillator
- Crystal Oscillator

The Wien-Bridge Oscillator

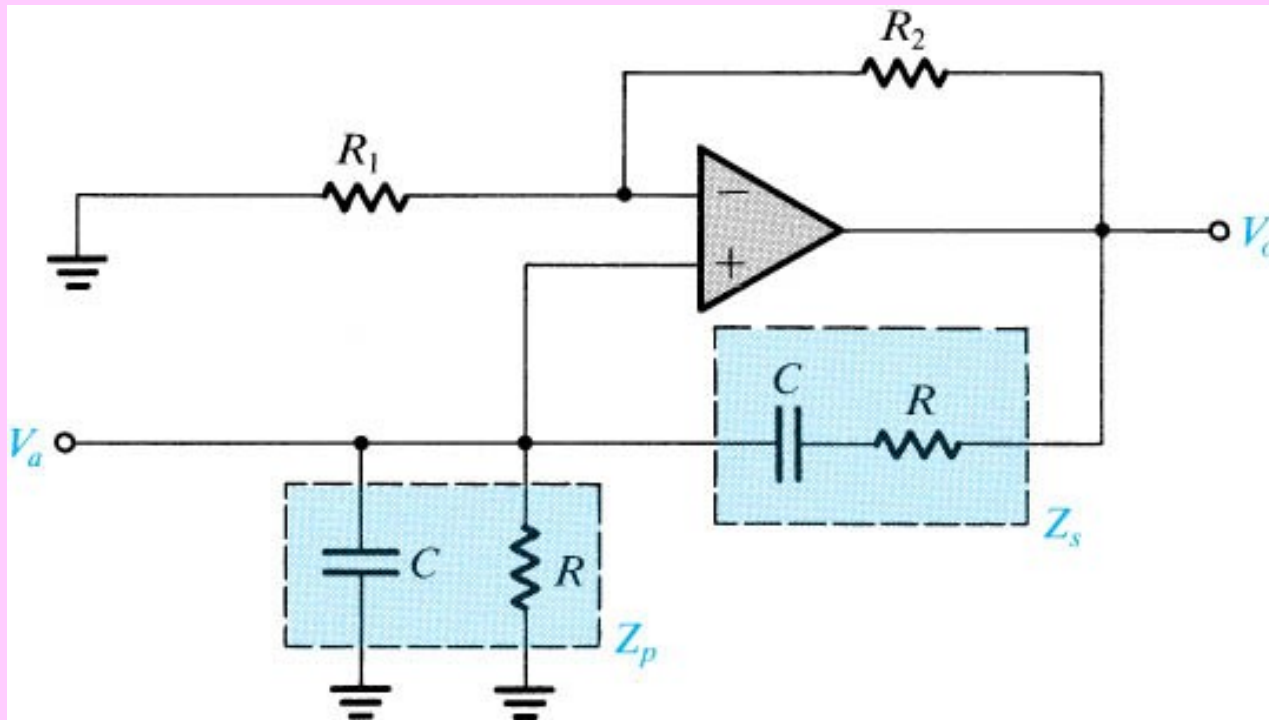

A Wien-bridge oscillator without amplitude stabilization.



The Wien-Bridge Oscillator

- The loop gain transfer function

$$L(s) = \frac{1 + R_2/R_1}{3 + sCR + 1/sCR}$$


- Oscillating frequency

$$\omega_0 = 1/RC$$

- To obtain sustained oscillation


$$R_2/R_1 = 2$$

The Wien-Bridge Oscillator

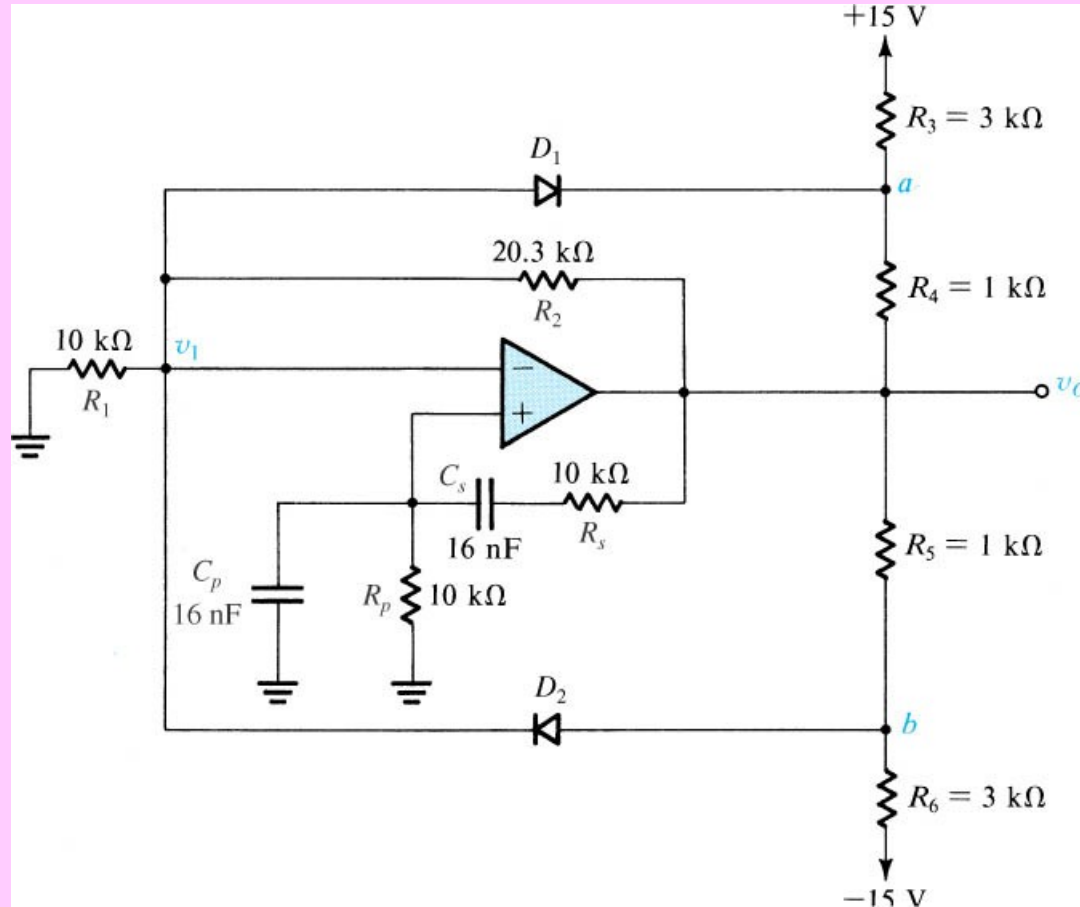

A Wien-bridge oscillator with a limiter used for amplitude control.

The Phase-Shift Oscillator

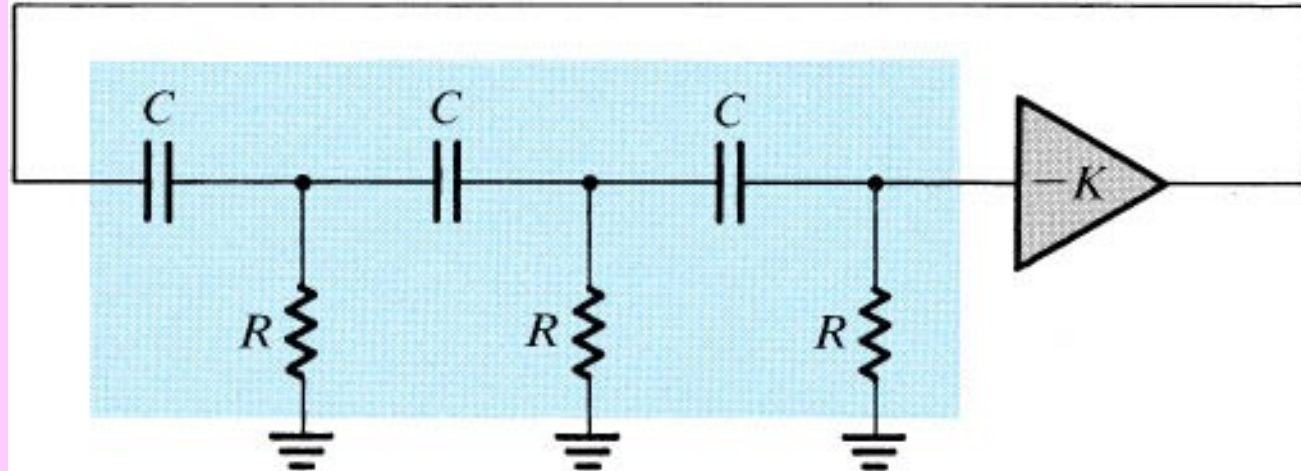


The circuit consists of a negative-gain amplifier and three-section RC ladder network.

Oscillating frequency is the one that the phase shift of the RC network is 180°




The Phase-Shift Oscillator

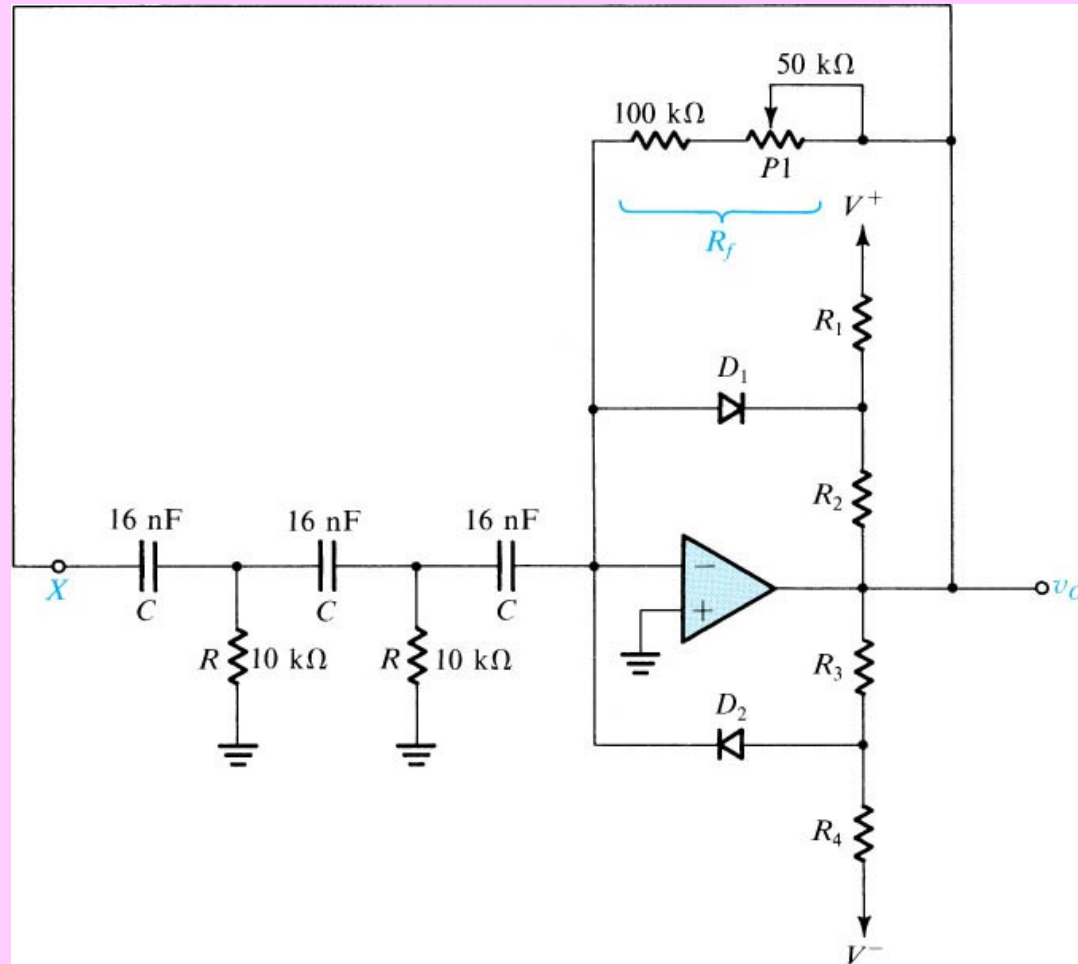

A practical phase-shift oscillator with a limiter for amplitude stabilization.



The LC-Tuned oscillator

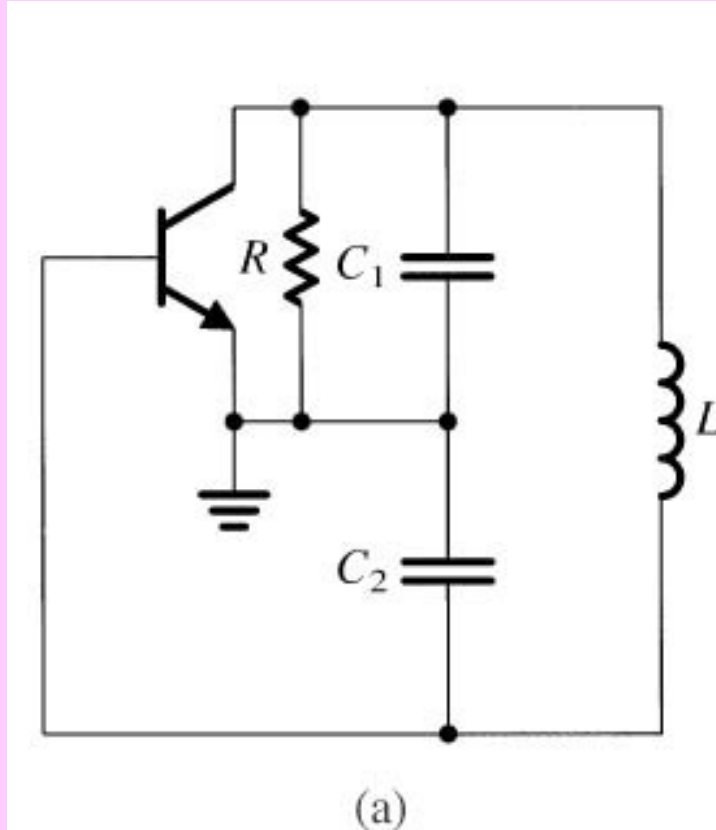

➤ Colpitts Oscillator


➤ A parallel LC resonator connected between collector and base.

➤ Feedback is achieved by way of a capacitive divider

➤ Oscillating frequency is determined by the resonance frequency.

$$\omega_0 = 1 / \sqrt{L \left(\frac{C_1 C_2}{C_1 + C_2} \right)}$$

The LC-Tuned oscillator

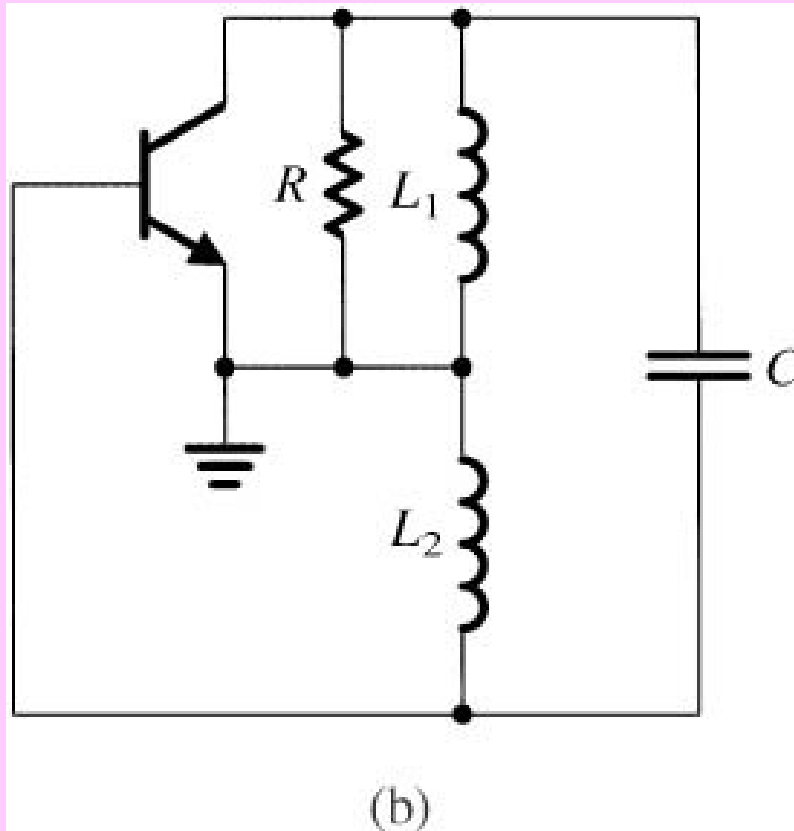

➤ Hartley Oscillator


➤ A parallel LC resonator connected between collector and base.

➤ Feedback is achieved by way of an inductive divider.

➤ Oscillating frequency is determined by the resonance frequency.


$$\omega_0 = 1 / \sqrt{L \left(\frac{C_1 C_2}{C_1 + C_2} \right)}$$

Crystal Oscillators

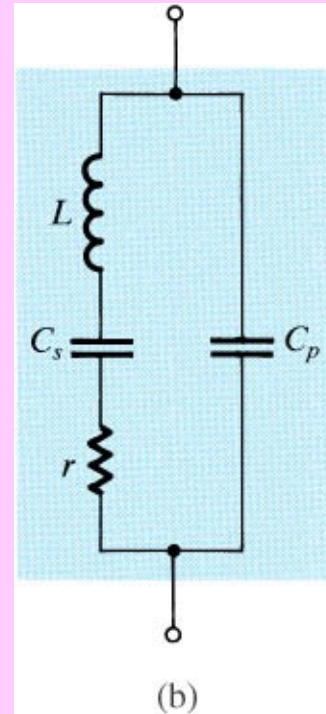

A piezoelectric crystal. **(a)** Circuit symbol. **(b)** Equivalent circuit.

Crystal Oscillators

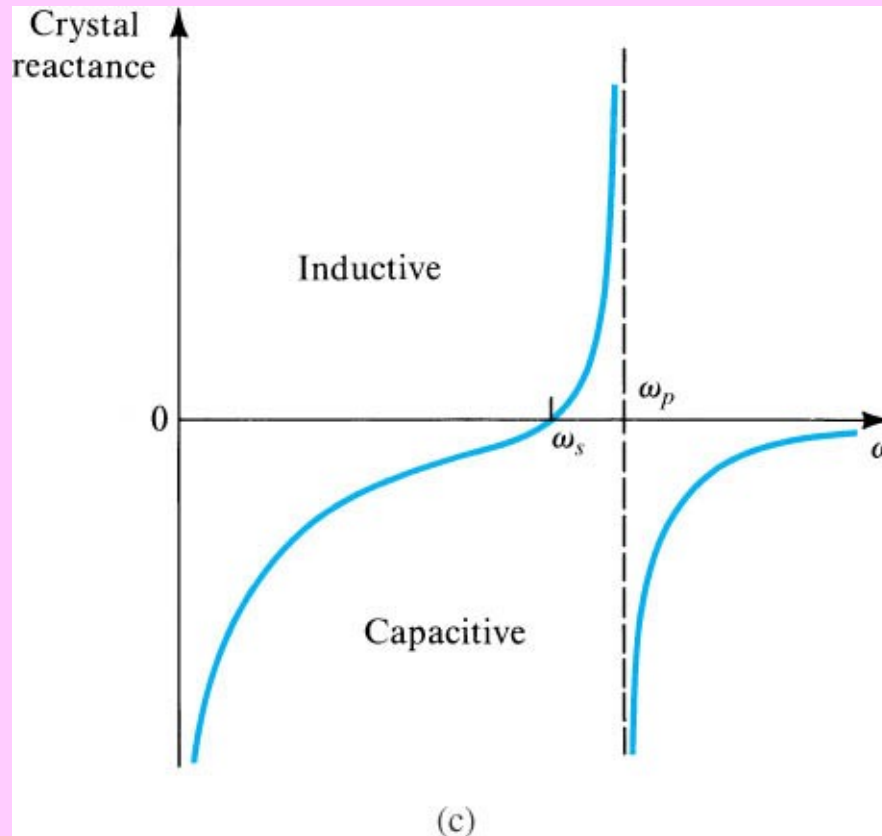

➤ Crystal reactance versus frequency (neglecting the small resistance r ,).


➤ A series resonance at

$$\omega_s = 1/\sqrt{LC_s}$$

➤ A parallel resonance at

$$\omega_p = 1/\sqrt{L\left(\frac{C_s C_p}{C_s + C_p}\right)}$$

Crystal Oscillators

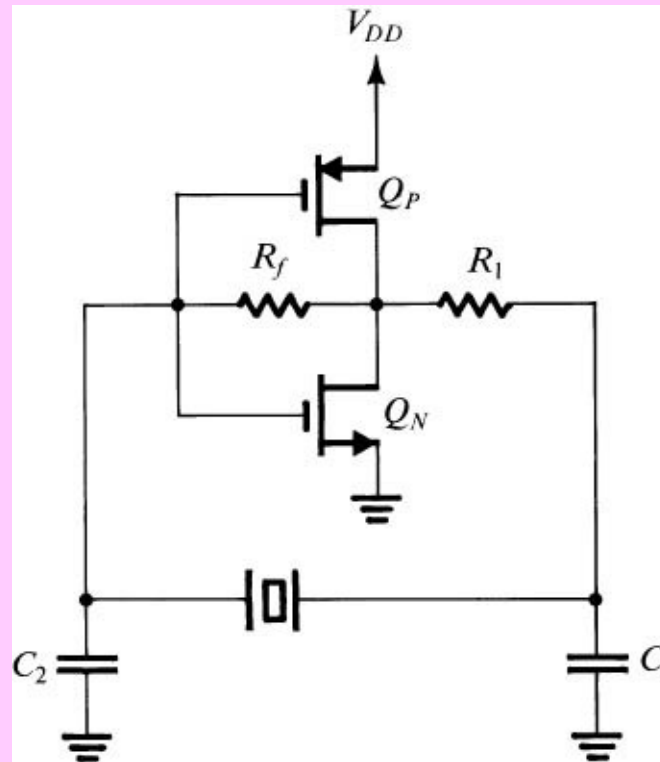

A Pierce crystal oscillator utilizing a CMOS inverter as an amplifier.



Power Amplifier



- Small-signal approximation and models either are not applicable or must be used with care.
- Deliver the power to the load in *efficient* manner.
- Power dissipation is as low as possible.



Classification of Power Amplifier


- Power amplifiers are classified according to the collector current waveform that results when an input signal is applied.
- Conducting angle.

Classification of Power Amplifier

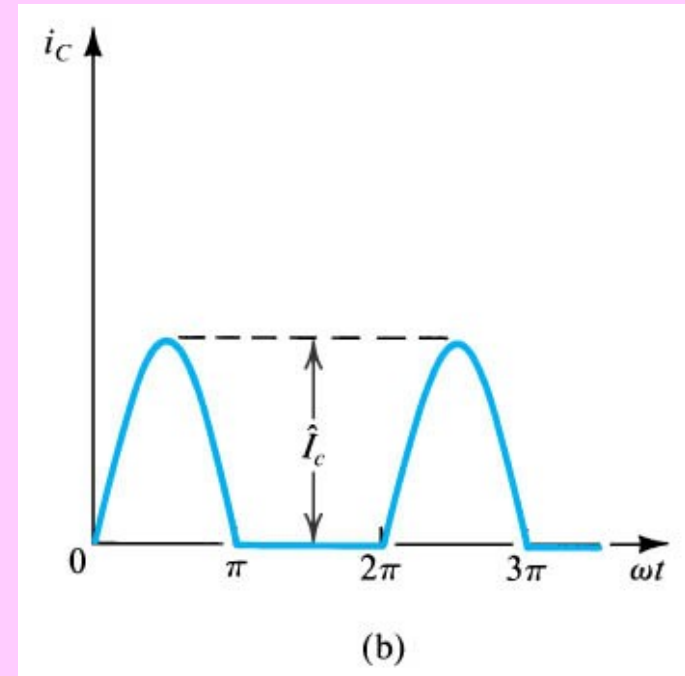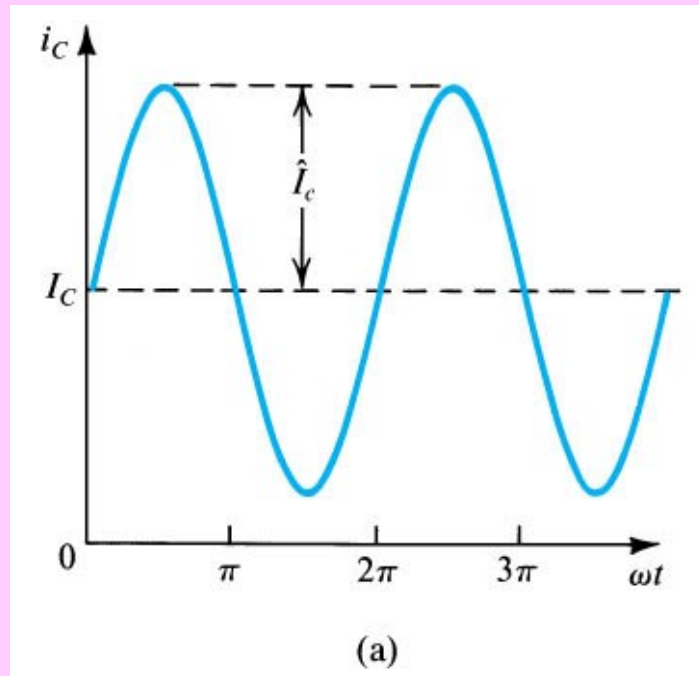


Collector current waveforms for transistors operating
in **(a)** class A, **(b)** class B

Classification of Power Amplifier

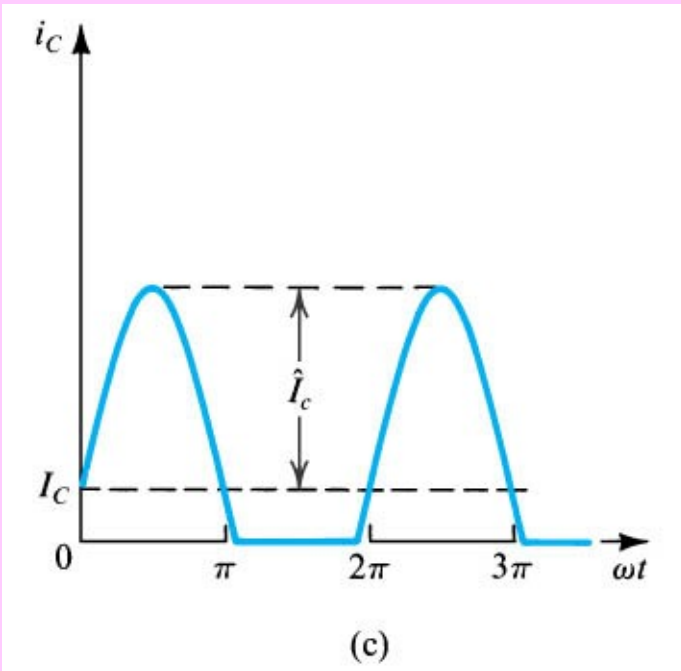


class AB

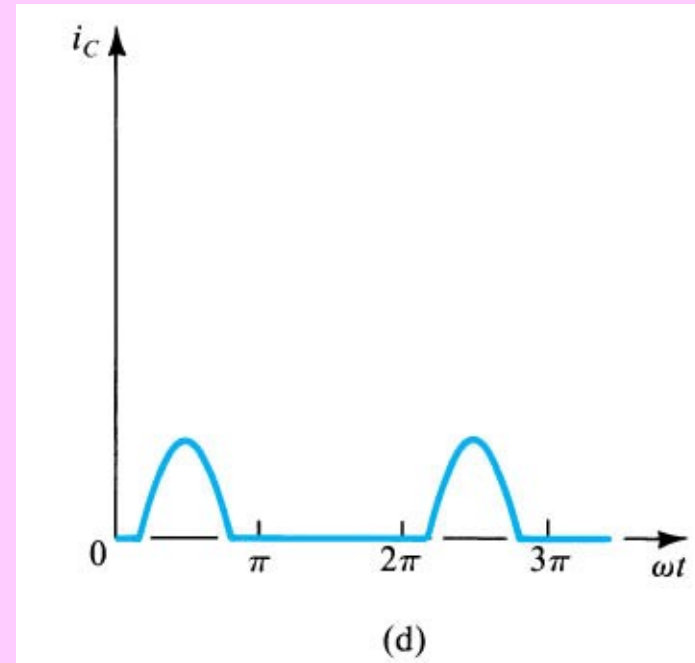

class C


Class B Output Stage

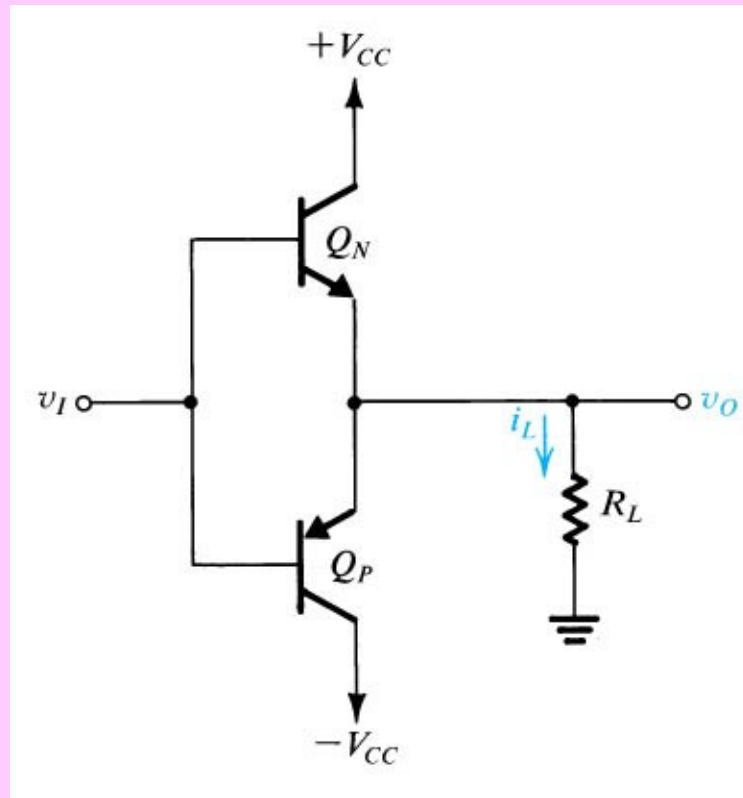

- A class B output stage.
- Complementary circuits.
- Push-pull operation
- Maximum power-conversion efficiency is 78.5%




Transfer Characteristic

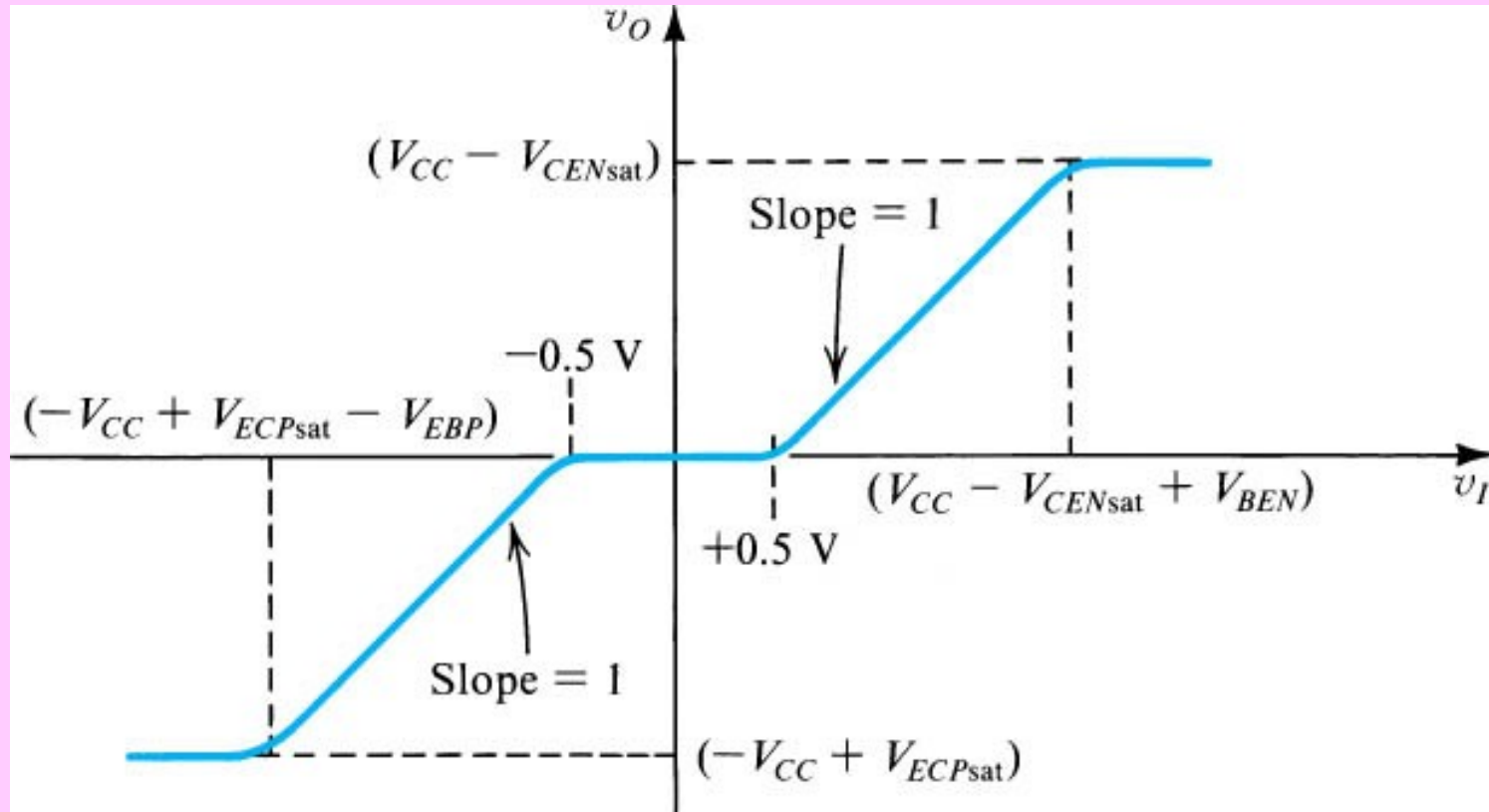



上海交通大学
Shanghai Jiao Tong University

Crossover Distortion

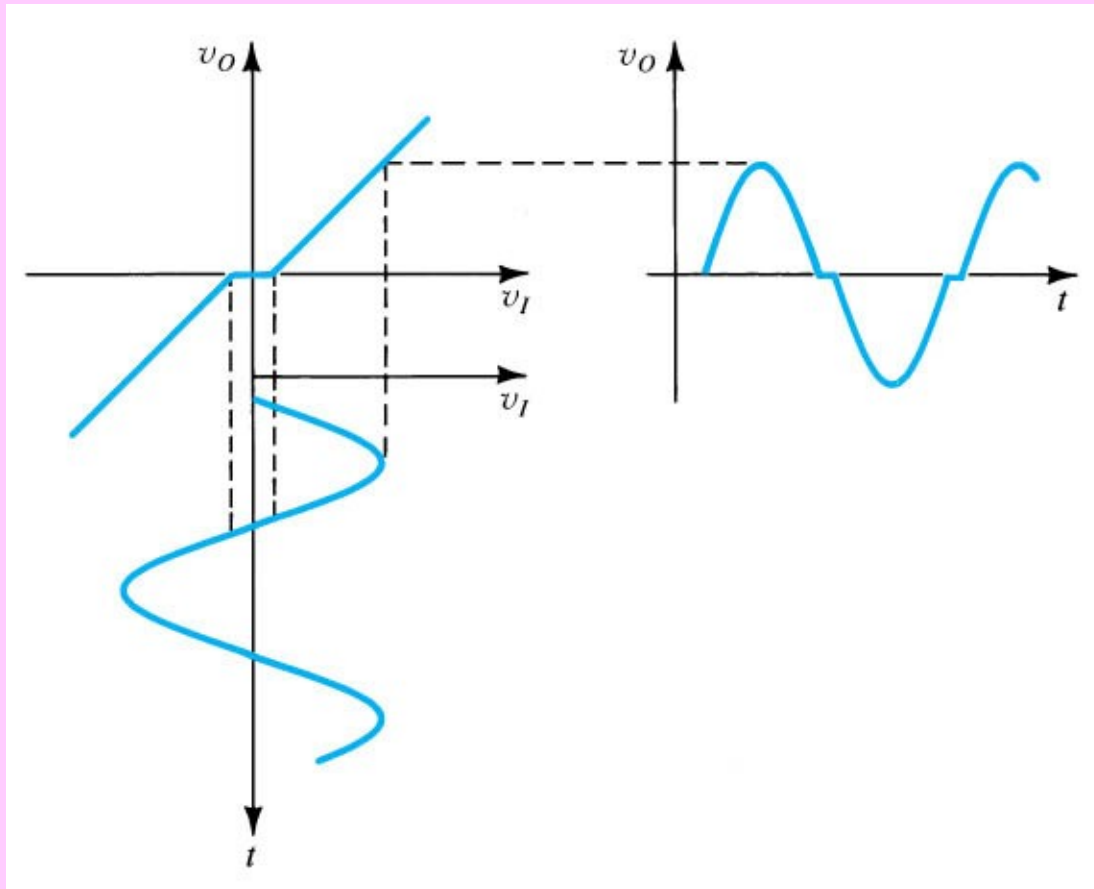



Power Dissipation

- The load power

$$P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

- Maximum load power

$$P_{L\max} = \frac{1}{2} \frac{\hat{V}_o^2}{R_L} \Big|_{\hat{V}_o = V_{CC}} = \frac{V_{CC}^2}{2R_L}$$



Power Dissipation

- Total supply power

$$P_s = \frac{2}{\pi} \frac{\hat{V}_o}{R_L} V_{CC}$$

- Maximum total supply power

$$P_{s \max} = \frac{2}{\pi} \frac{\hat{V}_o}{R_L} V_{CC} \Big|_{\hat{V}_o = V_{CC}} = \frac{2}{\pi} \frac{V_{CC}^2}{R_L}$$



Power Dissipation

- Power-conversion efficiency

$$\eta = \frac{\pi}{4} \frac{\hat{V}_o}{V_{CC}}$$

- Maximum power-conversion efficiency

$$\eta_{\max} = \frac{\pi}{4} \frac{\hat{V}_o}{V_{CC}} \Big|_{\hat{V}_o = V_{CC}} = 78.5\%$$



Power Dissipation


- Power dissipation

$$P_D = \frac{2}{\pi} \frac{\hat{V}_o}{R_L} V_{CC} - \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

- Maximum Power dissipation


$$\begin{aligned} P_{DN\max} = P_{DP\max} &= \frac{2}{\pi} \frac{\hat{V}_o}{R_L} V_{CC} - \frac{1}{2} \frac{\hat{V}_o^2}{R_L} \Big|_{\hat{V}_o = \frac{2}{\pi} V_{CC}} \\ &= \frac{2V_{CC}^2}{\pi^2 R_L} = 0.2P_{L\max} \end{aligned}$$

Class AB Output Stage

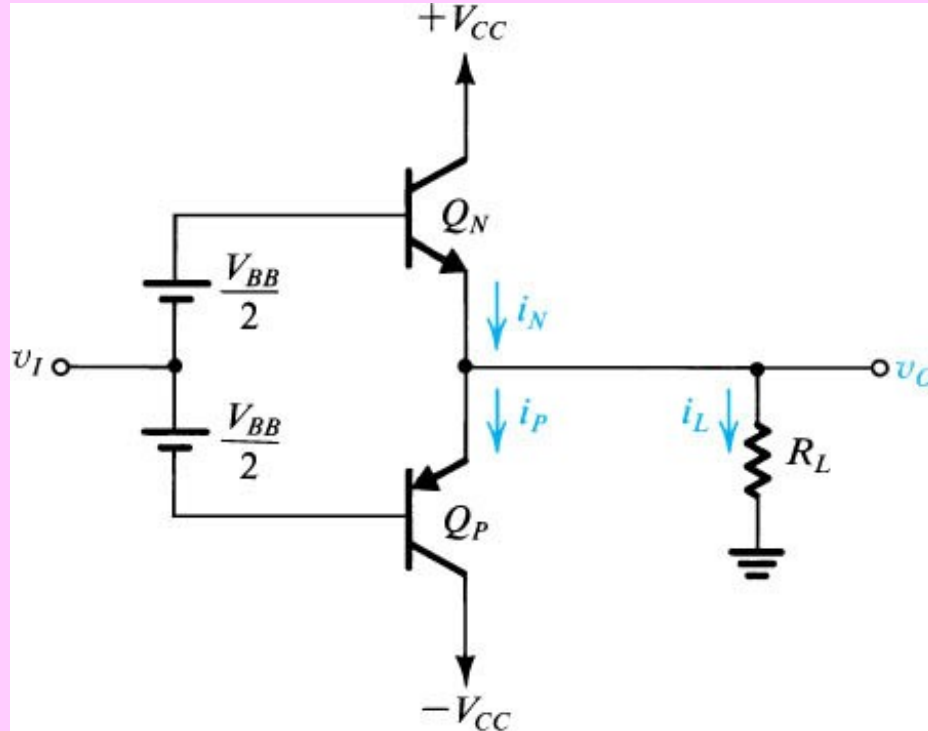

A bias voltage V_{BB} is applied between the bases of Q_N and Q_P , giving rise to a bias current I_Q . Thus, for small v_I , both transistors conduct and crossover distortion is almost completely eliminated.

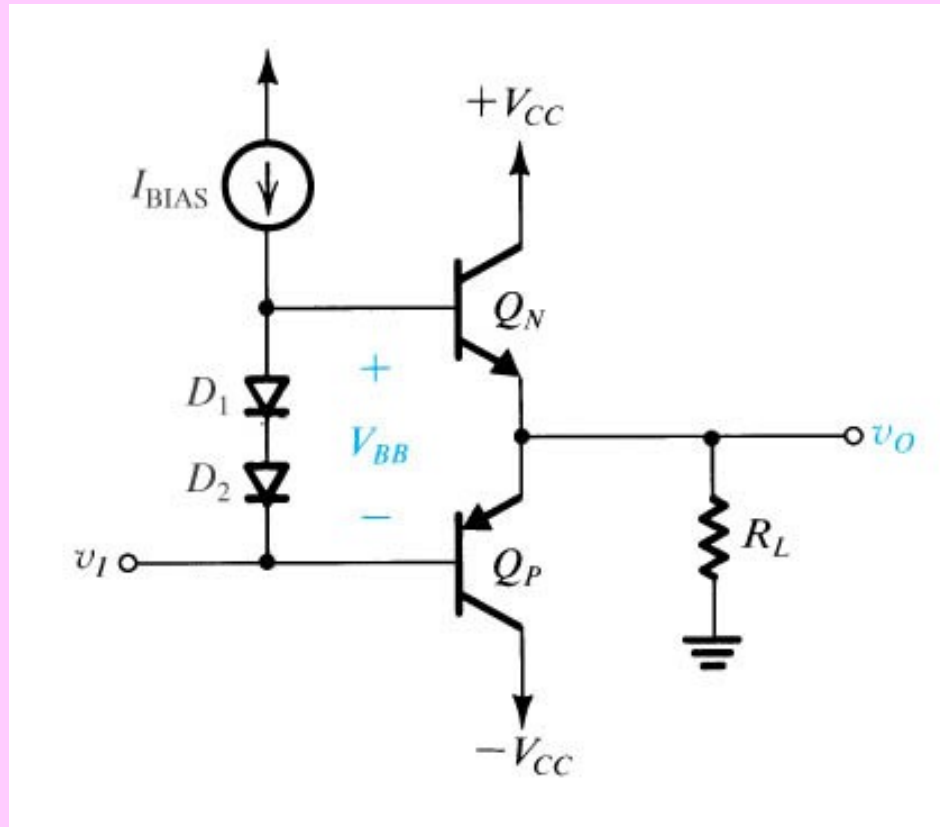A Class AB Output Stage Utilizing Diodes for Biasing



A Class AB Output Stage Utilizing A V_{BE} Multiplier for Biasing

