

# Chapter 9

## Output Stages And Power Amplifiers





Low Output Resistance – no loss of gain

Small-Signal Not applicable

Total-Harmonic Distortion (fraction of %)

Efficiency

Temperature Requirements

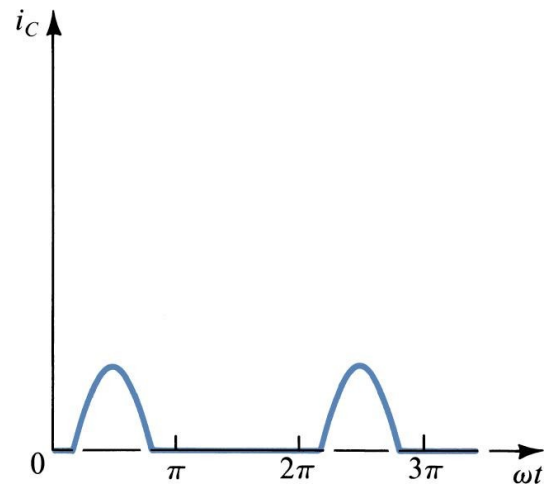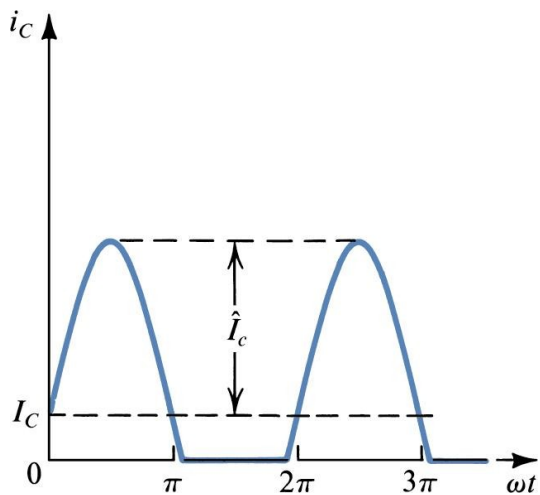
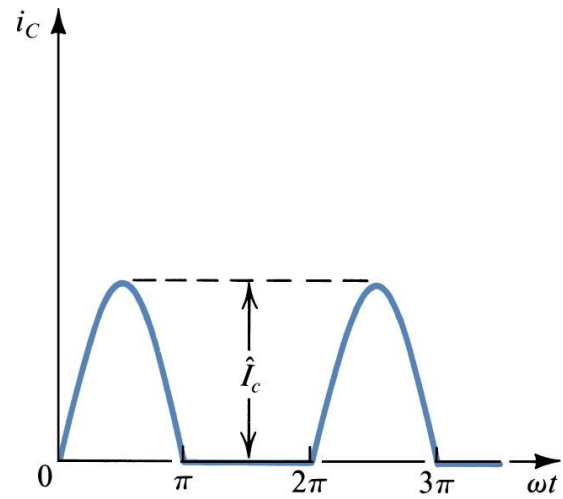
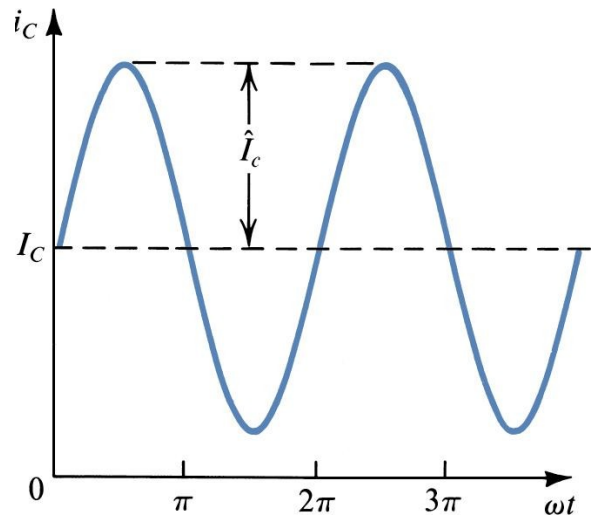


Collector current waveforms for transistors operating in (a) class A, (b) class B, (c) class AB, and (d) class C amplifier stages.

# Class A

An emitter follower ( $Q_1$ ) biased with a constant current  $I$  supplied by transistor  $Q_2$ .

## Transfer Characteristics

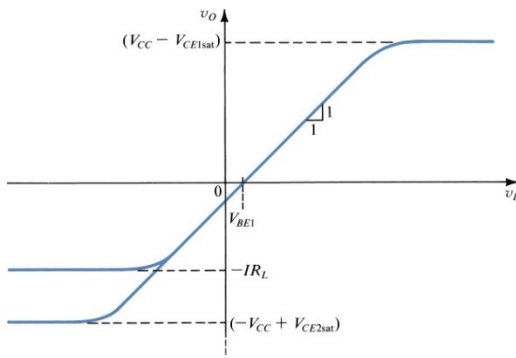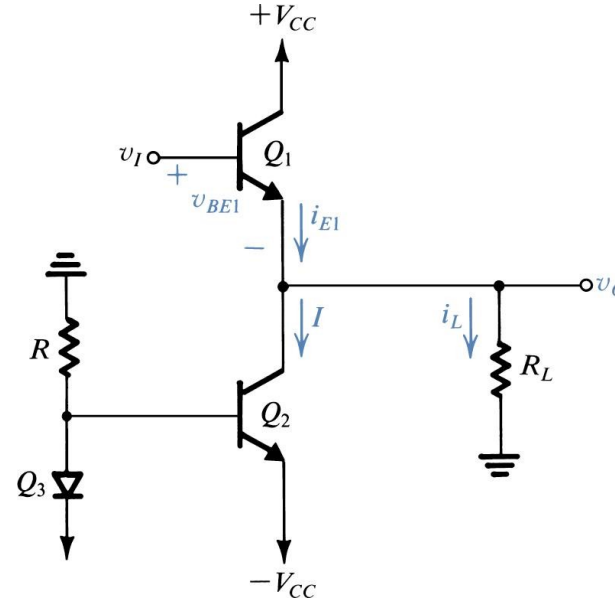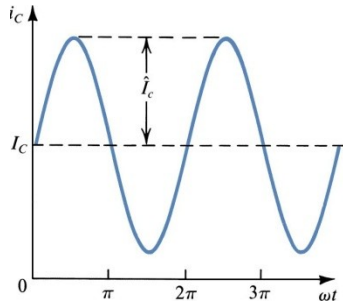

Transfer characteristic of the emitter follower. This linear characteristic is obtained by neglecting the change in  $v_{BE1}$  with  $i_L$ . The maximum positive output is determined by the saturation of  $Q_1$ . In the negative direction, the limit of the linear region is determined either by  $Q_1$  turning off or by  $Q_2$  saturating, depending on the values of  $I$  and  $R_L$ .


# Class A

## Transfer Characteristics

Crossover distortion can be eliminated by biasing the transistors at a small, non-zero current.

A bias Voltage  $V_{BB}$  is applied between  $Q_n$  and  $Q_p$ .

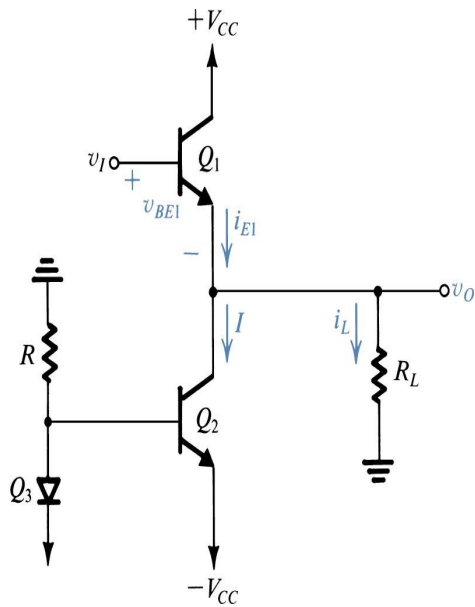For  $v_i = 0$ ,  $v_o = 0$ , and a voltage  $V_{BB}/2$  appears across the base-emitter junction of each transistor.



$$i_N = i_P = I_Q = I_S \cdot e^{\frac{V_{BB}}{2 \cdot V_T}}$$

$V_{BB}$  is selected to result the required quiescent current  $I_Q$

$$v_o = v_i + \frac{V_{BB}}{2} - v_{BEN}$$

$$i_N = i_P + i_L$$

$$v_{BEN} + v_{EBP} = V_{BB}$$


$$V_T \cdot \ln\left(\frac{i_N}{I_S}\right) + V_T \cdot \ln\left(\frac{i_P}{I_S}\right) = 2 \cdot V_T \cdot \ln\left(\frac{i_Q}{I_S}\right)$$

$$i_N^2 = I_Q^2$$

$$i_N^2 - i_L \cdot i_N - I_Q^2 = 0$$

# Class A

## Transfer Characteristics

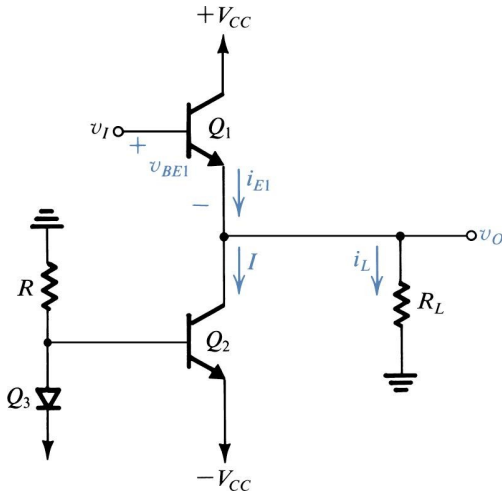

From figure 9.3 we can see that

$$v_{o\max} = V_{CC} - V_{CE1\text{sat}}$$

In the negative direction, the limits of the linear region is determined either by Q1 turning off


$$v_{O\min} = -I \cdot R_L$$

or by Q2 saturating

$$v_{O\min} = -V_{CC} + V_{CE2\text{sat}}$$

Depending on the values of I and  $R_L$ . The absolutely lowest output voltage is that given by the previous equation and is achieved provided that the bias current I is greater than the magnitude of the corresponding load current

$$I \geq \frac{|-V_{CC} + V_{CE2\text{sat}}|}{R_L}$$

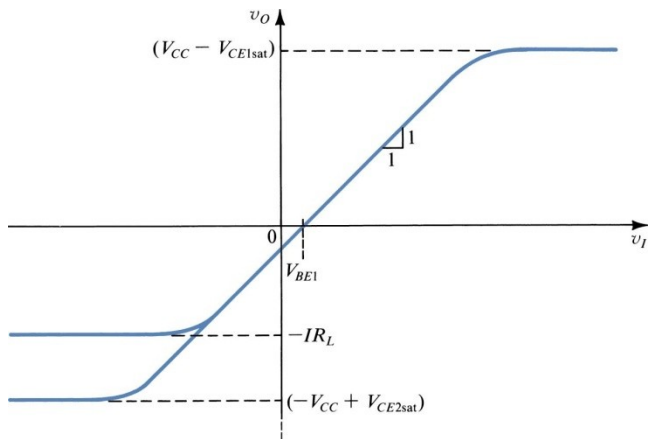






# **Class A**

**Transfer Characteristics**

**Exercises D9.1 and D9.2**

# Class A

## Signal Waveforms

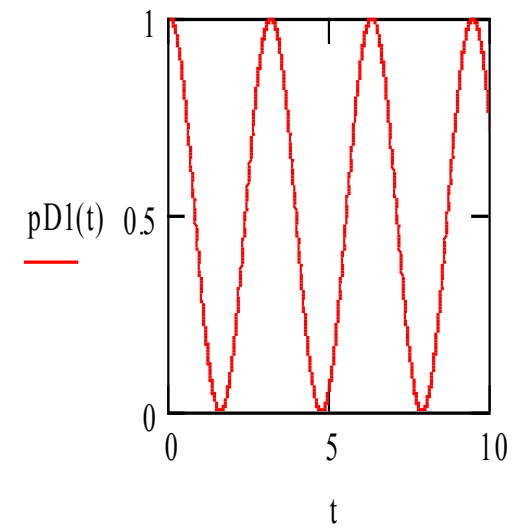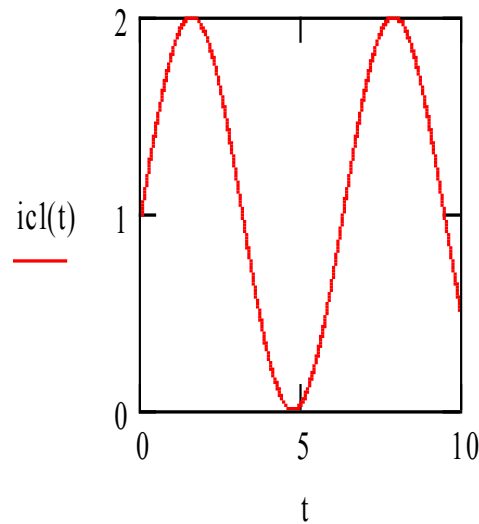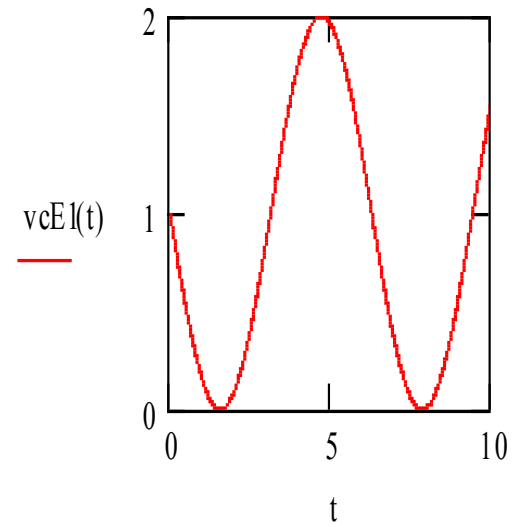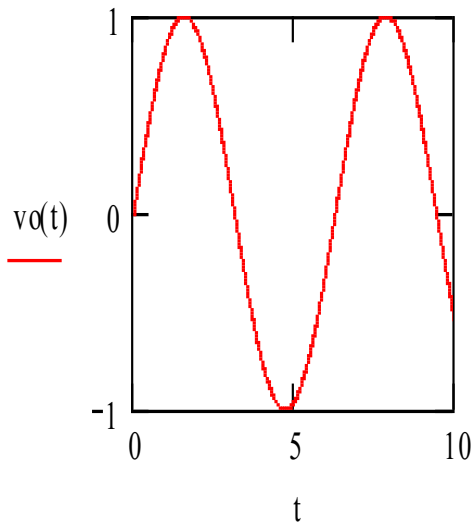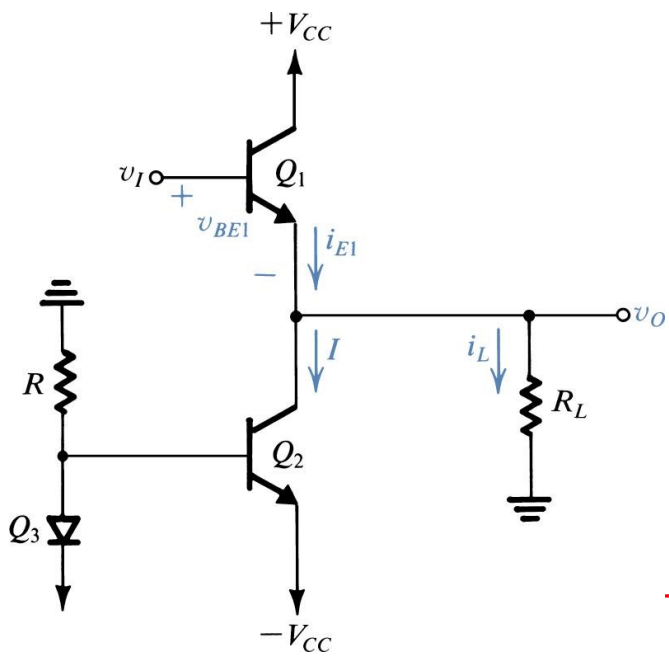

# Class A

## Power Dissipation

$$P = V_{CC} \cdot I$$

Largest Power Dissipation When  $v_o = 0$

Q1 must be able to withstand a continuous dissipation of  $V_{CC} \cdot I$

The power dissipation of Q1 depends on the value of  $R_L$ .

If  $R_L$  is infinite,  $i_{C1} = I$  and the dissipation in Q1 depends on  $v_o$ .

Maximum power dissipation will occur when  $v_o = -V_{CC}$  since  $v_{CE1}$  will be  $2V_{CC}$

$p_{D1} = 2V_{CC} \cdot I$ . This condition would not normally persist for a prolonged interval; the design need not be that conservative. The average  $p_{D1} = V_{CC} \cdot I$

When  $R_L$  is zero a positive voltage would result in a theoretically infinite current (practical value) would flow through Q1. Short-circuit protection is necessary.



# Class A

## Power Conversion Efficiency

$$\eta = \frac{\text{load\_power}(P_L)}{\text{supply\_power}(P_S)}$$

$$P_L = \frac{1}{2} \cdot \frac{V_o^2}{R_L} \quad V_o \quad \text{average voltage}$$

$$P_S = 2 \cdot V_{CC} \cdot I$$

$$\eta = \frac{1}{4} \cdot \frac{V_o^2}{I \cdot R_L \cdot V_{CC}} = \frac{1}{4} \cdot \left( \frac{V_o}{I \cdot R_L} \right) \cdot \left( \frac{V_o}{V_{CC}} \right)$$

$$V_o \leq V_{CC} \quad V_o \leq I \cdot R_L$$

maximum efficiency is obtained when

$$V_o = V_{CC} = I \cdot R_L$$

# Class A

## Exercise 9.4


$$V_{\text{peak}} := 8 \quad I := 100 \cdot 10^{-3} \quad R_L := 100 \quad V_{CC} := 10$$

$$P_L := \frac{\left( \frac{V_{\text{peak}}}{\sqrt{2}} \right)^2}{100} \quad P_L = 0.32$$

$$P_{\text{plus}} := V_{CC} \cdot I \quad P_{\text{plus}} = 1$$

$$P_{\text{minus}} := V_{CC} \cdot I \quad P_{\text{minus}} = 1 \quad P_S := P_{\text{plus}} + P_{\text{minus}}$$
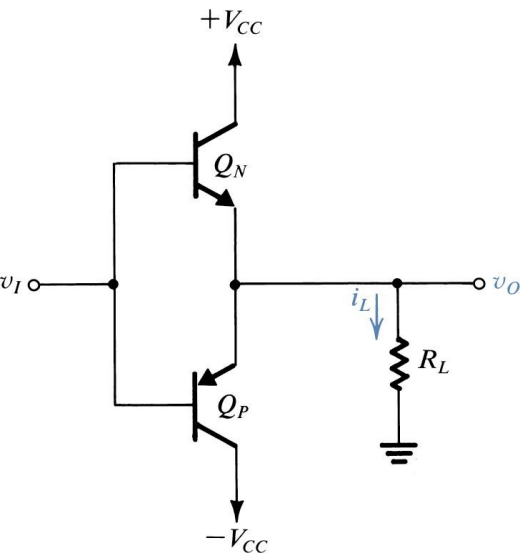
$$\eta := \frac{P_L}{P_S} \quad \eta = 0.16$$



## Biassing the Class B Output

- No DC current is used to bias this configuration.
- Activated when the input voltage is greater than the  $V_{be}$  for the transistors.
- npn Transistor operates when positive, pnp when negative.
- At a zero input voltage, we get no output voltage.

# Class A

## Power Conversion Efficiency

### CLASS A


Many class A amplifiers use the same transistor(s) for both halves of the audio waveform. In this configuration, the output transistor(s) always has current flowing through it, even if it has no audio signal (the output transistors never 'turn off'). The current flowing through it is D.C.

A pure class 'A' amplifier is very inefficient and generally runs very hot even when there is no audio output. The current flowing through the output transistor(s) (with no audio signal) may be as much as the current which will be driven through the speaker load at FULL audio output power. Many people believe class 'A' amps to sound better than other configurations (and this may have been true at some point in time) but a well designed amplifier won't have any 'sound' and even the most critical 'ear' would be hard-pressed to tell one design from another.

NOTE: Some class A amplifiers use complimentary (separate transistors for positive and negative halves of the waveform) transistors for their output stage.

# Class B

## Circuit Operation

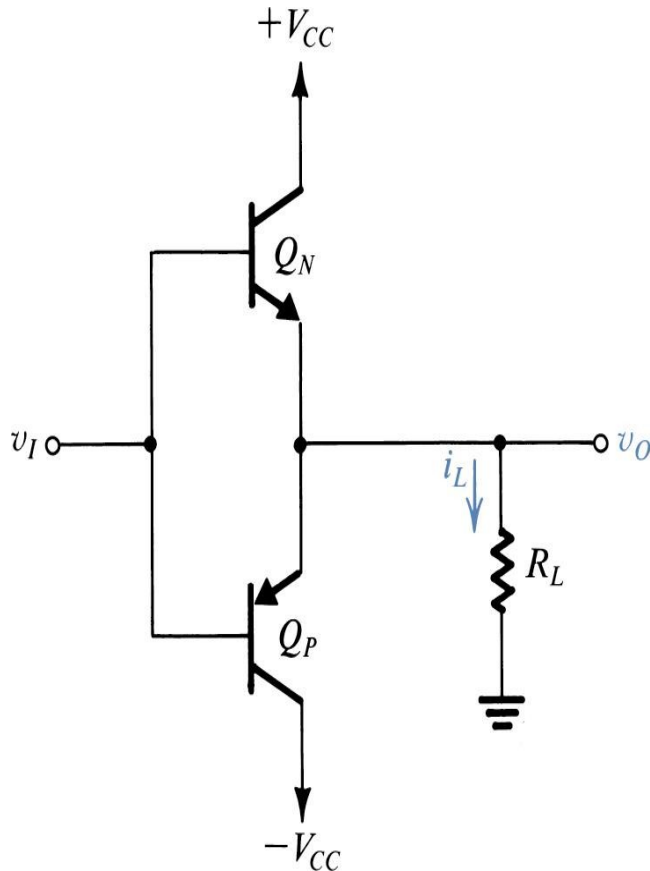

Class B output stage.

## CLASS 'B'



A class 'B' amplifier uses complimentary transistors for each half of the waveform.

A true class 'B' amplifier is NOT generally used for audio. In a class 'B' amplifier, there is a small part of the waveform which will be distorted. You should remember that it takes approximately .6 volts (measured from base to emitter) to get a bipolar transistor to start conducting. In a pure class 'B' amplifier, the output transistors are not "biased" to an 'on' state of operation. This means that the the part of the waveform which falls within this .6 volt window will not be reproduced accurately.

The output transistors for each half of the waveform (positive and negative) will each have a .6 volt area in which they will not be conducting. The distorted part of the waveform is called 'crossover' or 'notch' distortion. Remember that distortion is any unwanted variation in a signal (compared to the original signal). The diagram below shows what crossover distortion looks like.


# Class B

## Circuit Operation

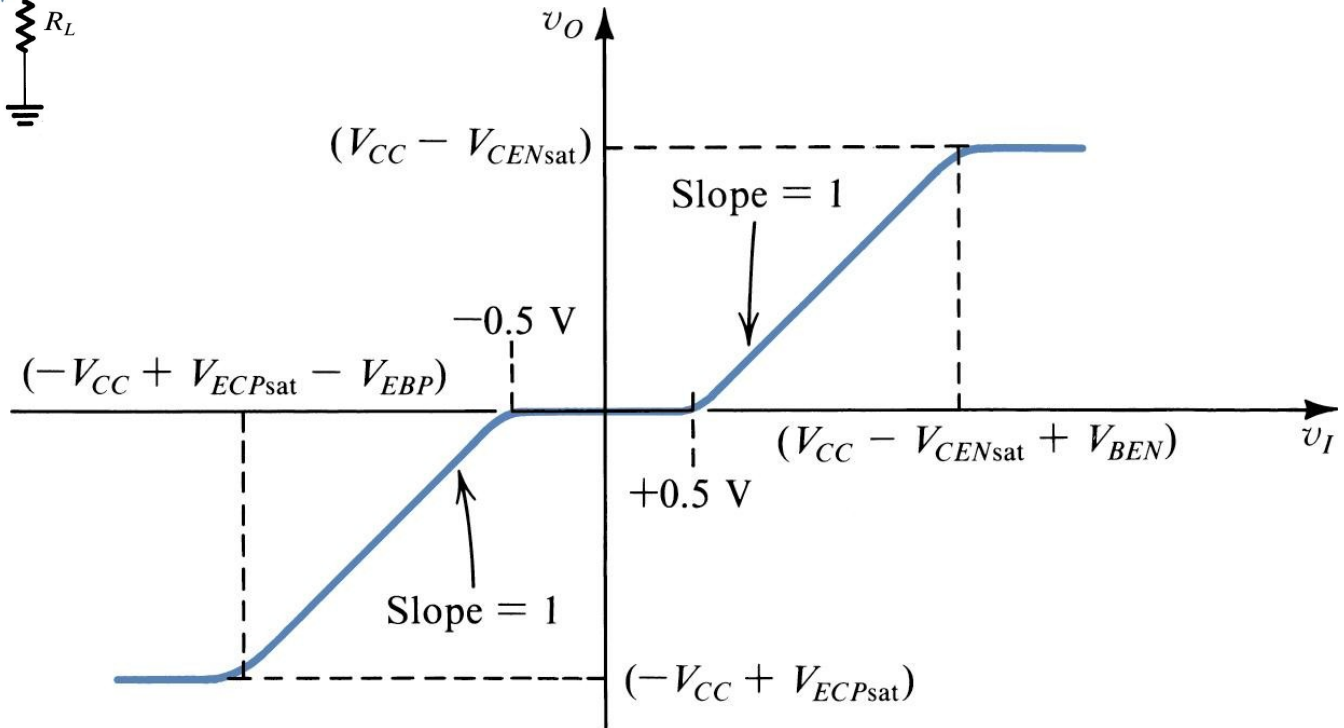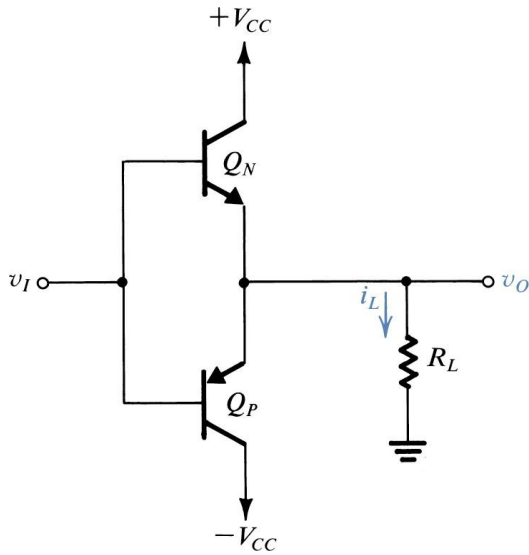

Transfer characteristic for the class B output stage in Fig. 9.5.

# Operation

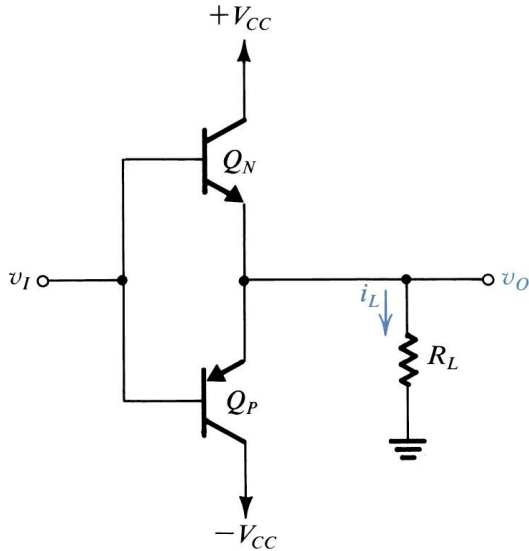


When the input voltage rises to be large enough to overcome the  $V_{be}$ , it will begin to cause an output voltage to appear. This occurs because  $Q_N$  begins to act like an emitter follower and  $Q_P$  shuts off. The input will be followed on the emitter until the transistor reaches saturation. The maximum input voltage is equal to the following:

$$v_{i\max} = V_{CC} - V_{CE\text{Nsat}}$$

The same thing will begin to happen if the input voltage is negative by more than the  $V_{eb}$  of the transistor. This causes the  $Q_P$  to act like an emitter follower and  $Q_N$  turns off. This will continue to behave this way until saturation occurs at a minimum input voltage of:

$$v_{i\min} = -V_{CC} + V_{EC\text{P}\text{sat}}$$
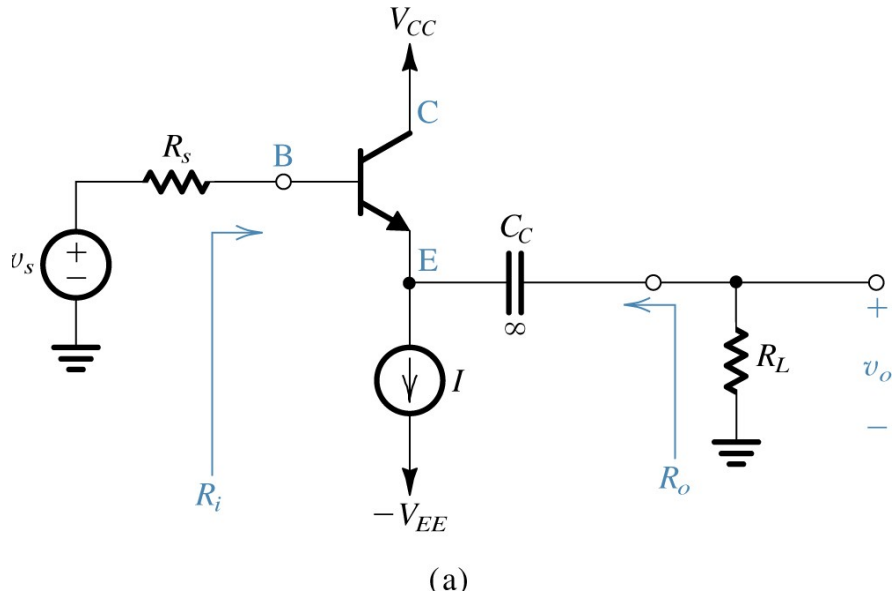
# Emitter Follower Configuration (Chapter 4)



$$\frac{v_b}{v_s} = \frac{(\beta + 1)(r_e + \text{par}(R_L, r_o))}{R_S + (\beta + 1)(r_e + \text{par}(R_L, r_o))}$$

$$\frac{v_o}{v_b} = \frac{\text{par}(r_o, R_L)}{r_e + \text{par}(r_o, R_L)}$$


$R_s$  will be small for most configurations, so the  $v_b/v_s$  will be a little less than unity. The same is true for  $r_e$ , so  $v_o/v_b$  will be a little less than unity making our  $v_o/v_s$  a little less than unity.


## Characteristics of the Emitter Follower:

- High Input Resistance
- Low Output Resistance
- Near Unity Gain



# Transfer Characteristic

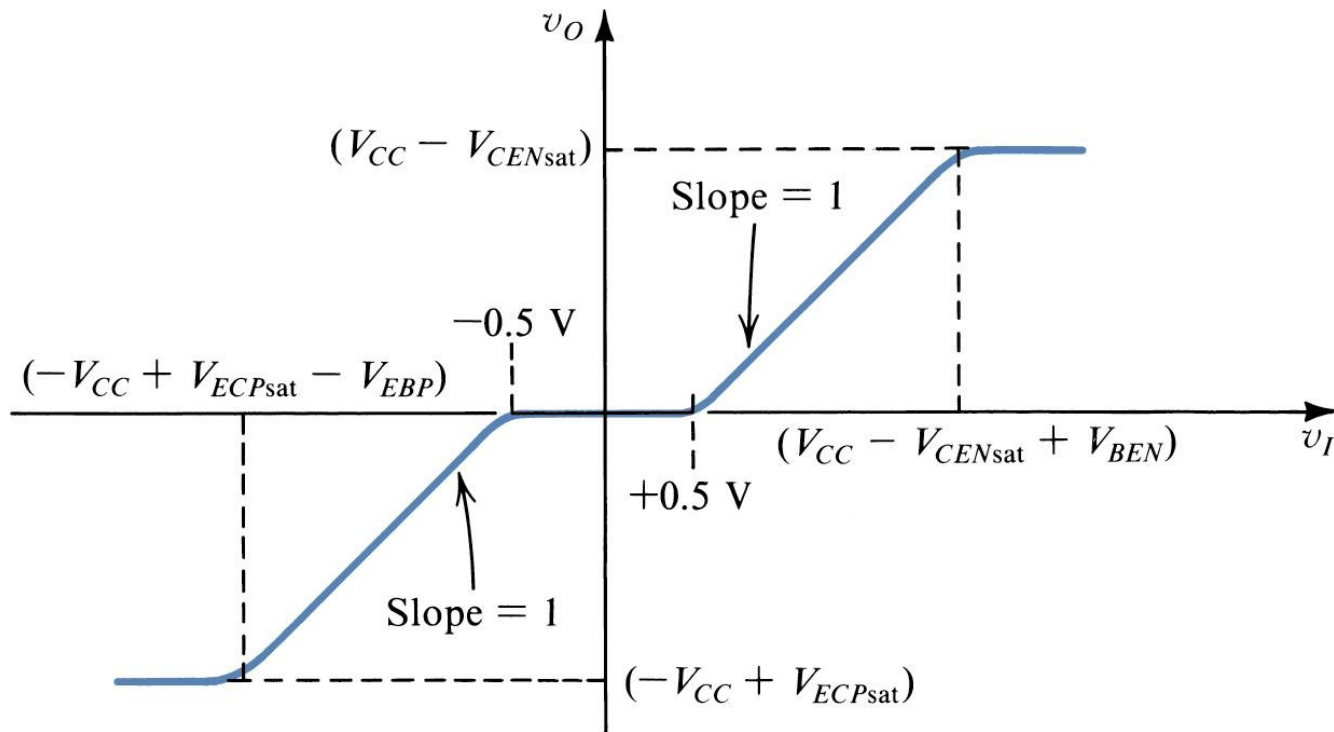

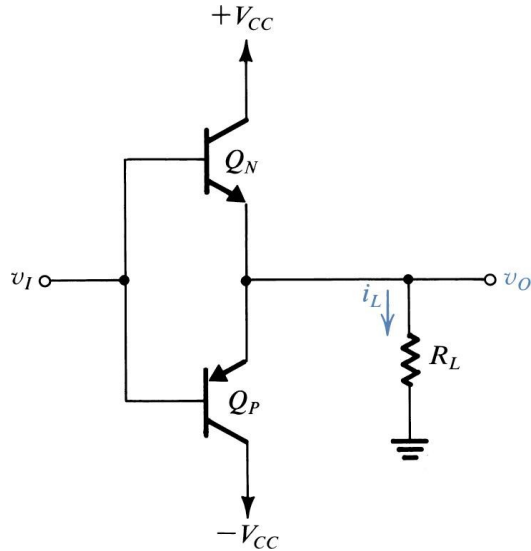


## Push-Pull Nature of Class B

- **Push:** The npn transistor will push the current to ground when the input is positive.
- **Pull:** The pnp transistor will pull the current from the ground when the input is negative.

## Crossover Distortion

The Crossover Distortion is due to the dead band of input voltages from  $-0.5V$  to  $0.5V$ . This causes the Class B output stage to be a bad audio amplifier. For large input signals, the crossover distortion is limited, but at small input signals, it is most pronounced.

# Graph of Crossover Distortion

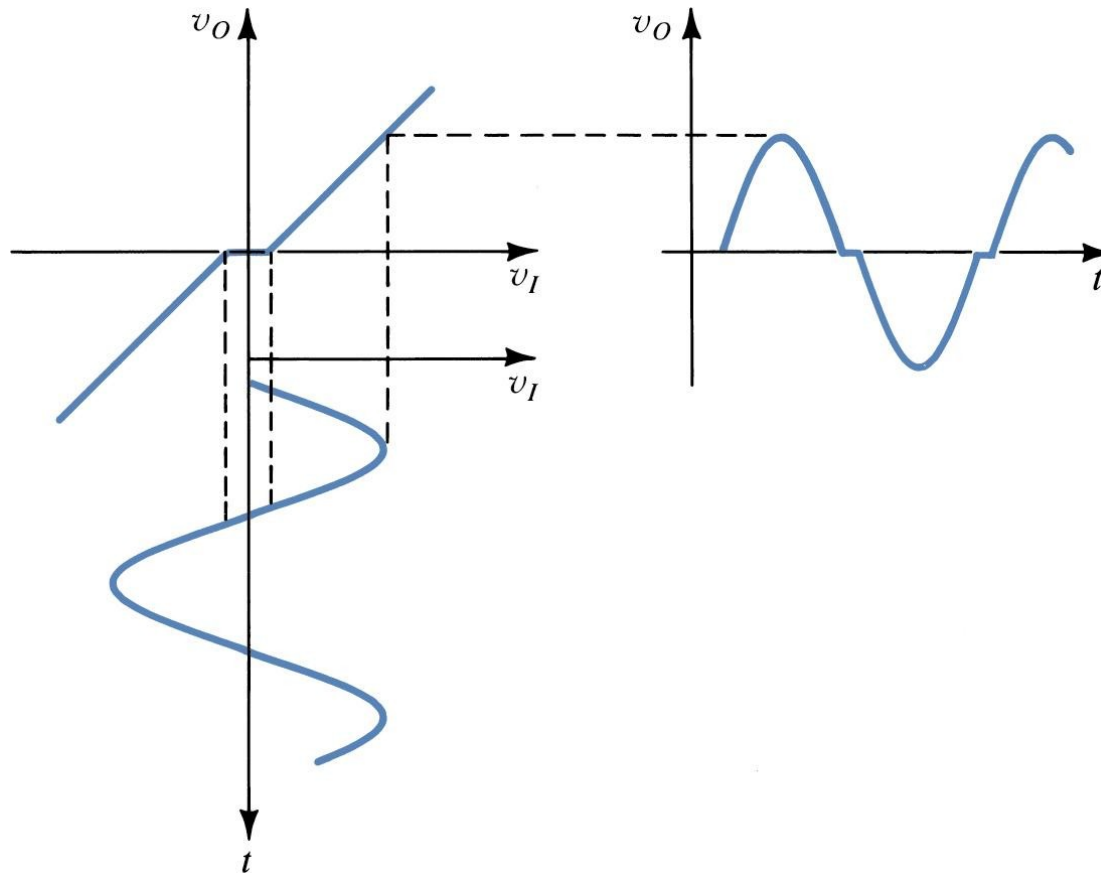

Illustrating how the dead band in the class B transfer characteristic results in crossover distortion.

# Power Efficiency

Load Power:

$$P_L = \frac{1}{2} \cdot \frac{V_{op}^2}{R_L}$$

Since each transistor is only conducting for one-half of the time, the power drawn from each source will be the same.

$$P_s = \frac{1}{\pi} \cdot \frac{V_{op}}{R_L} \cdot V_{CC}$$

$$\eta = \frac{P_L}{2 \cdot P_s} = \frac{\frac{1}{2} \cdot \frac{V_{op}^2}{R_L}}{2 \cdot \frac{1}{\pi} \cdot \frac{V_{op}}{R_L} \cdot V_{CC}}$$

This efficiency will be at a max when  $V_{op}$  is at a max. Since  $V_{op}$  cannot exceed  $V_{CC}$ , the maximum efficiency will occur at  $\pi/4$ .

$$\eta = \frac{\pi}{4} \cdot \frac{V_{op}}{V_{CC}}$$

$$\eta_{max} = \frac{\pi}{4}$$

This will be approximately 78.5%, much greater than the 25% for Class A.

# Class AB

## Circuit Operation

Crossover distortion can be eliminated by biasing the transistors at a small, non-zero current.

A bias Voltage  $V_{BB}$  is applied between  $Q_n$  and  $Q_p$ .

For  $v_i = 0$ ,  $v_o = 0$ , and a voltage  $V_{BB}/2$  appears across the base-emitter junction of each transistor.

$$i_N = i_p = I_Q = I_S \cdot e^{\frac{V_{BB}}{2 \cdot V_T}}$$

$V_{BB}$  is selected to result the required quiescent current  $I_Q$

$$v_o = v_i + \frac{V_{BB}}{2} - v_{BEN}$$


$$i_N = i_p + i_L$$

$$v_{BEN} + v_{EBP} = V_{BB}$$

$$i_N^2 = I_Q^2$$

$$i_N^2 - i_L \cdot i_N - I_Q^2 = 0$$
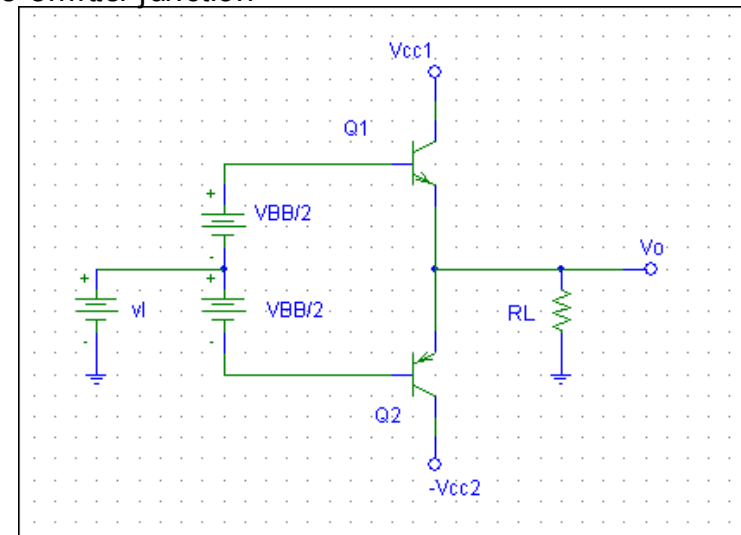
$$V_T \cdot \ln\left(\frac{i_N}{I_S}\right) + V_T \cdot \ln\left(\frac{i_p}{I_S}\right) = 2 \cdot V_T \cdot \ln\left(\frac{i_Q}{I_S}\right)$$



# **Class AB**

**Output Resistance**

# Class AB


## Exercise 9.6

### Calvin College - ENGR 332 Class AB Output Stage Amplifier

Consider the class AB circuit (illustrated below) with  $V_{CC}=15\text{ V}$ ,  $I_Q=2\text{ mA}$ ,  $R_L=100\text{ ohms}$ . Determine  $V_{BB}$ . Determine the values of  $i_L$ ,  $i_N$ ,  $i_P$ ,  $v_{BEN}$ ,  $v_{EBP}$ ,  $v_I$ ,  $v_O/v_I$ ,  $R_{out}$ , and  $v_o/v_i$  for  $v_O$  for  $v_O$  varying from  $-10$  to  $10\text{V}$ .

Note that  $v_O/v_I$  is the large signal voltage gain and  $v_o/v_i$  is the incremental gain obtained as  $R_L/(R_L+R_{out})$ . The incremental gain is equal to the slope of the transfer curve.

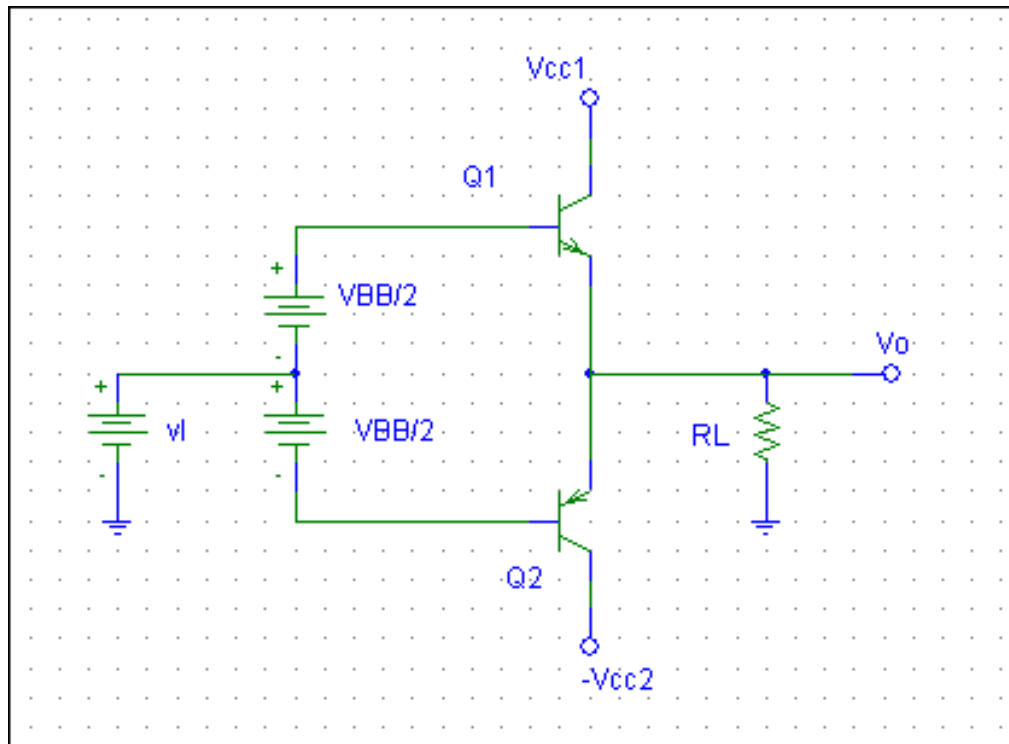
Assume  $Q_N$  and  $Q_P$  to be matched, with  $I_S=10\text{E-}13$ .





# Class AB

## Exercise 9.6

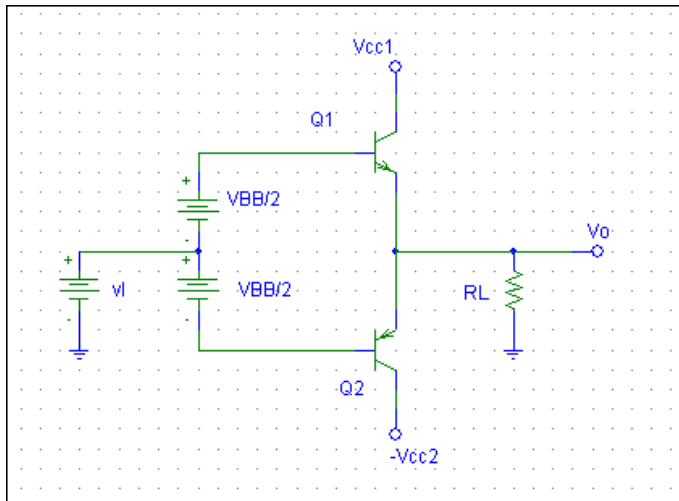

under quiescent conditions  $i_N = i_P = I_Q$   $v_O = v_I = 0$

Solving for  $V_{BB}$

$V_{BB} := 1$        $I_S := 10^{-13}$        $V_T := 0.025$        $I_Q := 2 \cdot 10^{-3}$        $R_L := 100$

Given


$$\frac{|V_{BB}|}{2}$$

$I_Q = I_S \cdot e$


$V_{BB} := \text{Find}(V_{BB})$        $i := 0..100$        $V_{BB} = 1.186$

# Class AB

## Exercise 9.6

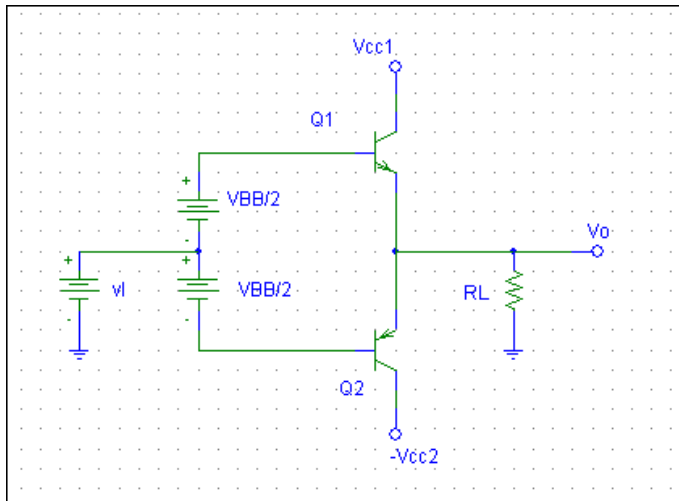

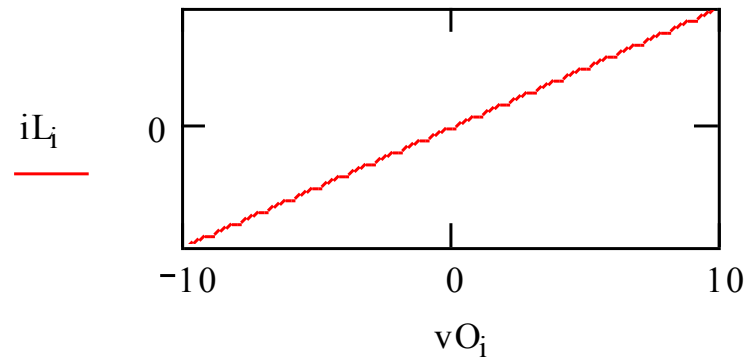
$$vO_i := -10 + \frac{i}{5} \quad iL_1 := \frac{vO_i}{RL}$$



# Class AB

## Exercise 9.6

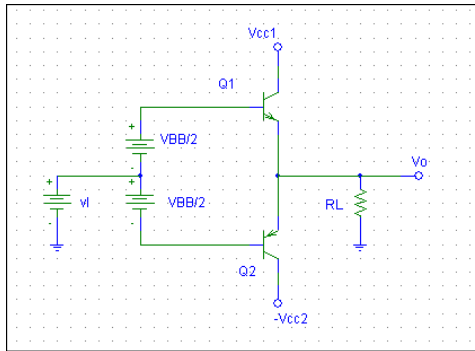

Solving for  $iN$

initial guesses  $iN := 0.02$

$iLD := 0.02$

$IQ := 0.002$

Given

$$iN^2 - iLD iN - IQ^2 = 0$$

$iNN(IQ, iLD) := \text{Find}(iN)$



$i := 0..100$        $IQ_i := 0.002$

$iLD_i := iL_1$

$iN_i := iNN(IQ_i, iL_1)$

$$iN_{10} = 4.997 \times 10^{-5}$$


$$iP_i := iN_i - iLD_i$$

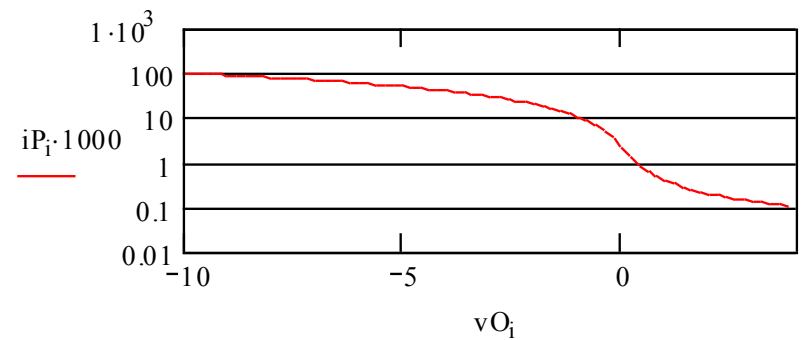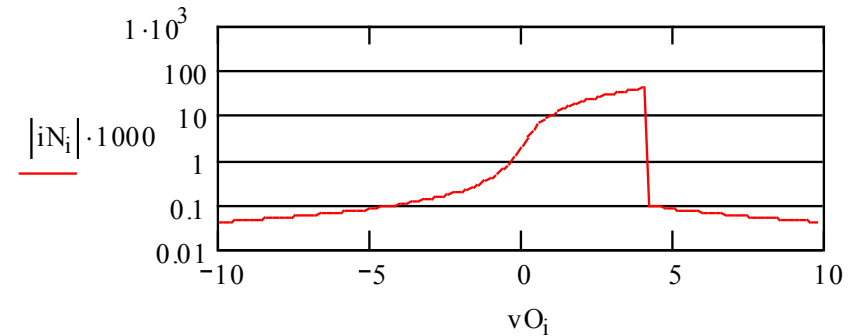

$(iN_i)$



# Class AB

## Exercise 9.6

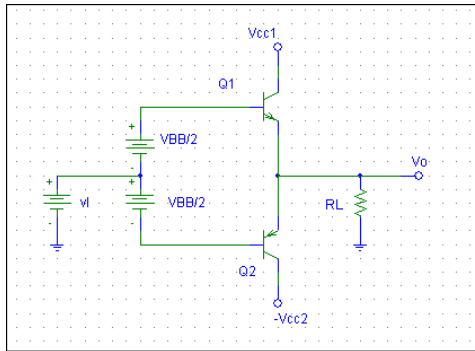


$$v_{BEN_i} := VT \cdot \ln \left( \frac{i_{N_i}}{IS} \right)$$
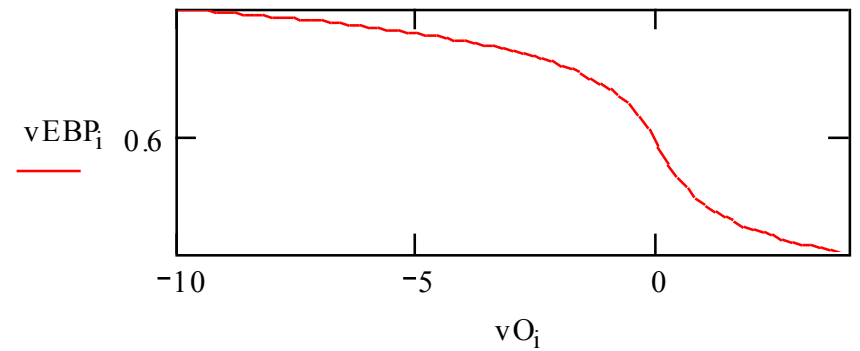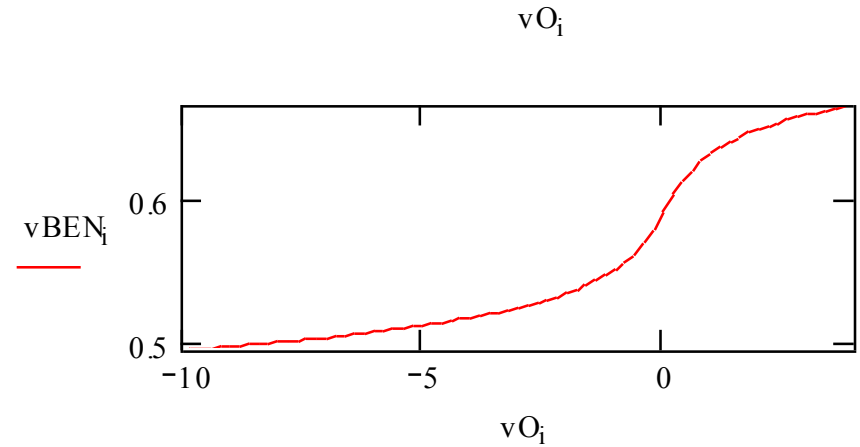
$$v_{EBP_i} := VT \cdot \ln \left( \frac{i_{P_i}}{IS} \right)$$



# Class AB


## Exercise 9.6

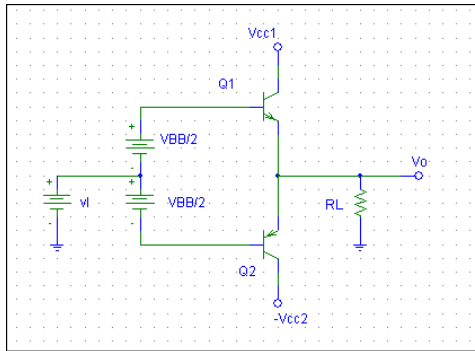


$$vI_i := vO_i + vBEN_1 - \frac{VBB}{2}$$

$$vOvI_i := \frac{vO_i}{vI_i}$$

$vI_i$

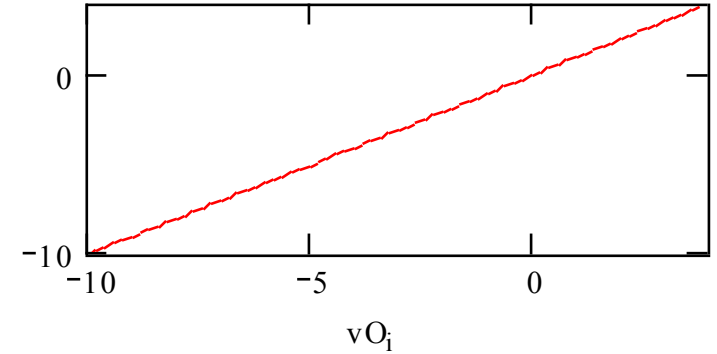


$vOvI_i$

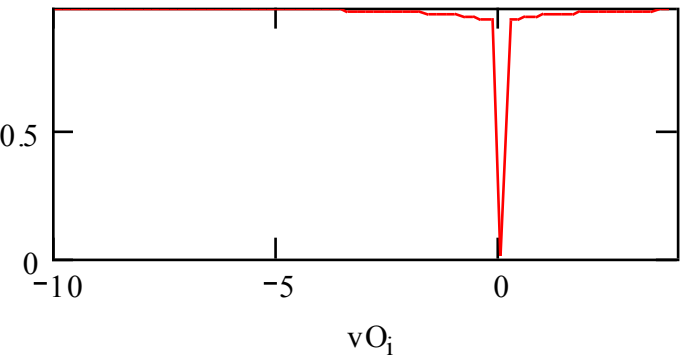



# Class AB


## Exercise 9.6

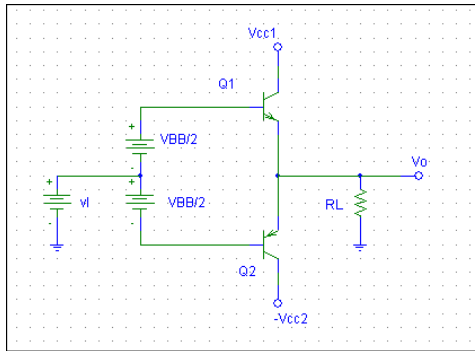


$$R_{out_i} := \frac{VT}{iP_1 + iN_1}$$

$$vov_i := \frac{RL}{RL + R_{out_i}}$$

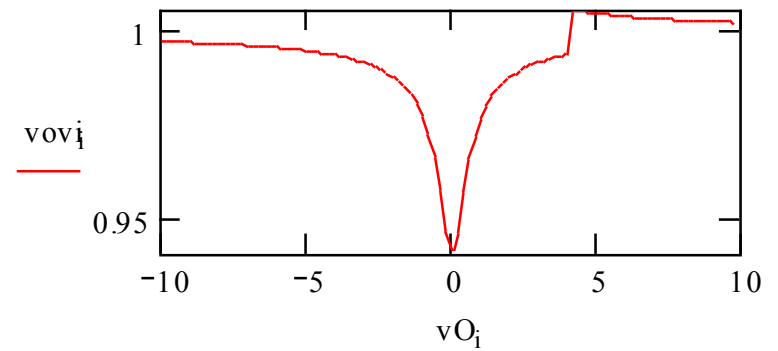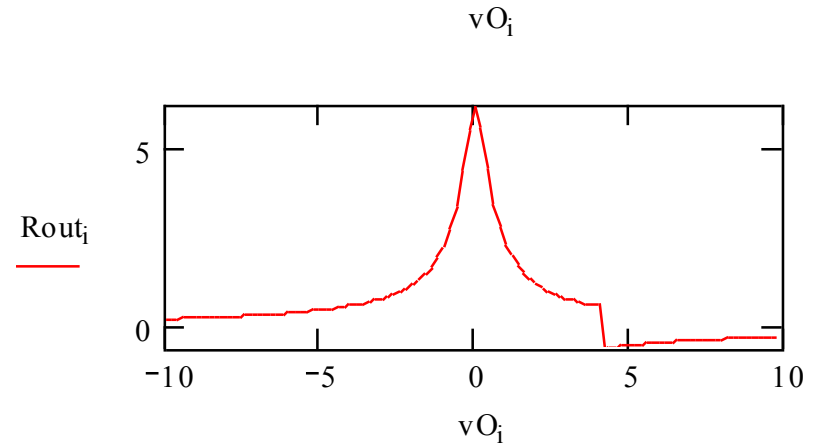

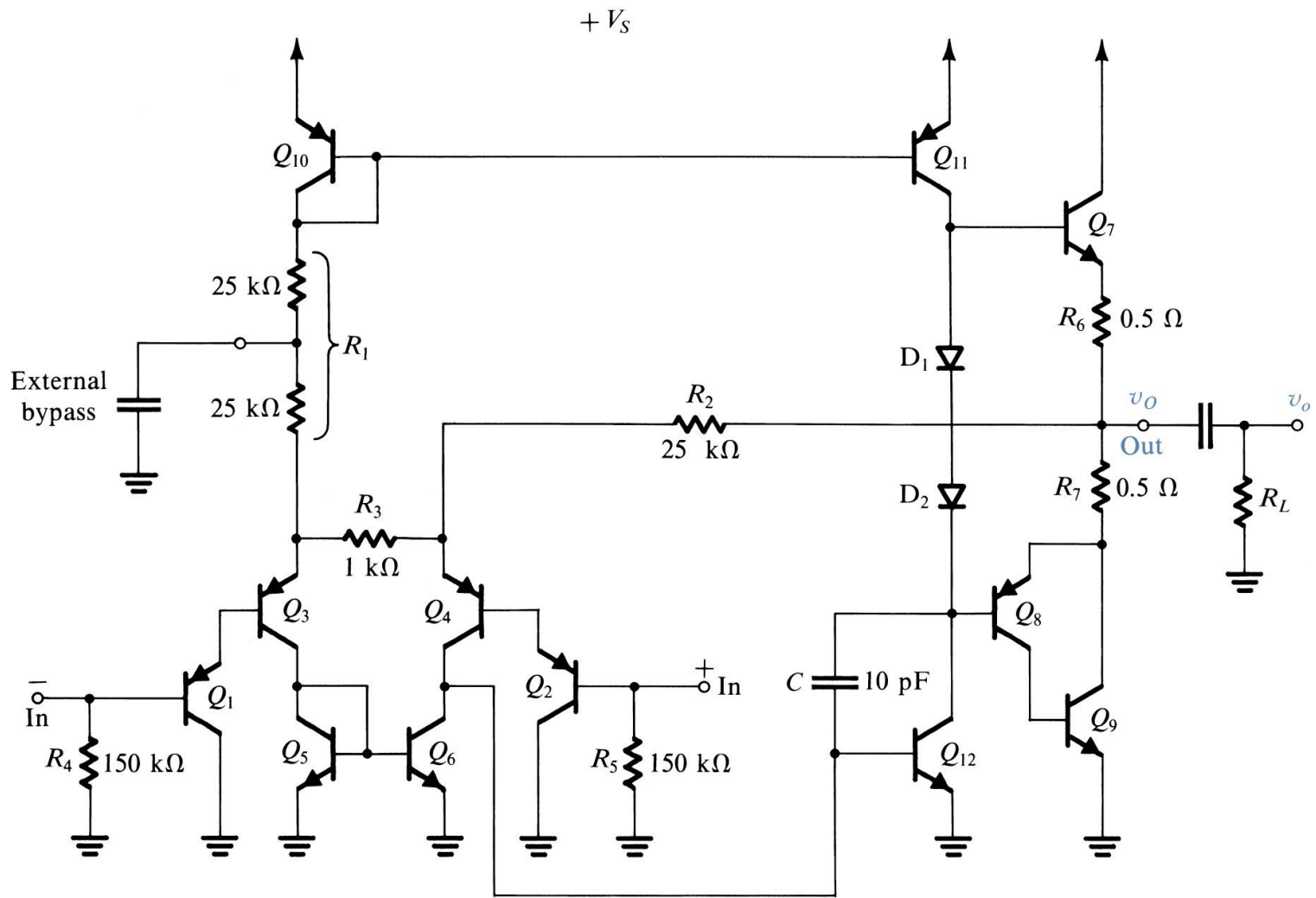


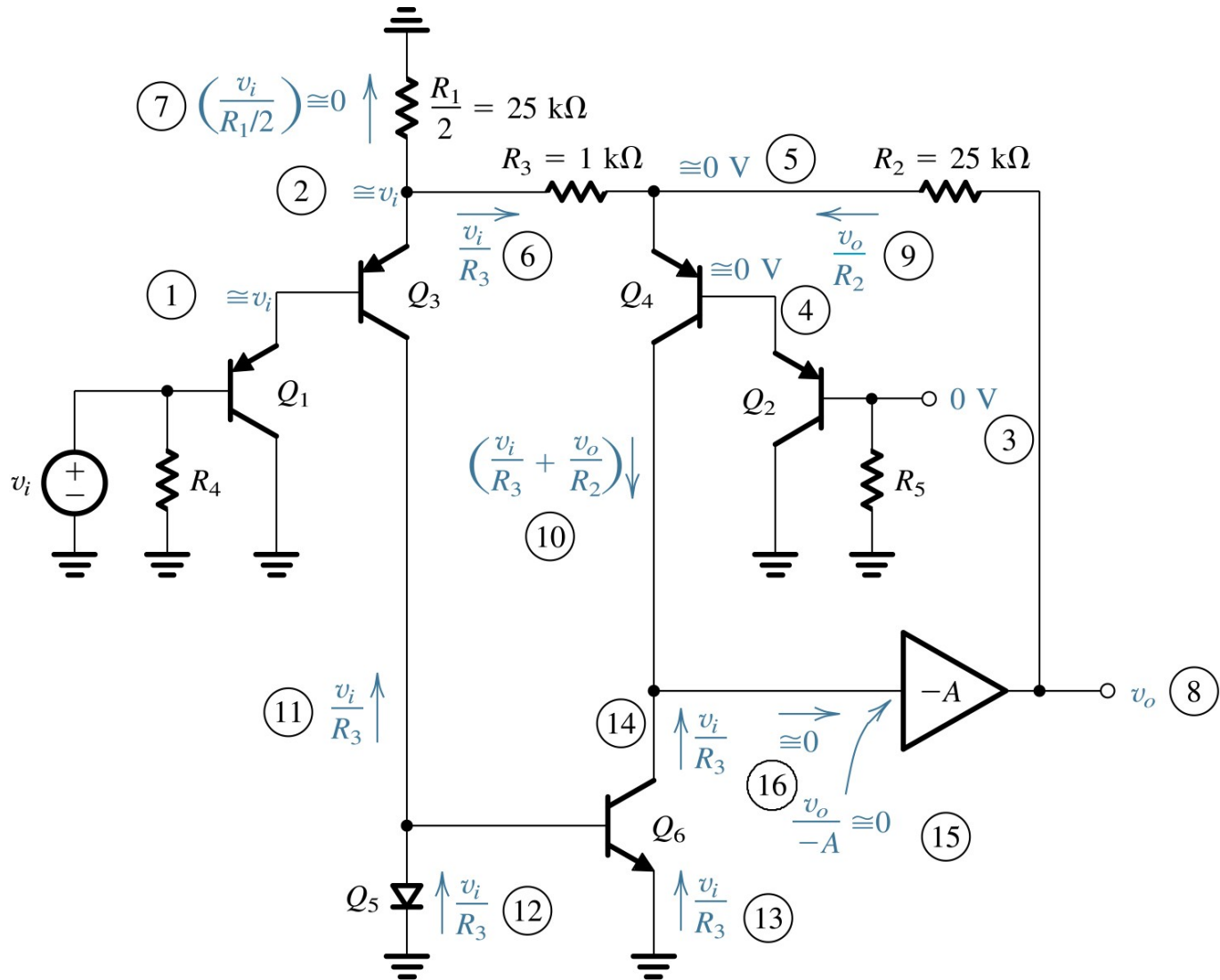Simplified internal circuit of the LM380 IC power amplifier (Courtesy National Semiconductor Corporation.)




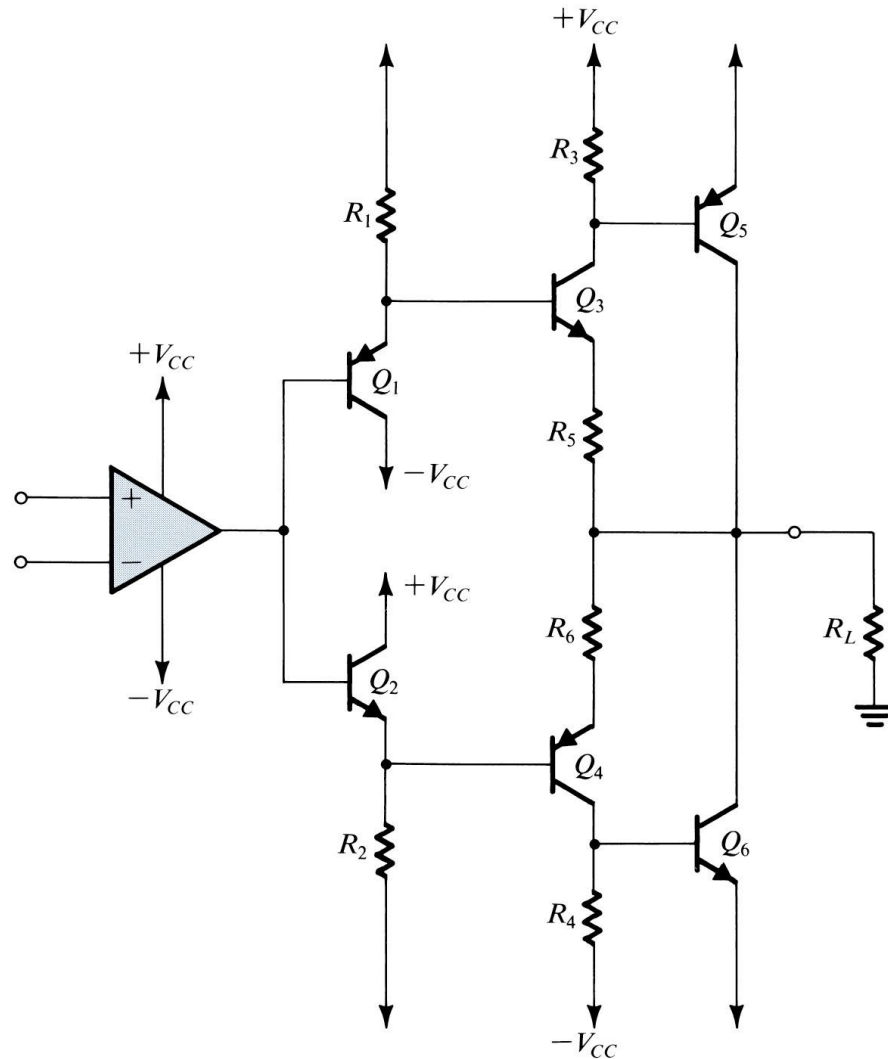Small-signal analysis of the circuit in Fig. 9.30. The circled numbers indicate the order of the analysis steps.






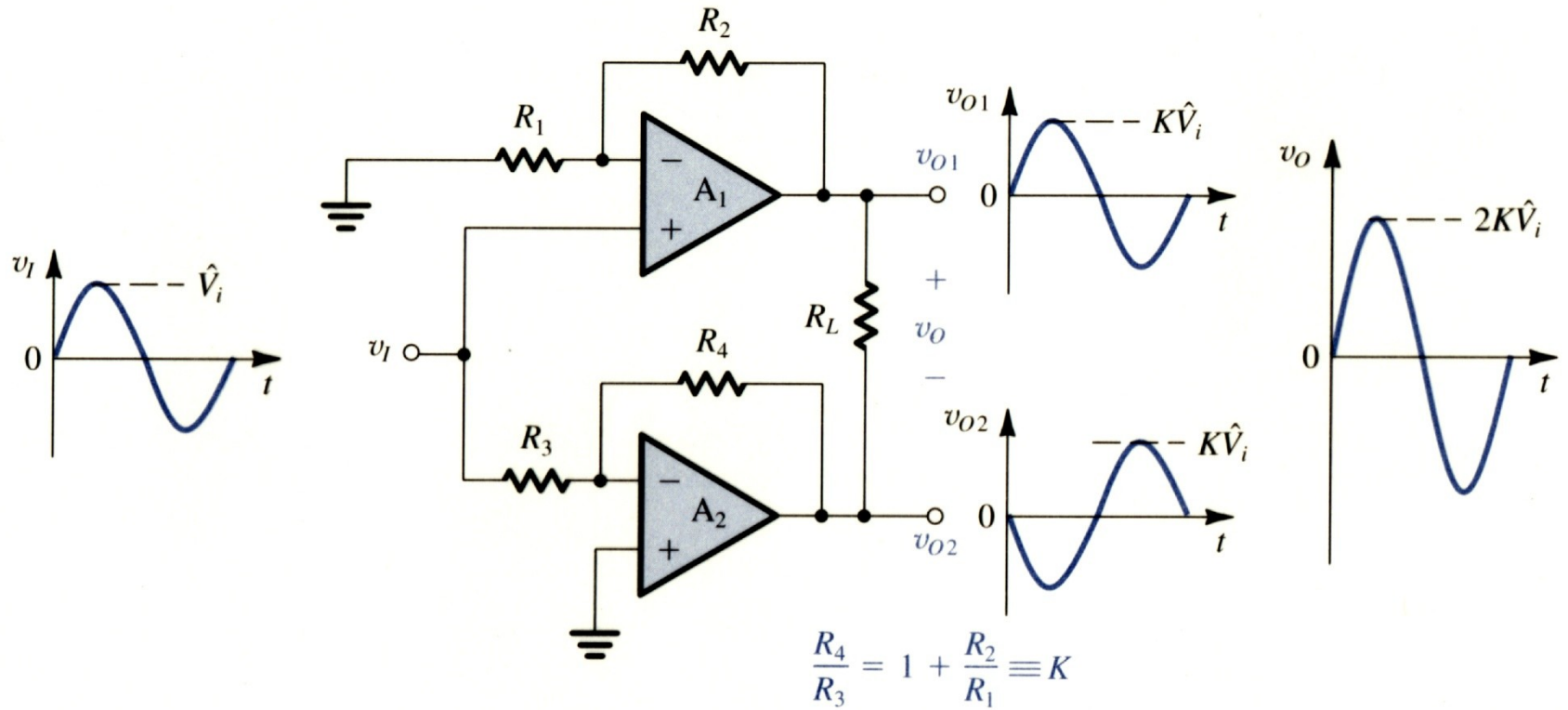
Structure of a power op amp. The circuit consists of an op amp followed by a class AB buffer similar to that discussed in Section 9.7. The output current capability of the buffer, consisting of  $Q_1$ ,  $Q_2$ ,  $Q_3$ , and  $Q_4$ , is further boosted by  $Q_5$  and  $Q_6$ .




The bridge amplifier configuration.

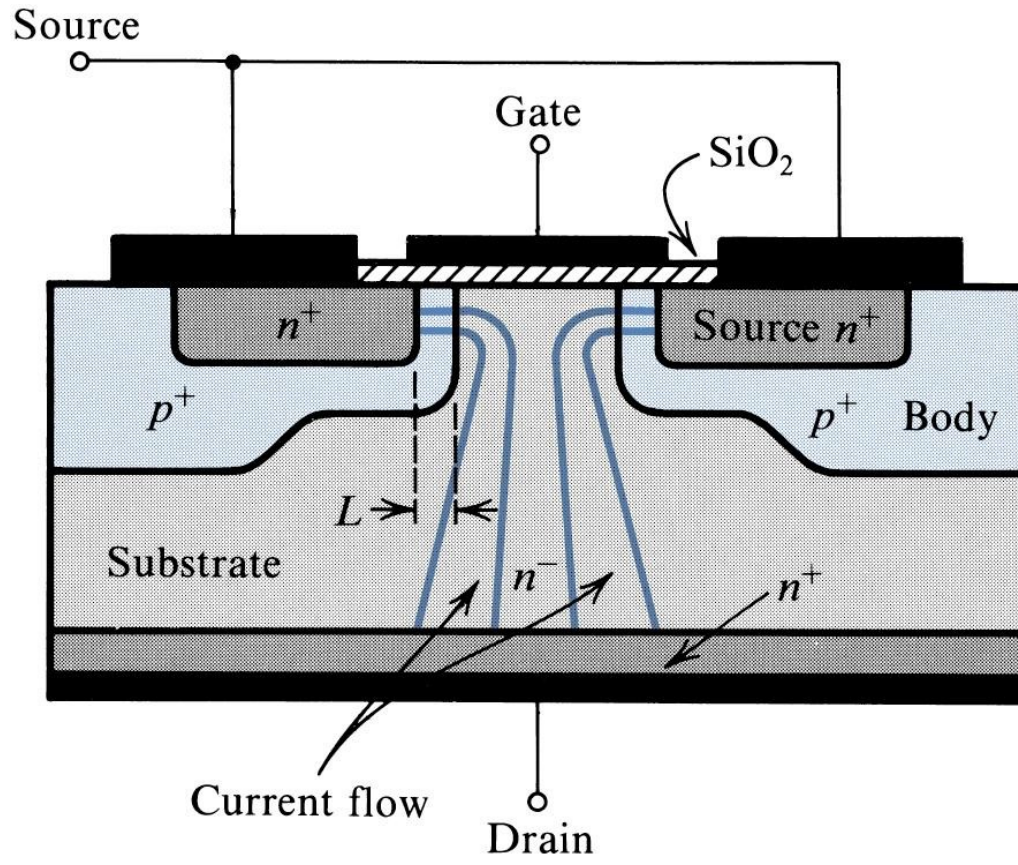

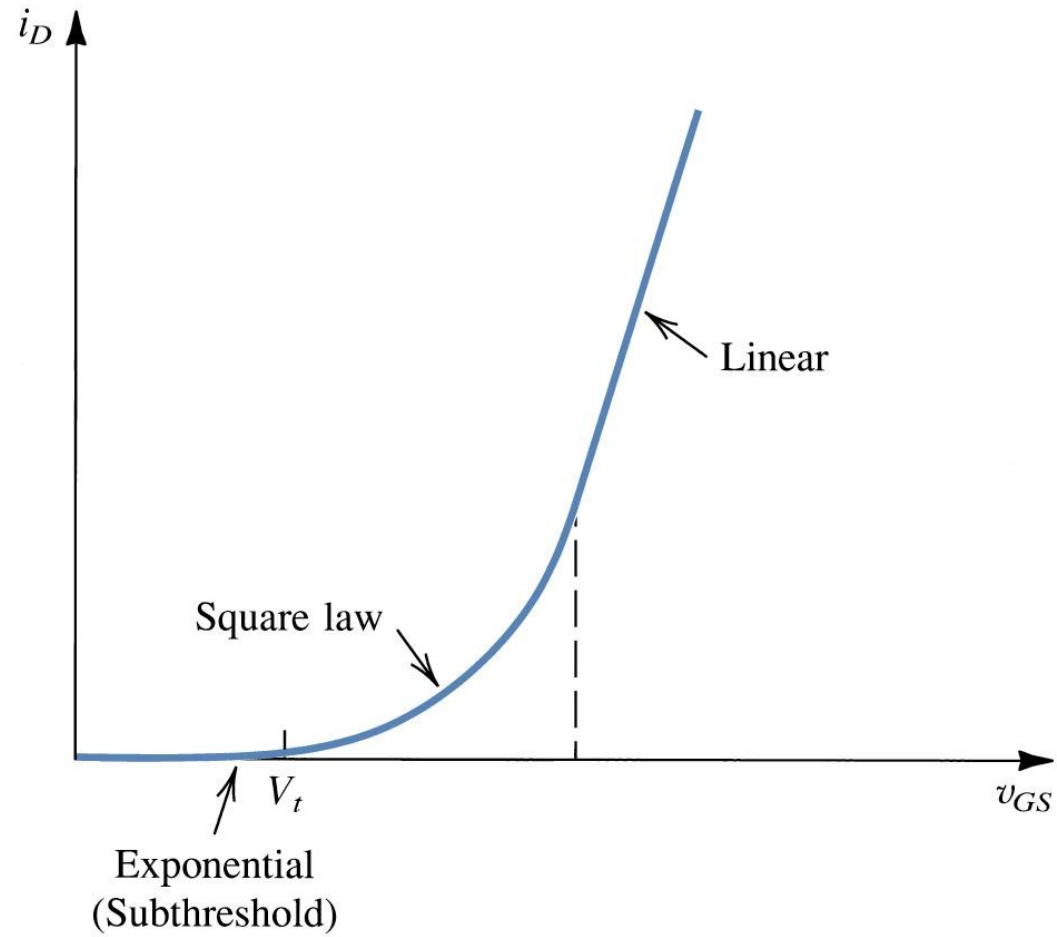Double-diffused vertical MOS transistor (DMOS).



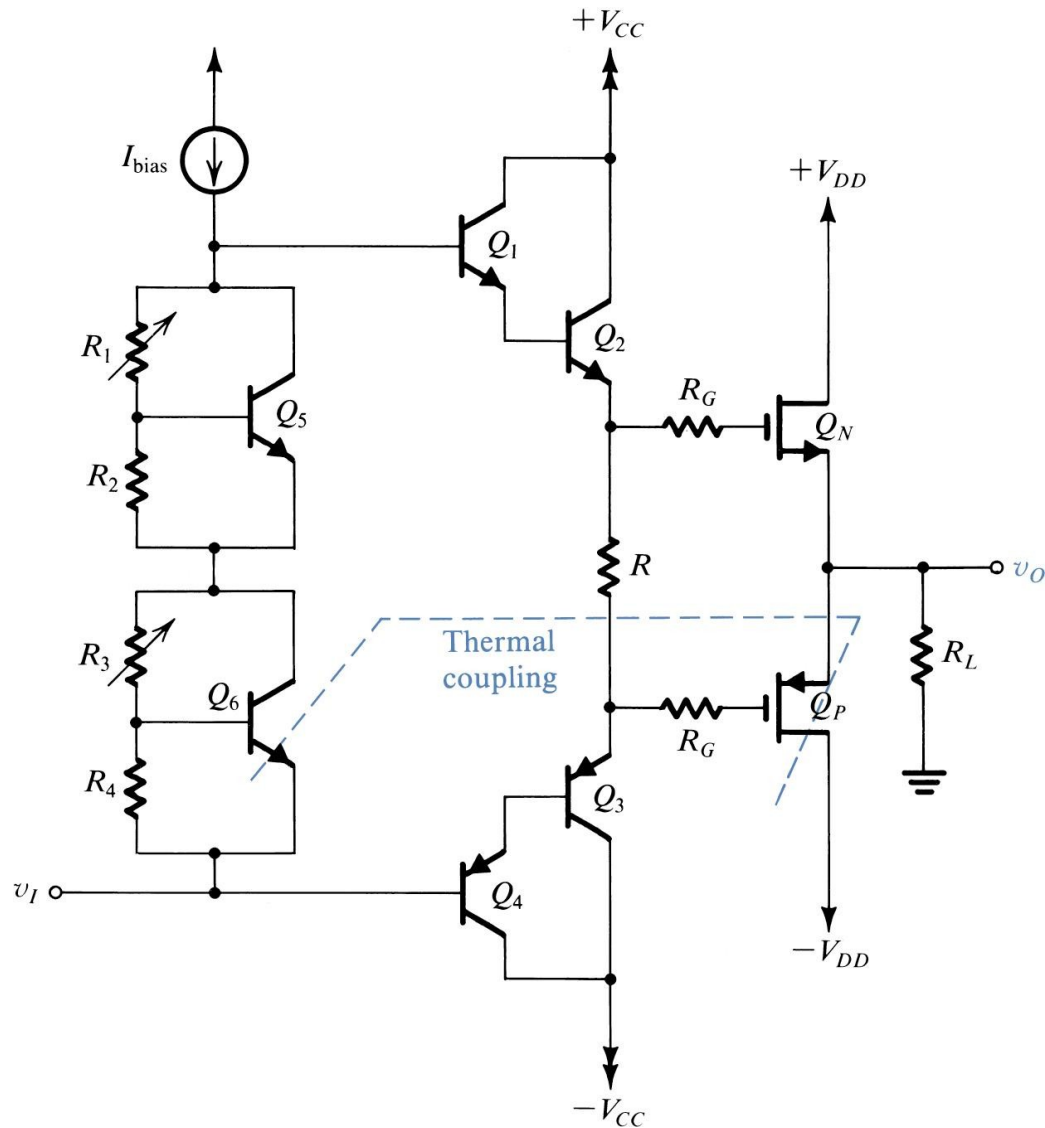Typical  $i_D$ - $v_{GS}$  characteristic for a power MOSFET.



A class AB amplifier with MOS output transistors and BJT drivers. Resistor  $R_3$  is adjusted to provide temperature compensation while  $R_1$  is adjusted to yield to the desired value of quiescent current in the output transistors.