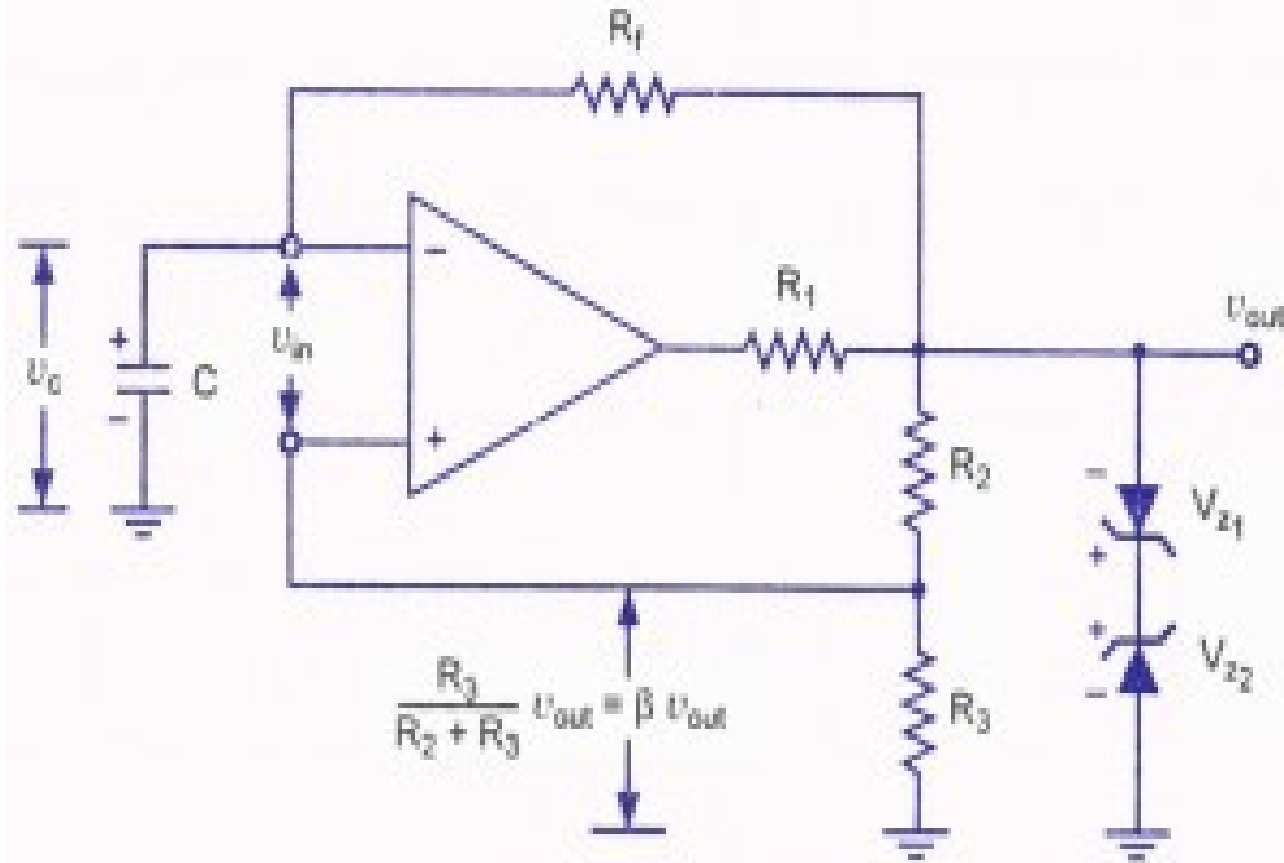


# WAVEFORM GENERATORS

- Most digital system requires some kind of timing waveform , a source of trigger pulses is required for all clocked sequential systems.
- In digital systems , a rectangular waveform is most desirable.
- The generators of rectangular waveforms are referred as multivibrators.
- Three type of Multivibrator:- Astable (free running), monostable (one shot), bistable (flip flop)

# Square wave generator (Free Running or Astable Multivibrator)



*OP-Amp Square-Wave Generator*

- The non-sinusoidal waveform generators are also called relaxation oscillators.
- The op-amp relaxation oscillator shown in figure is a square wave generator.
- In general, square waves are relatively easy to produce.
- Like the UJT relaxation oscillator, the circuit's frequency of oscillation is dependent on the charge and discharge of a capacitor  $C$  through feedback resistor  $R$ ,. The “heart” of the oscillator is an inverting op-amp comparator.

- The comparator uses positive feedback that increases the gain of the amplifier.
- comparator circuit offer two advantages.(i) the high gain causes the op-amp's output to switch very quickly from one state to an-other and vice-versa. (ii) the use of positive feedback gives the circuit hysteresis.
- In square-wave generator circuit, the output voltage  $v_{out}$  is shunted to ground by two Zener diodes  $Z_1$  and  $Z_2$  connected back-to-back and is limited to either  $V_{z2}$  or  $-V_{z1}$ .

- A fraction of the output is feedback to the (+) input terminal.
- Combination of RF and C acting as a low-pass R-C circuit is used to integrate the output voltage  $V_{out}$  and the capacitor voltage  $v_c$  is applied to the inverting input terminal in place of external signal.
- The differential input voltage is given as

$$v_{in} = v_c - \beta v_{out} \quad \text{Where } \beta = R3/(R3+R2)$$

When  $v_{in}$  is positive,  $v_{out} = -V_{z1}$  and when  $v_{in}$  is negative  $v_{out} = +V_{z2}$ .


- Consider an instant of time when  $v_{in} < 0$ .
  - At this instant  $v_{out} = +V_{z2}$ , and the voltage at the n (+) terminal is  $\beta V_{z2}$ , the capacitor C charges exponentially towards  $V_{z2}$ , with a time constant  $R_f C$ . The output voltage remains constant at  $V_{z2}$  until  $v_c$  equal  $\beta V_{z2}$ .
  - When it happens, comparator o/p reverses to  $-V_{z1}$ . Now  $v_c$  changes exponential towards
  - (negative) $V_{z1}$  with the same time constant and a gain the output makes a transition from  $-V_{z1}$  to  $+V_{z2}$ . when  $v_c$  equals  $-\beta V_{z1}$
- Let  $V_{z1} = V_{z2}$**

- The time period,  $T$ , of the output square wave is determined using charging and discharging phenomena of the capacitor  $C$ .

- The voltage across the capacitor,  $v_c$  when it is charging from  $-B V_z$  to  $+V_z$  is given by

$$V_c = V_z[1-(1+\beta)]e^{-t/\tau} \quad \text{Where } \tau = R_f C$$

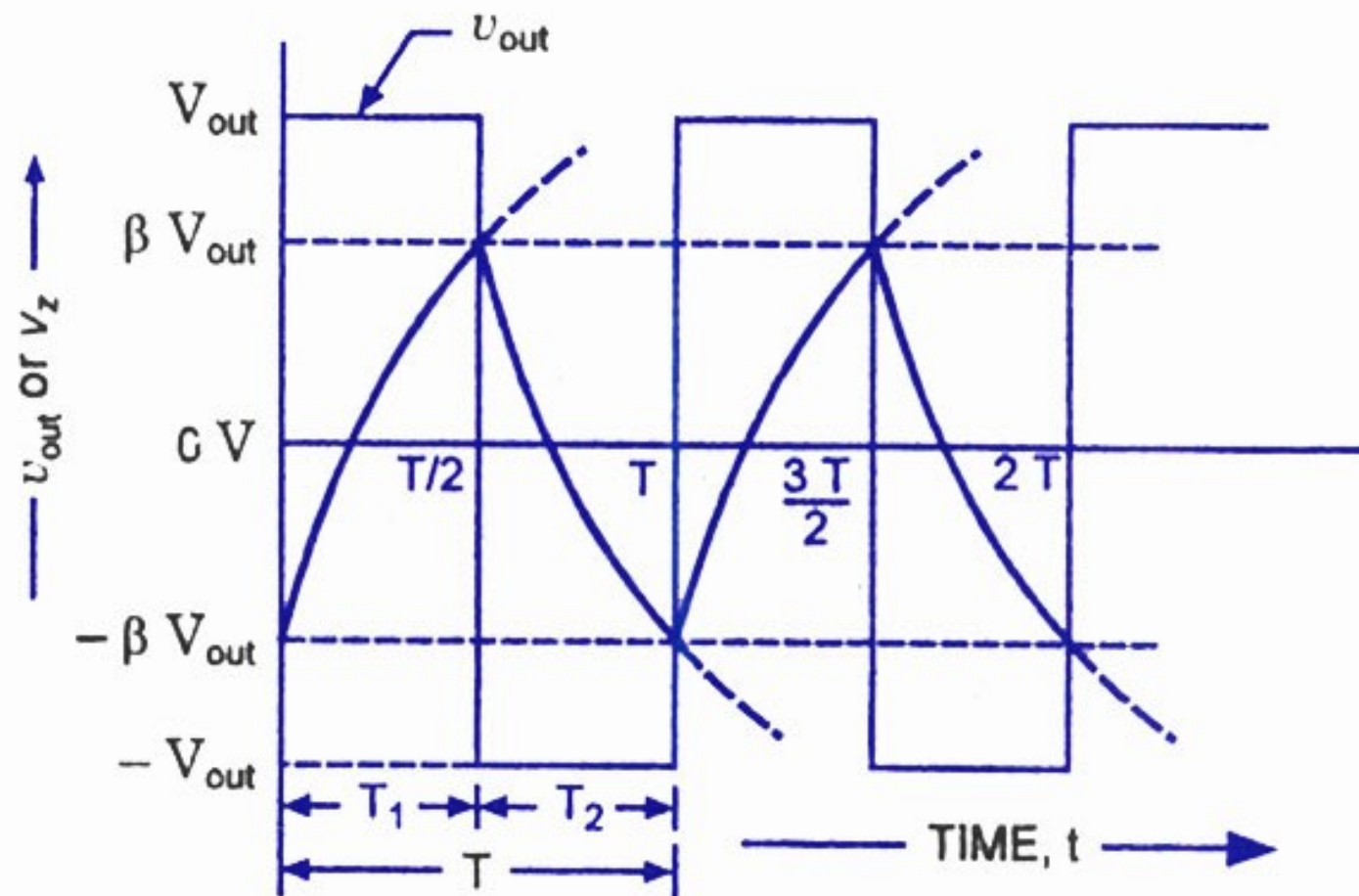- The waveforms of the capacitor voltage  $v_c$  and output voltage  $v_{out}$  (or  $v_z$ ) are shown in figure.




*Output and Capacitor Voltage Waveforms*




- When  $t = T/2$   $V_c = +\beta V_{z\text{ or}} + \beta V_{\text{out}}$   
Therefore  $\beta V_z = V_z [1 - (1 + \beta)e^{-T/2\tau}]$
- $e^{-T/2\tau} = 1 - \beta/1 + \beta$
- $T = 2\tau \log_e 1 + \beta/1 - \beta = 2R_f C \log_e [1 + (2R_2/R_1)]$

- ***The frequency,  $f = 1/T$  , of the square-wave is independent of output voltage  $V_{out}$ .***
- ***This circuit is also known as free-running or astable multivibrator because it has two quasi-stable states.***
- The output remains in one state for time  $T_1$  and then makes an abrupt transition to the second state and re-mains in that state for time  $T_2$ .
- The cycle repeats itself after time  $T = (T_1 + T_2)$  where  $T$  is the time period of the square-wave.
- The op-amp square-wave generator is useful in the frequency range of about 10 Hz -10 kHz.

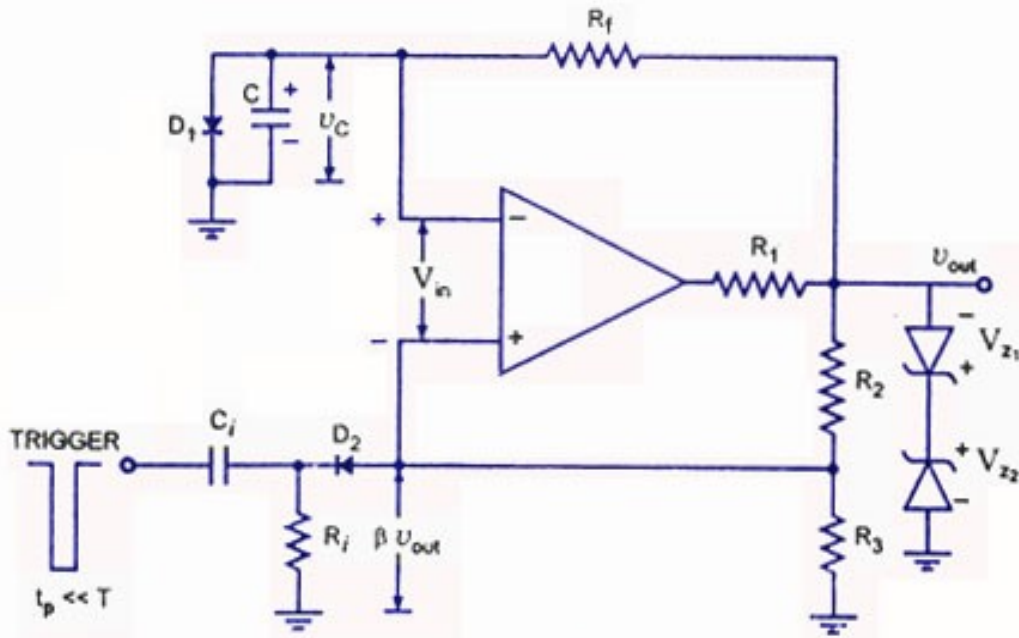
# PULSE GENERATOR (MONOSTABLE MULTIVIBRATOR)




(a) Basic Circuit

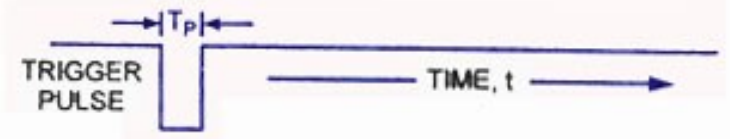

(b) Negative Trigger Pulse

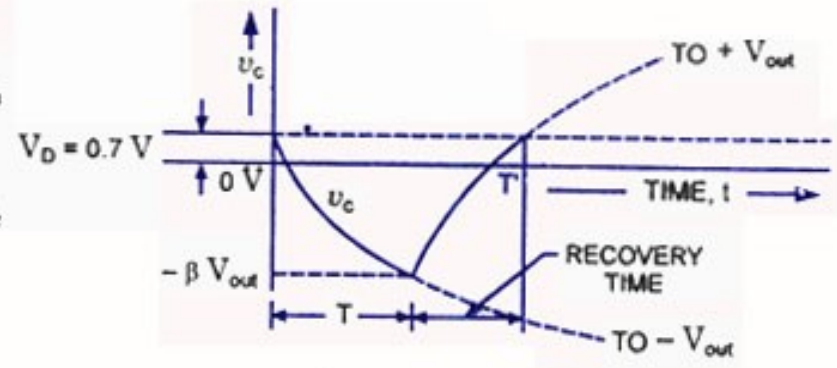

(c) Waveform of  $v_c$

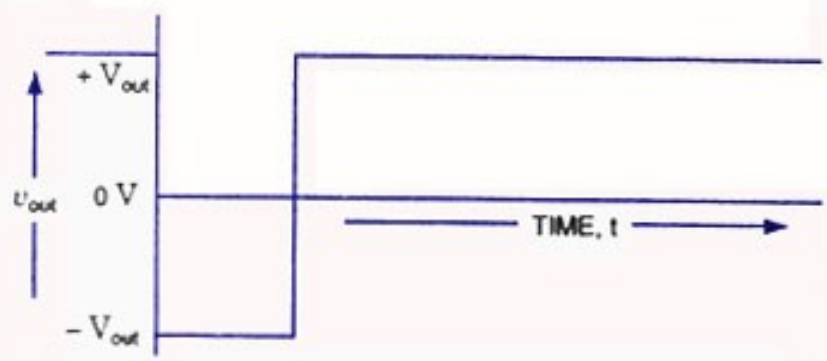

(d) Output Waveform

- A **monostable multivibrator** (MMV) has one stable state and one quasi-stable state.
- The circuit remains in its stable state till an external triggering pulse causes a transition to the quasi-stable state.
- The circuit comes back to its stable state after a time period  $T$ .
- Thus it generates a single output pulse in response to an input pulse and is referred to as a one-shot or single shot.

- Monostable multivibrator circuit is obtained by modifying the astable multivibrator circuit by connecting a diode  $D_1$  across capacitor  $C$  so as to clamp  $v_c$  at  $v_d$  during positive excursion.
- Under steady-state condition, this circuit will remain in its stable state with the output  $V_{OUT} = +V_{OUT}$  or  $+V_z$  and the capacitor  $C$  is clamped at the voltage  $V_D$  (on-voltage of diode  $V_D = 0.7\text{ V}$ ).
- The voltage  $V_D$  must be less than  $\beta V_{OUT}$  for  $v_{in} < 0$ . The circuit can be switched to the other state by applying a negative pulse with amplitude greater than  $\beta V_{OUT} - V_D$  to the non-inverting (+) input terminal.


- When a trigger pulse with amplitude greater than  $\beta V_{OUT} - V_D$  is applied,  $v_{in}$  goes positive causing a transition in the state of the circuit to  $-V_{out}$ .
- The capacitor  $C$  now charges exponentially with a time constant  $\tau = R_f C$  toward  $-V_{OUT}$  (diode  $D_1$  being reverse-biased). When capacitor voltage  $v_c$  becomes more negative than  $-\beta V_{OUT}$ ,  $v_{in}$  becomes negative and, therefore, output swings back to  $+V_{OUT}$  (steady-state output).
- The capacitor now charges towards  $+V_{OUT}$  till  $v_c$  attain  $V_D$  and capacitor  $C$  becomes clamped at  $V_D$ . The trigger pulse, capacitor voltage waveform and output voltage waveform are shown in figures respectively.

- The width of the trigger pulse  $T$  must be much smaller than the duration of the output pulse generated i.e.  $T_p \ll T$ .
  - For reliable operation the circuit should not be triggered again before  $T$ .
  - During the quasi-stable state, the capacitor voltage is given as
  - $v_c = -V_{OUT} + (V_{OUT} + V_D)e^{-t/\tau}$
- At instant  $t = T$ ,  $v_c = -\beta V_{OUT}$
- So  $-\beta V_{OUT} = -V_{OUT} + (V_{OUT} + V_D)e^{-T/\tau}$  or

- **$T = R_f C \log_e (1 + V_D/V_{OUT}) / (1 - \beta)$**
- Usually  $V_D \ll V_{OUT}$  and if  $R_2 = R_3$  so that if  $\beta = R_3/(R_2+R_3) = 1/2$  then,
- **$T = R_f C \log_e 2 = 0.693 R_f C$**



# Triangular Waveform Generator

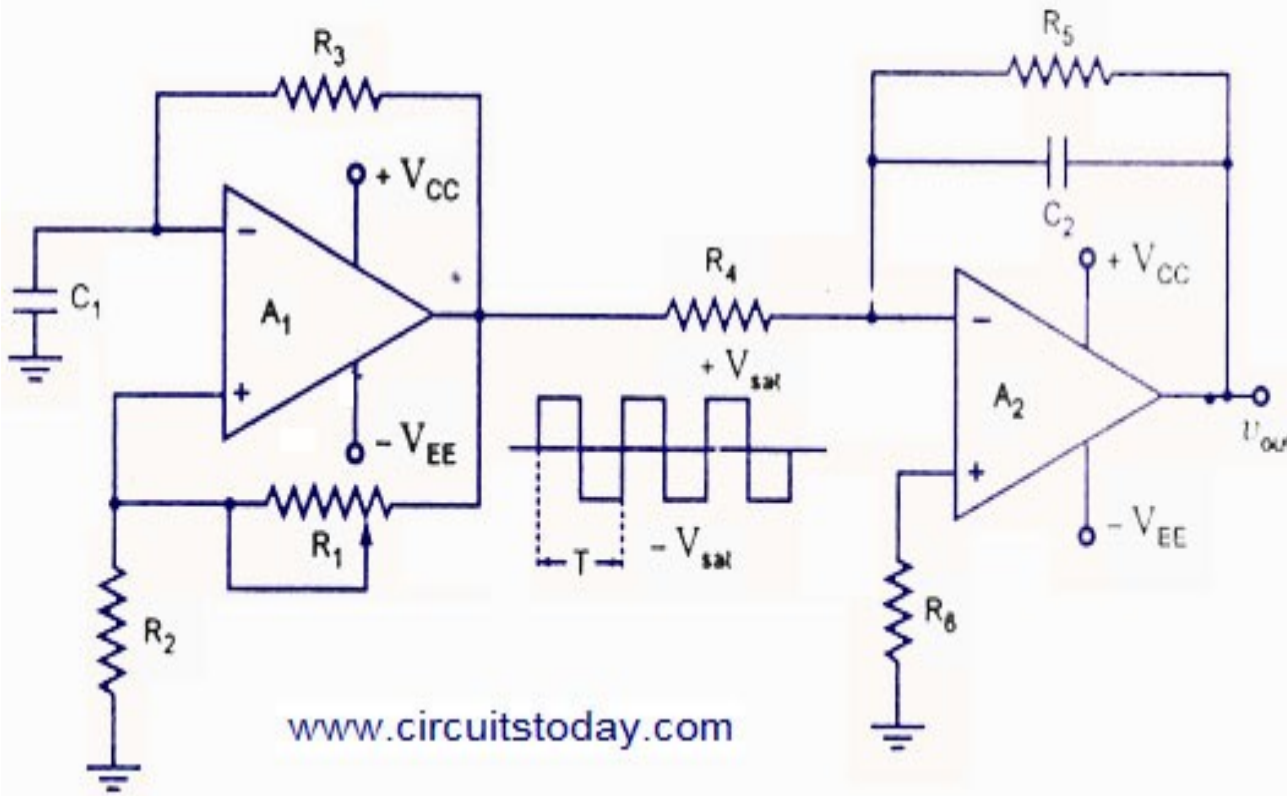

[www.circuitstoday.com](http://www.circuitstoday.com)

(a) Basic Circuit



(b) Output Waveform


Triangular Waveform Generator

- ***The op-amp triangular-wave generator is another example of a relaxation oscillator.***
- We know that the integrator output waveform will be triangular if the input to it is a square-wave.
- It means that a triangular-wave generator can be formed by simply cascading an integrator and a square-wave generator, as illustrated in figure.
- This circuit needs a dual op-amp, two capacitors, and at least five resistors.

- The rectangular-wave output of the square-wave generator drives the integrator which produces a triangular output waveform.
- The rectangular-wave swings between  $+V_{\text{sat}}$  and  $-V_{\text{sat}}$  with a time period determined from equation.
- The triangular-waveform has the same period and frequency as the square-waveform.
- Peak to-peak value of output triangular-waveform can be obtained from the following equation.  $V_{\text{out}}(\text{p-p}) = v_{\text{in}} / 4 f R_5 C_2$


- The input of integrator  $A_2$  is a square wave and its output is a triangular waveform, the output of integrator will be triangular wave only when  $R_4 C_2 > T/2$  where  $T$  is the ( period of square wave).
- $R_4 C_2$  should be equal to  $T$ .
- It may also be necessary to shunt the capacitor  $C_2$  with resistance  $R_5 = 10 R_4$  and connect an offset volt compensating network at the (+) input terminal of op-amp  $A_2$  so as to obtain a stable triangular wave.
- Since the frequency of the triangular-wave generator like any other oscillator, is limited by the op-amp slew-rate, a high slew rate op-amp, like LM 301, should be used for the generation of relatively higher frequency waveforms.

# SAWTOOTH WAVE GENERATOR

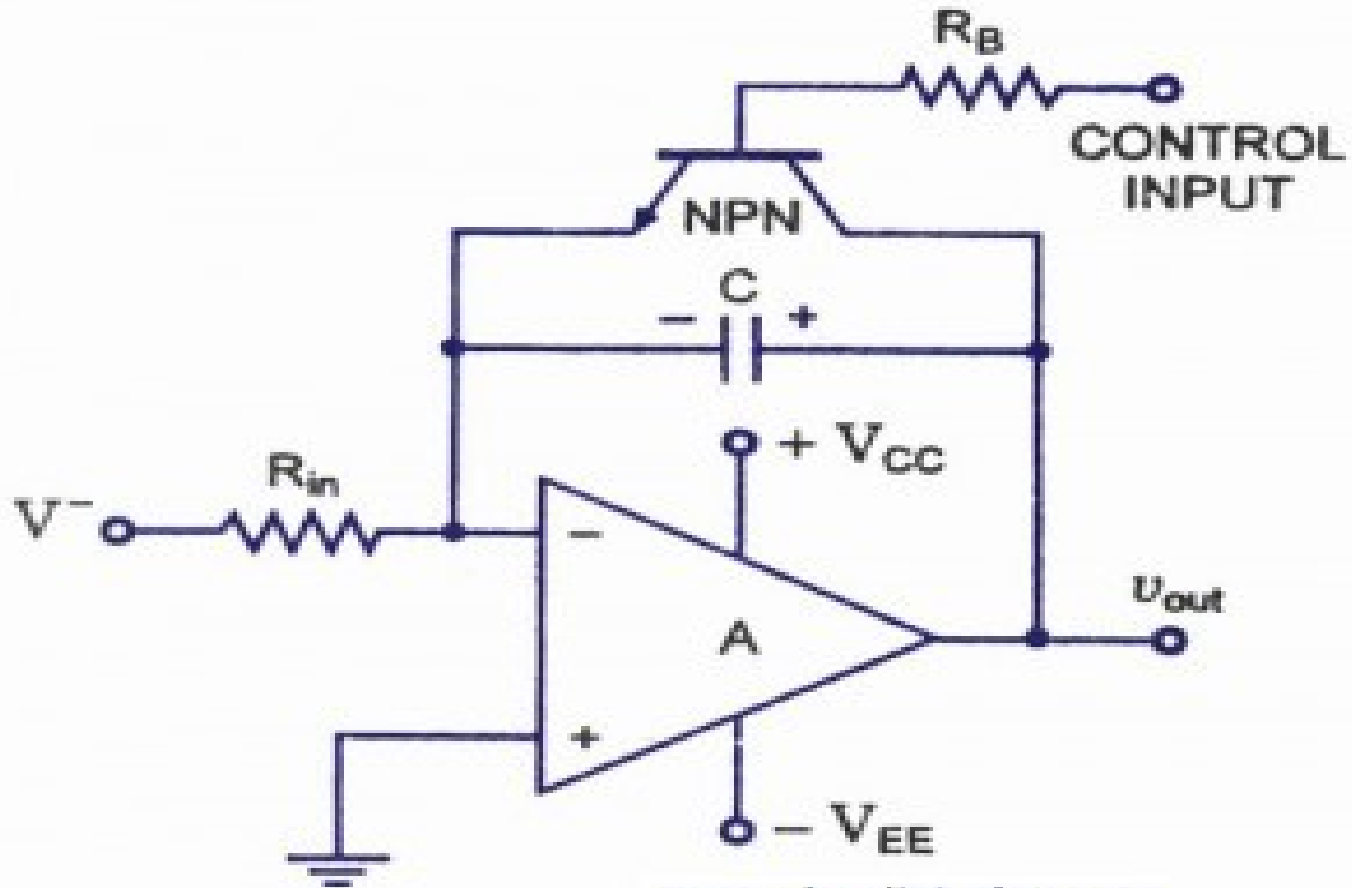


[www.circuitstoday.com](http://www.circuitstoday.com)


*BJT Controlled Ramp Generator*

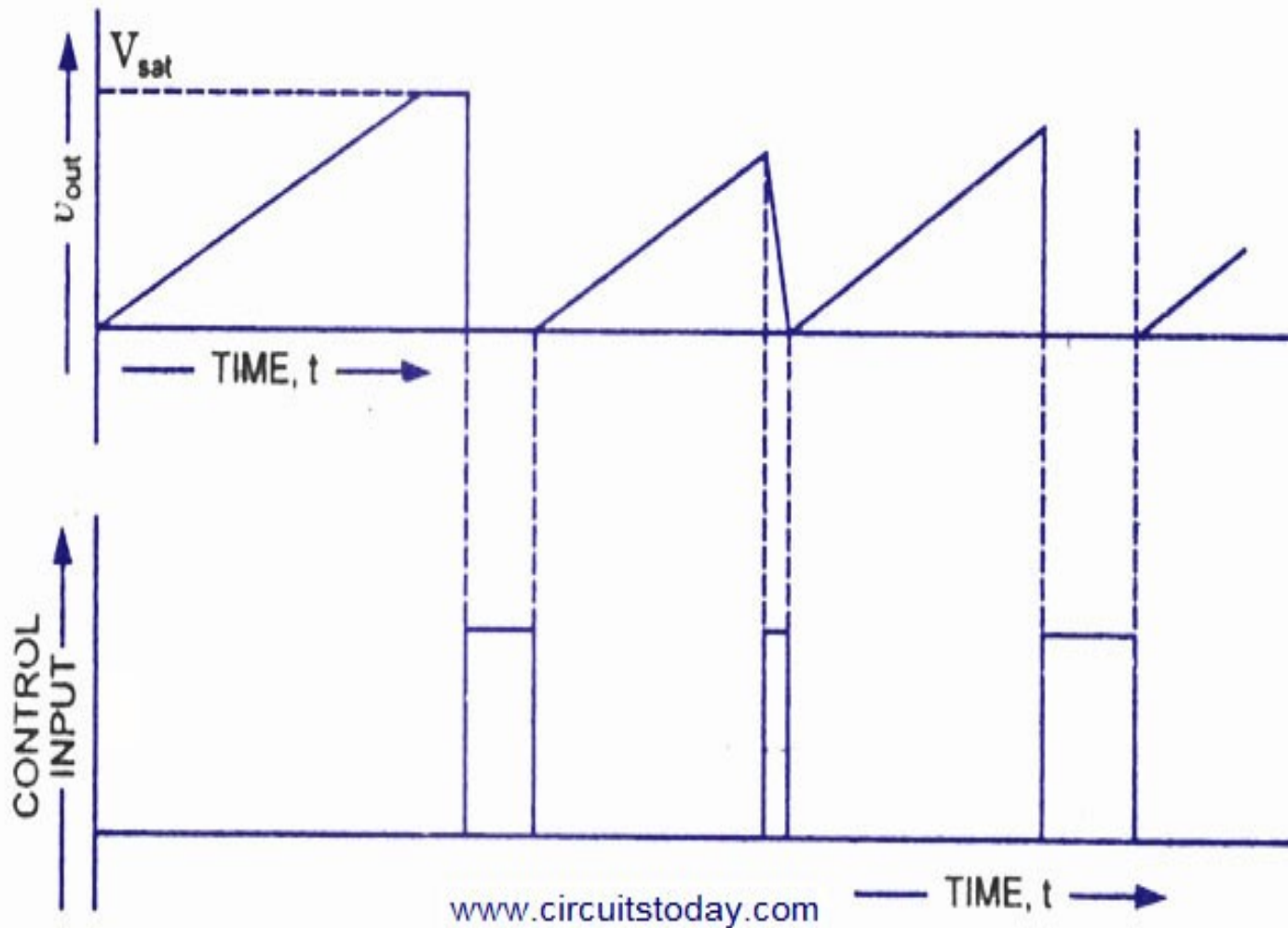

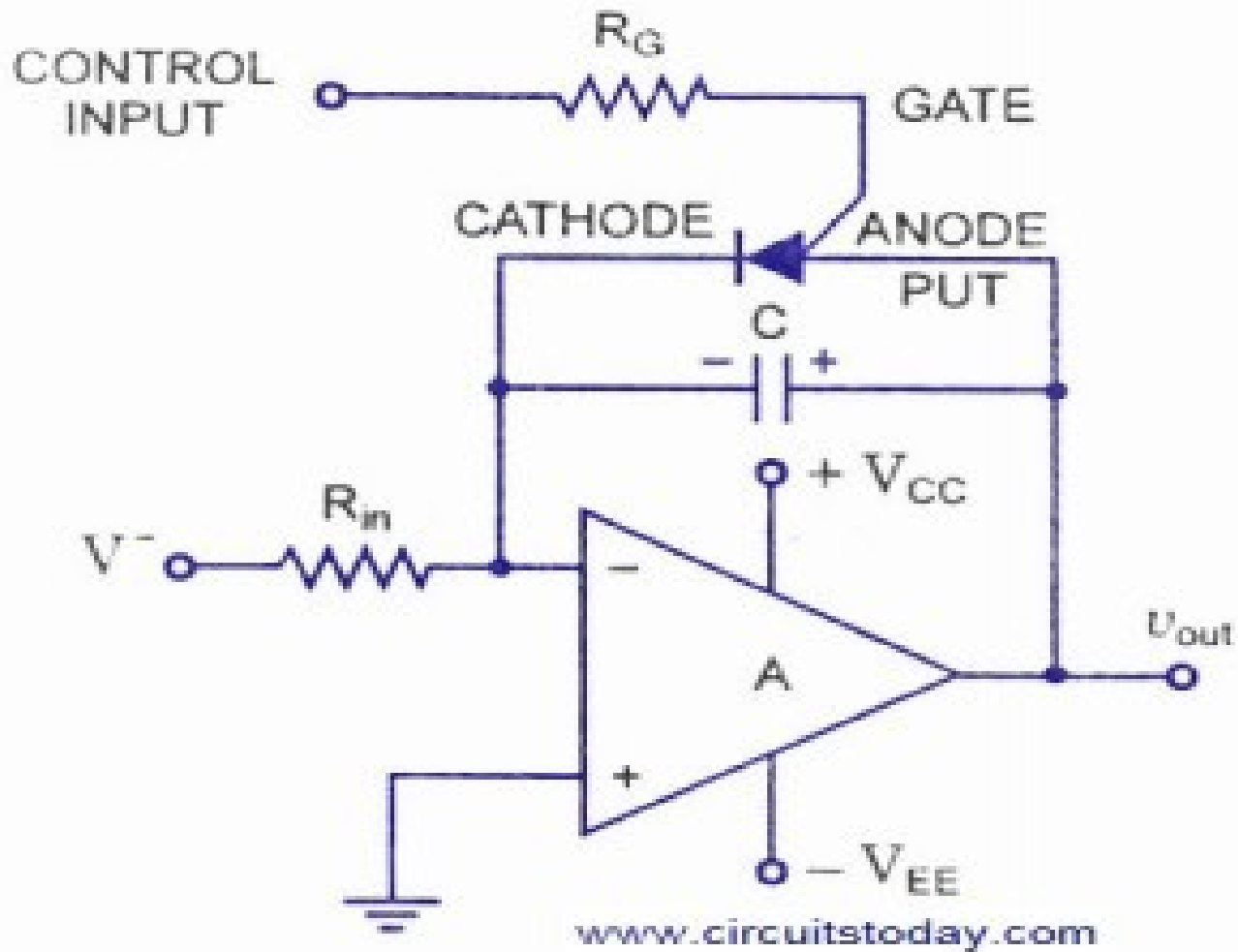*Control Input Signals Effect on The Ramp Generator's Output*



*PUT Controlled Sawtooth Generator*

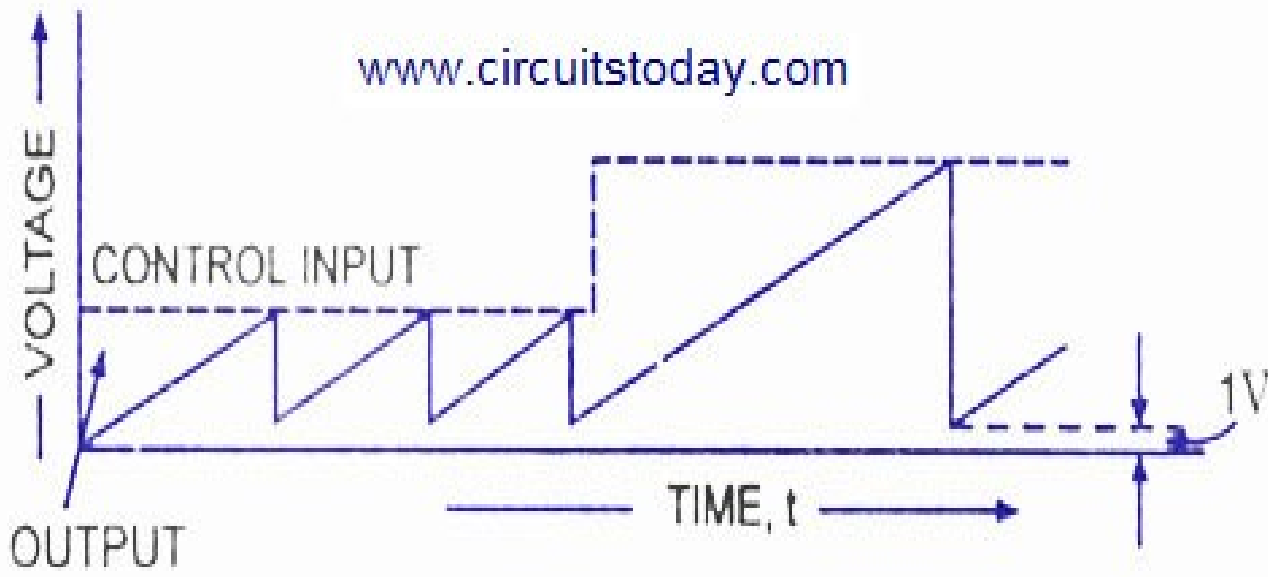

*Control Input and Output From a PUT  
Controlled Sawtooth Generator*