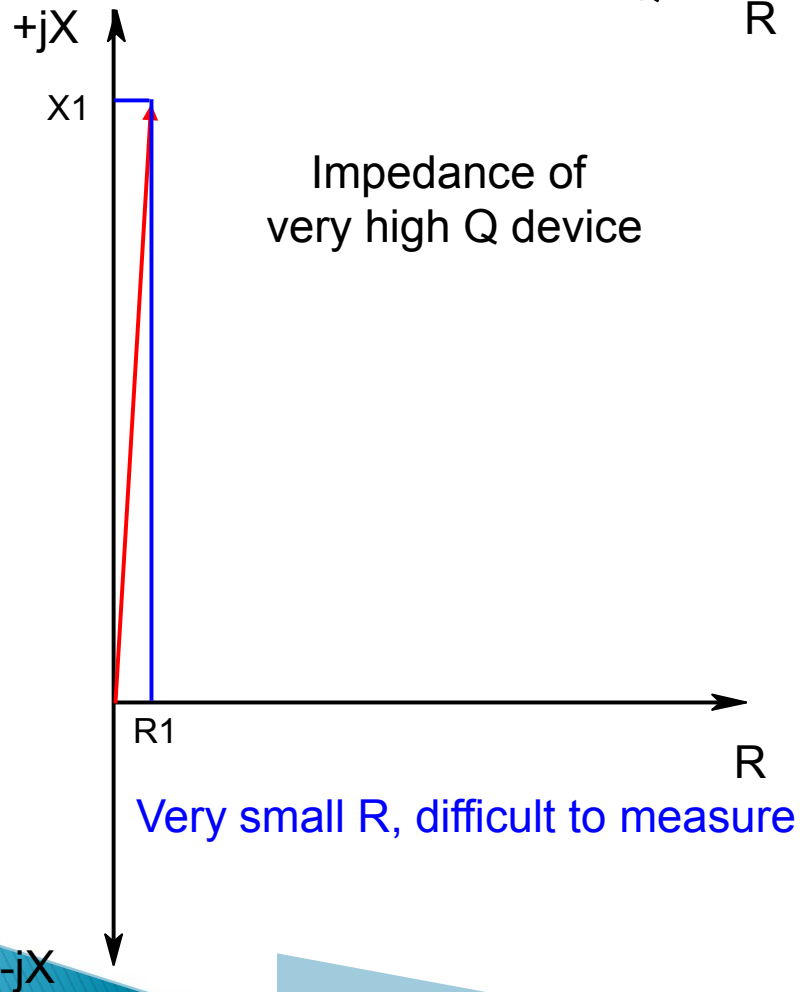


Q METERS


$$Q = \frac{X_1}{R}$$



Resonance (Q - Meter) Technique

Theory of Operation

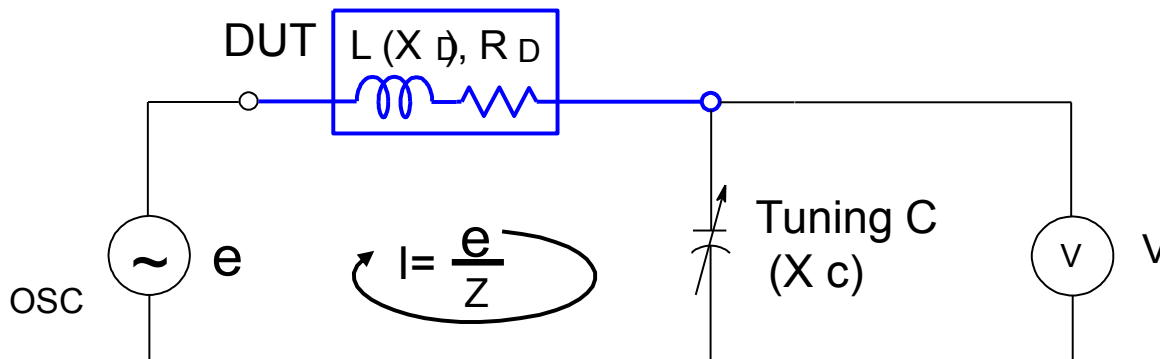- Tune C so the circuit resonates
- At resonance $X_D = -X_C$ only R remains



$$X_C = \frac{V}{I} = \frac{R_D V}{e} \quad (\text{at resonance})$$

$$Q = \frac{|X_D|}{R_D} = \frac{|X_C|}{R_D} = \frac{|V|}{e}$$

Resonant Method

Advantages and Disadvantages

Very good for high Q - low D measurements

Requires reference coil for capacitors

Limited L,C values accuracy

Vector

75kHz - 30MHz

automatic and fast

easy to use

limited compensation

Scalar

22kHz - 70MHz

manual and slow


requires experienced user

No compensation



I - V Probe Technique

Theory of Operation

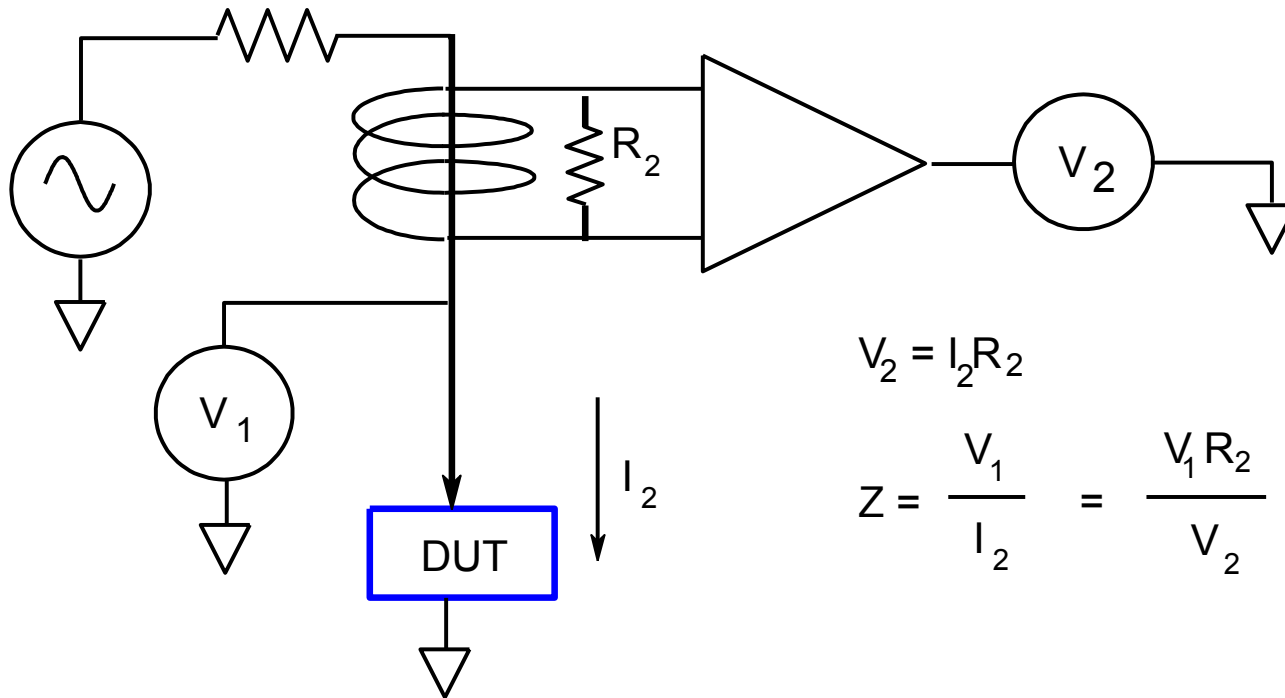

$$V_2 = I_2 R_2$$

$$Z = \frac{V_1}{I_2} = \frac{V_1 R_2}{V_2}$$

I-V (Probe)


Advantages and Disadvantages

- Medium frequency, $10\text{kHz} < f < 110\text{MHz}$
- Moderate accuracy and measurement range
- Grounded and in-circuit measurements
- Simple-to-use


RF Power Measurement

Theory of Operation

High Impedance Test Head

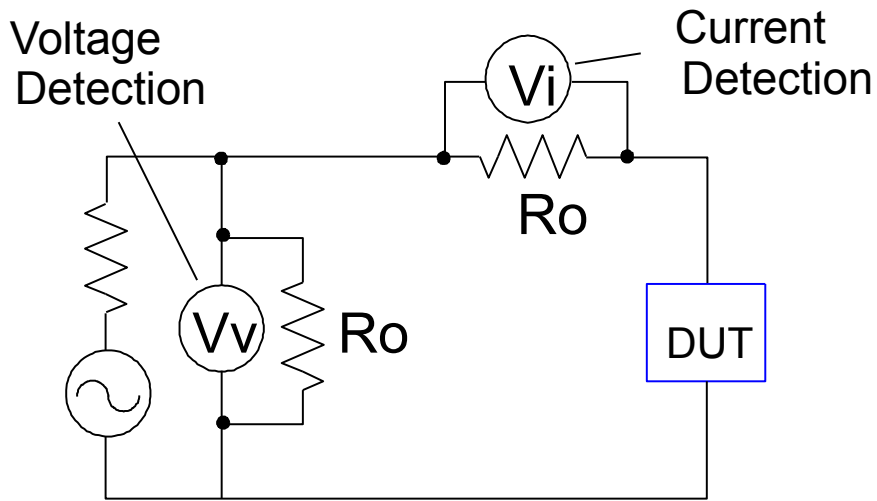

Low Impedance Test Head

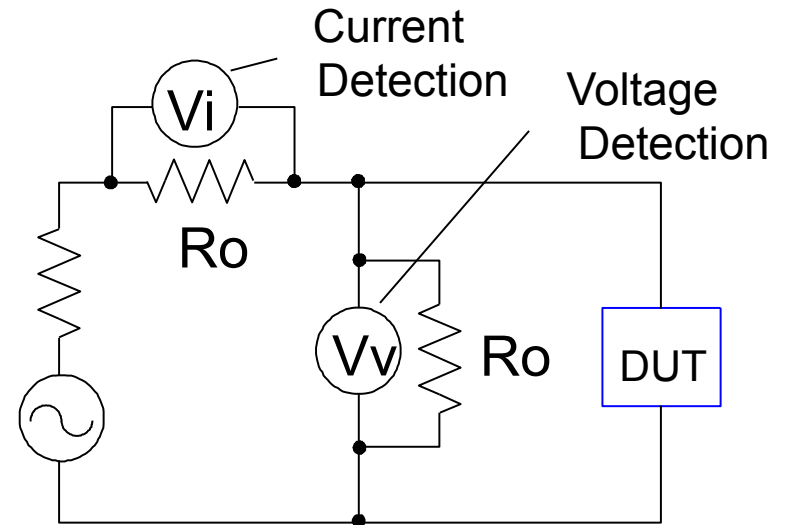

RF I-V

Advantages and Disadvantages

- High frequency, $1\text{MHz} < f < 1.8\text{GHz}$
- Most accurate method at $> 100\text{ MHz}$
- Grounded device measurement

VIRTUAL LAB LINK

- ▶ <http://iitkgp.vlab.co.in/?sub=39&brch=124&sim=1646&cnt=1>
- ▶