

LECTURE 3

Equivalent Circuit of Induction Machines

V_1 – stator voltage, per phase ($V_1 = V_{LL} / \sqrt{3}$)

R_1, R_2 – stator and rotor winding resistance

$X_1 = 2\pi f_1 L_1$ – stator leakage reactance

$X_2 = 2\pi f_1 L_2$ – rotor leakage reactance

R_c – resistance representing core loss, per phase

X_m – magnetizing reactance, per phase

N_1, N_2 – effective number of turns of stator and rotor windings.


$E_1 = 4.44 f_1 N_1 \Phi$, where Φ is flux per pole

$E_2 = 4.44 f_1 N_2 \Phi$

Equivalent Circuit of Induction Machines

- **Step2 Rotor winding is shorted**

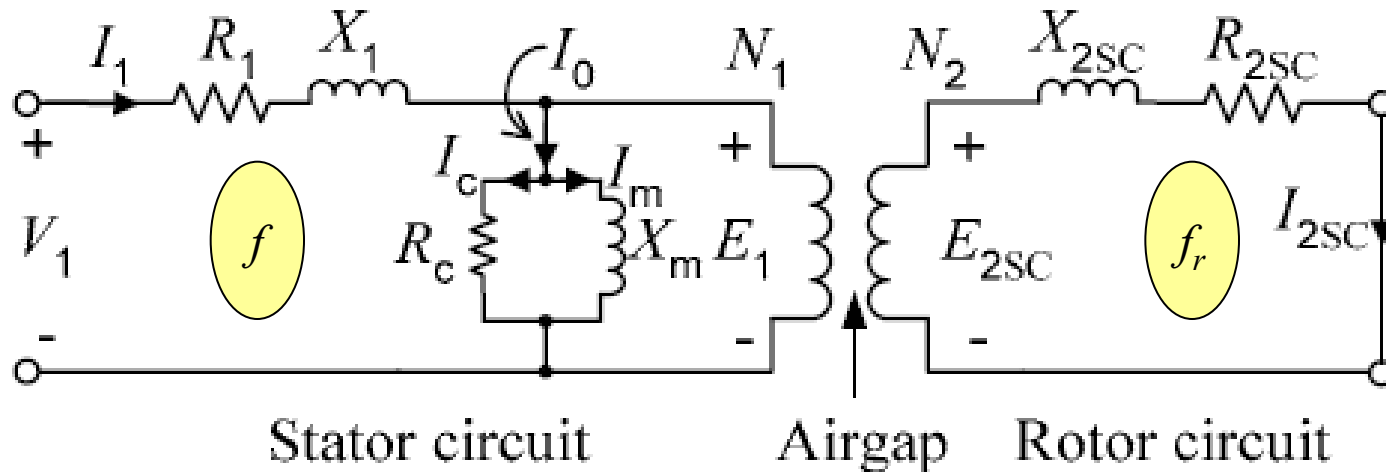
(Under normal operating conditions, the rotor winding is shorted. The slip is s)



- Note: the frequency of E_2 is $f_r = sf$ because **rotor is rotating**.

Equivalent Circuit of Induction Machines

- **Step3 Eliminate f_2**

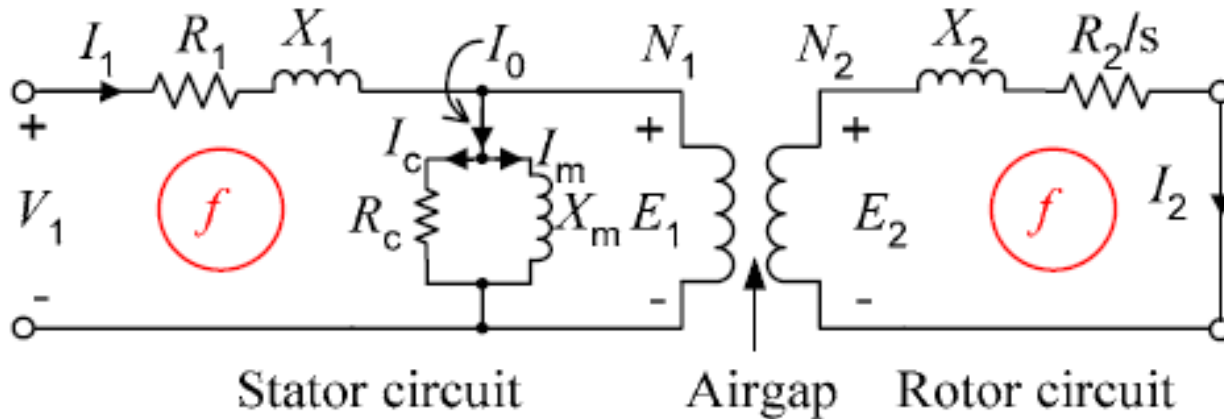


Keep the rotor current same:

$$I_{2sc} = \frac{E_{2sc}}{R_{2sc} + jX_{2sc}} = \frac{sE_2}{R_2 + jsX_2} = \frac{E_2}{\frac{R_2}{s} + jX_2} = I_2$$

Equivalent Circuit of Induction Machines

- **Step 4 Referred to the stator side**

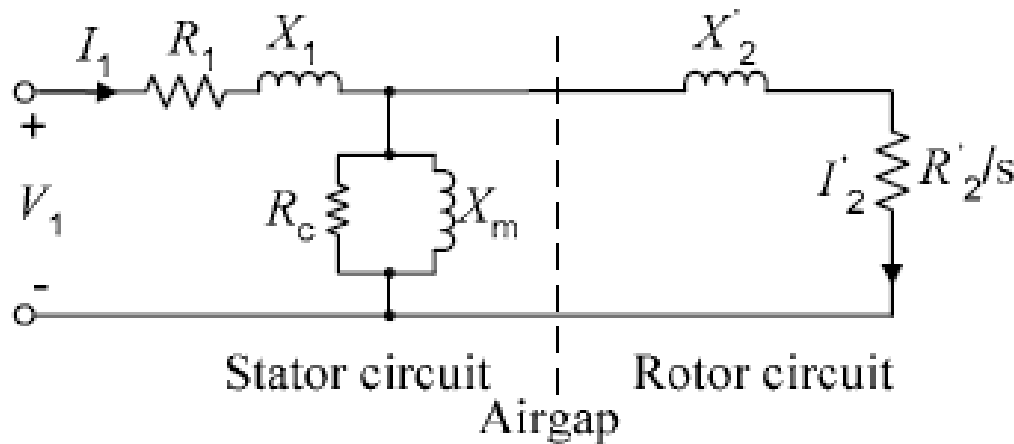

$$X'_2 = a^2 X_2,$$

$$R'_2 = a^2 R_2,$$

$$I'_2 = \frac{1}{a} I_2,$$


$$\text{where } a = \frac{N_1}{N_2}$$

- **Note:**

- X'_2 and R'_2 will be given or measured. In practice, we do not have to calculate them from above equations.
- Always refer the rotor side parameters to stator side.
- R_c represents core loss, which is the core loss of stator side.


Equivalent Circuit of Induction Machines

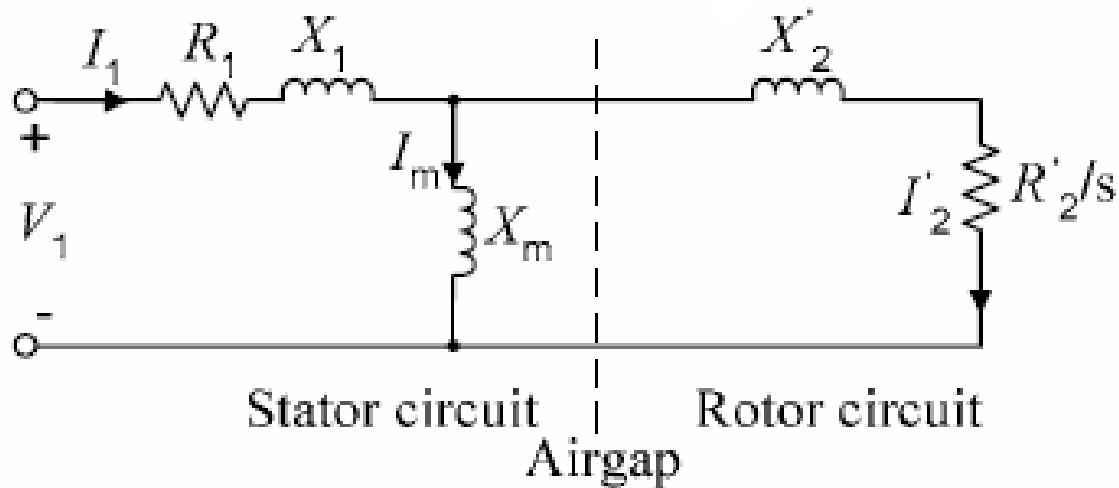- **IEEE recommended equivalent circuit**



Equivalent Circuit of Induction Machines

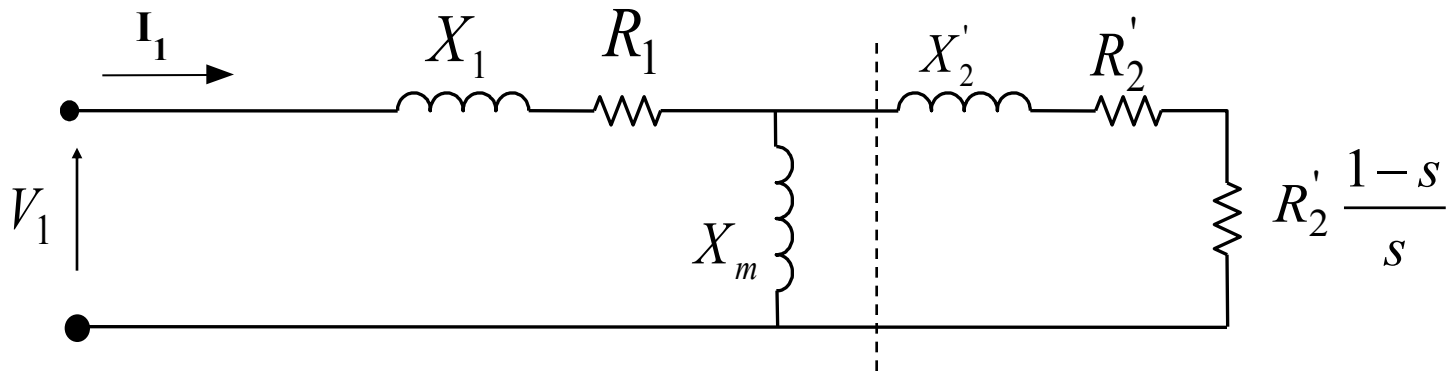- **IEEE recommended equivalent circuit**



Note: $\frac{R_2}{s}$ can be separated into 2 PARTS

$$\frac{R_2}{s} = R_2 + \frac{R_2(1-s)}{s}$$

- **Purpose :** to obtain the developed mechanical

Power Flow Diagram

$$\sqrt{3}V_s I_s \cos \theta$$

$$1hp = 746W$$

P_{in} (Motor)


P_{in} (Rotor)

$P_{developed}$
 $P_{mechanical}$
 $P_{converted}$
(P_m)

P_{out}, P_o

P_{in} (Stator)

$P_{air\ Gap}$
(P_{ag})

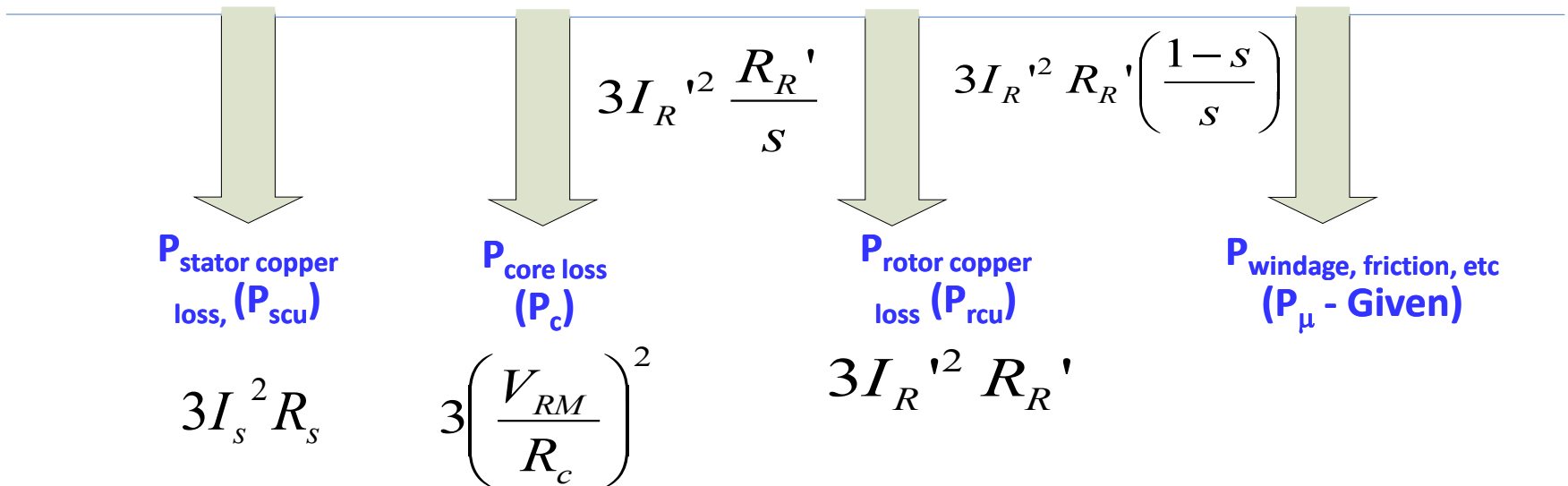

Torque-Equation

- Torque, can be derived from **power equation** in term of **mechanical power or electrical power**.

$$\text{Power, } P = \omega T, \text{ where } \omega = \frac{2\pi n}{60} (\text{rad / s})$$

$$\text{Hence, } T = \frac{60P}{2\pi n}$$

Thus,

$$\text{Mechanical Torque, } T_m = \frac{60P_m}{2\pi n_r}$$

$$\text{Output Torque, } T_o = \frac{60P_o}{2\pi n_r}$$

