
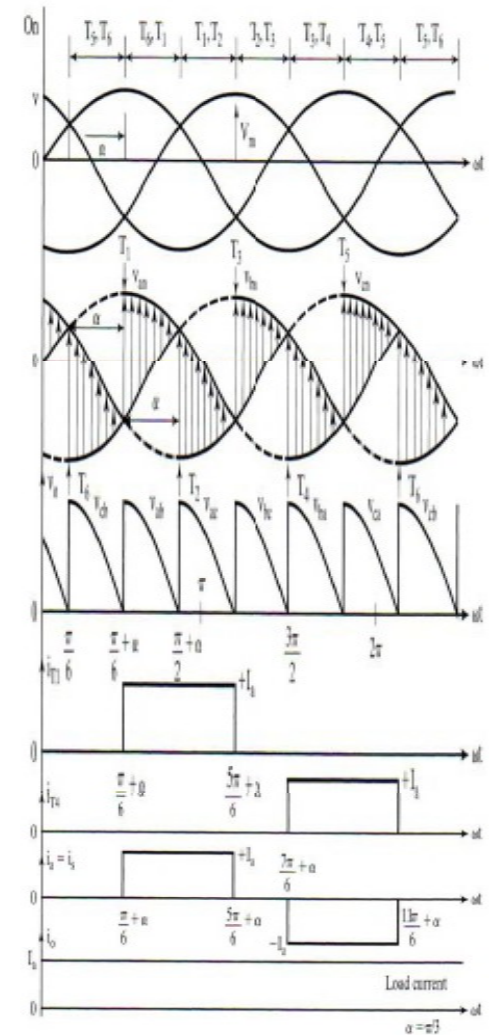


# 1. AC to DC Converters
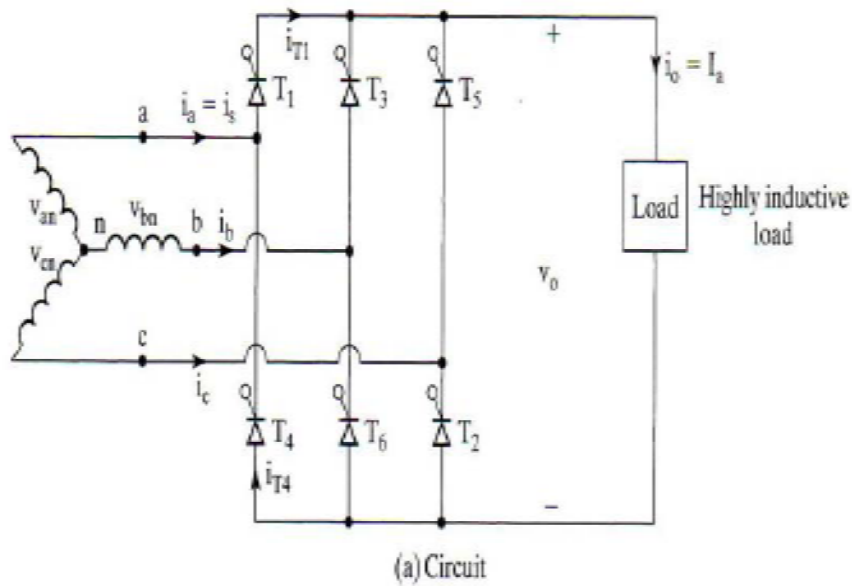
## -Three-phase, Full Wave AC to DC converter



If the line-to-neutral voltages are defined as

$$v_{an} = V_m \sin \omega t$$

$$v_{bn} = V_m \sin \left( \omega t - \frac{2\pi}{3} \right)$$

$$v_{cn} = V_m \sin \left( \omega t + \frac{2\pi}{3} \right)$$

the corresponding line-to-line voltages are

$$v_{ab} = v_{an} - v_{bn} = \sqrt{3} V_m \sin \left( \omega t + \frac{\pi}{6} \right)$$

$$v_{bc} = v_{bn} - v_{cn} = \sqrt{3} V_m \sin \left( \omega t - \frac{\pi}{2} \right)$$

$$v_{ca} = v_{cn} - v_{an} = \sqrt{3} V_m \sin \left( \omega t + \frac{\pi}{2} \right)$$

The average output voltage is found from

$$\begin{aligned} V_{dc} &= \frac{3}{\pi} \int_{\pi/6+\alpha}^{\pi/2+\alpha} v_{ab} d(\omega t) = \frac{3}{\pi} \int_{\pi/6+\alpha}^{\pi/2+\alpha} \sqrt{3} V_m \sin \left( \omega t + \frac{\pi}{6} \right) d(\omega t) \\ &= \frac{3\sqrt{3} V_m}{\pi} \cos \alpha \end{aligned}$$