

1-Phase Thyristor Converter


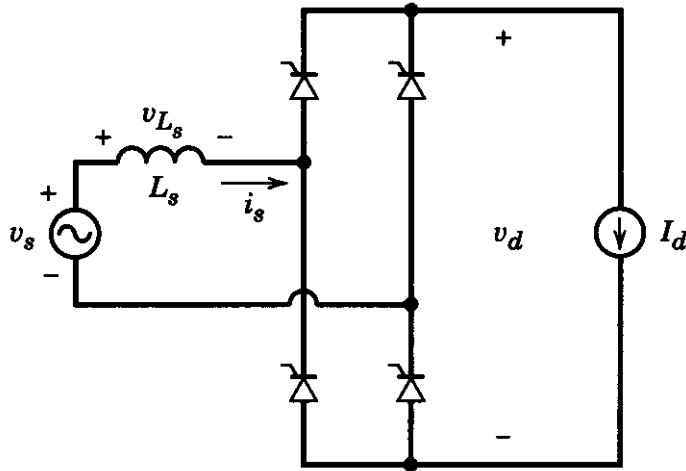
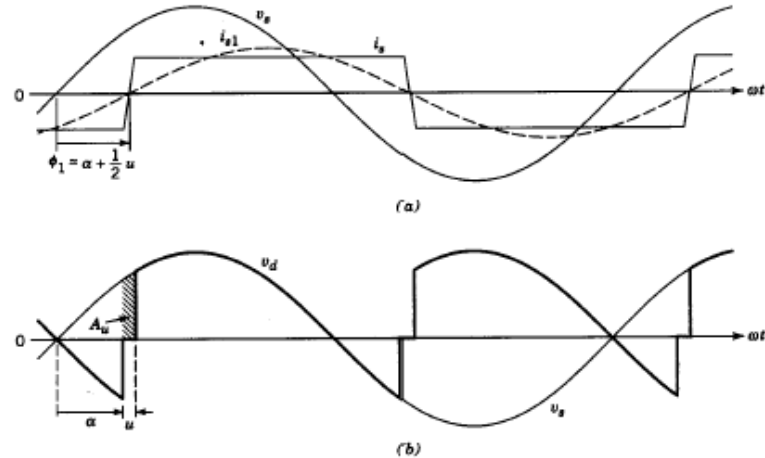


Figure 6-9 Single-phase thyristor converter with a finite L_s and a constant dc current.

- o AC side inductance is included, which generally cannot be ignored in practical thyristor converters.
- o For a given delay angle, there will be a finite commutation interval
- o Commutation process is similar to that in diode bridge rectifiers
- o During the commutation interval, all four thyristors conduct, and therefore, $v_d=0$, and the voltage $v_{L_s}=v_s$.

1-Phase Thyristor Converter

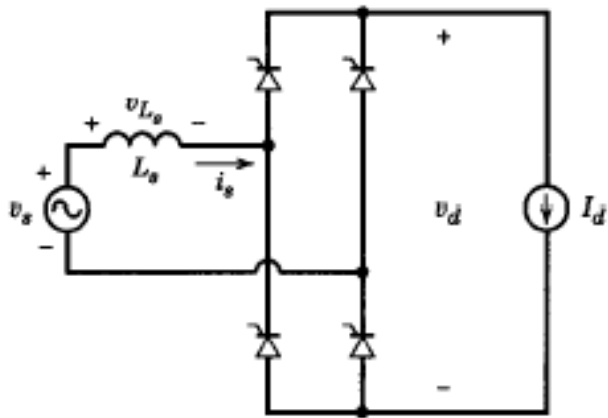

- o During the commutation interval, all four thyristors conduct, and therefore, $v_d=0$, and the voltage $v_{L_s}=v_s$.


$$v_s = v_{L_s} = L_s \frac{di_s}{dt}$$

$$\therefore A_\mu = \int_{\alpha}^{\alpha+\mu} \sqrt{2}V_s \sin(\omega t) dt = \omega L_s \int_{-I_d}^{I_d} di_s = 2\omega L_s I_d$$


$$\therefore A_\mu = \int_{\alpha}^{\alpha+\mu} \sqrt{2}V_s \sin(\omega t) dt = \sqrt{2}V_s [\cos \alpha - \cos(\alpha + \mu)] = 2\omega L_s I_d$$

$$\therefore \mu = \cos^{-1} \left[\cos \alpha - \frac{2\omega L_s I_d}{\sqrt{2}V_s} \right] - \alpha$$

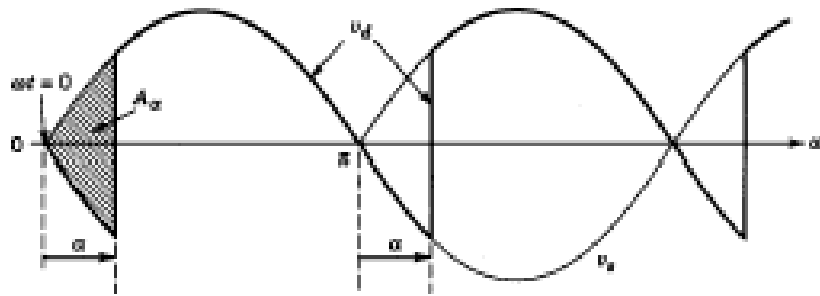1-Phase Thyristor Converter: with and without L_s



without L_s

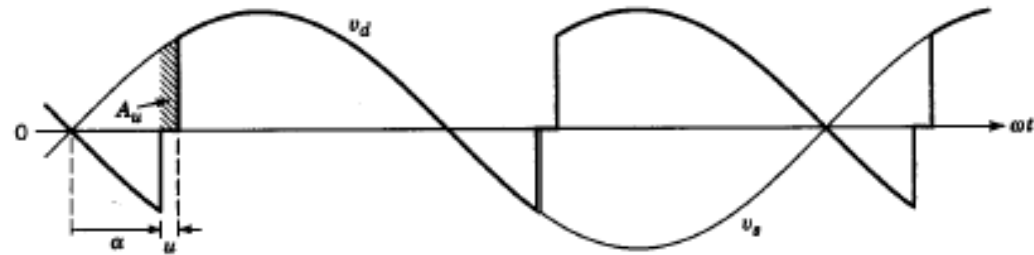

with L_s

- o Voltage drop due to the inclusion of L_s .


$$\Delta V_{d\mu} = \frac{A_\mu}{\pi} = \frac{2\omega L_s I_d}{\pi}$$

$$V_{d[\mu=0]} = 0.9V_s \cos \alpha$$

$$V_{d[\mu \neq 0]} = 0.9V_s \cos \alpha - \frac{2\omega L_s I_d}{\pi}$$

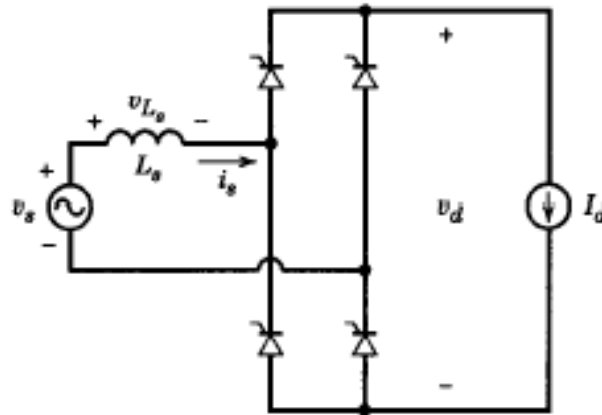Example

In the converter circuit, L_s is 5% with the rated voltage of 230 V at 60 Hz and the rated volt-ampere of 5 kVA. Calculate the commutation angle μ and V_d/V_{d0} with the rated input voltage, power of 3 kW, and $\alpha=30^\circ$.



Solution

$$I_{rated} = \frac{5000}{230} = 21.74 \text{ A}$$

$$Z_{base} = \frac{V_{rated}}{I_{rated}} = 10.58 \ \Omega$$

$$L_s = \frac{0.05 Z_{base}}{377} = 1.4 \text{ mH}$$

$$\alpha = 30^\circ$$

$$P_d = V_d I_d = \left[0.9 V_s \cos \alpha - \frac{2}{\pi} \omega L_s I_d \right] I_d = 3000$$

$$I_d = 17.3 \text{ A}$$

$$\mu = \cos^{-1} \left[\cos \alpha - \frac{2 \omega L_s I_d}{\sqrt{2} V_s} \right] - \alpha = 5.9^\circ$$

$$V_d = 0.9 V_s \cos \alpha - \frac{2}{\pi} \omega L_s I_d = 173.5 \text{ V}$$