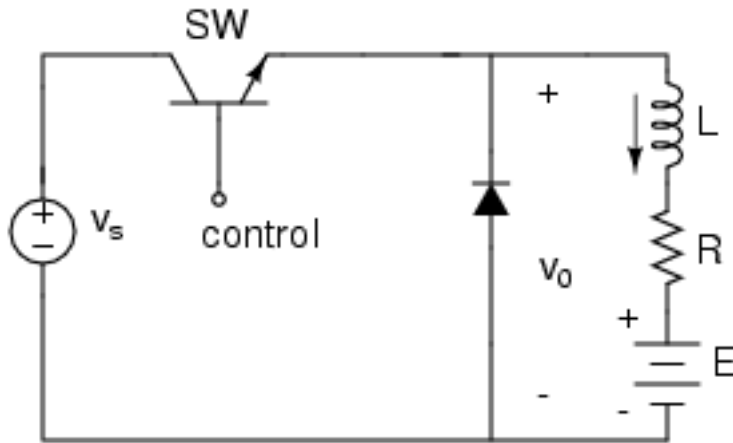


# DC-DC Converters (choppers)

- The objective is to convert a fixed DC voltage to a variable DC voltage
- It is possible to step up and step down voltage.

# Voltage step down (buck converter)



First, suppose  $L=0$ ,  $E=0$ .

The diode is not needed.


$$V_a = (t_{on}/T)V_s$$

$k = t_{on}/T$  is the duty cycle

$$V_{RMS} = k^{1/2}V_s$$

$$P_{out} = (kV_s^2)/R$$

# Step down converter with RL load

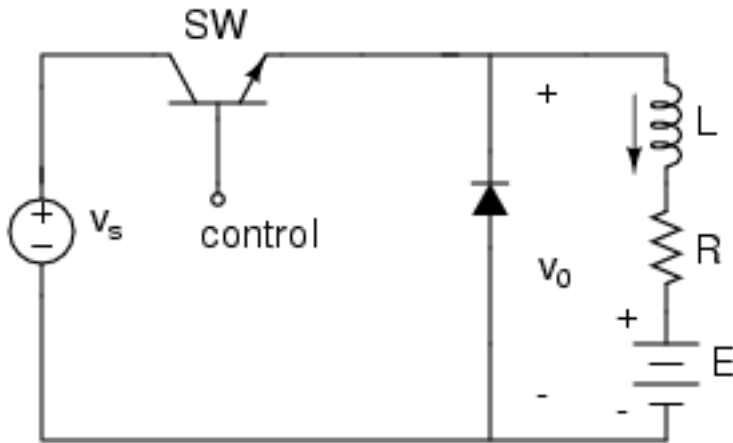

Mode 1 (On)

$$i_1(t) = I_1 e^{-tR/L} + \frac{V_s - E}{R} (1 - e^{-tR/L}), \quad 0 \leq t \leq kT$$

Mode 2 (Off):  $I_2 = i_1(kT)$ , and

$$i_2(t) = I_2 e^{-(t-kT)R/L} + \frac{V_s - E}{R} (1 - e^{-(t-kT)R/L}), \quad kT \leq t \leq T.$$



For a steady state current

$$i_1(0) = i_2(T),$$

$$I_1 = \frac{V_s}{R} \left( \frac{1 - e^{kT(R/L)}}{1 - e^{T(R/L)}} \right) - \frac{E}{R} = \frac{V_s}{R} \left( \frac{1 - e^{kz}}{1 - e^z} \right) - \frac{E}{R}$$

$$I_2 = \frac{V_s}{R} \left( \frac{1 - e^{-kz}}{1 - e^{-z}} \right) - \frac{E}{R}, \quad z = T \frac{R}{L},$$
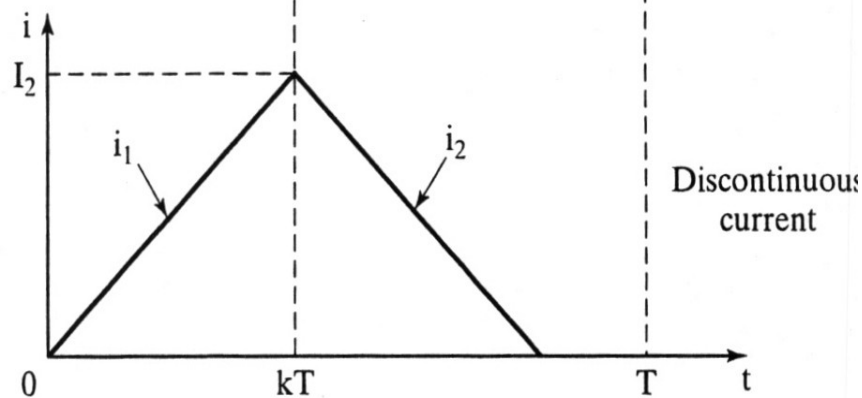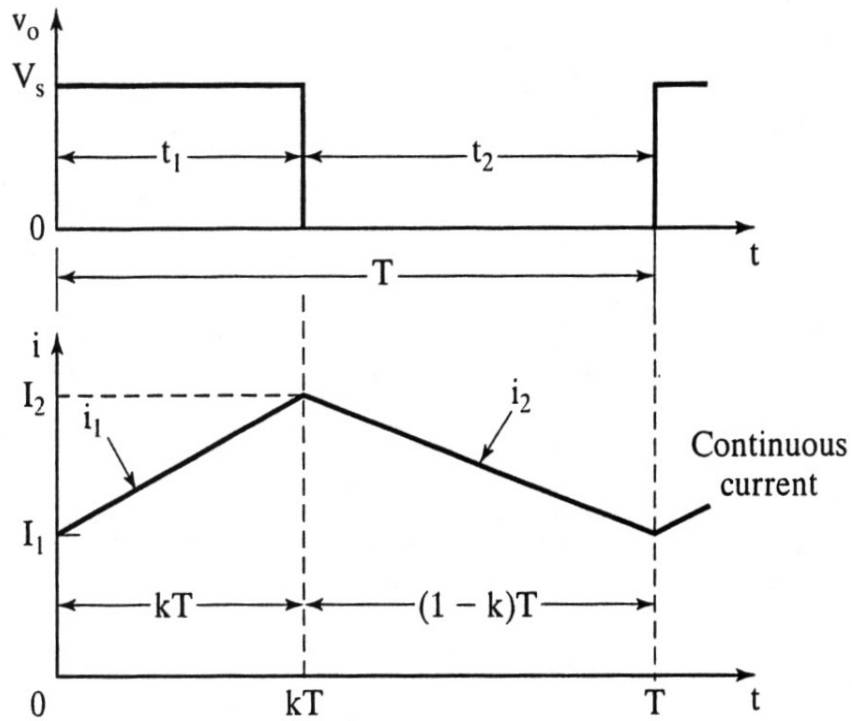
$$\frac{E}{V_s} \leq \frac{1 - e^{kz}}{1 - e^z} \quad \text{for cont. current}$$



(b) Waveforms

### Example 5.2


$$I_a = \frac{1}{2}(I_1 + I_2)$$


$$I_o = (I_1^2 + \frac{1}{3}\Delta I^2 + I_1\Delta I)^{1/2}$$

$$I_s = kI_a$$

$$I_R = \sqrt{k}I_o$$


(A) chopperscript.dat (active)

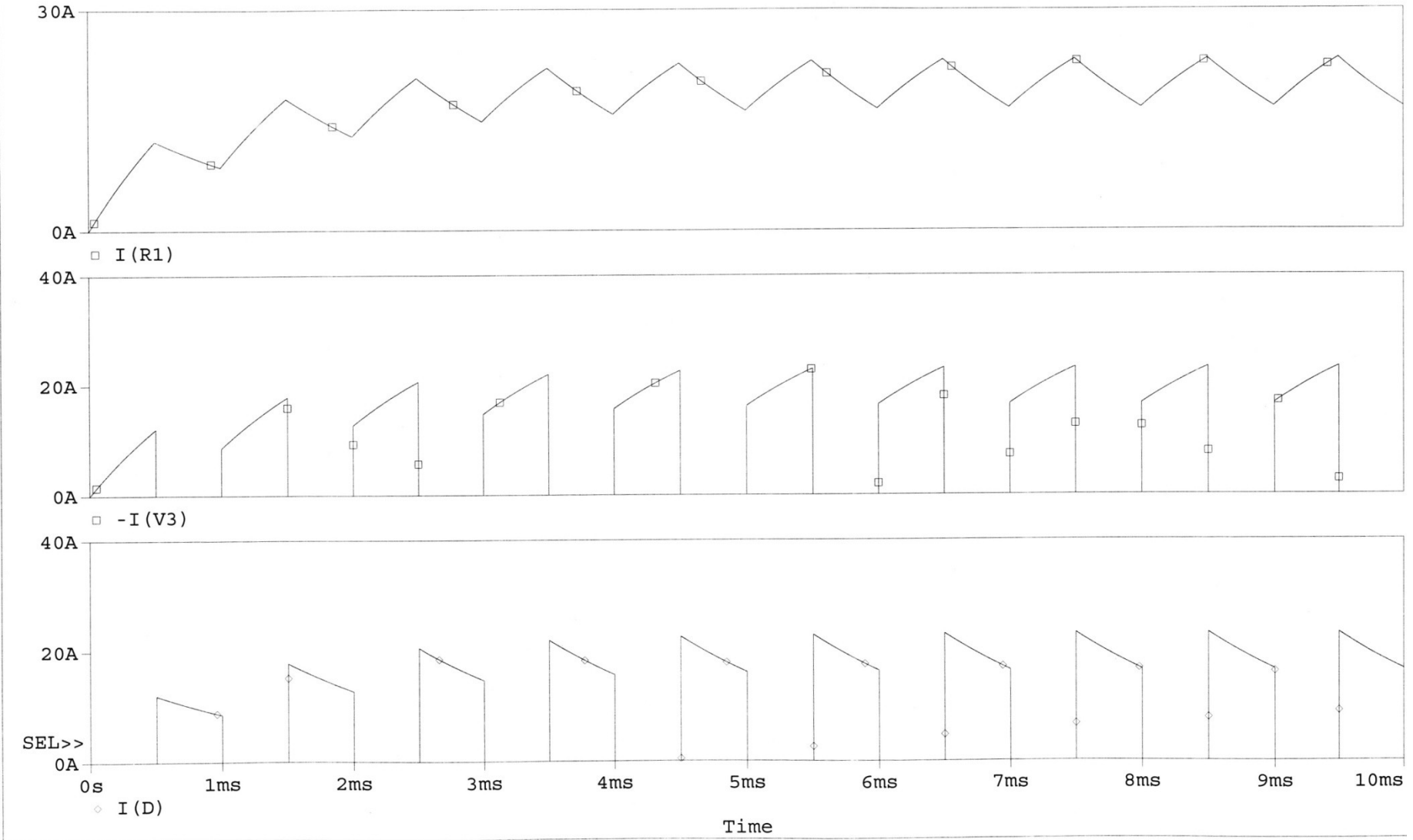

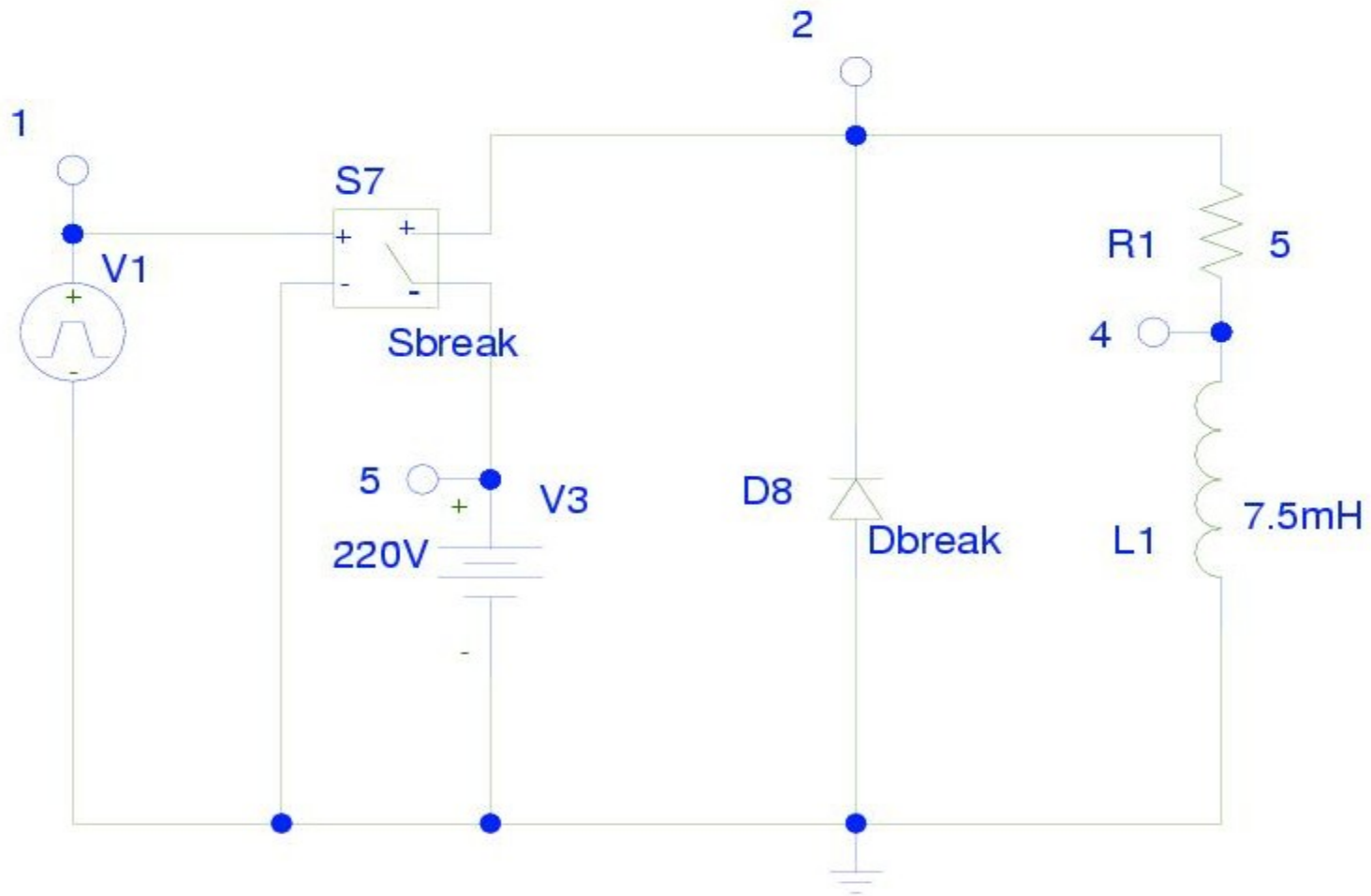

Pspice schematics Step down dc-dc converter


# Voltage step up (boost) converter

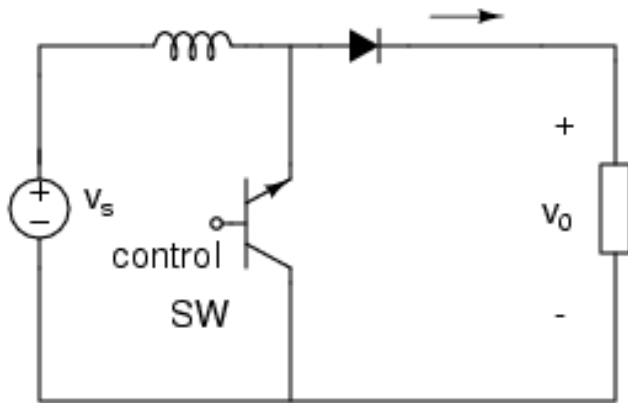

"On" mode:  $V_L = L(di/dt)$



"Off" mode: Assume current decreases at a constant rate. Then

$$V_o = V_s + V_L$$

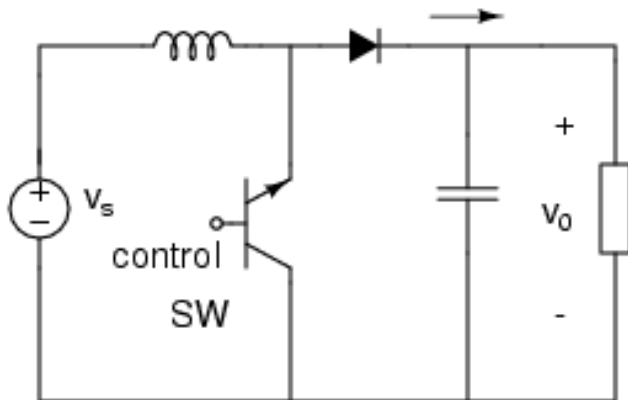

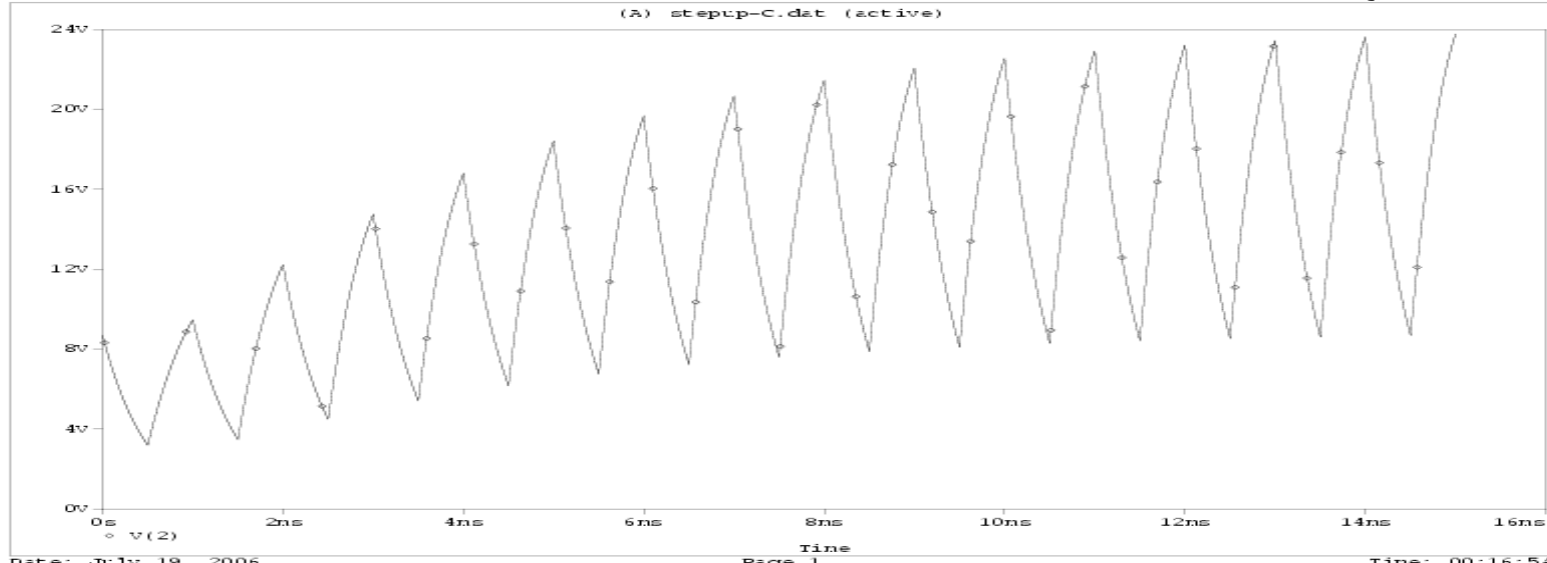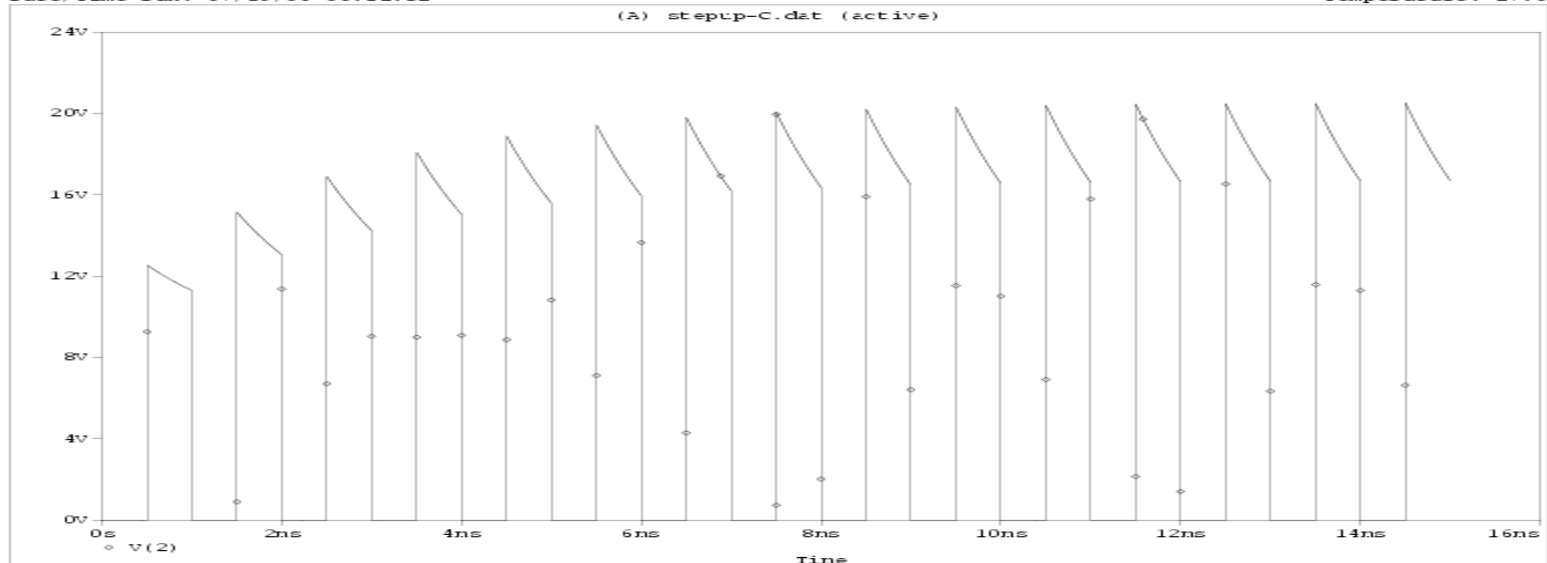To ensure continuous current flow, a capacitor is included.





Performance of a step up converter with resistive load (C=0).

Mode 1 (On)

$$i_1(t) = \frac{V_s}{L}t + I_1, \quad 0 \leq t \leq kT$$

Mode 2 (Off): , and

$$I_2 = i_1(kT) = \frac{V_s}{L}kT + I_1 \quad \text{and}$$

$$i_2(t) = I_2 e^{-(t-kT)R/L} + \frac{V_s - E}{R}(1 - e^{-(t-kT)R/L}), \quad kT \leq t \leq T.$$

At steady state  $i_1(0) = i_2(T)$ ,

$$I_1 = \frac{V_s}{R} \left( \frac{kze^{(k-1)z}}{1 - e^{(k-1)z}} \right) + \frac{V_s - E}{R}$$

$$I_2 = \frac{V_s}{R} \left( \frac{kz}{1 - e^{(k-1)z}} \right) + \frac{V_s - E}{R}, \quad z = T \frac{R}{L},$$

$$\Delta I = \frac{V_s}{L}kT, \quad I_{a,\text{load}} = \frac{I_1 + I_2}{2}(1 - k)$$

$$\frac{E}{V_s} \leq 1 \quad \text{for continuous inductor current}$$