

# General Operation of a 6-Step Thyristor Inverter

## General Schematic of Thyristor Inverter

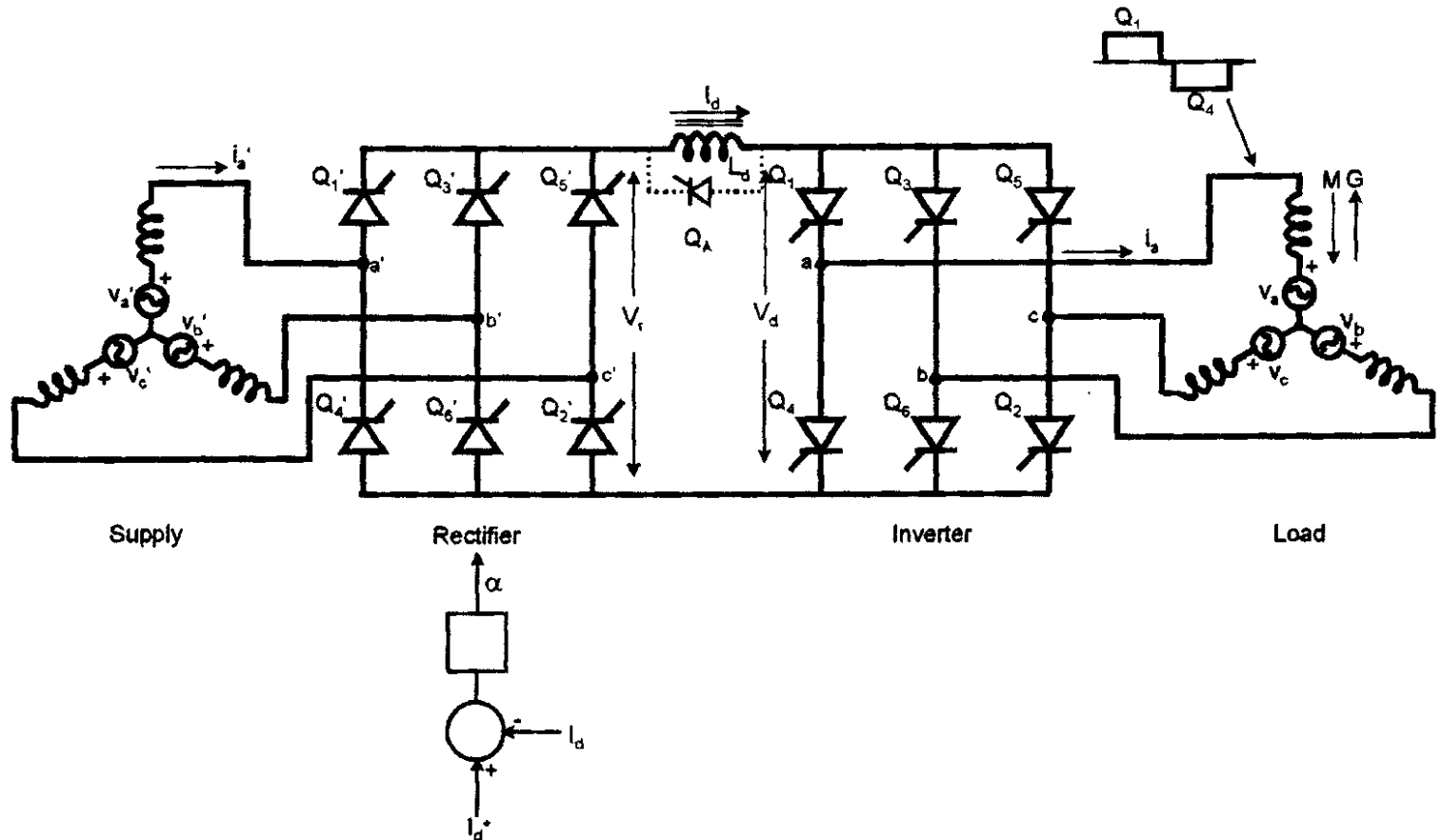


Figure 6.1 General power circuit of thyristor converter system

# General Operation of a 6-Step Thyristor Inverter (cont'd)

Initially, ignore commutation considerations.

Induction motor load is modeled by back emf generator and leakage inductance in each phase of the winding.

The constant dc current  $I_d$  is switched through the thyristors to create a  $3\Phi$  6-step symmetrical line current waves as shown on the next slide.

# General Operation of a 6-Step Thyristor Inverter (cont'd)

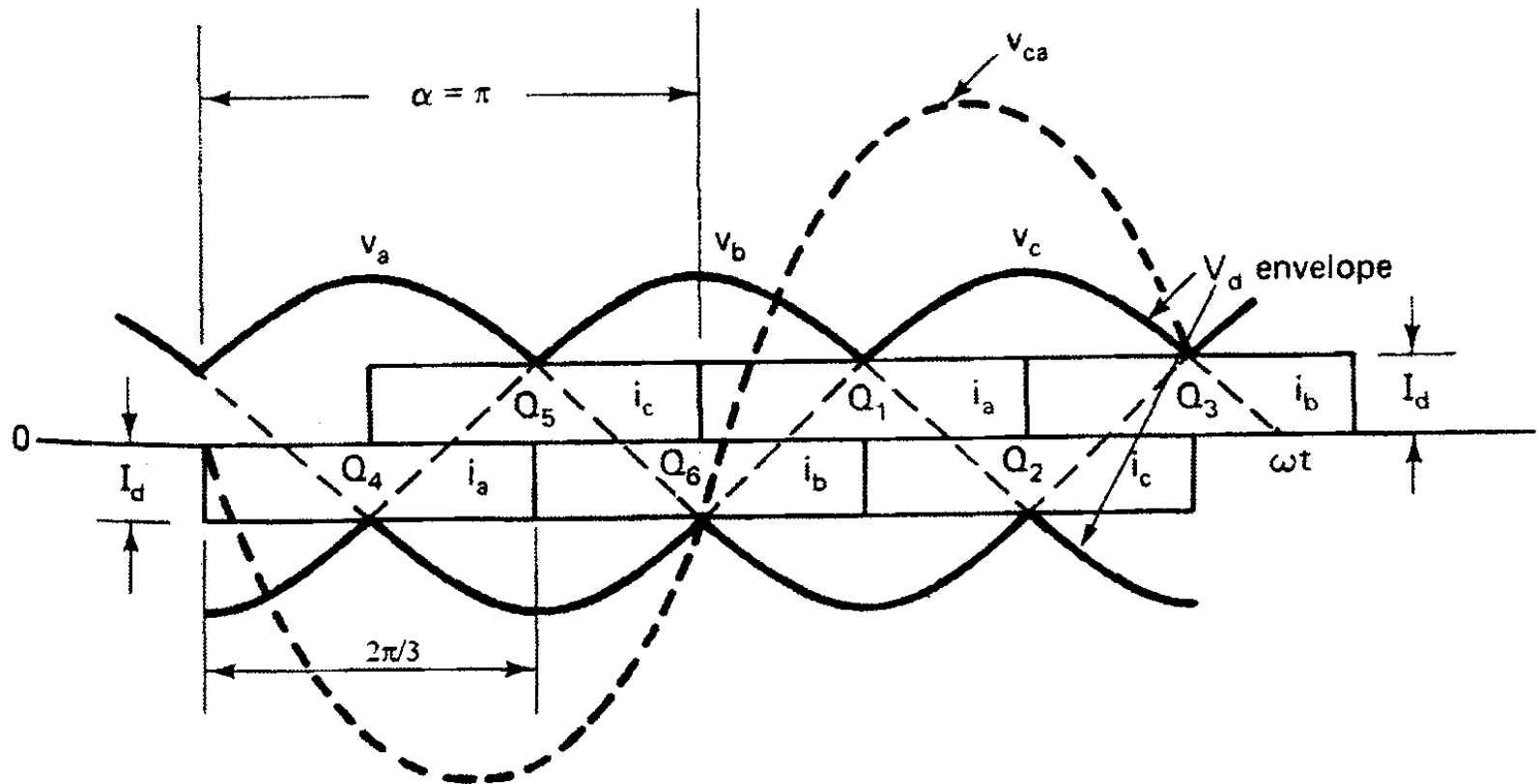


Figure 6.2 Idealized voltage and current waves of six-stepped thyristor inverter

# General Operation of a 6-Step Thyristor Inverter (cont'd)

The load or line current may be expressed by a Fourier series as:

$$i_a = \frac{2\sqrt{3}}{\pi} I_d \left[ \cos \omega t - \frac{1}{5} \cos 5\omega t + \frac{1}{7} \cos 7\omega t - \dots \right]$$

where the peak value of the fundamental component is given . Each thyristor conducts for radians. At any instant one upper thyristor and one lower thyristor conduct.

# General Operation of a 6-Step Thyristor Inverter (cont'd)

The dc link is considered harmonic-free and the commutation effect between thyristors is ignored.

At steady state the voltage output from the rectifier block = input voltage of inverter.

For a variable speed drive the inverter can be operated at variable frequency and variable dc current  $I_d$ .

# General Operation of a 6-Step Thyristor Inverter (cont'd)

If thyristor firing angle  $\alpha > 0$ , inverter behavior.

If thyristor firing angle  $\alpha=0$ , rectifier behavior.

Max. power transfer occurs when  $\alpha=\pi$ .

# NPTTEL LINK

- <https://www.youtube.com/watch?v=WMi-ZN3qtSs>