

# DC Choppers


# Introduction

- Chopper is a static device.
- A variable dc voltage is obtained from a constant dc voltage source.
- Also known as dc-to-dc converter.
- Widely used for motor control.
- Also used in regenerative braking.
- Thyristor converter offers greater efficiency, faster response, lower maintenance, smaller size and smooth control.



# Choppers are of Two Types

- Step-down choppers.
- Step-up choppers.
  - In step down chopper output voltage is less than input voltage.
  - In step up chopper output voltage is more than input voltage.

# Principle Of Step-down Chopper

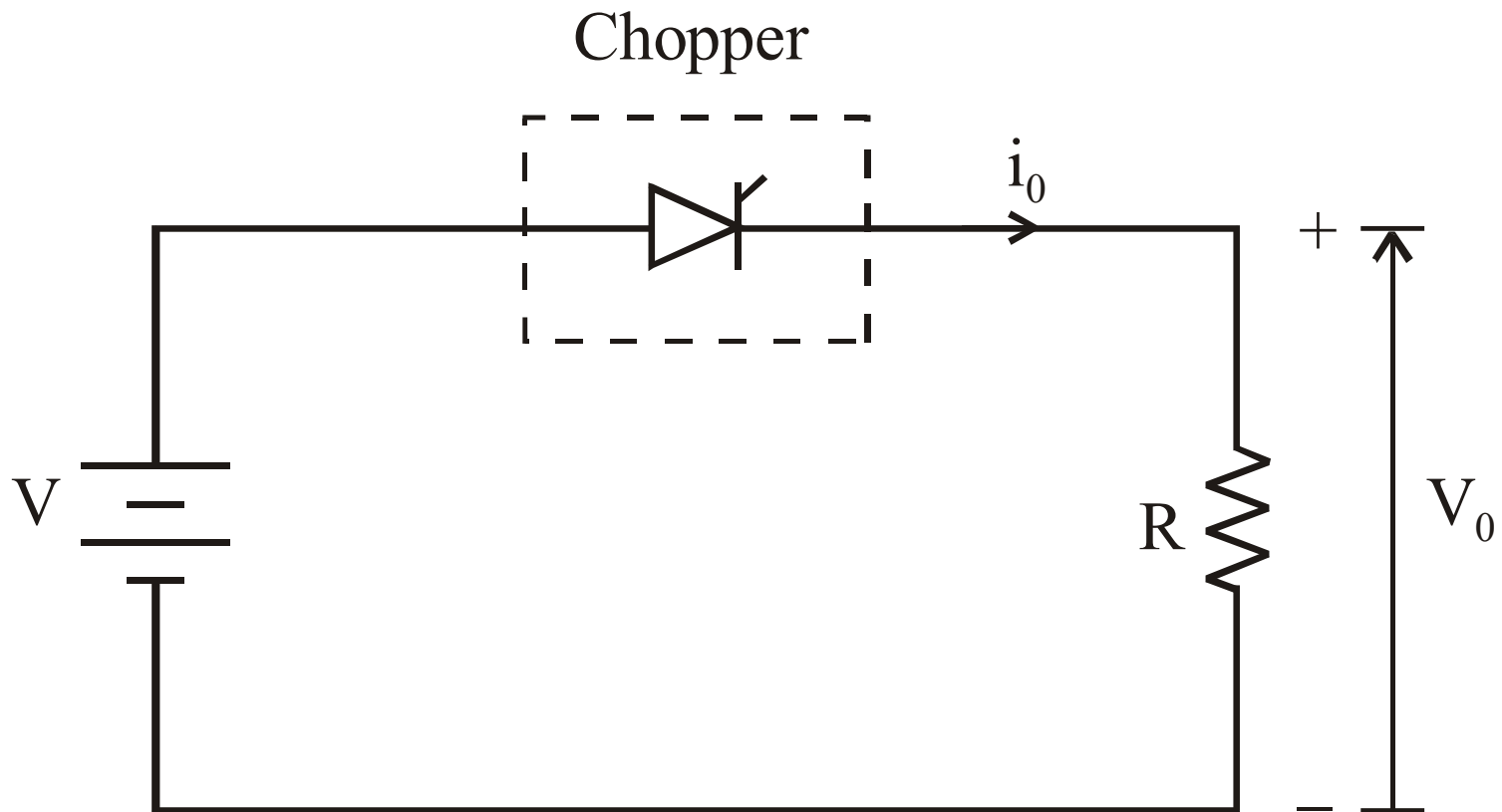

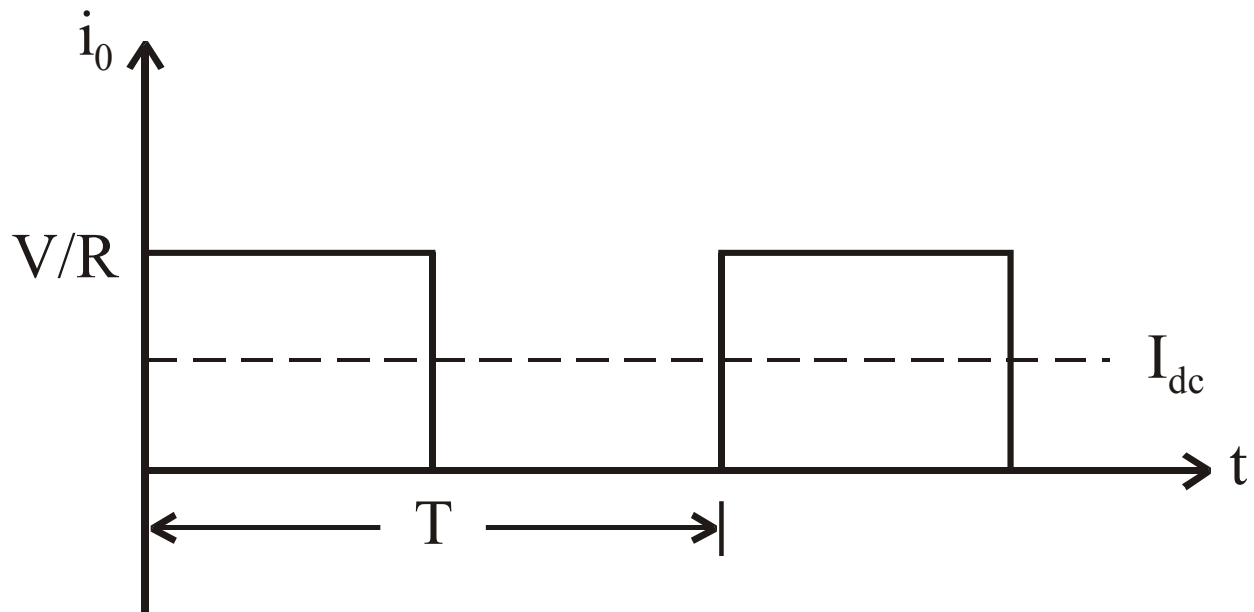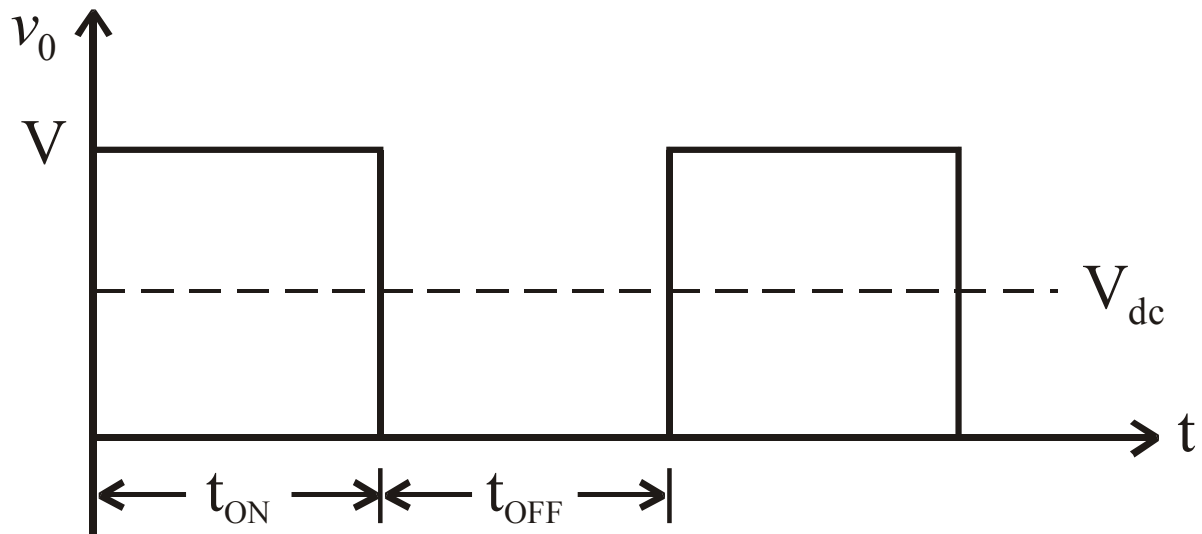- A step-down chopper with resistive load.
- The thyristor in the circuit acts as a switch.
- When thyristor is ON, supply voltage appears across the load
- When thyristor is OFF, the voltage across the load will be zero.



$V_{dc}$  = Average value of output or load voltage.

$I_{dc}$  = Average value of output or load current.

$t_{ON}$  = Time interval for which SCR conducts.

$t_{OFF}$  = Time interval for which SCR is OFF.

$T = t_{ON} + t_{OFF}$  = Period of switching or chopping period.

$f = \frac{1}{T}$  = Freq. of chopper switching or chopping freq.