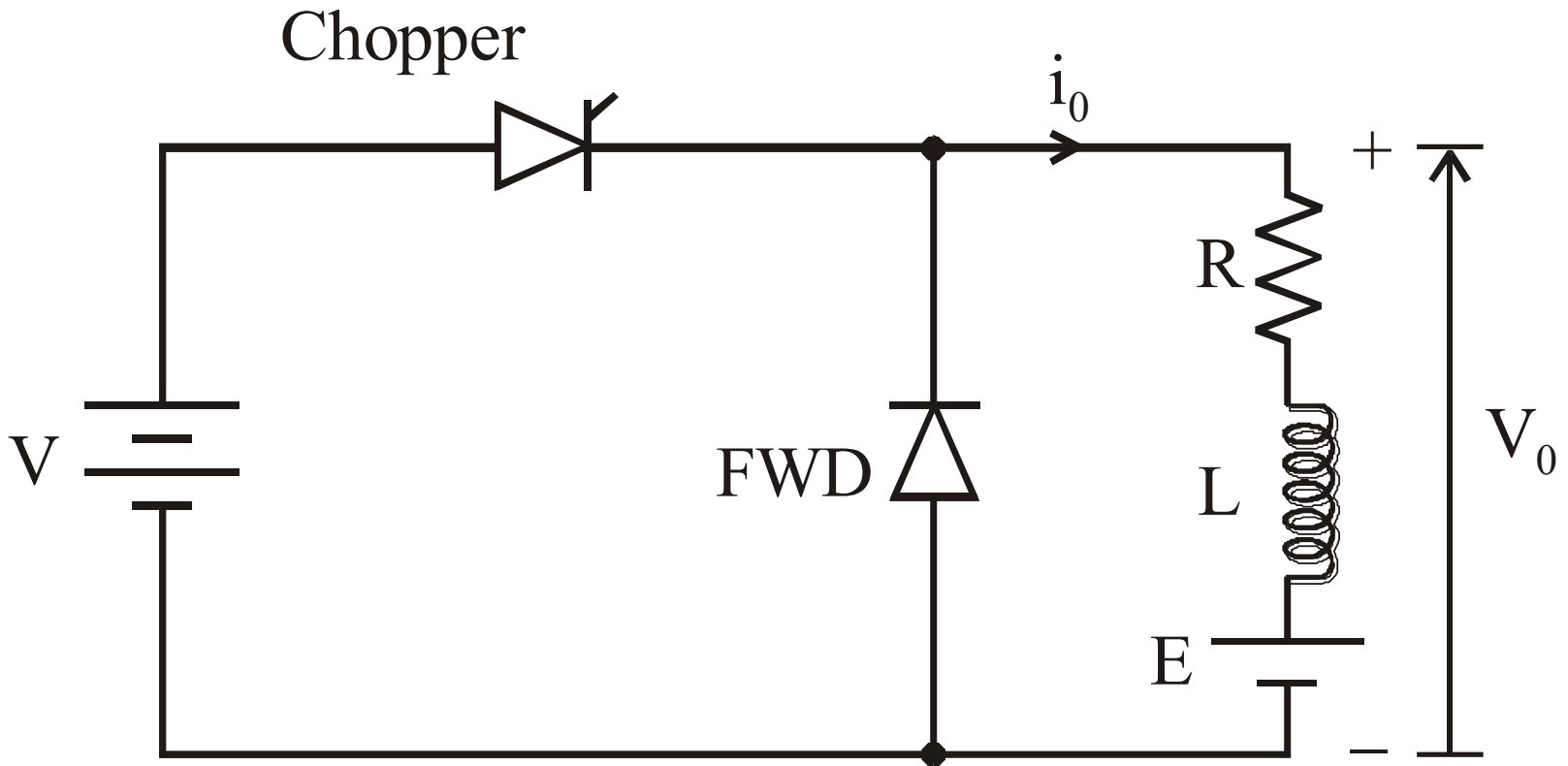



Methods Of Control

- The output dc voltage can be varied by the following methods.
 - Pulse width modulation control or constant frequency operation.
 - Variable frequency control.


Step-down Chopper With R-L Load



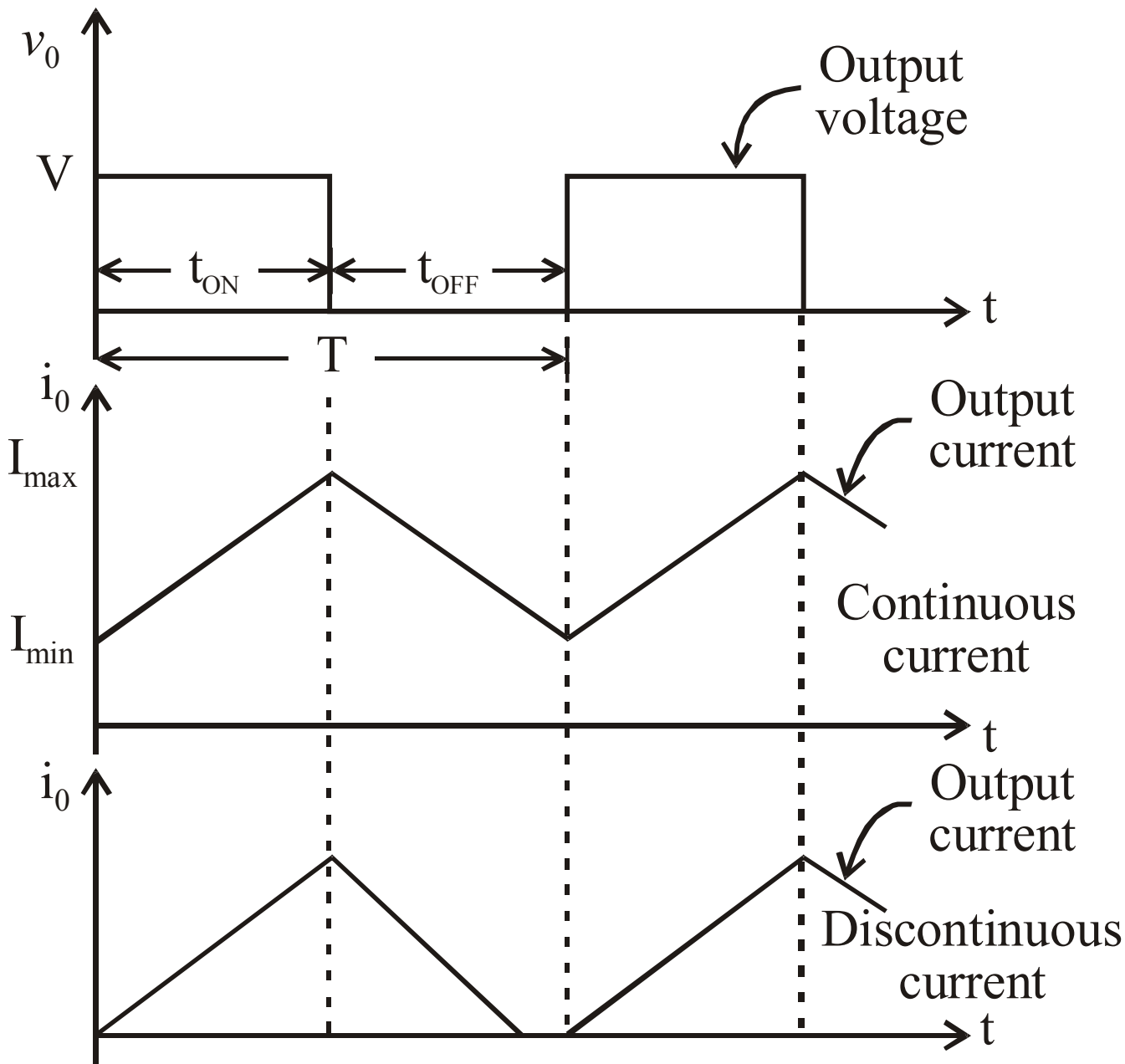- When chopper is ON, supply is connected across load.
- Current flows from supply to load.
- When chopper is OFF, load current continues to flow in the same direction through FWD due to energy stored in inductor ' L '.



Principle Of Step-up Chopper

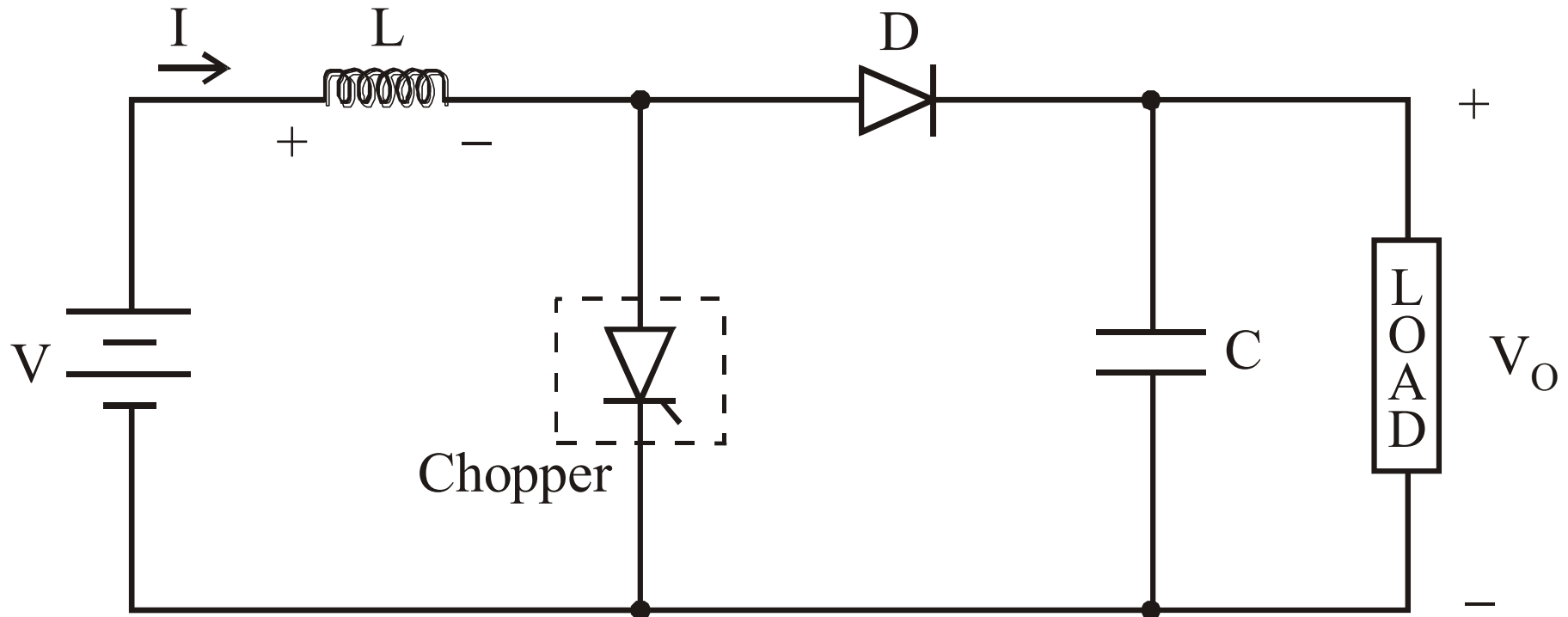

- Step-up chopper is used to obtain a load voltage higher than the input voltage V .
- The values of L and C are chosen depending upon the requirement of output voltage and current.
- When the chopper is ON , the inductor L is connected across the supply.
- The inductor current ' I ' rises and the inductor stores energy during the ON time of the chopper, t_{ON} .

- When the chopper is off, the inductor current I is forced to flow through the diode D and load for a period, t_{OFF} .
- The current tends to decrease resulting in reversing the polarity of induced EMF in L .
- Therefore voltage across load is given by

$$V_o = V + L \frac{dI}{dt} \quad i.e., \quad V_o > V$$

- A large capacitor 'C' connected across the load, will provide a continuous output voltage .
- Diode D prevents any current flow from capacitor to the source.
- Step up choppers are used for regenerative braking of dc motors.

Expression For Output Voltage

Assume the average inductor current to be I during ON and OFF time of Chopper.

When Chopper is ON

Voltage across inductor $L = V$

Therefore energy stored in inductor

$$= V \cdot I \cdot t_{ON}$$

Where t_{ON} = ON period of chopper.

When Chopper is OFF

(energy is supplied by inductor to load)

Voltage across $L = V_o - V$

Energy supplied by inductor $L = (V_o - V) I t_{OFF}$

where $t_{OFF} = OFF$ period of Chopper.

Neglecting losses, energy stored in inductor

$L =$ energy supplied by inductor L

$$\therefore VIt_{ON} = (V_o - V) It_{OFF}$$

$$V_o = \frac{V [t_{ON} + t_{OFF}]}{t_{OFF}}$$

$$V_o = V \left(\frac{T}{T - t_{ON}} \right)$$

Where

T = Chopping period or period
of switching.

$$T = t_{ON} + t_{OFF}$$

$$V_o = V \left(\frac{1}{1 - \frac{t_{ON}}{T}} \right)$$

$$\therefore V_o = V \left(\frac{1}{1 - d} \right)$$

Where $d = \frac{t_{ON}}{T} =$ duty cycle