

Inverter Operation Modes

Two inverter operation modes are established depending on the thyristor firing angle:

1) **Load-commutated** inverter

Applies when $\pi/2 < \alpha < \pi$.


2) **Force-commutated** inverter

Applies when $\pi < \alpha < 3\pi/2$.

Load-Commutated Inverter Mode

Consider $\alpha = 3\pi/4$. In this case $v_{ca} < 0 \Rightarrow$ thyristor Q_5 is turned off by the load. This requires load to operate at leading power factor \Rightarrow motoring mode of a synchronous machine operating in over-excitation.


$$V_d = -V_{d0} \cos \alpha$$

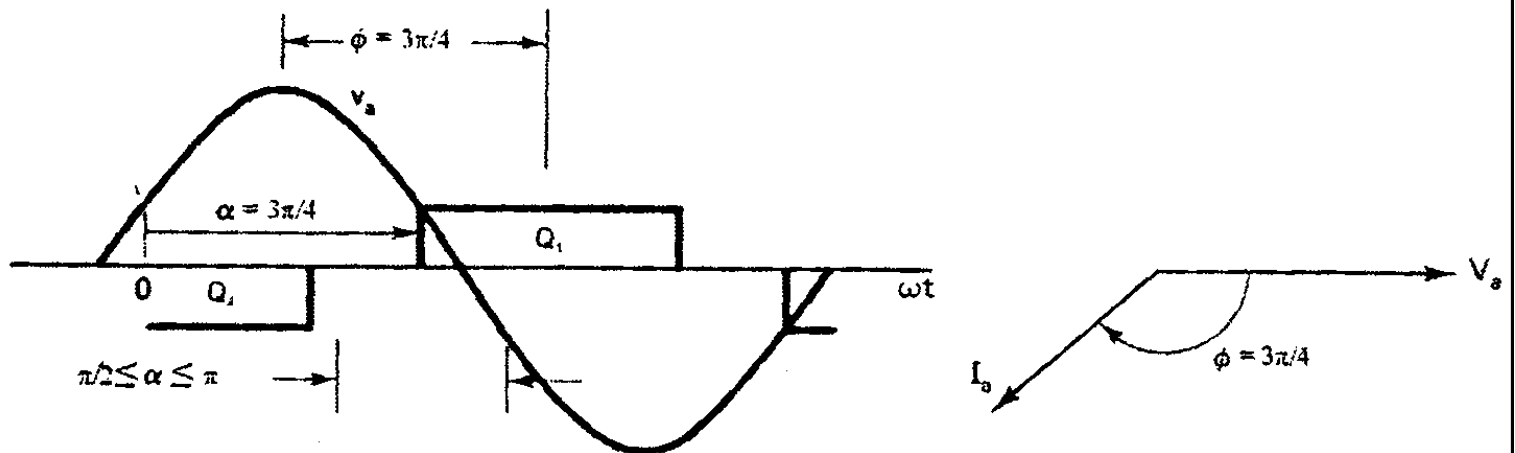

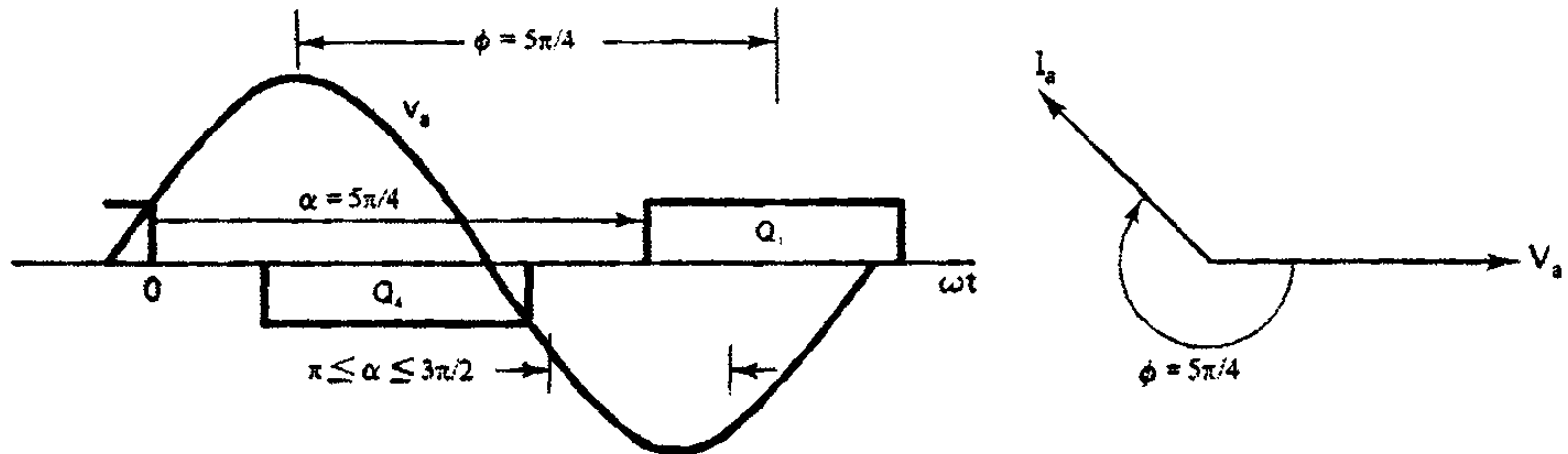(b) Mode 2: $\pi/2 \leq \alpha \leq \pi$

Force-Commutated Inverter Mode

Consider $\alpha = 5\pi/4$. In this case $v_{ca} > 0$ and so thyristor Q_5 is not turned off by the load. Thus some type of forced commutation is required in this case. Lagging VAR is consumed by the load \Rightarrow motoring mode of an induction motor. $V_d = -V_{d0} \cos\alpha$



(c) Mode 3: $\pi \leq \alpha \leq 3\pi/2$