
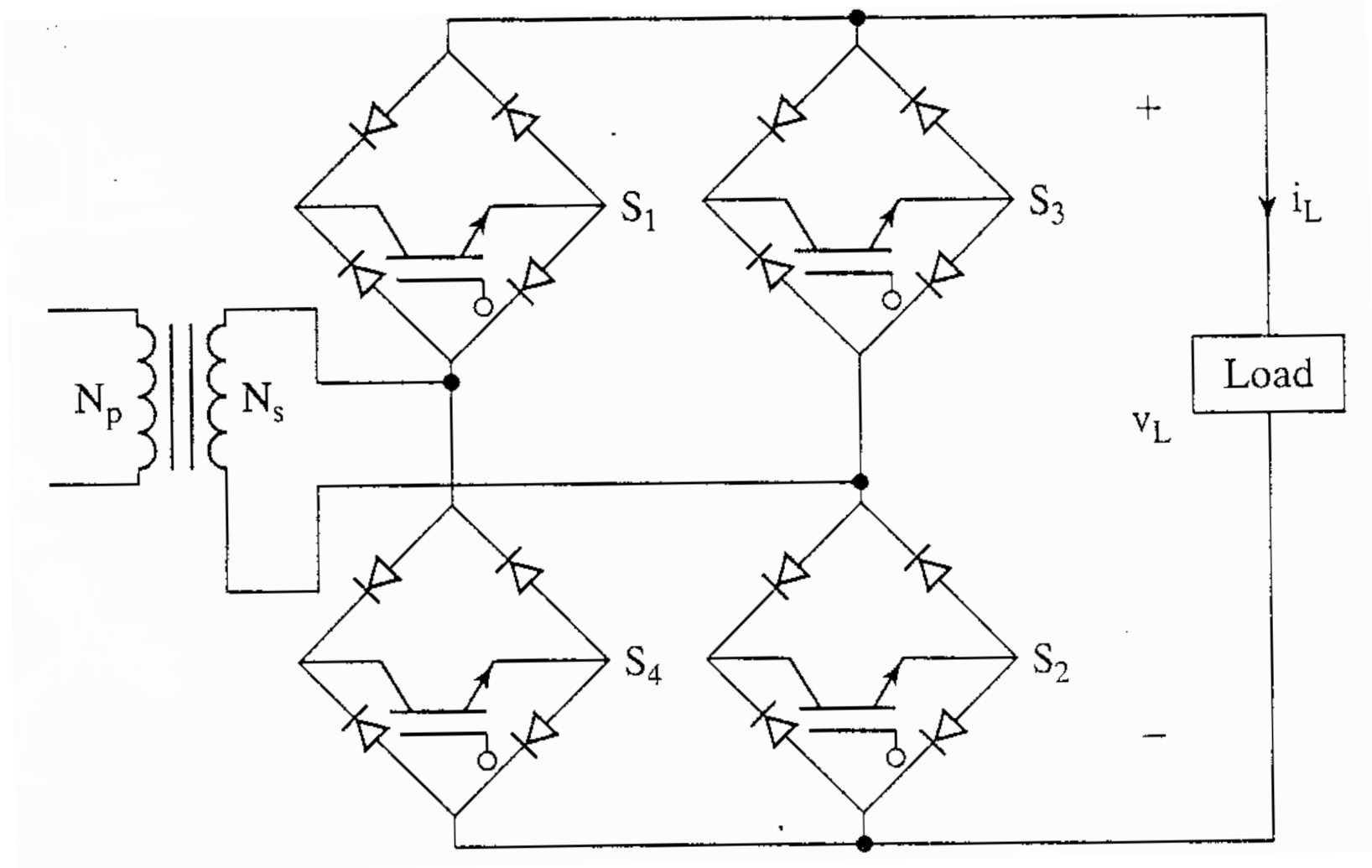



# Cycloconverter

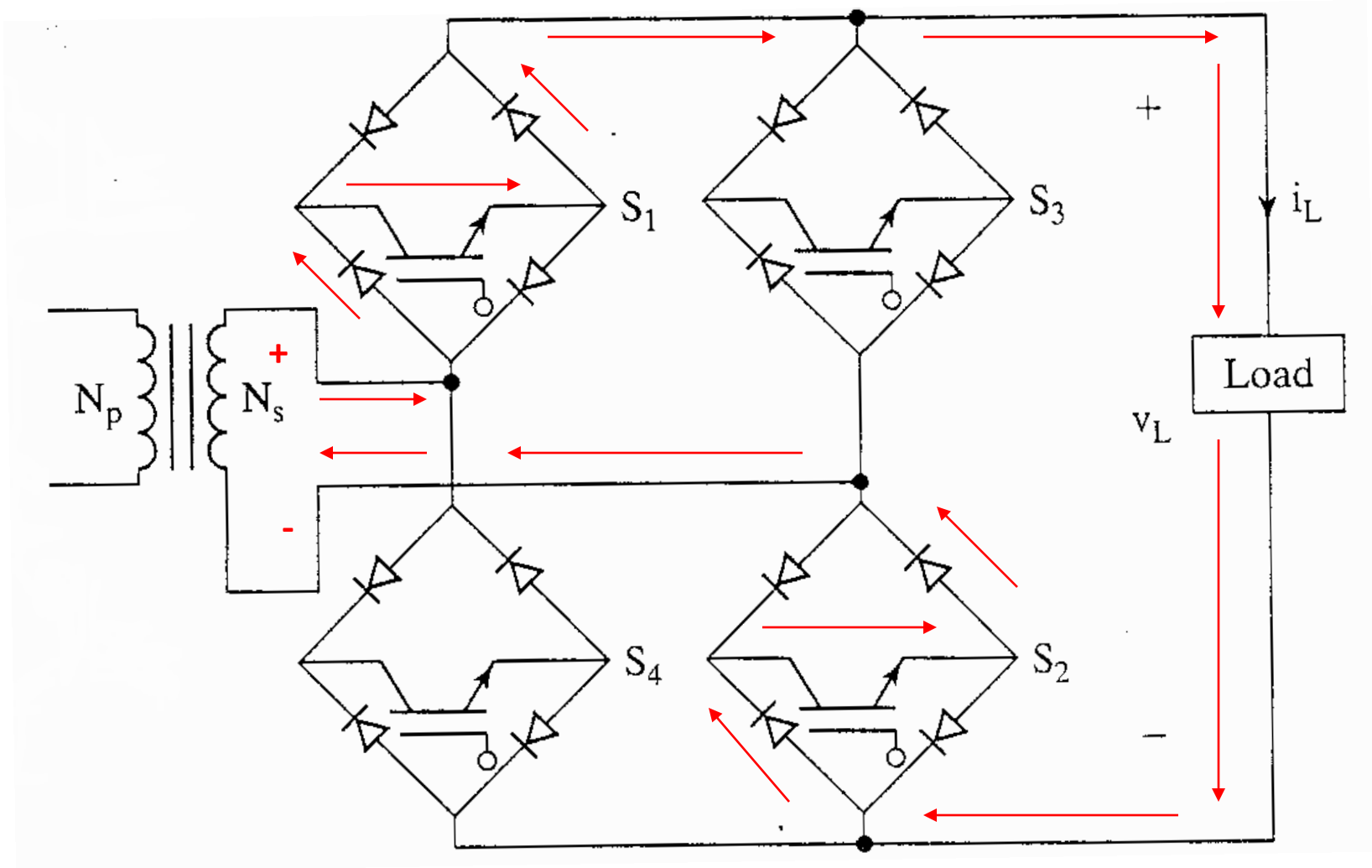


# Transformer Polarity as shown, $S_1$ and $S_2$ ON



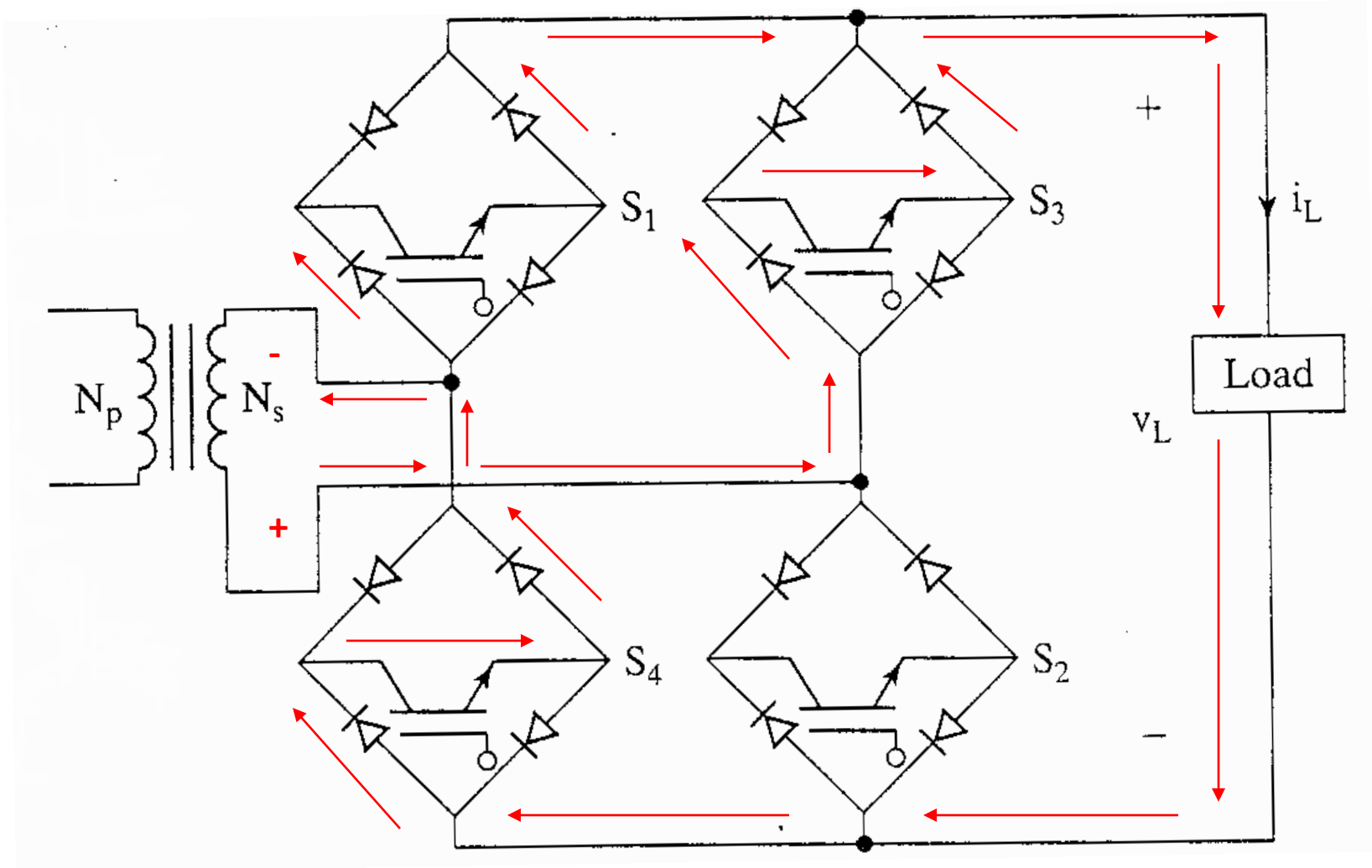
# Transformer Polarity as shown, $S_3$ and $S_4$ ON



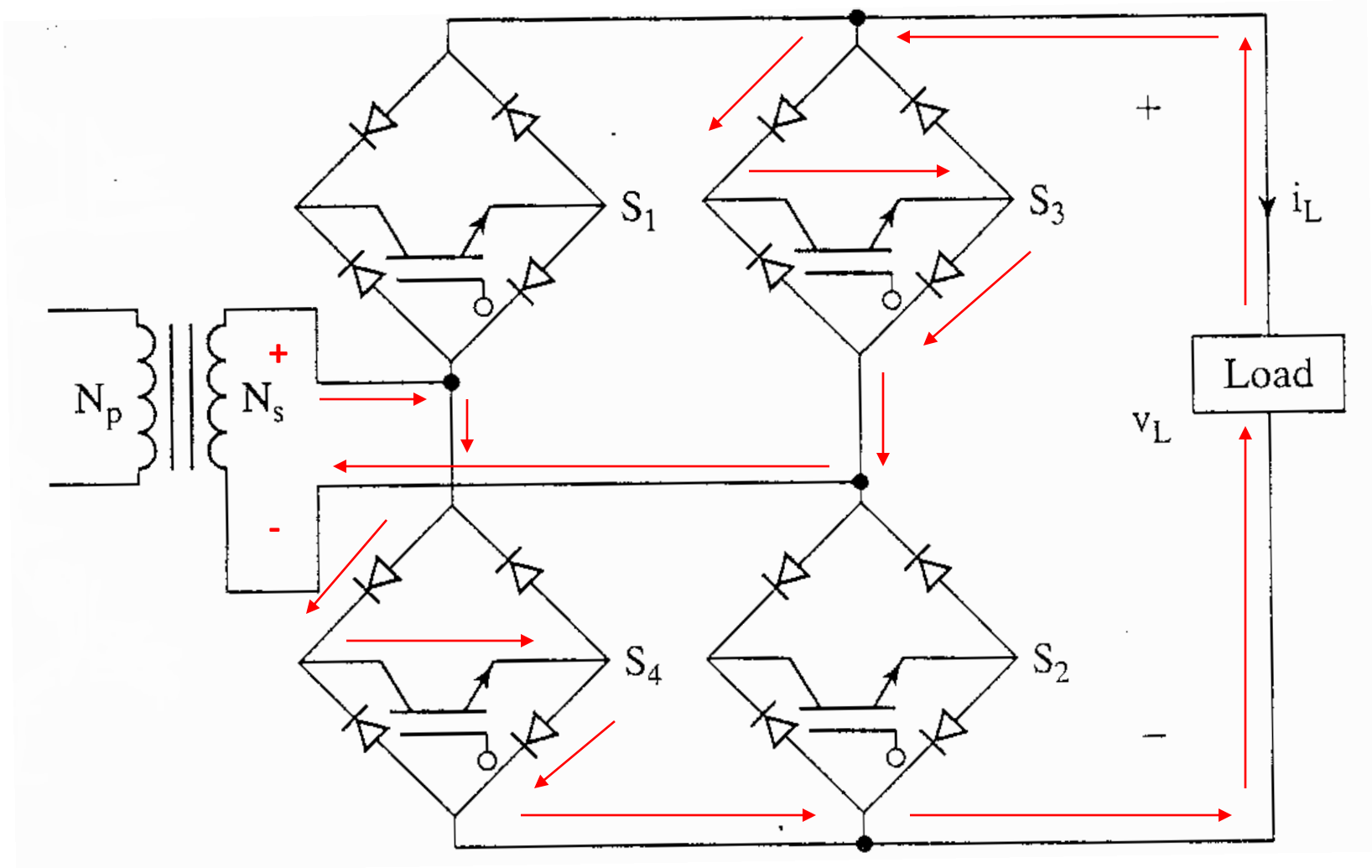
# Transformer Polarity as shown, $S_3$ and $S_4$ ON


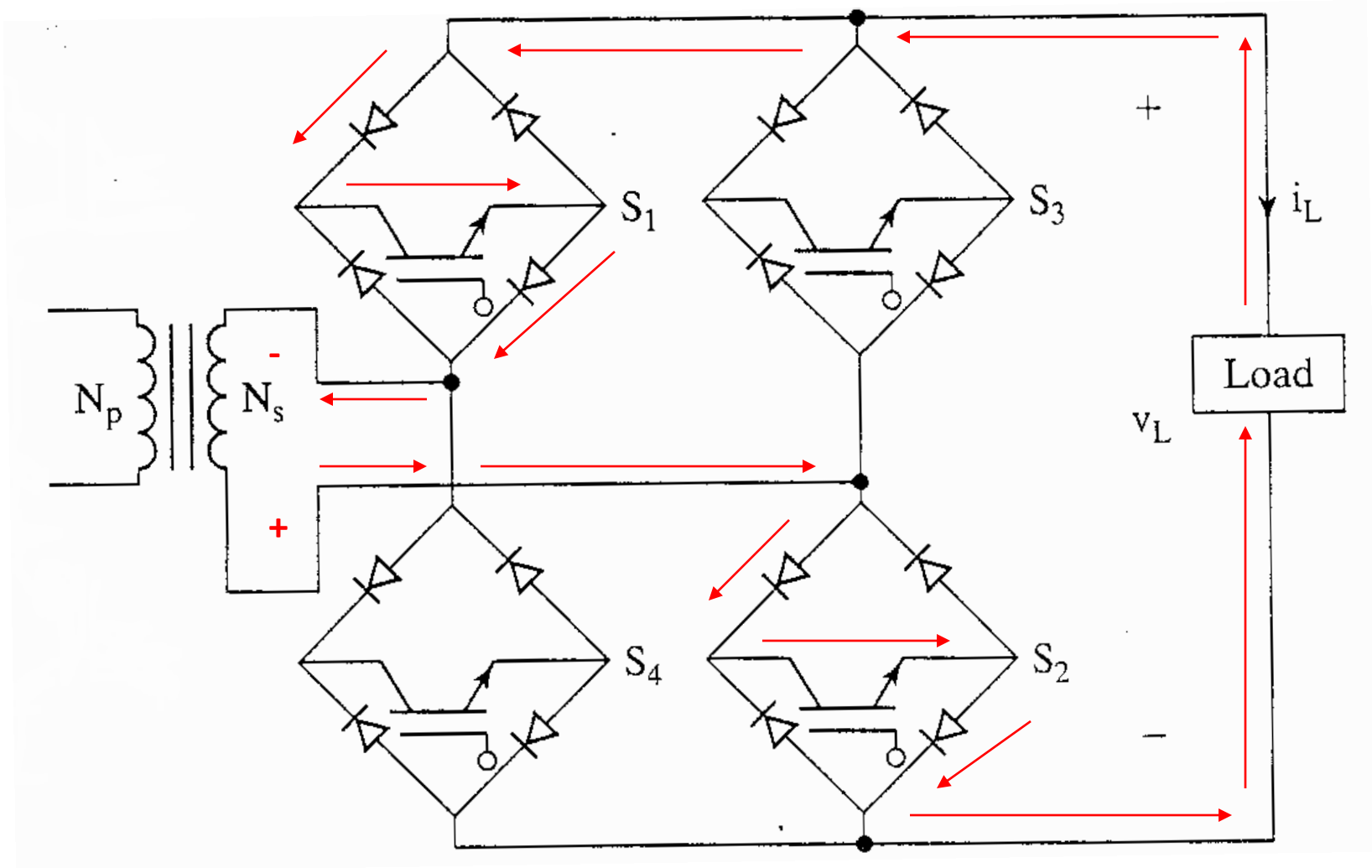
# Transformer Polarity as shown, $S_1$ and $S_2$ ON




# Look At The Voltages

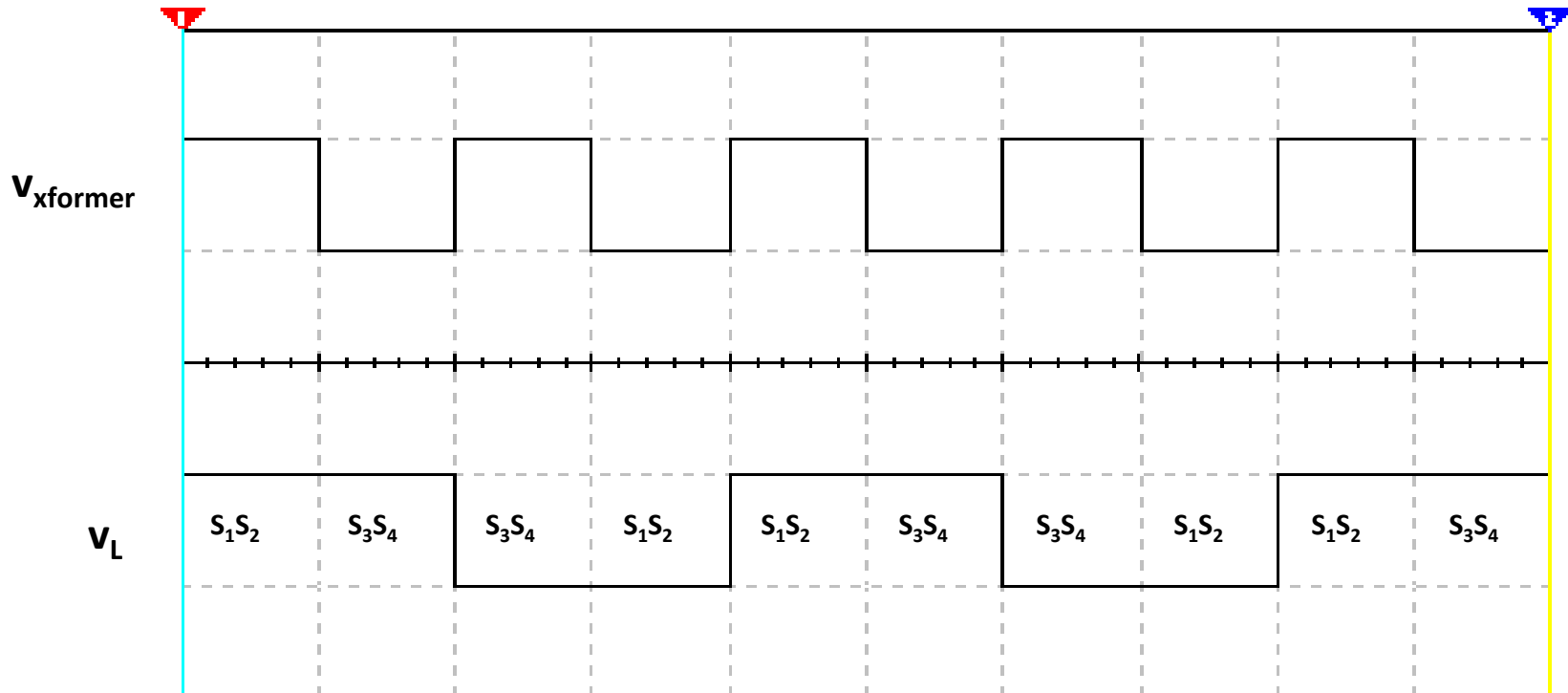


$v_L$  has a lower frequency than  $v_{x\text{former}}$

# Replace The Load With A Battery

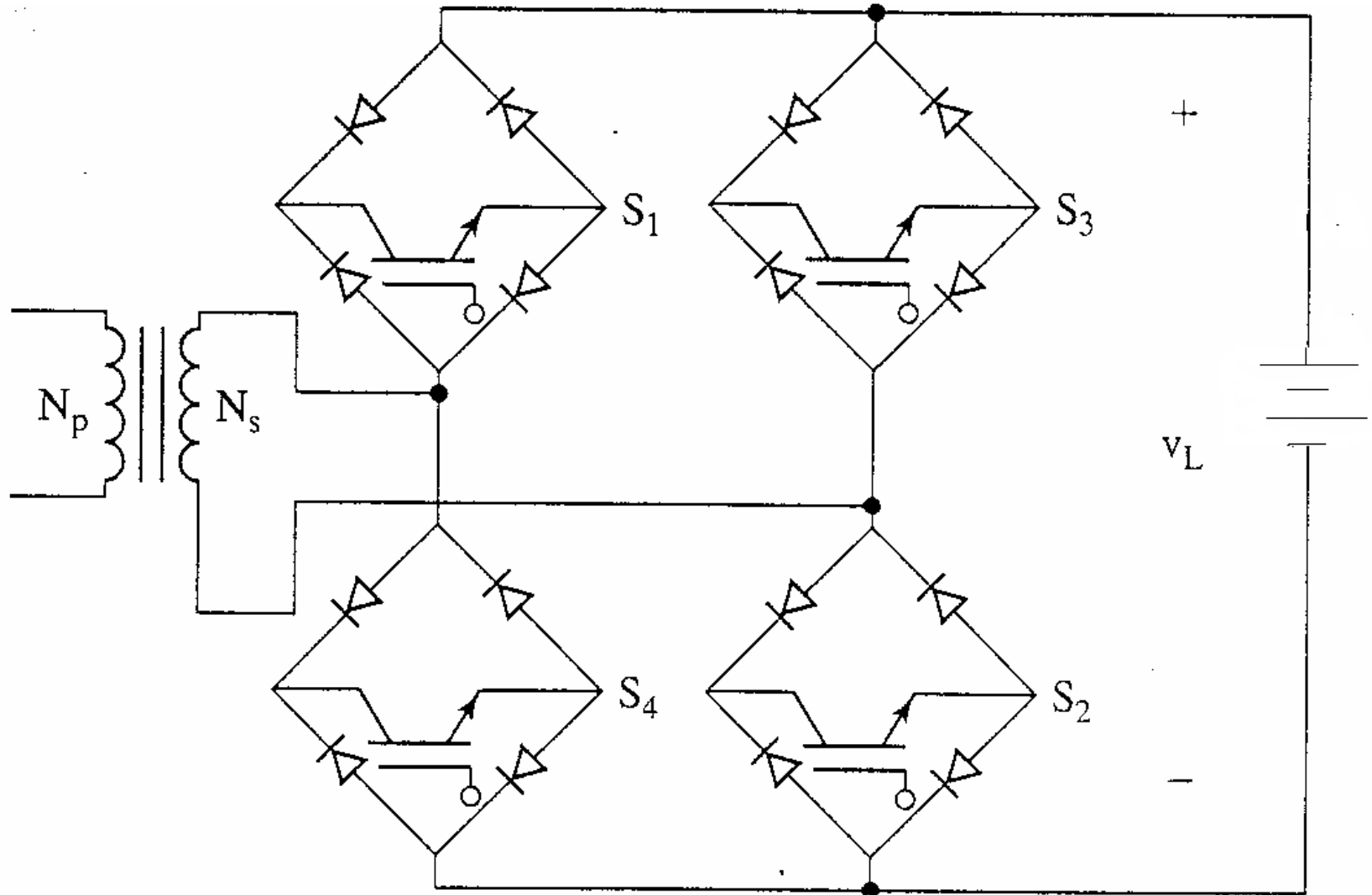


Turn  $S_1$  and  $S_2$  ON

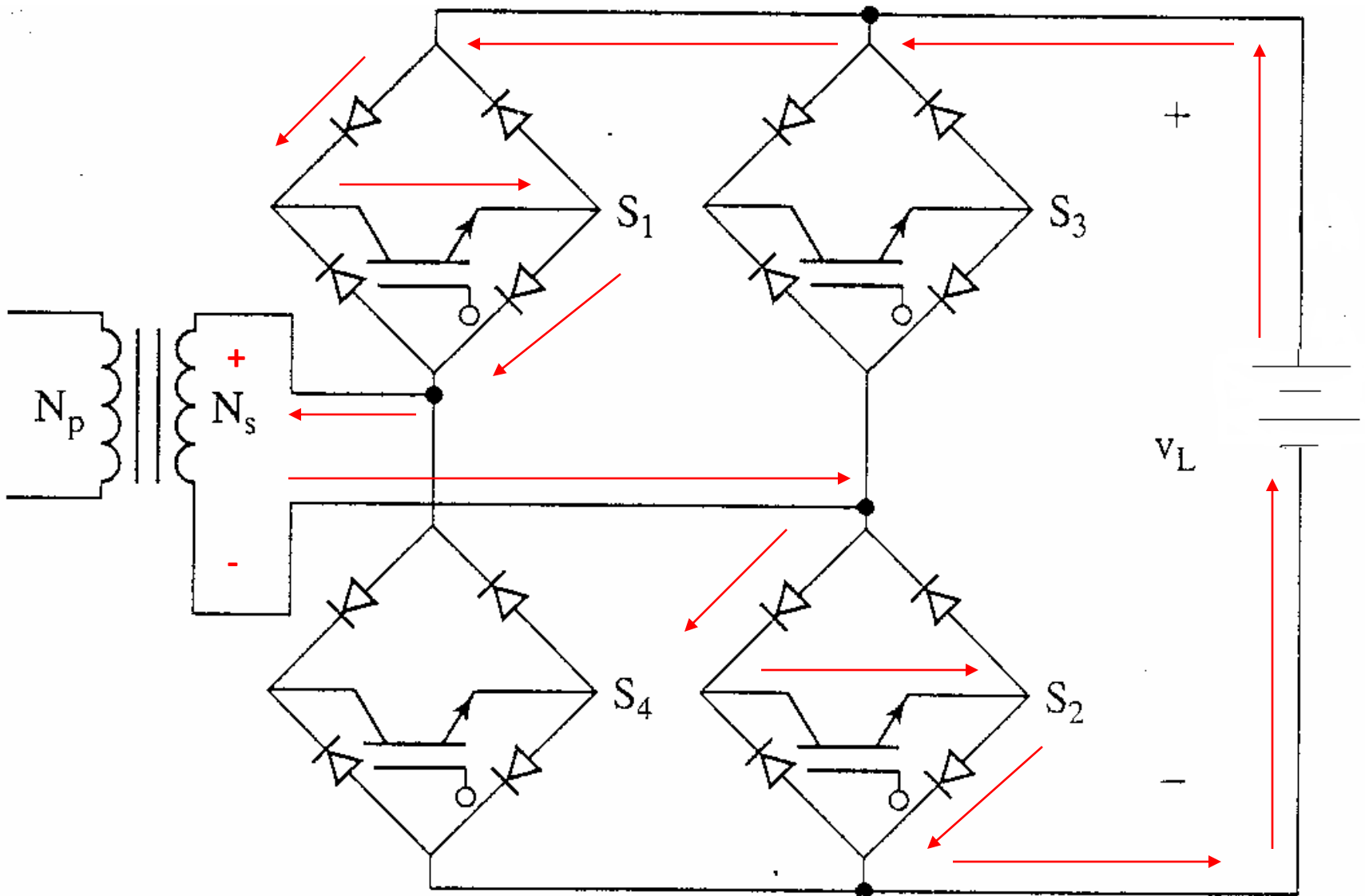



Turn  $S_3$  and  $S_4$  ON

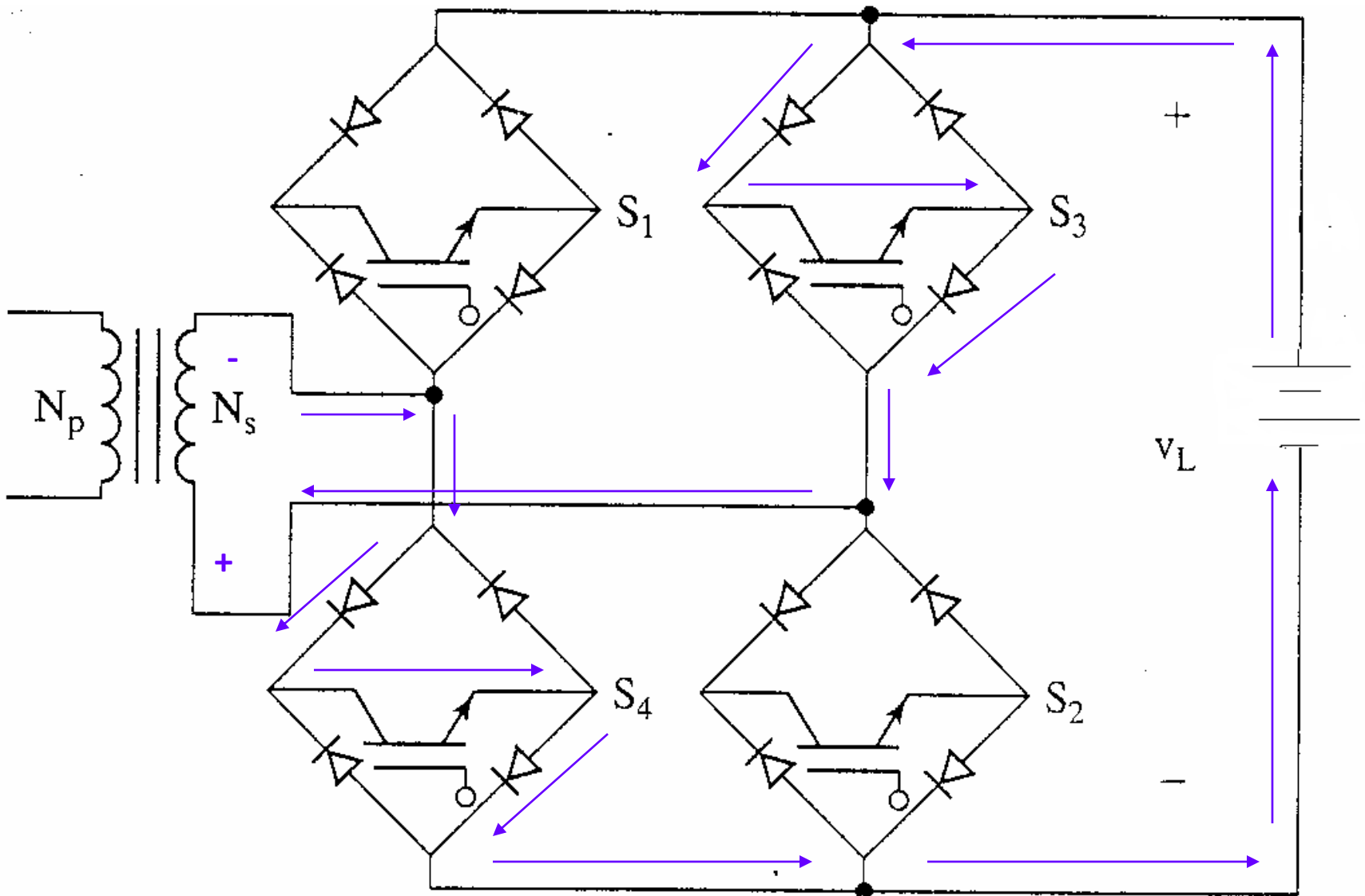

# LECTURE 29

# DC DRIVES

- DC DRIVES: Electric drives that use DC motors as the prime movers
- DC motor: industry workhorse for decades
- Dominates variable speed applications before PE converters were introduced
- Will AC drive replaces DC drive ?
  - Predicted 30 years ago
  - DC strong presence – easy control – huge numbers
  - AC will eventually replace DC – at a slow rate

## DC Motors

- Advantage: simple torque and speed control without sophisticated electronics
- Limitations:
  - Regular Maintenance
  - Expensive motor
  - Heavy motor
  - Sparking

# General Torque Equation

Translational (linear) motion:

$$F = M \frac{dv}{dt}$$

F : Force (Nm)

M : Mass (Kg )

v : velocity (m/s)

Rotational motion:

$$T = J \frac{d\omega}{dt}$$

T : Torque (Nm)

J : Moment of Inertia (Kgm<sup>2</sup> )

$\omega$  : angular velocity ( rad/s )

# Torque Equation: Motor drives

$$T_e = T_L + J \frac{d\omega}{dt} \quad \text{or} \quad T_e - T_L = J \frac{d\omega}{dt}$$

$T_e$  : motor torque (Nm)       $T_L$  : Load torque (Nm)

$$T_e - T_L > 0 \quad \text{Acceleration}$$

$$T_e - T_L < 0 \quad \text{Deceleration}$$

$$T_e - T_L = 0 \quad \text{Constant speed}$$


# ...continue

Drive accelerates or decelerates depending on whether  $T_e$  is greater or less than  $T_L$

During acceleration, motor must supply not only the load torque but also dynamic torque,  $( Jd\omega/dt )$ .

During deceleration, the dynamic torque,  $( Jd\omega/dt )$ , has a negative sign. Therefore, it assists the motor torque,  $T_e$ .

# Torque Equation: Graphical

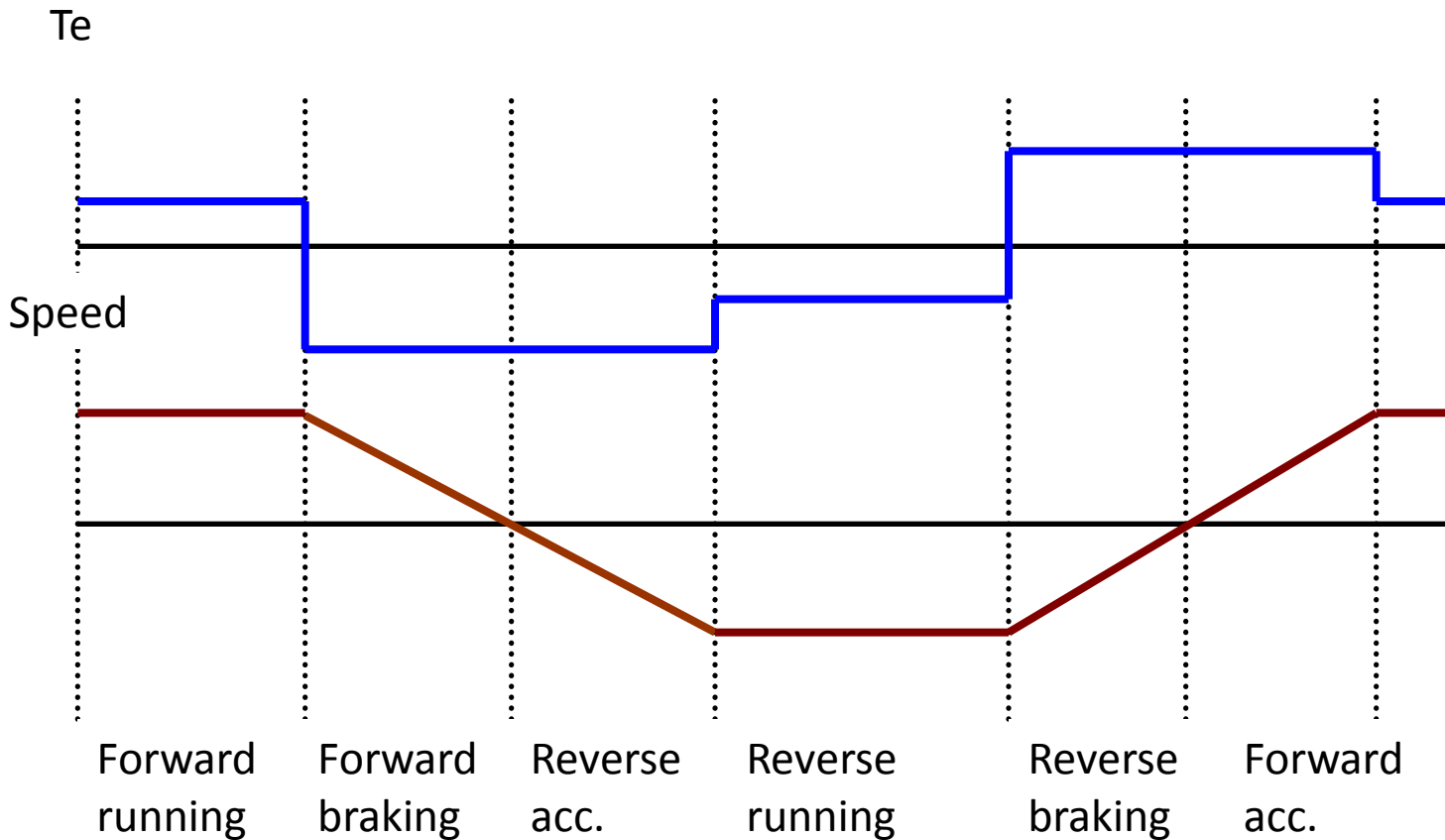




# Load Torque

Load torque,  $T_L$ , is complex, depending on applications.

In general:

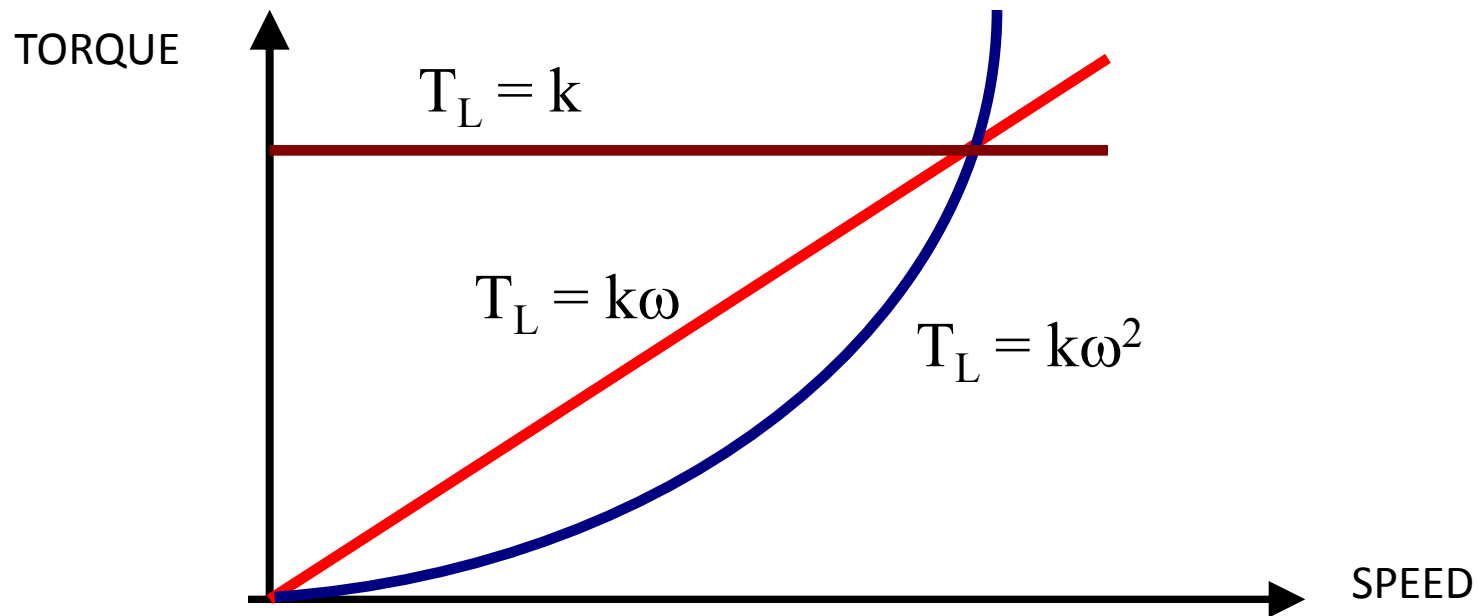

# DC MOTOR DRIVES

Principle of operation

Torque-speed characteristic

Methods of speed control

Armature voltage control

Variable voltage source

Phase-controlled Rectifier

Switch-mode converter (Chopper)

1Q-Converter

2Q-Converter


4Q-Converter

# Principle of Operation

## DC Motors

Stator: field windings


Rotor: armature windings

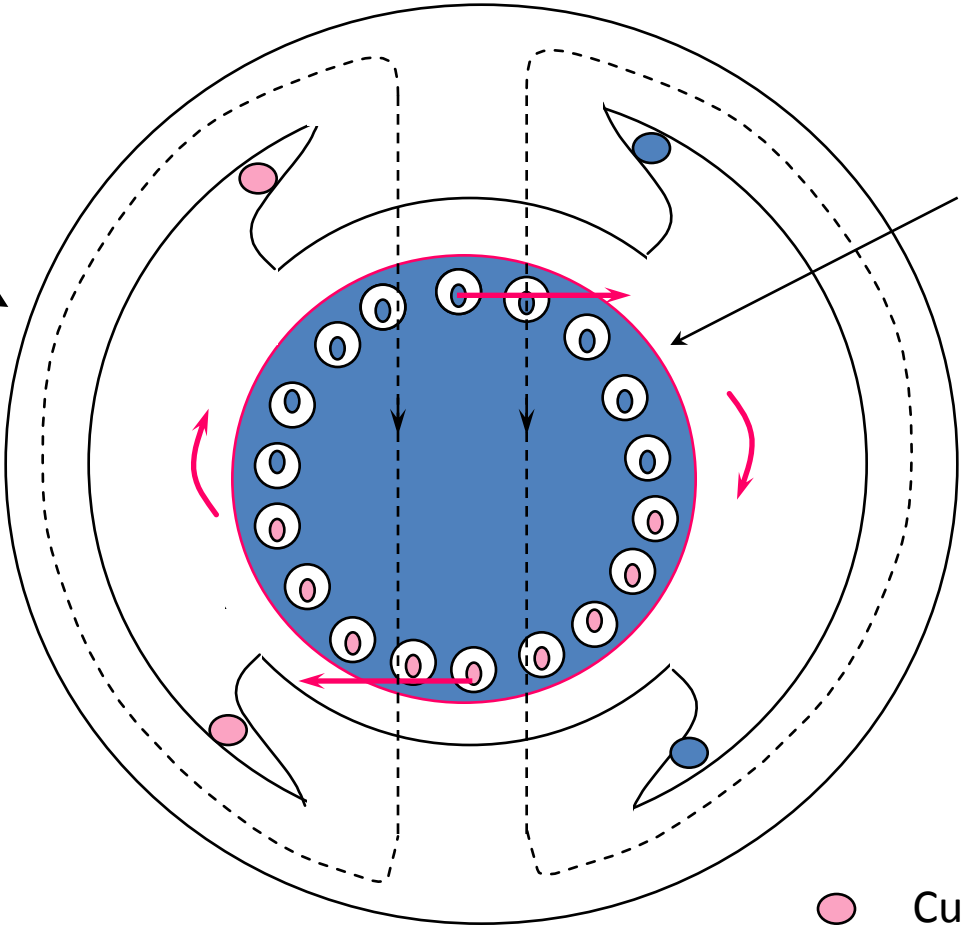

● Current in

● Current out

## Equivalent circuit of DC motor

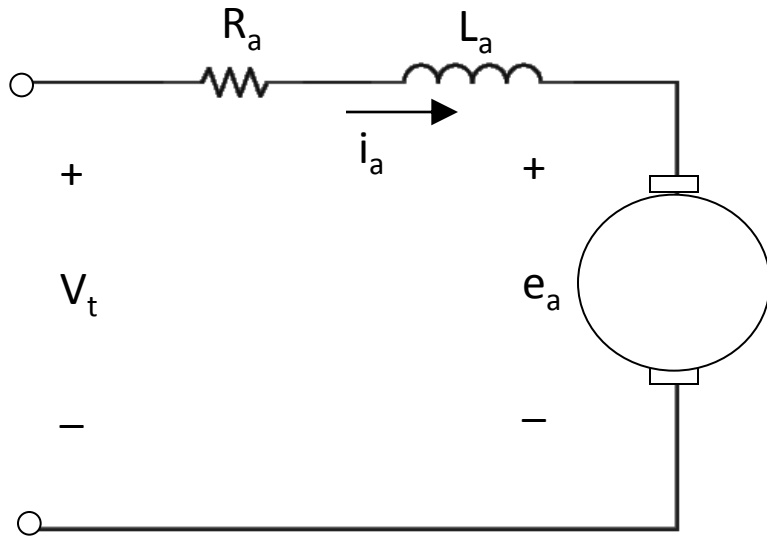


$$v_t = R_a i_a + L \frac{di_a}{dt} + e_a$$

$$T_e = k_t \phi i_a$$

Electromagnetic torque

$$e_a = k_E \phi \omega$$

Armature back e.m.f.

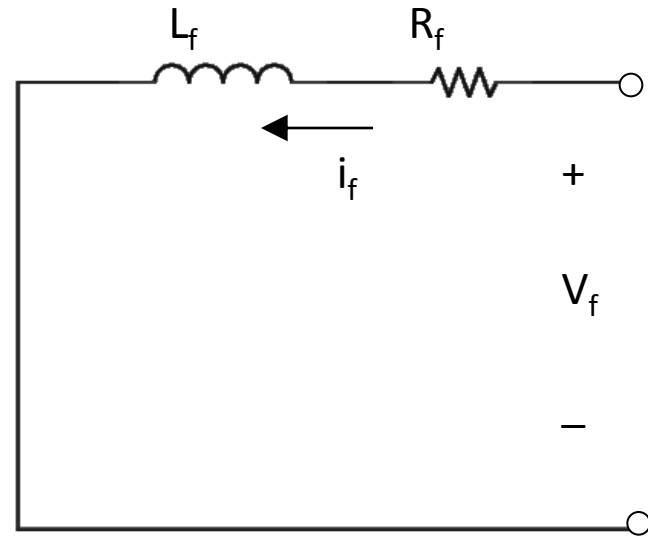

$$v_f = R_f i_f + L \frac{di_f}{dt}$$

# NPTTEL LINK

- <https://www.youtube.com/watch?v=1Auay7ja2oY&list=PL3A9EE4428285E166>