

Torque-speed characteristics

Armature circuit:

$$V_a = R_a i_a + L \frac{di_a}{dt} + e_a$$

In steady state,

$$V_a = R_a I_a + E_a$$

Therefore speed is given by,

$$\omega = -\frac{R_a}{(k_T \phi)^2} T_e + \frac{V_a}{k_T \phi}$$


Three possible methods of speed control:

Armature resistance R_a

Field flux Φ

Armature voltage V_a


Torque-speed characteristics of DC motor

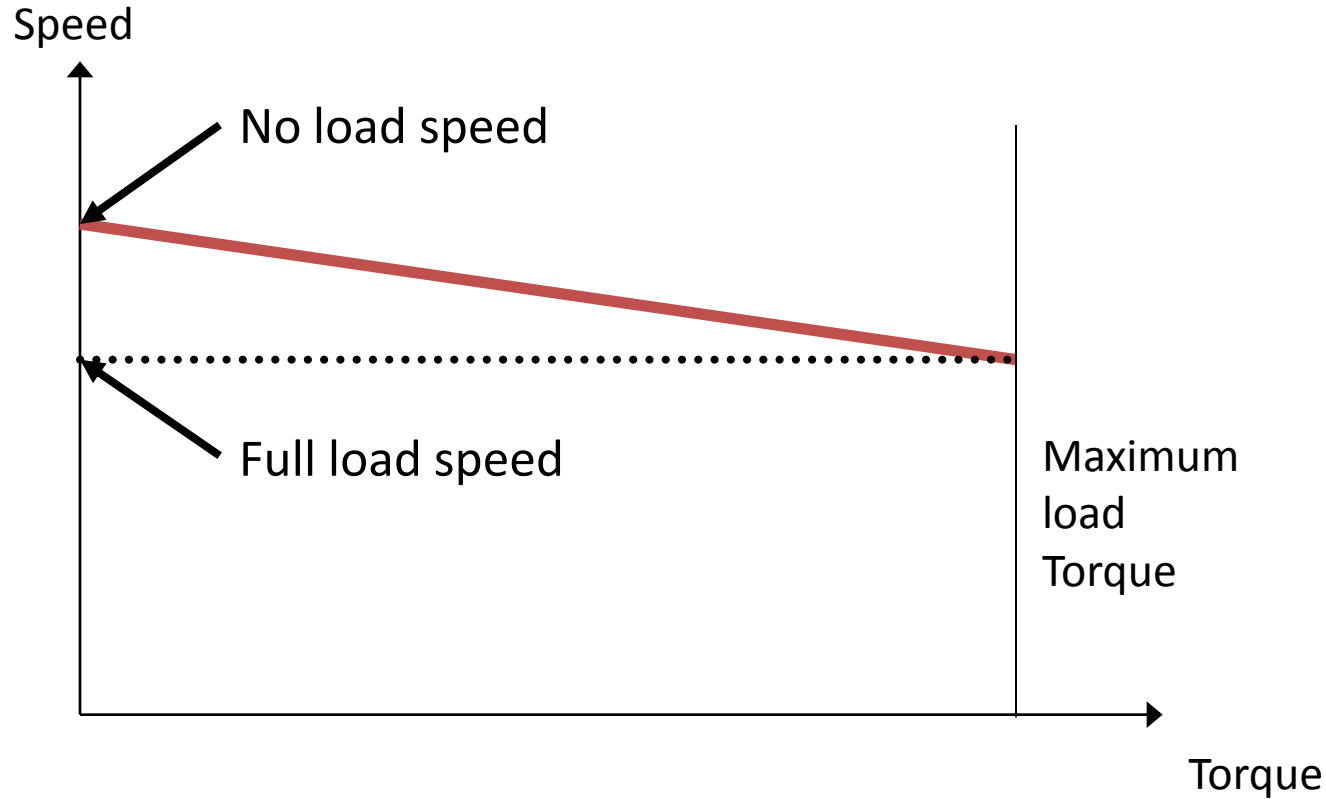

Separately excited DC motors have good speed regulation.

DC Motor Speed Control


By Changing R_a

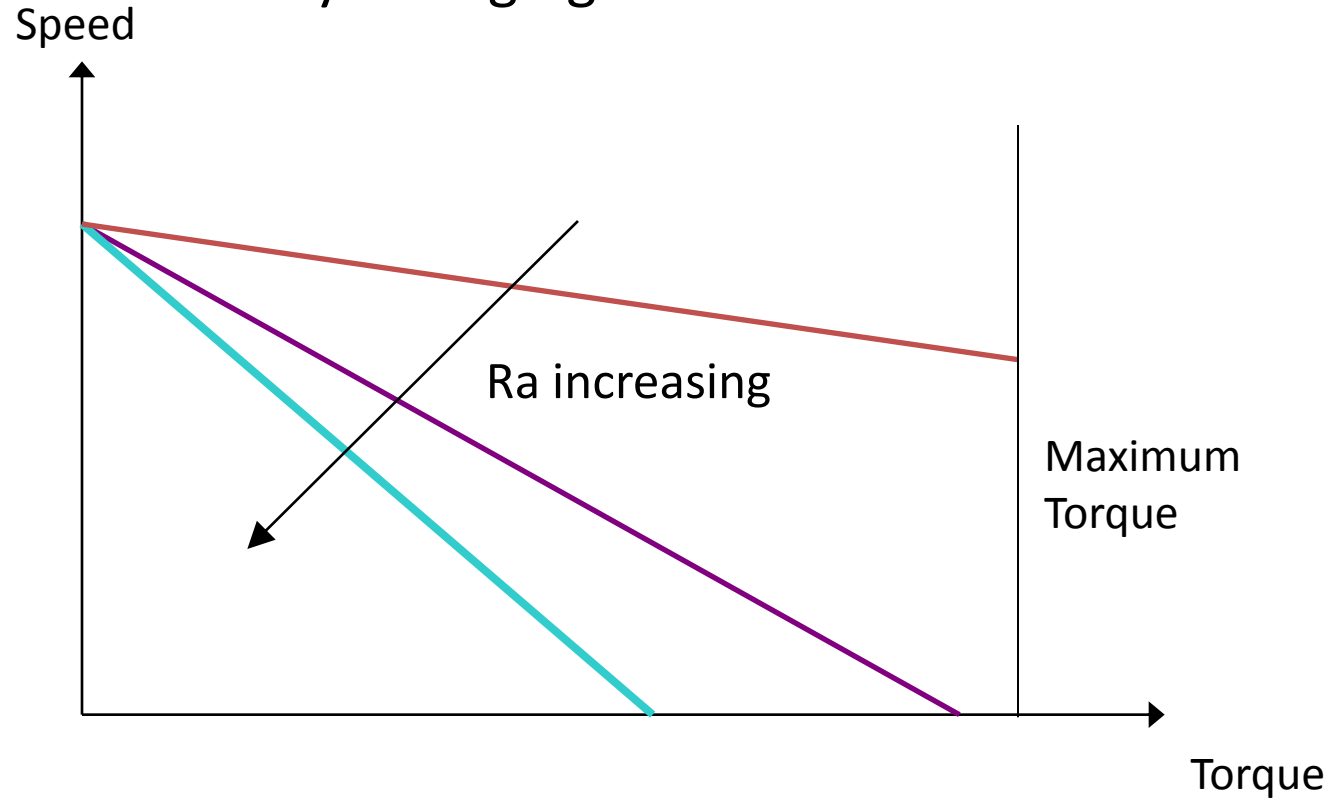

- Power loss in R_a
- Does not maintain maximum torque capability
- Poor speed regulation

DC Motor Speed Control


By Decreasing Flux

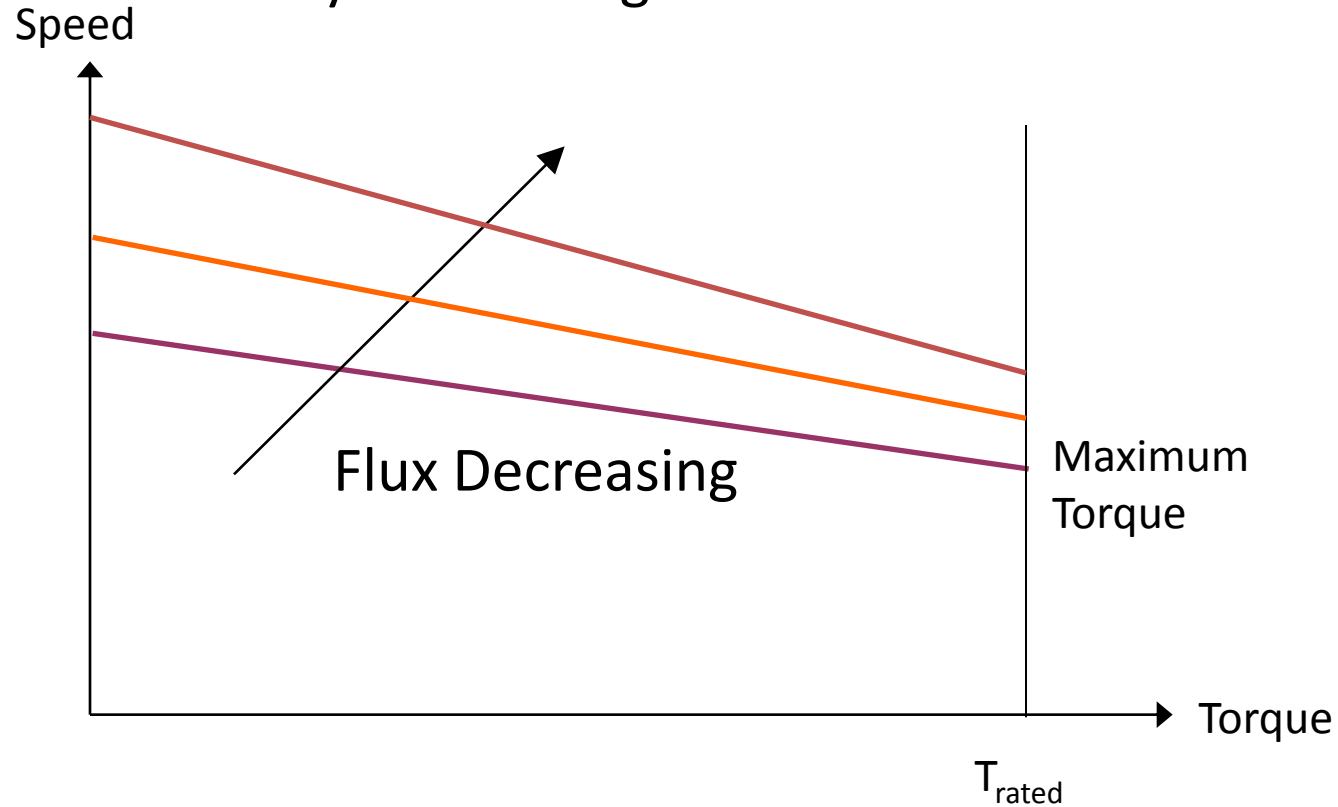

- Slow transient response
- Does not maintain maximum torque capability

DC Motor Speed Control

By Changing Armature voltage

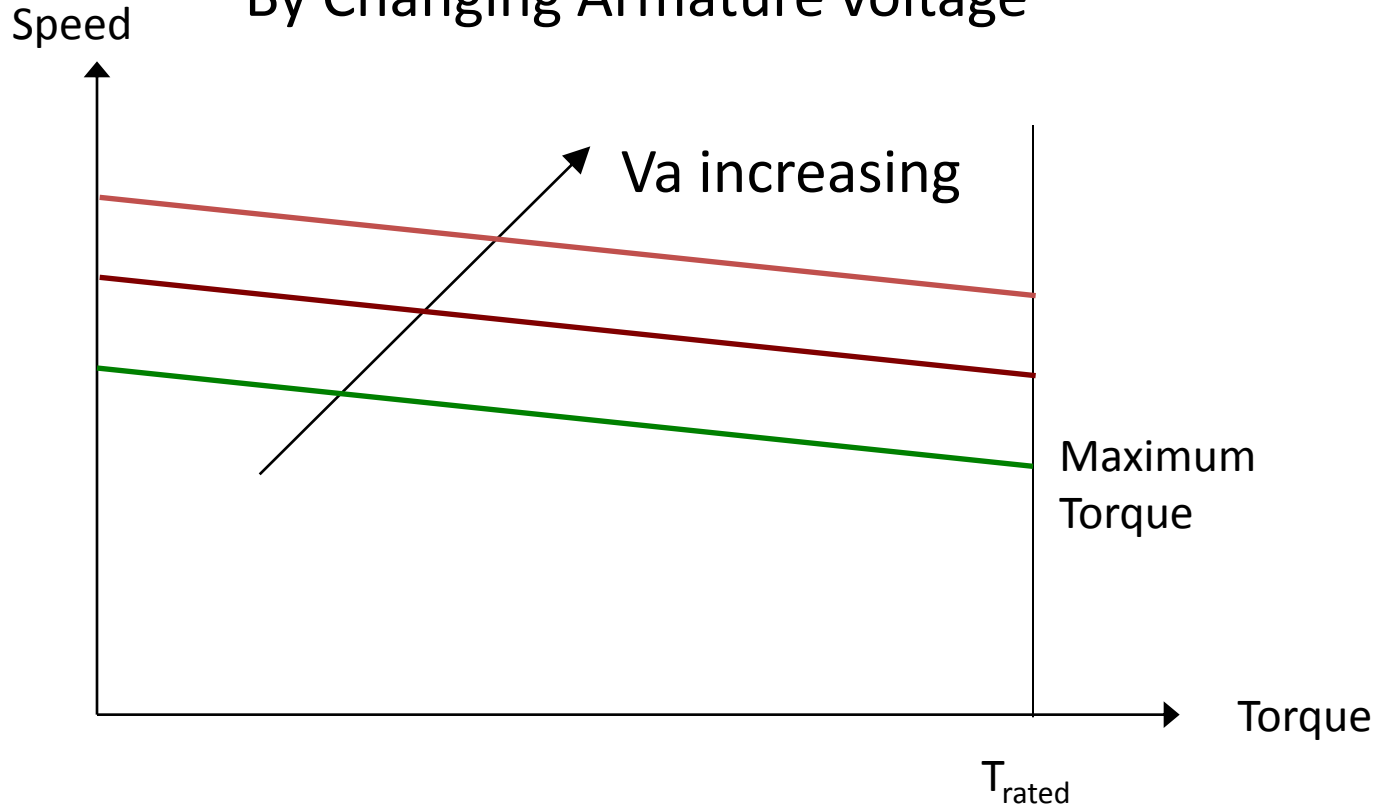


- good speed regulation
- maintain maximum torque capability

Speed control of DC Motors

Below base speed: Armature voltage control (retain maximum torque capability)

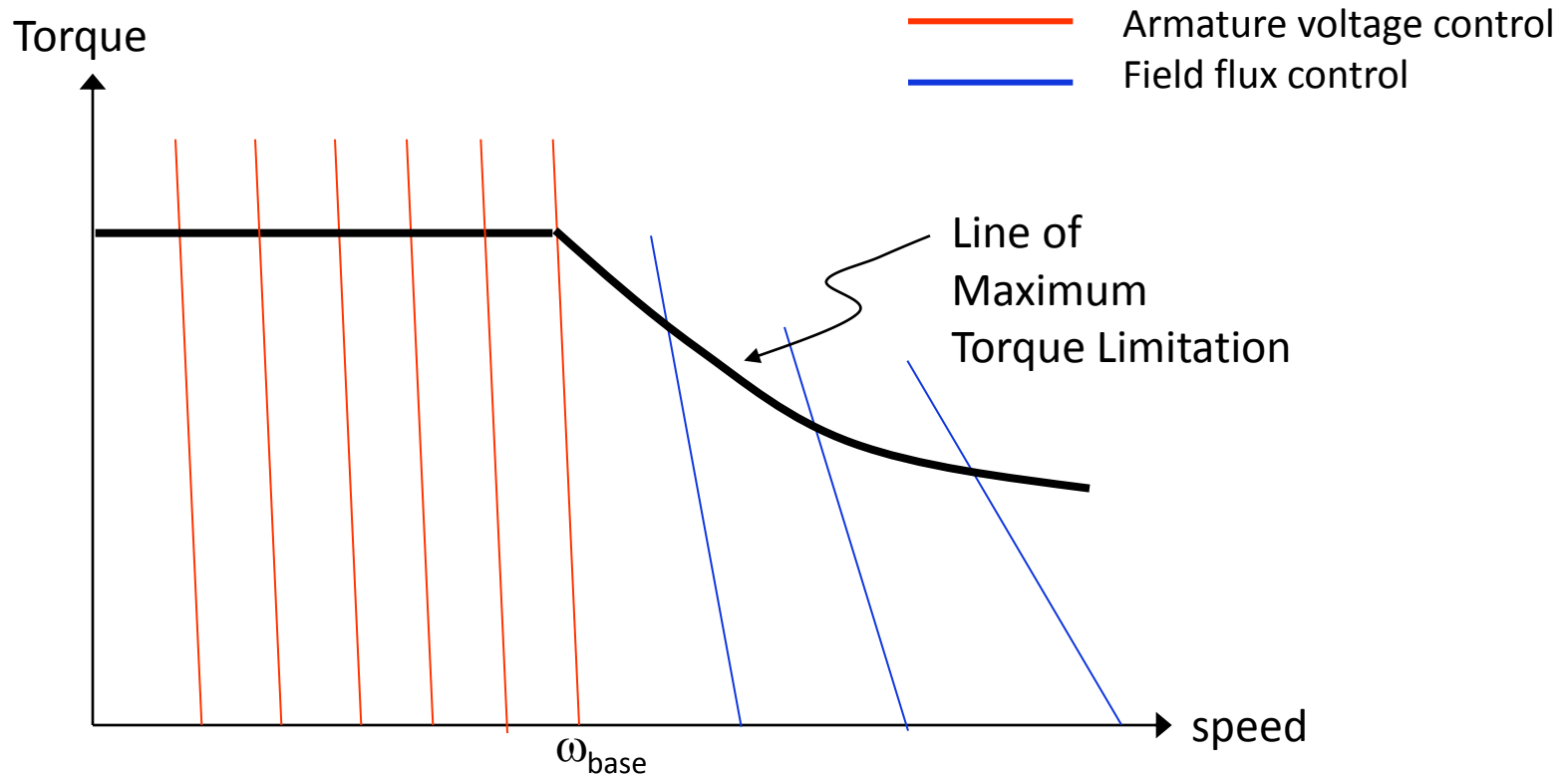Above base speed: Field weakening (i.e. flux reduced) (Trading-off torque capability for speed)



Methods of Armature Voltage Control

Phase-controlled rectifier (AC-DC)

