# Lecture 1

**POWER SYSTEMS** 

# CHAPTER 1 Per Unit Calculations

### 1. Power System Representation

Power Component		<u>Symbol</u>	Power Component		<u>Symbol</u>
	=	Generator	<del>-X-</del>	=	Circuit breaker
	=	Transformer		=	Transmission line
	=	Motor		Π	Feeder + load
	=	Busbar (substation)			

Power components and symbols



#### Department of Electrical & Communication Engineering

## **POWER SYSTEMS**

Interconnections among these components in the power system may be shown is a so-called one-line diagram or single-line diagram. Single-line diagram represents all  $3-\phi$  of balanced system. For the purpose of analysis, the single-line diagram of a particular power system network is represented to its equivalent <u>reactance</u> or <u>impedance diagram</u>. A sample of a interconnected of individual power component is shown in Figure 1.1. This represent a circuit diagram of a power network which is referred to as a single-line diagram.

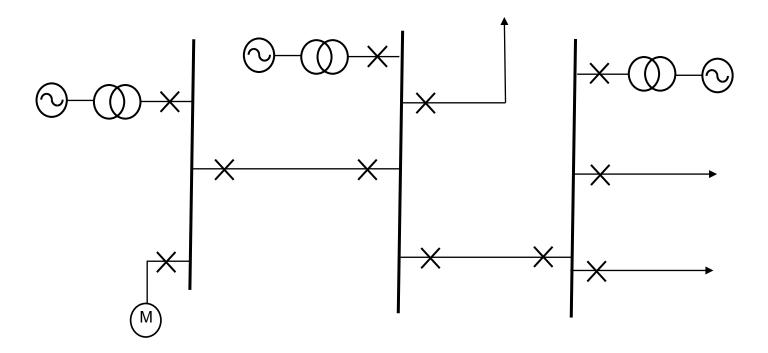


Figure 1.1 – Single-line diagram


## **POWER SYSTEMS**

## Impedance diagram

In power system fault calculations it is often that a single-line diagram representing a typical power network in  $3-\phi$  be converted into its per phase impedance diagram. Some assumptions for converting from single-line diagram into its equivalent impedance diagram needed to be considered.

- (i) A generator can be represented by a voltage source in series with an inductive reactance. The internal resistance of the generator is assumed to be negligible compared to the reactance.
- (ii) The loads are usually inductive represented by resistance and inductance.
- (iii) The transformer core is assumed to be ideal, and the transformer may be represented by a reactance only.
- (iv) The transmission line is represented by its resistance and inductance, the line-to-ground capacitance is assumed to be negligible.

Let us consider the following on how the single-line diagram of Figure 1.2 converted into its impedance diagram counterpart.

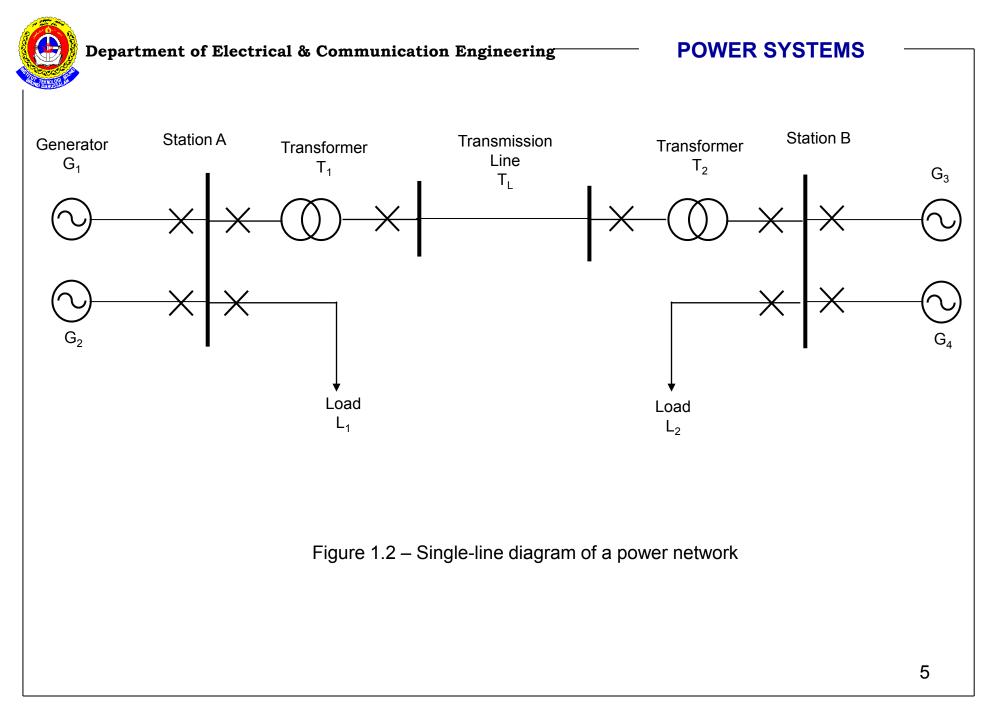

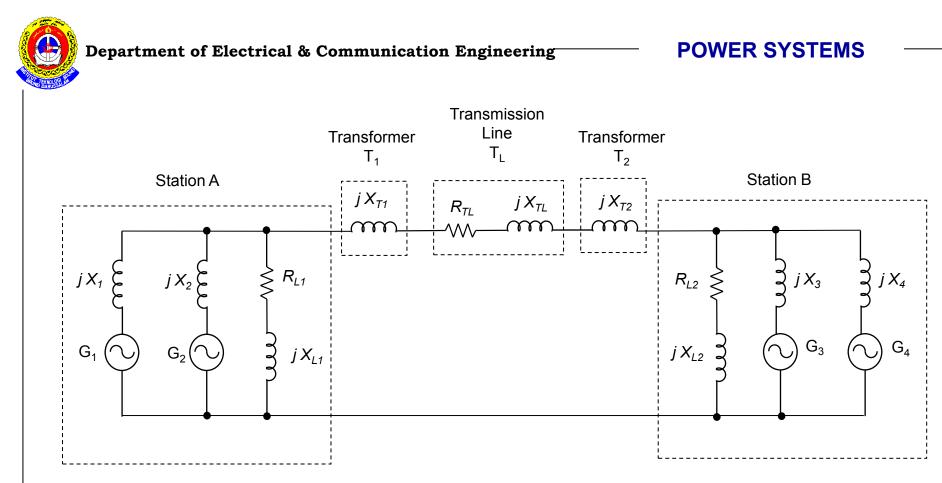


Figure 1.3 – Impedance diagram of Figure 1.2