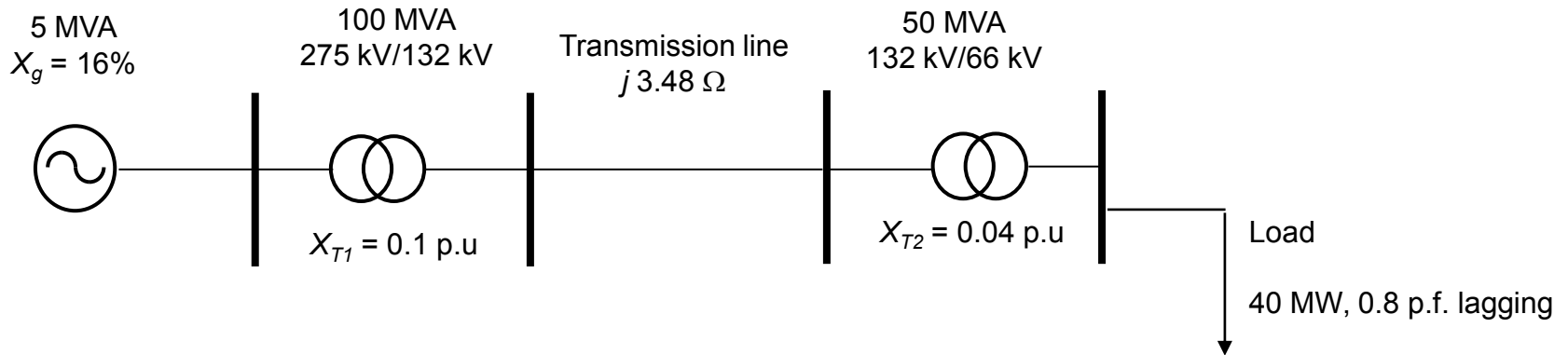


Lecture 3

Example 1

Determine the per-unit values of the following single-line diagram and draw the impedance diagram.



Solution:

Chosen base: Always choose the largest rating, therefore $S_{base} = 100 \text{ MVA}$, $V = 66 \text{ kV}$, 132 kV and 275 kV

Per-unit calculations:

Generator G1:

$$Z_{NEW} (pu) = Z_{OLD} \times \left[\frac{kV_{base\ OLD}}{kV_{base\ NEW}} \right]^2 \times \frac{MVA_{base\ NEW}}{MVA_{base\ OLD}}$$

$$X_g (pu) = 0.16 \times \frac{100}{50} = 0.32 \text{ p.u.}$$

Transformer T1:

$$X_{T1} (pu) = 0.1 \text{ p.u.}$$

Transmission line TL:

$$Z_{base} = \frac{[kV_{base}]^2}{MVA_{base}} \quad Z_{pu} = \frac{Z_{actual}}{Z_{base}}$$

$$X_{TL}(pu) = \frac{3.4 \times 100}{132^2} = 0.0195 \text{ p.u.}$$

Inductive load:

$$Z_{actual} = \frac{66 \times 10^3 / \sqrt{3}}{40 \times 10^6 / (\sqrt{3} \times 66 \times 10^3 \times 0.8)} = 87.12 \angle 36.87^\circ \quad \Omega$$

$$Z_L(pu) = \frac{87.12 \angle 36.87^\circ \times 100}{66^2} = 2 \angle 36.87^\circ \text{ or } (1.6 + j1.2) \text{ p.u.}$$

Transformer T2:

$$X_{T2}(pu) = 0.04 \times \frac{100}{50} = 0.08 \text{ p.u.}$$

Now, we have all the impedance values in per-unit with a common base and we can now combine all the impedances and determine the overall impedance.

